AUSTRALIA'S NUMBER ONE ELECTRONICS MAGAZINE DECEMBER 1983 AUST \$2.30 NZ \$2.60 New Chase 'N' Chomp game New generation hand-held computer **Breakerless** ignition for your car

00

UB


G

10

R

What's the latest in video cameras?

We test Sony's PCM adaptor

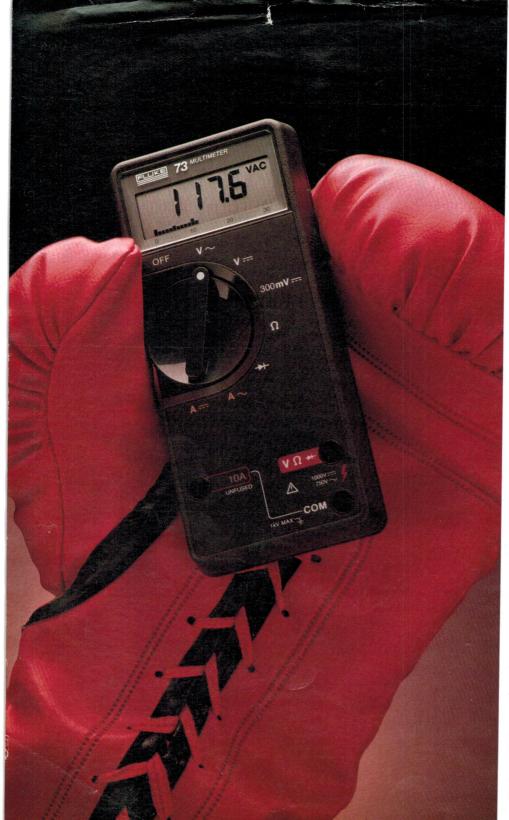

The Digital vs. Analog battle is over.

From

\$110* buys you the new champion.
The new Fluke 70 Series.

They combine digital and analog displays for an unbeatable two-punch combination.

Now, digital users get the extra resolution of a 3200-count LCD display.

While analog users get an analog bar graph for quick visual checks of continuity, peaking, nulling and trends.

Plus unparalleled operating ease, instant autoranging, 2,000+ hour battery life and a 3-year warranty.

All in one meter.

Choose from three new models. The Fluke 73, the ultimate in simplicity. The feature-packed Fluke 75. Or the deluxe Fluke 77, with its own multipurpose protective holster and unique "Touch Hold" function (patent pending) that captures and holds readings, then beeps to alert you.

Each is Fluke-tough to take a beating. American-made, to boot. And priced to be, quite simply, a knockout.

So call or write for more information.

Fluke 73

\$110 *
Analog/digital display
Volts, ohms, 10A, diode

Autorange
0.7% basic dc accuracy
2000 + hour battery life
3-year warranty

Fluke 75

\$129 *
Analog/digital display
Volts, ohms, 10A, mA,
diode test

Audible continuity
Autorange/range hold
0.5% basic dc accuracy
2000+ hour battery life
3-year warranty

Fluke 77

\$165 *
Analog/digital display
Volts, ohms, 10A, mA.

Audible continuity
"Touch Hold" function
Autorange/range hold

0.3% basic dc accuracy 2000 + hour battery life 3-year warranty







P.O. Box 30, Concord, N.S.W. 2137 13-15 McDonald Street, Mortlake, N.S.W. Telephone (02) 736 2888 Telex 25887 P.O. Box 107, Mt. Waverley, Victoria 3149 21-23 Anthony Drive, Mt. Waverley, Victoria. Telephone (03) 233 4044 Telex 36/206

G.P.O. Box 2360, Brisbane, Queensland 4001. 243 Milton Road, Milton, Queensland. Telephone (07) 369 8688. Telex 44062.

Adelaide: (08) 271 1839 Perth: (09) 398 3362



N.S.W. Ames Agency 699 4524 • George Brown 519 5855. (049) 69 6399 • Bryan Catt 522 4923 • DGE Systems (049) 69 1625 • Davred 267 1385 • Macelec (042) 29 1455 • Radio Despatch 211 0191 • Sheridan Electronics 699 6912 • Standard Components 896 1755 N.T. Thew & McCann (089) 84 4999 4.C.T. George Brown (062) 80 4355 VIC. Radio Parts 329 7888 • Browntronics 419 3986 • G.B. Telespares 328 4301 • Eliastronics 561 5844 • Stewart Electronic Comps 543 3733 • Sirs Sales (052) 78 1251 QLD. L.E. Boughen 36 1277 • Colourview Cholesale 275 3188 • ECO Electronics 376 5677 • Electronic Shop (075) 32 3632 • W. G. Watson (079) 27 1099 • GEC Electrical Wholesale (079) Sorvice 278 7488 W.A. Atkins Carlyle 321 1010 • Protronics 362 1044 • Brookeades 276 8888 • Cairns Instrument Services 325 3144 TAS. GHE Electronics (002) 34 2233 & (003) 31 6533.

* All prices are plus Sales Tax if applicable and subject to change without notice.



SOLD & SERVICED IN AUSTRALIA BY

ELMEASCO

Instruments Pty. Ltd.


AUSTRALIA'S LARGEST SELLING ELECTRONICS MAGAZINE

ELECTRONICS Volume 45, No. 12, December 1983 AUSTRALIA



On the cover

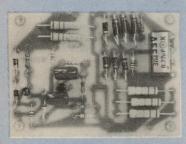Featuring a 40-column by 8-line LCD, Tandy's new TRS-80 Model 100 is the first of a new breed of portable computers. It is significant not only for what it offers but also for the possibilities it foreshadows. Turn to page 92 for our indepth review.




Electronic ignition

Want to convert your car to electronic ignition? This new circuit uses a Hall Effect device to replace the points in the distributor. It's easy to install, locks in engine tune, and is virtually maintenance free.

VK Powermate

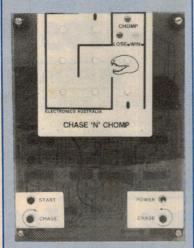Power your amateur rig from the mains with the VK Powermate. It provides 13.8V DC at up to 10A (intermittent) and features overvoltage protection. See page 62.



Chase 'N' Chomp

Chase 'N' Chomp is a handheld gobble-em-up electronic game. It uses novel bi-colour LEDs, features simple sound effects, and can be difficult to play. Turn to page 52.

Features_

- 28 ACROSS THE PACIFIC BY HELICOPTER A hazardous shipboard landing
- 100 MAKING PCBs IN SMALL QUANTITIES Kalextronics has the gear
- 119 50 & 25 YEARS AGO Pedal wireless and the flying doctor
- 133 EA CROSSWORD And the solution for November
- 156 COMING NEXT MONTH New projects
- 158 INDEX TO VOLUME 45 Projects, features & reviews

Hifi, Video and Reviews.

- 12 HOME VIDEO CAMERAS Discover the facts & learn by doing
- 20 BETAMOVIE CAMERA/RECORDER Will it establish a new trend?
- 38 HIFI REVIEW Sony PCM adapter for VCRs

Projects and Circuits.

- 42 BREAKERLESS IGNITION FOR YOUR CAR Uses a Hall Effect device
- 52 CHASE 'N' CHOMP An easy-to-build electronic game
- 62 VK POWERMATE 13.8V supply for amateur transceivers
- 78 DESIGNING RHYTHM GENERATORS: PT 2 Some practical circuits
- 86 ELECTRONIC BALLAST FOR FLUORESCENT LAMPS How it works
- 82 CIRCUIT AND DESIGN IDEAS NICd charger, stereo sound for TV

Personal Computers

- 92 TANDY MODEL 100 PORTABLE COMPUTER
 First of a new breed
- 136 PERSONAL COMPUTERS

 Dulmont Magnum portable computer

Columns

- 34 FORUM
 - We musn't kill CD for a few easy bucks
- 72 THE SERVICEMAN
 A tricky intermittent, more on TV fires
- 127 SHORTWAVE SCENE FEBC operating from Saipan on shortwave
- 128 RECORD REVIEWS
 Classical, popular and special interest

Departments.


- 3 EDITORIAL
- 6 NEWS HIGHLIGHTS
- 106 NEW PRODUCTS
- 116 BOOKS AND LITERATURE
- 122 LETTERS TO THE EDITOR
- 150 INFORMATION CENTRE
- 156 MARKETPLACE



After months of speculation, the new 'Betamovie' video camera/recorder has arrived. The system is revolutionary and could establish a whole new trend in home movie making. Our report starts on page 20.

FOR PERFORMANCE & VALUE AARON HAS TO BE YOUR FIRST SCOPE CHOICE

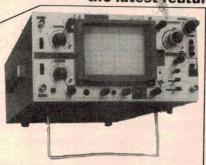All these scopes are dual trace and incorporate the latest features such as high brightness rectangular CRTs.





- 7.7nS risetime
- Single sweep
- Trigger delay
- TV sync
- X-Y, dual, chop, add,

1270.20

45MHz/1mV

- 21 range timebase
- 100mS-1 µS trigger delay
- Front panel trace rotate
- X-Y, dual, chop, add. subtract etc

\$1015.00

35MHz/1mV BS635 \$875

COMPONENT TESTER





- Check components on screen
- 19 range timebase
- Triggerable to over 30MHz
- 17nS risetime

\$620.60

20MHz/5mV

- 2 hour operation from builtin NiCad battery
- Automatic recharging
- Auto trigger free run
- TV sync

15MHz/2mV BS310 \$795

COLINE SP100 PROBE

Professional 100MHz probe offering x1, ref, x10 positions. 1.5m lead with BNC connector and selection of tips. Complete in heavy duty plastic pouch.



QUICK SPEC CHECK

ARON

MODEL	B'WIDTH	SENS	SIG DEL	TRIG DEL	SCREEN	T'BASE
625	45MHz	1mV	Y	Y	150mm	0 2uS - 0 5S div
635	35MHz	1mV	N	Y	150mm	0 1uS - 0 5S div
601	20MHz	5mV	N	N	150mm	0 5uS - 0 5S div
310	15MHz	2mV	N	N	95mm	0.5uS - 0.5S div

All prices are plus sales tax if applicable and subject to change without notice

MAIL COUPON FOR **FREE GUIDE**

Please send me a copy of your shortform oscilloscope guide.

TELEPHONE

P.O. Box 30. Concord N.S.W. 2137 13-15 McDonald Street. Mortlake, N.S.W. Telephone (02) 736 2888 Telex 25887

Instruments Pty. Ltd.

P.O. Box 107, Mt. Waverley Victoria 3149 21-23 Anthony Drive, Mt. Waverley, Victoria Telephone (03) 233 4044 Telex 36206

Adelaide: (08) 271 1839 Brisbane: (07) 369 8688 Perth: (09) 398 3362



N.S.W. Ames Agency 699 4524 ◆ George Brown 519 5855. (049) 69 6399 ◆ Davred 29 6601 ◆ DGE Systems (049) 69 1625 ◆ Macelec (042) 29 1455 ◆ Radio Despatch 211 0191 ◆ Sheridan VIC. G.B. Telespares 328 4301 QLD. Colourview Wholesale 275 3188 ◆ St. Lucia Electronics 52 7466 ◆ Electronic Shop (075) 32 3632 ◆ W. G. Watson (079) 27 1099 ◆ Nortek (077) 79 860 ◆ Integrated Technical Services (070) 51 8400 S.A. Trio Electrix 51 6718 ◆ Protronics 212 3111 W.A. Atkins Carlyle 321 0101 TAS. GHE Electronics (002) 34 2233 & (003) 31 6533.

FDITOR

Leo Simpson B. Bus. (NSWIT)

ASSISTANT EDITOR

Greg Swain, B.Sc. (Hons. Sydney)

EDITORIAL CONSULTANT

Neville Williams F.I.R.E.E. (Aust.) (VK2XV)

TECHNICAL PROJECTS

John Clarke, B.E. (Elect. NSWIT) Peter Vernon, B.A. L.L.B. (NSW)

Jeff Skeen Colin Dawson

PRODUCTION Danny Hooper

GRAPHICS

Robert Flynn

SECRETARIAL Christine Cleary

ADVERTISING MANAGER

Selwyn Savers

CIRCULATION MANAGER Alan Parker

Editorial and Advertising Office

57 Regent St, Chippendale 2008

Phone (02) 699 3622 Telex 25027 Postal Address: PO Box 163, Chippendale,

2008

Advertising Sales Manager: Sel Sayers.

Melbourne - 392 Little Collins St, Melbourne

3000. Phone (03) 602 3033. Representative: Mark Christian.

Adelaide - Charles F. Brown & Associates

Ltd, 178 Fullarton Rd, Dulwich 5065 Representative: Sandy Shaw (08) 332 7711.

Perth - 454 Murray Street, Perth 6000.

Representative: Ashley Croft (09) 321 8217.

Circulation Office

Unit 3B, Sydneygate, Waterloo, 2018.

Phone (02) 699 2388.

Subscriptions

Subscription Dept, John Fairfax & Sons Ltd,

GPO Box 506, Sydney 2001

Enquiries: Phone (02) 699 2388

Registered by Australia Post -

publication No. NBP0240.

ISSN 0313-0150

*Recommended and maximum price only.



Editorial Viewpoint

More TV fires than we thought

The article on TV fires in the October issue has created quite a deal of interest among readers. Predictably, some wanted to be reassured that their particular set and type of on-off switch had a clear bill of health. That is something we are unable to give.

The October article by the Serviceman referred to sets having a specific type of push-on, push-off power switch as being a potential hazard. There may well be other components in sets which also represent a potential hazard but we do not know about them. That there is a significant fire risk in TV sets is indicated by figures

compiled by the NSW Fire Brigade.

In the 12-month period ending on January 31st, 1983, there were 68 fires in NSW attributed to TV malfunctions. Of these, 44 were in colour sets and the remainder in B & W sets. The figure for B & W sets is not in proportion to the number in use and would seem to indicate that the older a set becomes the more likely it is to catch fire.

Some people may doubt the figures supplied by the NSW Fire Brigade and it would have to be admitted that in some cases the fire may have had some other cause. Equally, many fires are listed as having an unknown cause and some of these may have been due to a TV fault. In some of the fires, the TV set alone would have been destroyed but in many cases the damage goes much further and has led to loss of

If the NSW experience is repeated throughout Australia, it seems likely that there are over 200 domestic fires which could be attributed to faults in TV sets. When you consider the millions of sets in use the figure of 200 is not very large but if you happen to be one of the victims that would be no consolation.

Whichever way you look at it, the possibility of a TV fire in your own home cannot be ignored and while the statistical risk may be small it certainly must become larger as a TV set ages. For peace of mind, turn off your set at the wall socket while it is not in use. And don't run a TV set for long periods while no-one is the house. While it may be a popular ploy to foil burglars it could lead to worse consequences.

1983 draws to a close

Most people would agree that 1983 has been a tough year. Against this, 1984 shows more promise with a likely flow-through from a turnaround in the agricultural sector coupled with the much-heralded lift in the US economy. Even that is not without its problems though, as shortages in semiconductors have become prevalent, particularly in CMOS ICs. Let us hope that will be temporary.

Whatever the economic climate, 1984 will certainly continue the headlong process of technological development. We will keep you up-to-date and we have some

really interesting projects planned for the next 12 months.

I thank all our readers and advertisers for your solid support in 1983. Best wishes to you all from the staff at EA for a Happy Christmas and a prosperous New Year.

Leo Simpson

Printed by Magazine Printers Pty Ltd, Regent Street, Chippendale and Masterprint Pty Ltd, Dubbo, NSW for Magazine Promotions, Regent St, Chippendale

Copyright. All rights reserved.

Information is furnished in this magazine without responsibility for its ultimate use or for any failure of equipment to operate as expected, or for any damage, loss or injury which may be sustained. Patents may apply to devices or arrangements depicted in this magazine. Material intended for publication is submitted at the sender's risk and while care will be taken, responsibility for any possible loss will not be accepted by "Electronics Australia"

Distribution: Distributed in NSW by Magazine Promotions, 57 Regent St, Chippendale, in Victoria by Magazine Promotions, 392 Little Collins Street, Melbourne; in South Australia by Magazine Promotions, 101-105 Waymouth St, Adelaide; in Western Australia by Magazine Promotions, 454 Murray Street, Perth; in Queensland by Gordon and Gotch (A'asia) Ltd; in Tasmania by Ingle Distributors, 93 Macquarie St, Hobart; in New Zealand by Gordon and Gotch (NZ) Ltd, Adelaide Rd, Wellington.



re computer

We agree! The IBM PC is a superb computer. But look at the priceway over six thousand for a usable computer - then you have to start buying programs!

Now there's a brilliant alternative: the Dick Smith Challenger. For less than half the price of the IBM PC you get much, more computer. Just for starters, how about 128K RAM as standard – expandable to 256K (IBM give you 64K) and BOTH Centronics and RS232C ports as standard? (IBM charges you extra!)

And the quality is guaranteed!

Each Dick Smith Challenger is individually 100% computer tested and accompanied by its own test certificate confirming it meets all specifications. Beat that, IBM PC.

High Resolution Video Monitor not Video Monitor not included in price included in price (Cat X-1220, \$249.00)

Is it really IBM compatible?

We haven't found one IBM PC program that won't work in the Challenger (and we've checked hundreds!) Just pop in an IBM PC diskette – and away it goes! Not only that, but all plugin IBM PC hardware is also compatible.

OUTSTANDING FEATURES:

- True 16-bit machine (uses full 16-bit 8086 processor, not the partly 8-bit 8088 processor used in the IBM).
- Comes in two versions either the basic model or the fully expanded 128K, twin disk drive model . . . both of which are less than half the price of the IBM PCI
- And the expanded computer gives you BOTH Centronics AND R\$232C ports. PLUS twin double density, double sided 'slimline' disk disk drives offering an incredible 640K of storage!

 Memory expandable up to an incredible 256K just by plugging in
- some extra chips.
- Offers virtually ALL of the hardware any computer user is likely to want. And if you DO want more, there are 6 expansion slots.



Cat X-8600

Here it is: the new Dick Smith Challenger. It's the ideal computer for the business user, the professional or the serious hobbyist. Featuring a HUGE 128K memory - more than you're likely to need - with an equally large 40K ROM.

includes

- RF/ Video output
- Microsoft Extended BASIC, plus diagnostic in ROM.
- Four I/O ports: cassette, joystick, light pen & Centronics type for printer.
- 84 key high tactile keyboard
- (detachable).

 Built-in speaker for sound programs

The IBM model with equivalent features would cost at least if they'd sell you one!

YOU SAVE \$

Keyboard slips inside case for storage!

*Quoted prices do not include video monitor!

a look at the new

for half the price!

SPECIFICATIONS: (Expanded Computer)

CPU: 16 bit 8086 running at 4.77MHz RAM: 128K (int expandable to 256K) plus 16K Video.

ROM: 40K (includes BASIC, cassette o/s,

diagnostic)
KEYBOARD: Full 84 key tactile, detachable
CHARACTER SET: 256 expanded ASCII, in

RESOLUTION: 320 x 200 or 640 x 200 COLOUR/GRAPHICS: 16, with scroll & reverse

PLUS: Software worth over \$1500 - FREE!

Yes - Software worth over FIFTEEN HUNDRED DOLLARS is included with the Challenger Expansion Unit at no extra charge. With the IBM PC it's all optional at extra cost.


We don't give you useless software, either. In dark you deless sollware, ellifet. It days all the software you're likely to need: a disk operating system (DOS), disk BASIC, a word processing system, a filing system and an electronic spreadsheet. In most cases you

won't need anything else.
MICROSOFT MS-DOS, DISK BASIC – most widely used disk operating system and disk BASIC for IBM PC Itself. With the IBM these cost you over \$60 extra!


PERFECT WRITER - one of the most popular word processing systems in the world. Worth at least \$550 alone!

PERFECT FILER – lets you design your own filing systems and mailing lists. Worth over \$600! PERFECT CALC - the electronic spreadsheet to beat them all. Worth over \$300 as well!

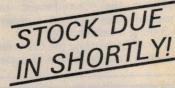All of this software comes complete with user manuals, and it's included FREE with the Challenger Expansion Unit!



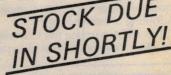Interested in leasing? No problem - we can



arrange it for you!



All the expansion you're likely to need (hardware & software)

for only \$

Add the Challenger Expansion unit and you get unbelievable computing power – far more than the IBM PC gives you. Twin 320K disk drives included. PLUS disk operating system (DOS) included. Both Centronics and RS-232 interfaces included. PLUS (of course) everything the Challenger itself

And full IBM PC compatibility - not just software, but the plug-in hardware devices

includes

- Twin slimline double sided, double density disk drives.
- RS-232C serial communications port
- 6 extra expansion slots (4 IBM PC compatible
- 2 true 16 bit).
 PLUS the following fantastic software:
 Genuine (licensed!) Microsoft MS-DOS
- Genuine (licensed) Perfect Writer, Perfect Filer, and Perfect Calc.
- And compatibility with all known IBM PC software and that's a heck of a lot to choose from!

IBM PC configured with similar features to Dick Smith Challenger would cost you

well over \$7000

CHALLENGER TOTAL SYSTEM ONLY \$2990* YOU \$



See page 120 for full address details.



News Highlights

Telecom should manufacture here says ATEA

Telecom should be directly involved in the manufacture of telecommunications equipment, says the Australian Telecommunications Employees Association (ATEA).

In a submission to Senator John C. Button, the Minister for Industry and Commerce, the Association argues that without direct Government involvement, Australia would lag further and further behind in microelectronics and telecommunications manufacture. The ATEA quotes a 1983 report of the High Technology Financing Committee of the Australian Academy of Sciences, which states:

"This committee knows of no country which has succeeded in establishing a climate for investment in high technology enterprises without the Government taking positive action and, at a minimum, adopting a catalytic role".

The ATEA is urging the Government to allow Telecom to use its extensive

laboratories and research expertise as the basis for an expansion into commercial manufacturing. Government telecommunications authorities in countries such as Canada and Sweden routinely enter into joint ventures with private companies, and in Sweden the state telecommunications organisation, Televerket, itself produces much of the equipment it uses.

Televerket owns half of an R&D company called Ellemtel, the other half of which is owned by the leading private company L. M. Ericsson — one of the largest suppliers to Telecom Australia.

Australia's balance of trade in high technology imports is now almost \$10 of imports for every \$1 of exports, compared with Japan's one to five, the United States one to two and Canada's three to one ratios.


The ATEA points out that the great majority of manufacturers in Australia are subsidiaries of overseas-owned companies. The only large Australian-owned enterprise is AWA. Research and development carried out by these subsidiaries is aimed solely at the local market, as the overseas parent companies provide no incentive for export-oriented development and manufacturing.



STC completes wiring for the domestic satellite

Standard Telephones and Cables Pty Ltd has completed and delivered the first wiring system to be incorporated into the AUSSAT domestic satellite. The work was performed at STC's Liverpool, NSW plant in a factory built to manufacture

Fibre optics for aircraft inspection

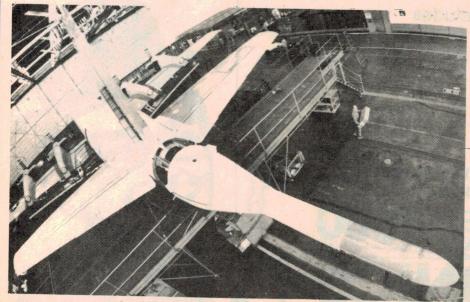

The photograph shows an unusual view of a Lockheed P-3C Orion provided by a camera's fish-eye lens which emphasises one of the aircraft's key sensing devices — the Magnetic Anomaly. Detector (MAD) boom extending from the centre to the right hand side of the photograph. The aircraft itself is dwarfed on the left hand side. The MAD system, which is built by Texas Instruments, is about to be attached to the aft section of the Orion at the Lockheed-California Company's Burbank plant.

The MAD boom helps crewmen to identify the presence of submarines beneath the sea, since large metal objects such as submarines subtly skew the magnetic field of the earth and the MAD system detects these alterations. The MAD detector must be kept well away from the magnetic fields generated by the aircraft. More than 560 of the P-3 series aircraft have been delivered to eight countries since the program began



repeater units for the ANZCAN oceanic cable, and is part of Hughes Aicraft Company's program to meet the offset requirements of the domestic satellite manufacturing contract.

The photograph above shows the delicate wiring harness under assembly. Eventually it will form part of the orbital guidance system of Australia's first domestic satellite.

According to recent reports it seems likely that Telecom Australia will have control of the satellite.

Memory chip holds half a million bits

An experimental computer memory chip that can store more than a half-million bits of information — nearly twice the capacity of any chip yet reported — was described at a technical conference recently by engineers from IBM's semiconductor facility in Essex Junction, Vermont.

The new component is a 512K bit dynamic random access memory (RAM) chip. Since, in computer terminology, "K" stands for 1024, the chip actually holds 524,288 bits of information. It is the first complete chip ever to use an electronic technique called "plate pushing" to read data out of its storage cells.

Plate pushing — previously used only in greatly simplified test circuits — produces an electrical signal nearly twice as large as that produced by conventional data reading methods. With this stronger signal, it is possible to increase the chip's density and reliability while maintaining high performance.

The new chip measures 7.96mm by 8.6mm and data can be retrieved from its storage cells in 120 nanoseconds. The smallest photolithographic images in the chip's circuit pattern are just 1.5 micrometers wide, about 1/50 the diameter of a human hair.

Several lots of wafers containing the




An IBM technician examines a wafer carrying the new experimental 512K bit memory chips.

new chip have been fabricated at the IBM laboratory, and testing of these chips has confirmed that all circuits function as intended.

in the 1960s.

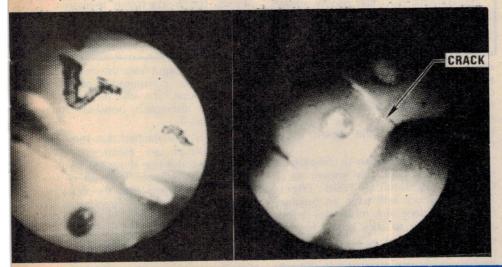US Navy technicians use fibre optic instruments to inspect the P-3 Orion craft just as doctors use fibre optics to probe their patients. Areas of the Orion craft which are difficult to inspect can be examined for possible damage or malfunction through the use of fibre



optics systems. Each fibre consists of a bundle of more than 40,000 glass fibres which carry the image to the borescope viewer, while another group of glass fibres carries the light for illuminating the part under examination.

Each fibre independently transmits an image of a minute part of the area under examination, so the eyepiece produces a magnified mosaic of the area for the viewer. The image resembles a photograph which has been screened for newspaper publication.

This technique has been found far more convenient than the use of flashlights and mirrors. A small diameter cable can be used to view an area over three metres away. The fibre optic cable can be inserted through a small hole in a panel, whereas the use of other viewing techniques would have required the removal of the complete panel.

- Brian Dance

News Highlights

Geoff Wood opens new electronics store

Geoff Wood, manager of Radio Despatch Service for many years, has opened an electronic components store at Rozelle to serve the hobbyist, technical laboratories and small manufacturers.

Geoff will be stocking a very wide range of semiconductors, passive components, hardware and test equipment. He intends, especially, to carry a wide variety of National Semiconductor devices and reckons "it will be a one-stop shop for ICs and semiconductors." Other items to be stocked will include kits for magazine projects, together with a range of PCBs and front panels.

Geoff Wood Electronics is at 656 Darling Street, Rozelle, NSW 2039 (see advertisement on page 57).


And now. . . the bionic nose!

A team working at the University of Warwick in England has built an "Electronic Nose" which is able to distinguish between different types of odours. This prototype nose employs three semiconductor gas sensors each of which produces a slightly different response to various types of molecule. The ratio of the signals from the different detectors is computed to identify a particular type of smell.

The team, under the leadership of Dr George Dodd, is developing their electronic nose by working on the principle that the human nose employs millions of cells, each slightly different, and that the combined response from these various cells serves to create a distinctive pattern of signals which are fed to the brain for the identification of the particular smell. However, the response of the various individual cells to any smell is thought to show only small differences.

The Warwick workers have subjected their prototype nose to 21 different smells including single substances having only one type of molecule and very complex mixtures such as lilac, jasmin, rose, sage and clove oil. However, the team is confident that their equipment is capable of distinguishing many other types of smells.

The three detector system in current

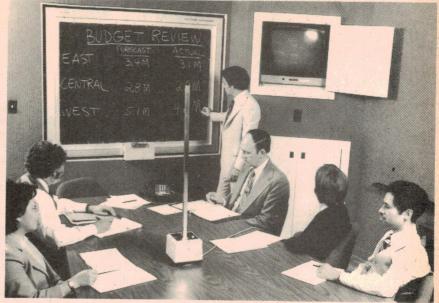

AWA launches teleconferencing system

Amalgamated Wireless Australasia has released a teleconferencing system designed by its Telephone Switching Group. By using the system, groups of people can hold meetings without travelling, communicating over the telephone lines using equipment located in their own conference rooms.

The advantages of teleconferencing include savings of time and money spent travelling and the availability of documents and other support from all participants. The teleconference can take place from point to point or between many locations simultaneously and can be organised and set up within minutes.

The conferencing system offered by AWA is a series of modules which can be purchased separately and added to as required. The minimum requirement is a high quality audio link which connects to the ordinary phone system. The microphone is an 80cm high wand which sits on the

conference table on top of a built-in loudspeaker.

The simple audio conference can be extended by the addition of an "Electronic Blackboard" and TV monitor at each end to provide graphics. People at either end of the conference link can write on the board with chalk and the images appear on the monitor screens at both ends. An additional telephone line is used to carry graphics information.

If hard copy is required a high speed facsimile transmission system can be added. Copies of A4-sized documents can be transmitted to another location in 20 seconds, again over a separate phone line.

A slow scan television system can also be used for the display of still pictures of people, documents and objects. The "freeze frame" television image is transmitted in about 40 seconds over a normal telephone

use is only the first step. The workers now plan to fabricate a much more complex bionic nose which will incorporate 100 different smell sensing devices together with the circuitry required to process the signals from these devices.

Subsequently they plan to develop a special chip provisionally known as a Chem-FET (Chemical Field Effect Transistor) which will have an organic film on its surface. Any molecules in the air will be able to stick briefly to this surface and in doing so will produce a minute change in the electric field in the device which the transistor itself will

amplify. The output from the chip will be appropriately computed and it is expected that it will be able to accurately distinguish between many types of smell.

Eventually it is planned that the team will construct an electronic nose containing about one thousand sensors, each slightly different from all of the others. It is hoped that the resulting device will be widely applicable to industrial processes, such as the monitoring of food products (especially materials like coffee) and of other products such as perfume.

- Brian Dance.

New Release Oscilloscopes from TRIO

CS-1022 20MHz Dual-Trace Economy and Style in an all new workhorse 20MHz scope



\$649 + Tax\$746.35 Inc. Tax

* High sensitivity - 1 mV/div

* 150mm rectangular CRT (6KV) with illuminated inner-face

* 20nS/div maximum sweep for display of fast changing signals

*±3% accuracy for precision waveform measurement

* Video clamping for reliable synching

* Eight divisions of dynamic range

* Ergonomic front panel layout

* Observation of intensity modulated signals

* X-Y mode

* Vertical signal output

CS-1040/1060 40/60MHz

A Thoroughly updated design in a 3-channel, 6-Trace Scope

Price does not include probes



CS-1040 \$1,175 + Tax\$1,351.25 Inc. Tax

\$1,495 + Tax\$1,719.25 Inc. Tax

Price does not include probes

*3-channel, 6-Traces using alternate delayed sweep

*Extremely high sensitivity of 1mV

*Bright, sharp, autofocus 16kV CRT (12KV for CS-1040)

* Maximum sweep speed 5nS/div (10nS/div for the CS-1040)

* ±3% accuracy for precise waveform measurements

* Eight full divisions of dynamic range

* Vertical axis signal output

* Video clamping

* Delayed sweep can have zero delay enabling magnification of even the leading edge of a signal

CS-2110 100MHz 4-channel Oscilloscope A New Standard in 100MHz Scope Performance



\$2,495 + Tax\$2,869.25 Inc. Tax

High sensitivity 1mV all the way to 100MHz

* 2nS/Div. maximum sweep speed

* Delayed sweep for partial waveform expansion

4-Channels, 8-Traces with wide range of waveform display functions

* Dual sweep functions

* Accuracy ±2% for precise waveform measurements

*Bright, sharp, 150mm rectangular CRT (20KV)

* Pushbutton switches with LEDs for simplicity and reliability

* Guaranteed channel-to-channel time accuracy

* All position controls are on the front panel for operator convenience

* Optimum multi-clamping of video signals

Probes — Model 88100 DC to 100MHz probes to suit all the above scopes \$33 + tax \$39.60 including tax

Special Introductory Offer

Price does not include probes

Parameters is giving away a hand held DMM with any of these scopes purchased before December 30,


Buy a CS-2110, CS-1040, or a CS-1060 and receive at no extra charge a Parameters Model 7040

Buy a CS-1022 and receive at no extra charge a DMM. Parameters Model 601 DMM.

Hurry, call us today to reserve your oscilloscope/DMM - Offer definitely expires at close of trading December 30, 1983.

Sydney: 41 Herbert St. ARTARMON 2064 Phone: (02) 439 3288 Melbourne: 53 Governor Rd. MORDIALLOC 3195 Phone: (03) 580 7444

PARAMETERS PERFECTION IN MEASUREMENT

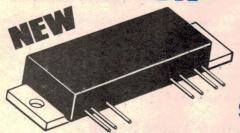

PLEASE NOTE

AMATEURS

MASSIVE SCOOP PURCHASE! MANUFACTURERS DISTRESS STOCK!

Jaycar has purchased a quantity of genuine Brand New MOTOROLA Brand MHW-710-1 UHF Power
Amplifier modules. These units are designed for industrial and commercial FM transmitters!
The unit (pictured) is a rugged, tuned train of RF Power Amplifier transistors featuring thin-film gold metallization, laser trimmed Nichrome resistors and MOS capacitors. The MHW-710-1 bolts to any flat SPECIFICATIONS:

SPECIFICATIONS:

- RF POWER OUT @ 12.5V 13 WATTS - RF POWER OUT @ 15V 17 WATTS!!

(BOTH OF THE ABOVE RATINGS ARE LIKELY TO BE EXCEEDED AS MOTOROLA'S POWER RATING CLAIMS ARE CONSERVATIVE)

- 19.4 de (Min) POWER GAIN. TYPICAL DRIVE LEVEL TO FULL POWER 90 - 150mW

- FREQUENCY BAND 400 - 440MHz. Will work to 450MHz and therefore covers the AUSTRALIAN UHF AMATEUR BAND!!

CIRCUIT DIAGRAM INCLUDED

Each MHW-710-1 comes individually packed with full manufacturers data. A manufacturers recommended circuit is included (only a few external components required), as well as a PCB pattern for the circuit. This component makes an ideal base for a "Home Brew" UHF Linear Amplifier! GREAT for SERVICEMEN

The MHW-710-1 has been used extensively in Australian Manufactured UHF Mobile 2-way radios. If you own or service a UHF radio that uses this part, now is your chance to grab a spare at an unrepeatable price! The MHW-710-1 sells for A\$68 plus tax in the USA.

QUANTITIES STRICTLY LIMITED

To be fair to all, we have limited this offer to 2 per person. Jaycar's Scoop offers are so successful that usually hundreds miss out. Even at 2 per customer we will probably run out quickly. Be early to avoid disappointment!!

STAGGERING VALUE! ONLY \$39.95!! - Cat. ZK-8882

PH 1005A

Square Super Horn for PA's, Disco's etc. Very efficient. Around 50Wrms equivalent capacity Cat. AS-3100 \$9.95

Hi Fi version Cat. AS-3102

Jaycar has broken the price barrier for Piezo Horn Speakers!!

We now DIRECT IMPORT a range of piezo horns at prices that will stagger
you. Similar units are used everywhere in P.A., Disco and Hi Fi applications. PH 1038A
Only Jaycar, however, can bring you these products at low Jaycar prices!!

We now stock the most popular piezo models at new low prices.

Hi Fi versi
Cat. AS-31

VK POWERMATE - NEW MODEL

on of the PH 1005A. Slightly less sensitive but a smoother response. \$9.95



TWIN SCREENED AUDIO CABLE

Twin screened round audio cable. (Two screened conductors NOT fig. '8')

This cable normally sells for \$0.48/metre or \$42.00/roll.

\$20.00/roll

SAVE **OVER** 50%. . .

Ref: EA Dec. '82 Get up to 13.8V @ 10 amps to run those The Jaycar kit is complete.

PER ROLL

\$89.95 comp

LOW IMPORT PRICE

T151-650R

This is the 650 volt version (for extra safety) of the C122E SCR which we use in the popular 'Fluorescent Lamp Starter' Kit as described in October 1982 EA. Normally \$1.50 each. This month only \$0.95 each! (Minimum 5 pieces). Makes the Fluoro starter kit very cheap! (PCB's for the kit) Cat. HP8747

ONLY \$1.95



TRANSISTOR

BD677 DARLINGTON

Cat. ZX7022 (8 amp 650V SCR)



Keep your precious (and expensive) magazines in order for easy references. Smart blue colour with gold lettering. Heavy gauge and richly chromed metal

NORMALLY \$4.95 ea

MAGAZINE BINDER

fittings.

Cat BB7000



\$19.95

Unique regular phase design drives the entire diaphragm, uniformly and completely in phase over the full frequency range. The performance of an electrostatic speaker with the ruggedness and ease of use of a dynamic.

Cat. CE:2042 NORMALLY \$36.50 ea

ONLY \$19.95 - SAVE \$16.95

- 91dB sensitivity
- 50W system power

\$3.95 each or \$3.50 each 4 up MARSHALL

EQUIPMENT HANDLES Either for speakers or P. A. Heavy duty. Cat. HS-8010 ONLY \$9.95 ea







- FUSE/DIODE PROTECTED!
 4mm BANANA SOCKET PROBES!
 BIFURCATED SELECTOR SWITCH CONTACTS!
 ABS IMPACT-RESISTANT CASE:
 LARGE! MEASURES 90(w) x 135(h) x 45(d)mm
 SPECIFICATIONS:
 DC 0 0.25 AC 0 10
 0 10 0 50
 0 550 0 250
 0 250 0 1000
 0 1000 AT 9,000 ohms/volt
 AT 20,000 ohms/volt
- RESISTANCE 0 -- 5K 0 -- 50K 0 -- 500K DC CURRENT 0 - 0.05 0 - 25 0 - 250mA
- dB: -20 to +22dB

 BATTERY CHECK FACILITY: AA, C & D CELLS
 ACCURACY: DC +/-3% F.S. AC +/-4% F.S.

 BANANA PLUG PROBES AND BATTERY INCLUDED

 This is an enabligable area became in Normally, this unit

This is an unbelievable meter bargain for around \$25. Japanese made quality. Cat. QM-1005 nally this unit would sell

• 5,000-40,000Hz

No voice coil



With this kit and the interface electronics you can forget about contact breaker point problems! Cat. KJ-6655

New PCB for TAI Kit includes Hall Effect interface. Cat. HP-8786 ONLY \$3.95

OVER A DOZEN DIFFERENT ADAPTOR PLATES FOR YOUR PARTICULAR DISTRIBUTOR OTHER HARDWARE (i.e. SCREWS etc.)
YOU CAN REMOVE THIS SYSTEM AND RE-EQUIP YOUR CAR WITH THE ORIGINAL—BREAKER POINTS WHEN YOU SELL THE CAR!

- AS EASY TO INSTALL AS A SET OF POINTS!
- INSTRUCTIONS (SIMPLE-TO-FOLLOW) INCLUDED!
This set is designed to fit most European and Japanese cars. In fact it will also fit many Australian cars fitted with Lucas, Bosch, Motorcraft, AC Delco or Autolite electrics. If you wish to check first, please send SAE for car/distributor list. send SAE for car/distributor list.

Because we have no way of knowing, you get the fitting set for ALL of the distributors available. Basically you end up with a jar full of parts that you don't need to use! (Perhaps for your next car?) Ouite frankly, we are amazed that we can supply such a comprehensive kit for this price. To produce a kit that will adapt to the dozens of different distributors around is amazing!


Remember, once you have installed a breakerless system it will never wear out and that part of your system will remain in tune FOR EVER.

Call Us

the largest range of kits in Australia. We stock kits for most of the projects described by the magazines over the last few years. Space does not permit us to include ALL kits in our ads, all the time. So if you are after a specific kit - call us first. We can probably help you!!

ETI 492 Sound Bender

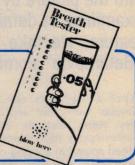Ref: ETI Feb 1982
Short form kit of a device to give either your voice, musical instrument or other source: that Dalek, metallic sound – as well as other sounds! \$24.50



1.9 10.19 20 or more 1.10 .99 .90 1.20 1.08 .99 1.40 1.26 1.15 XE3530 C10 1.10 XE3540 C20 1.20 XE3545 C30 1.40 The quality tapes are supplied to us in boxes of 20, so to make it easier we've got a special

In all states and territories in Australia it is an offence to drive a vehicle with an alcohol/blood concentration above a certain limit. In most states it's 0.05 others 0.08. Either way it's only a relatively small number of alcoholic drinks.

Because it's only a small number of drinks, many people (quite wrongly) believe that they remain below the statutory limit.

The KA1522 Breath Tester can help here. A unit with the same circuit diagram was featured in May "Electronics Australia". It CANNOT give you an actual blood/alcohol content reading, however it can go close. And it can give you a relative reading between inebriated friends!!! Great at parties!!!

Grab the whole kit now for only \$29.95. You never know, it may save your licence or your life!

Cat KA1522

VIDEO ENHANC

Ref: EA Oct 1983 Get improved performance from your VCR. Cat. KE-7016





TRANSISTOR TESTER KIT

Check your transistors in circuit. Saves removing them. Ref: EA sept. 1983. Cat. KA-1532

ONLY \$15

TV Crosshatch/Dot Hatch Generator

Ref: EA Nov. 1983 Great new version of this handy piece of test gear. Now you can generate Crosshatch, Dots and Blank (white) video signals. This is handy for TV/Video

alignment.
Cat. KA-1530 Basic (short form) kit inc. Jiffy box
ONLY \$24,95
Cat. L.T-3800 Video Modulator to suit
Power Supply to suit
\$8,95

95



ETI15000 METAL DETECTOR

The Performance of a \$500 metal detector for only \$219! This is a fully discriminating VLF T/R instrument (yes) the same principle as those expensive American ones) with ground balance. Control facilities are comprehensive — including an 'auto tune' button. This kit includes all parts including a fully built search head and handle assembly and special meter and case.

Cat. KE-1460

SEE ETI DEC 1980 and JAN/FEB 1981



Touch Sensitive Ref: EA April 1983 Light Dimmer

Cat. KA-1508

Complete kit including quality HPM wall plate with attractive brushed metal insert. The Javcar kit is absolutely complete including a small dial spring which can be used to connect the PCB to the wall plate. (Beware of other kits that do not include this). In addition to the above, we supply the High Voltage Resistors ALREADY SOLDERED in as a foolproof safety

build your own speakers &



4000/1 4-way System Cat. CE-2430 Speakers only \$525 (set of 8 spkrs with x/overs)

4000/2 3-way System Cat. CE-2440 Speakers only \$397 (set of 6 spkrs with

Incorporating

ELECTRONIC AGENCIES

117 YORK STREET - PHONE: (02) 264 6688and (02) 267 1614 TELEX: 72293

CARLINGFORD
CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444 CONCORD 115 - 117 PARRAMATTA ROAD - PHONE; (02) 745 3077

HURSTVILLE 121 FOREST ROAD - PHONE: (02) 570 7000

NUMBER 1 FOR KITS

POST AND PACKING CHARGES \$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20) \$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50) \$100 - \$198 (\$8.00) Over \$199 (\$10) "Free INSURANCE for Road & Registered Post over \$200" r bulky items (over 20kg.) sent Comet Road Freight \$12.00 and

in Australia.

SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE

Mon — Fri 9am — 5.30pm: Sat — 9am — 12pm: Thurs night 8.30pm

SHOP HOURS YONEY

Mon — Fri 8.30am — 5,30pm: Sat — 8.30am — 12pm: Thurs night 8.30pm

MAIL ORDERS AND CORRESPONDENCE: BOX K 39 HAYMARKET, SYDNEY 2000



HOME VIDEO CAMERAS

First discover the facts — then learn by doing

We can't make you an instant expert in video photography; only hands-on experience can do that. But we can put you into the picture by discussing video cameras generally and examining in detail a typical current model. In a follow-up feature, we take a close look at the new, trend-setting "Betamovie" combination camera/recorder.

Until a few years ago, home video cameras were few and far between. They were relatively expensive and predominantly monochrome, with very limited appeal in a world of colour films and colour television. Many of them ended up being used for surveillance

rather than entertainment.


But, with the '80s, came a veritable explosion in world sales of VCRs (video cassette recorders) and that, in turn, produced a keen demand for video cameras to use with them — hopefully compatible in terms of sound, colour,

resolution and price. The challenge was quickly taken up.

Currently, most VCR manufacturers either supply or recommend suitable domestic video cameras which meet those criteria, while many also offer portable VCRs intended for on-themove, outdoor video photography. The proportion of VCR owners with a video camera is still quite modest but, even so, video camera users are becoming a familiar sight at outings and holiday resorts.

Their number would probably be higher if it were not for the fact that many still regard a video camera as a rather daunting and mysterious piece of equipment. In fact, it need not be so for

MAJOR OPERATING CONTROLS AND THEIR FUNCTIONS 1) Auto Focus Switch--24 Auto/Man Button -23 Accessory Shoe 2 Ultrasonic Horn_ 22 EVF Display Controls 3 Boom Microphone-Remote Connector 20 Indoor/Outdoor Switch VTR Start/Stop Switch -(19) White Balance Switch Handle Strap 18 Colour Adjustment Adjusting Lock Pivot Knob AGC ON/OFF Switch Adjustable Handle Grip 16 Iris Close/Auto/Open Adjustment Focus Ring 15 Zoom Speed Switch Zoom Ring 14 VHS/VTR Lens Connector Compatibility Switch (on the bottom) 12 Auto Focus Connector 13 Fade In/Out Switch

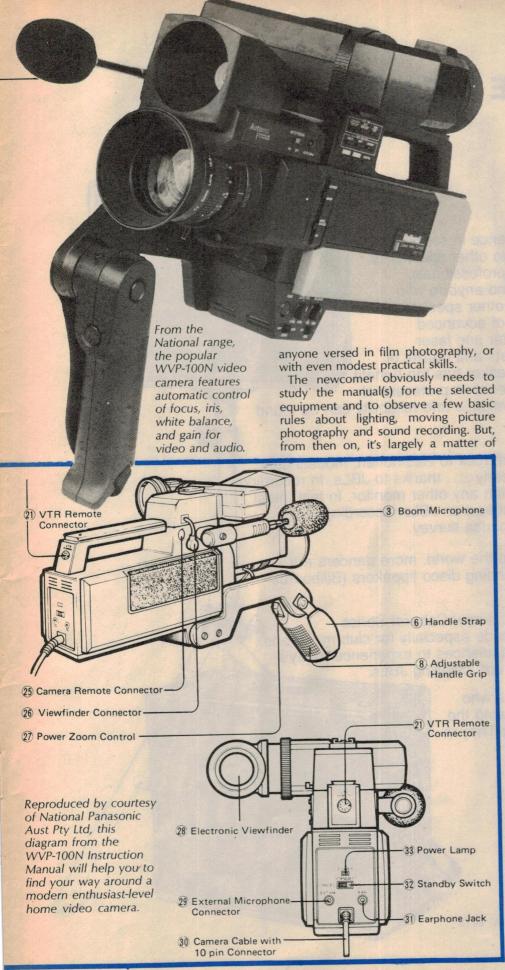

learning by doing. The great advantage of video photography is that one can practice for hours on end, with all manner of subjects, without wasting film and at virtually no extra cost.

But let's look at the actual equipment. Virtually all present-day home video cameras depend for their operation on a miniature evacuated camera tube, identified by a variety of copyright trade names but essentially a descendant of the original Vidicon, first used in the '50s. Even the very latest Sony/Sanyo/Toshiba "Betamovie" uses an "SMF Trinicon" tube, while the National WVP-100N, mentioned later, features a "Saticon".

Concerted efforts are being made throughout the industry to develop a solid state equivalent — eg a CCD or "charge coupled device" — but with only limited success so far. When they do become fully competitive, as they inevitably will, they should offer a significant advantage in terms of space, weight and current drain.

In the meantime, camera tubes themselves are being progressively refined, with smaller dimensions for a given order of resolution, reduced "drag" with bright moving objects, improved colour rendition, and higher effective sensitivity.

A couple of years back, manufacturers were happy enough to quote a minimum illumination figure of 100 lux (10 foot candles) equivalent to a room with fairly subdued lighting. One half or even one third of that minimum figure is now fairly commonplace and, while video photography at such light levels may not be the best, occasions can arise when the extra sensitivity would make the difference between a picture or no picture.


The camera tubes in current models typically have an image electrode or "target", on which the desired scene is focused, with a nominal diameter of between 12 and 17mm — a startlingly small figure when it is realised that the tiny image may ultimately be viewed on a screen having an equivalent corner-to-corner "diameter" of at least 63cm.

Even so, with a resolution rating of 300 lines in the centre of the picture, the detail available from a modern home video camera compares favourably with that from typical VCRs and, for that matter, from a fair proportion of the film prints broadcast by TV stations.

The optical system required to capture and focus the image is reminiscent of what is commonly found in an enthusiast-level 35mm film camera or a home movie camera. The same expressions appear in the literature: lens mounting, aperture, focal length, focus system; zoom and macro facilities; illumination requirements, colour temperature, filter diameter, and so on.

- WHERE THE MUSIC HAPPENS

Whenever and wherever excellence in sound is essential, JBLs are essential. No other speaker is good enough for top recording professionals, performing musicians on tour and anyone who listens for a living. Because no other speaker is created with JBLs combination of advanced design, high-technology computer and laser research, extensive listening tests and quality of craftsmanship. And no other speaker has the benefit of over three decades of experience in professional sound. The JBL heritage of excellence and reliability can be found in a wide variety of applications.

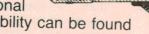

At outdoor concerts ranging from rock to Beethoven, thousands of listeners can hear the artists clearly . . . thanks to JBLs. In recording studios, you'll find more JBLs than any other monitor. In fact, most major albums are mixed or mastered on JBLs, according to a recent Recording Institute of America survey.

Under the lights at discos around the world, more dancers are moving to JBLs . . . by far the leading disco speakers (Billboards International Disco sourcebook).

Nightclub performers rely on JBL's new Cabaret Series loudspeakers — the first JBLs made especially for club musicians Theatre owners who want their audiences to experience today's great new multiple sound tracks are installing JBLs.

And serious musician/songwriters who rely on home recording are following the lead of the big recording studios: They're turning to JBLs, too. Wherever excellence belongs, you'll find JBL.



When JBL plays, everyone listens.

DISTRIBUTED BY harman australia pty. ltd.

Unit A2, 6-8 Byfield Street, North Ryde. Postal Address L.M.B. 12, North Ryde, N.S.W. 2113 Telephone: (02) 887-3233. Telex AA2487



HOME-VIDEO CAMERAS

To many photographic enthusiasts, this will have a familiar ring, as will the list of optional extras available for the more pretentious models: large ratio zoom, supplementary lenses, filter kit, film/slide copy adaptor, remote controls, tripod, etc — gadgets for the enthusiast to delight in, pay for and carry around!

Budget model home video cameras are most commonly provided with a TTL (through the lens) or other optical viewfinder, with appropriate provision for manual focusing, as in a normal film camera. However, while an optical viewfinder does show the scene in natural colour, it gives no clue to the operator as to the quality of the actual video image being generated and recorded.

In consequence, video cameras in the middle to upper price range now almost invariably offer an electronic viewfinder involving a miniature monochrome picture tube (30mm diag. approx) mounted behind a lift-up eyepiece. This gives the user the option of inspecting the image through a lens or viewing it directly from a few centimetres further back.

While a colour presentation might be seen as the ultimate objective — but a difficult one to achieve at this stage — a high definition monochrome image does permit critical examination of the luminance structure of the picture in terms of focus and focal range, composition, general lighting, highlights, shadows and contrast range. In practical terms, a well set up monochrome image in the viewfinder provides a fairly solid guarantee of a satisfying colour picture on the TV screen.

An electronic viewfinder has the important advantage that, without too much extra complication, it can be used to provide instant, on-the-spot replay of tape that has just been recorded. A video photographer can therefore check on what he/she has taken before packing up and moving off to the next point of interest.

No less importantly, the tape can be reset to a particular point, in preparation for the next shot, as an aid to good presentation of successive scenes — in short, for on-the-spot "assembly" or "serial" editing.

In an advanced design, an electronic viewfinder can also carry graphics to indicate to the user the status of the camera or VCR — in lieu of the more usual array of coloured LEDs. Graphics such as date and time may even be



Accessories to quicken the pulse of any video enthusiast. At top left is a film/slide copying lens, complete with holders (below). At top centre is a 12X power zoom and, immediately below it, a 1.5X tele converter lens. At the top right is an extension lead for remote camera control and viewfinder. Below it is a filter kit for novel optical effects. At the bottom left is an arrange control unit for the associated VCR.

displayed for ultimate inclusion in the video image.

During the past year or so, a number of home video cameras have appeared on the market featuring fully automatic focus, involving either infrared or ultrasonic technology. Both methods work well in the majority of situations and it is a real boon to be able to forget focus and be free to concentrate on other things. The automatic function can be disabled to cope with special requirements or to conserve battery power when the focus can be left set for long periods.

To scan the scene on the target electrode of the camera tube, all home video cameras, these days, have their own in-built field and line timebase circuits, which deflect the scanning beam within the camera tube and ultimately provide standard field and line synchronising pulses for the associated equipment: VCR, monitor, receiver, etc.

The provision of reliable time base/scanning/sync circuitry in any form posed a major problem in the valve era, and remained a difficult one, even with discrete transistors. The development of suitable special-purpose ICs has made all the difference in terms of cost, compactness, reliability and economy of current drain.

Much the same observation applies to the highly complex circuitry which is necessary to process the pulses from the camera tube into orderly luminance and chrominance information and to assemble it, along with the synchronising pulses, into a standard PAL format video signal.

In the process, the video circuitry reacts to the incoming light level and opens or closes the iris diaphragm in the lens system accordingly. It monitors and controls the video signal levels and facilitates compensation for the colour temperature of the light. Some cameras provide supplementary user controls for hi/lo light levels, indoor/outdoor shooting, incident or back lighting, etc, but control of the video signal is, for the most part, automatic.

In fact with automatic focus, white balance, iris and exposure control, and automatic level control for the microphone, some cameras are getting quite close to the stage where they can operate on a "point-and-shoot" basis.

The sound pick up provision in a home video camera is normally fairly basic and distinct from the video circuitry. It usually involves a directional electret microphone, mounted in the front of the camera body, or on a short telescopic support which extends to about level with the front of the lens.

A microphone attached to the camera is fair enough for recording incidental environmental sound but leaves much to be desired for recording voices to match anything but a close-up shot. For this reason, many cameras also have provision to plug in an external

microphone, which can be positioned closer to the source of the sound.

Home video cameras normally require an external power supply source, typically 12V DC at around 0.5A for normal operation and somewhat less in standby modes, where such apply.

With a portable video system, the camera normally picks up its supply from within the VCR, via the same multi-lead cable and plug which carries the video, audio and control circuitry. The system as a whole may then typically operate from a rechargeable battery pack, from a 12V DC car or boat electrical system, from an in-built AC power supply, or from a separate AC mains supply/charger unit.

A few mains-powered domestic VCRs also provide for a camera with a multipin socket and internal power supply, but most simply have "Camera Input" and "Camera Remote" sockets for video in and remote pause control, plus a Camera/Tuner selector switch. In such cases it is normally necessary to purchase a matching external camera supply/adaptor, which plugs into the mains and operates between the camera and the VCR.

In practice, a video camera coupled to a non-portable domestic VCR is rather limited in its uses, even when an extension camera cable can be provided. It makes good sense, in such a case, to choose a fairly simple, inexpensive model.

For portable or on-the-move video photography, the considerations are much the same as for film photography. Some will prefer a simple, uncomplicated camera, for minimum hassle, even though it may impose a few compromises. Many, however, tend to take the reverse view on the grounds that, if they are going to take up video photography, they may as well do it properly!

But, whatever your ideas in this respect, check carefully through the available range of cameras. Note whether the facilities they offer match your needs, and whether the user manual adequately explains those facilities. If a particular model appeals to you, hold it in the taking position for 10 minutes while you are talking and note whether it is beginning to feel heavy and awkward. Make sure the viewfinder is right for your good eye, and so on.

And, last but not least, favour a model which carries the same brand name as your VCR, or is specifically recommended by a manufacturer as being fully compatible. One of the most frequent complaints heard in the industry is from enthusiasts who have tried to use this camera with that VCR, on the vague assumption that "she'll be right mate". The problem is that, when a discrepancy



Controls for the viewfinder and onscreen display, reminiscent of VCR programming.

is enountered, it is difficult to find anyone in a position to identify it readily and correct it.

Against this general background, we suggest you spend a while studying the diagrams herewith of a typical modern home video camera — the National WVP-100N. We selected it because it has proved a "best seller" since its release earlier this year and it is well endowed with features to illustrate what we have been talking about.

We suggest you break off here, for a few minutes, to study the accompanying diagrams, as a substitute for being able to handle the real thing.

In the Instruction Manual, each point is keyed by the numbers to an explanatory paragraph but it is not practical to reproduce it all here. However, a few points warrant special comment:

The ultrasonic transmitter/receptor for auto focus is shown at (2). It can be disabled by switch (1) but even in the manual position, the lens can be refocussed quickly and automatically by briefly pressing button (24). Most auto focus systems have this handy feature,



A group of picture-taking controls. The Iris knob allows compensation for very light or dark backgrounds.



On the rear of the camera, the Standby switch and provision for external mic and monitoring earphone.

which helps conserve battery power in the field.

The lens (4) is a 6:1 power zoom (12.5mm to 75mm at F1:4) which is typical of current model home video cameras. The two-speed zoom (six secs and 10 secs) is a refinement, as also is the provision for interchanging lenses and the use of special effects filters, tele conversion lens and film/slide copier, as illustrated.

In addition to providing automatic edit—an instantaneous noise-free change from scene to scene—switch (13) produces a smooth fade out/fade in transition between scenes for both video, and audio. It is a pleasant alternative but one that should be used sparingly. Overdone, it can become as tedious as too frequent use of the zoom.

Switch (20) presets the camera colour circuitry to suit ambient light temperatures of 3200°K for typical indoor photography or 5500°K for outdoor shots. Any further correction for colour balance is performed automatically by operating switch (19).

The EVF (electronic view finder) controls can be used rather like the time set controls in a VCR to set the date and a stopwatch timing function in minutes (up to 60), seconds and tenths of a second. These can be superimposed on the tape image, for noting lap times, etc. A dozen or so cues (displayed but not recorded) have to do with the status of the system: eg battery condition, light level, white balance, auto focus off-on, etc.

Socket (21) provides a connection for the on-camera VCR remote control unit, which slides into position on top of the handle.

Sockets (25) and (26) accommodate the extension lead for remote control of the camera and remote viewfinder — good for special situations like bird photography, where the operator needs to remain out of sight.

At one stage, we had it in mind to round off this article with a full review of the WVP-100N camera but we simply ran out of time and space. To review a camera properly, one really needs to use it in a variety of planned situations, under a variety of lighting conditions, not only to see how it performs, but how acceptable it is in terms of handling and control.

The best we could do at the time was to use it around the home, taking shots of shrubs and spring flowers, zooming in on individual blooms, and cutting to whatever else offered — garden birds, low-flying planes, passing cars, pedestrians and their pets!

The automatic focus and power zoom handled all this without the slightest

Continued on p.23

NERRY CHRISTMAS FROM MAGRATHS



DOUBLE SIDED DOUBLE DENSITY 80 TRACKS PER SIDE

1.0M BYTES UNFORMATTED

KIT SUPPORT FOR THE MICROBEE

EPROM PROGRAMMER

Versatile, low cost and easy to build. Plugs straight into the microbee 1/0 port. Suitable for 2716, 2732, 2532, 2732A and 2764 Eproms. Burn your games programmes and eliminate cassette loading time. KIT FEATURES Sockets for all other IC's 1 x 2716 supplied - get started straight away. Front Panel and Mains (SEC approved transformer 28 pin and 16 pin wire wrap sockets to flush mount personality plugs (2 included) and ZIF socket (included) DB 15 Plug. Complete to last nut and bolt.

K9668 \$55.00

RADIOTELETYPE DECODER

Display RTTY encoded messages on your video Monitor. Receive up to date weather information, International News before the Papers, all sorts of coded military info. Simple circuit uses PLL techniques Single PCB Construction. Kit includes DB15 Plug and backshell for connection to microbee. Shielded pretinned PCB



MAGRATHS PRODUCT OF THE MONTH DIGITAL MULTIMETER

% and 0.25% Basic DCV Accuracy Overload Protected on All Ranges 2,000 and 200 Hour Battery Life Current Ranges to 10 Amps Hi-Lo Volt Resistance Tests Rugged construction 26 Ranges 31/2 Digits

Low Cost

MICROBEE LIGHT PEN

AT LAST—a light pen for the Bee. This pen works in the low-resolution graphics mode and connects directly to the 1/0 port

* Complete kit including DB 15+2m CORD

* Fully documented with software example.

PERSONAL CONTACT WITH YOUR BEE!

K9673

99.50

This project allow you to decode the signals of shortwave stations, transmitting radio facsimile weather maps, satellite pictures etc and then reproduce them on your dot-matrix

- lete kits of parts includes DB15 Ribbon Cable
- SOFTWARE LISTING

24.50



TEST C	LIPS
14PIN	\$7.00
16PIN	\$7.34
16PINLF1	\$13.80
18PIN	\$15.43
20 PIN	\$17.68
22 PIN	\$19.65
24 PIN	\$20.33
20 DIN	\$22 44

\$29.85

MULTIPROM INTERFACE FOR THE MICROBEE

*44K OF PROGRAM STORAGE * FULLY SOFTWARE SELECTABLE * SUITS BOTH IC AND PLUS MACHINES *8 OUTPUTS FOR CONTROL APPLICATIONS*

ational new kit for the MICROBEE, requires n A sensational new kit for the MICROBEE, requires no modification to the computer except for the fitting of a 50 pin expansion socket. This project is easy to build and will allow you to store and software select up to 44f of eprom storage—acts like a mind idsk drive system with the speed of RAM. Extra units may be added to further increase storage.

- Full set of IC sockets
 Double sided, plated through board
 Assembled connection lead to Microbee
- Fully documented
 Cassette monitor included
- (plus sourcefile)

THE MICROBEE KIT OF 1983

STEREO SYNTHESIZER FOR VCR'S AND TUNERS

Synthesize realistic stereo from virtually any monophonic source by simply connecting this unit between the source and your stereo amplifier.

- Quality Phillips MN3001 (not second source dropout).
- Selection of either source via front panel switch.
- Normal or stereo sound selection.

 Provision for 2 different signal sources
- Complete kit includes all hardwear, cables etc., even solder.

K5810 \$55.00

REGULATOR 0.40 Volts @ 5 Amps – that's 200 Watts Current limiting 0.5 Amps variable

- Specifications Second to None Free from the hum and noise sometimes
- associated with other techniques.

A PROFESSIONAL SUPPLY

K3325

ALL PRICES INCLUDE SALES TAX

YOUR GAMES WILL NEVER BE THE SAME

A computer music synthesizer that is easy to build and easy to use, connects to any computer with a Centronics-style parallel port and provides music over a five octave range and a wide ariety of sound effects.

COMPUMUSE

*EXPERIMENTAL KIT-PCB, COMPONENTS & SOFTWARE

26.50

KITS

SOUNDBENDER RADIO MICROPHONE ELECTRONICIGNITION \$31.88

MICROBEE EPROM PROGRAMMER \$52.96 \$91.39 NEGATIVE ION GENERATOR \$39.28

SUPER BARGAINS AT



4 independently switched power outlets

Day of week. Calculator-type key entry for 4 independently switched power outlets.

Equipped with a programmable computer which can switch four power outlets independently to control most appliances up to 10 amps. The computer is programmed via a calculator type key entry facility to perform up to 20 daily or weekly switching functions.

Ideal for both home and industry, the Bosch Digitimer DT201 can be used for:

- Shop Window Lighting.
- · Radio/Hi-Fi.
- Electric Blankets
- Air Conditioners and Heaters.
- Most Kitchen Appliances.

MAGRATHS ELECTRONICS Phone or Mail. 55 A'BECKETT STREET, MELBOURNE, 3000 Tele (03) 347 1122, Telex AA31001 | borkere

Prices subject to change without notice.

welcome here

S

X

PARABOLIC MICROPHONE

Build a low cost parabola, along with a high gain headphone amplifier to help when listening to those natural activities such as babbling brooks, singing birds or perhaps even more sinister noises. The current cost of components for this project is around \$15 including sales tax, but not the cost of batteries or headphones.



TV PATTERN GENERATOR

KITS

X-S

KITS

KITS

\$20.00

Make sure your TV is up to the mark with this low cost Pattern Generator which uses just seven ICs and gives three patterns: Dot, crosshatch and blank raster. The current cost of parts for this project is approximately \$25 which includes sales tax but not the cost of a modulator or 9V mains plugpack.

EA NOVEMBER '83

\$41.50

83

MAY



ETI-268 NICAD FLOAT CHARGER

\$9.00 ETI MARCH '83

Keep your NiCad batteries in tip-top condition with this cheap, simple charger



ETI-1512 **ELECTRIC FENCE** TESTER

\$24.50

ETI FEB '83


No more checking the 'feel' of a fence with a blade of grass (and maybe ending on your . .). This project tells you how much your fence energiser delivers and can be used fault-finding on a fence.



ETI-1516 MODEL ENGINE **IGNITION SYSTEM**

ETI JUNE '83

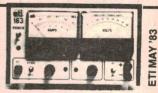
Get sure starts every time and no more glow plug burnouts on your model engines.



ETI-163 LAB SUPPLY

\$159

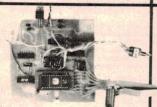Fully variable 0-40 V current limited 0-5 A supply with both voltage and current metering (two ranges: 0-0.5 A/0-5 A). This employs a conventional series-pass regulator, not a switchmode type with its attendant problems, but dissipation is reduced by a unique relay switching system switching between laps on the transformer secondary.



MICROBEE EPROM PROGRAMMER

ETI FFR '83

Simple, low cost programmer for the MicroBee can program 2716s, 2732s and 2764s.



ETI JUNE '83

ETI-153

Can measure temperature from -50°C to +150°C. It simply plugs into your multimeter—great for digital multimeters. Accuracy of 0.1°C resolution of 0.1°C.



ETI-323 HEADLIGHT \$17.50 **DELAY UNIT**

Park your car and turn off the lights. Can't see where you're going? Press the button and the headlights come on to light your way, switching off automatically after 50 seconds. This is a simple, easy to build, low cost project




ETI-1515 DRILL/BLENDER SPEED \$27.50 CONTROLLER

This project provides a full range of speed control for appliances having universal ac motors. Once the speed is set, the motor will maintain heavy-load. Great for drills, blenders, grinders, etc.



ETI-162 30 V/1 A FULLY PROTECTED POWER SUPPLY \$47.50 ETI DEC '83

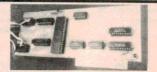The last power supply we did was the phenomenally popular ETI-131. This low cost supply features full protection, output variation from 0 V to 30 V and selectable current limit. Both voltage and current metering is provided



ETI-654 APPLE II ANALOGUE/DIGITAL INTERFACE

\$159.00 ETI MARCH '83

This project will give your Apple a set of 8-bit digital inputs and outputs plus one analogue input and one analogue output. Applications include: driving a robot, recording science experiment results, etc. (digital only shown)



\$47.50 ETI JUNE '83

Every digital workshop should have one! Can be used to program the popular fusible-link PROMs like the 74S188/288. 82S23 and 82S123



ETI-461 GENERAL PURPOSE BALANCED \$20.00 INPUT PREAMP ETI DEC '83

This project can be used as a balanced mic amp. with low impedance input, a low or high impedance input differential amplifier or a balanced input instrumentation amplifier.



ETI-164 ZENER TESTER

\$9.50 ETI MAY '83

A simple, low cost add-on for your multimeter. This checks zeners and reads out the zener voltage directly on your multimeter. It can also check LEDs and ordinary diodes.



ETI-334 AUTO TESTER \$17.00 ETI JAN '83

Just the thing to keep in the glovebox or toolkit to find those nasty electrical bugaboos that occur at awkward times. Simple to build, simple to



ETI-335 PUSHBUTTON-PROGRAMMABLE WIPER CONTROLLER

\$28.50 ETI MARCH '83

No more fiddling with knobs and not getting the delay between wipes that you want—this windscreen wiper controller is simply 'programmed' with two pushbuttons to provide the wiping delay you need



RADIOTELETYPE CONVERTER FOR THE MICROBEE

Have your computer print the latest news from the internation shortwave news service. Just hook up this project between your shortwave receiver's audio output and the MicroBee's parallel port. A simple bit of software does the decoding. Can be hooked up to other computers too. 83

48-50 A'BECKETT ST, MELBOURNE 3000 VIC

PHONE (O3) 347 9251

ROD IRVING ELECTRONICS 425 HIGH ST. NORTHCOTE 3070 VIC. PHONE (02) 480 813

VIDEO ENHANCER VIDEO ENHANCER ENHANCE

Like tone controls in a hifi amplifier, touch up the signal with this Video Enhancer.

EA OCTOBER 83

\$35 NAIL FINDER

Essential for the home handyman the Nail Finder will help locate timber studs behind Gyprock or plasterboard wall surfaces as well as locating pipes and wiring buried in walls.

EA OCTOBER 83


\$10 SPEED SENTRY

EA OCTOBER 83

Paying speeding fines can be a painful business. Build this Speed Sentry and avoid further pains in the wallet.

TRANSISTOR TESTER

S15

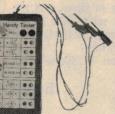

Have you ever desoldered a suspect transistor, only to find that it checks OK? Troubleshooting Trouble shooting exercises are often hindered by this type of false alarm, but many of them could be avoided with an "in-circuit" component tester such as the EA Handy Tester.

SOIL HEATING UNIT

\$70



A little heat applied to the soil using this device may just do the trick.

WATTMETER

\$65

\$11



The unit described here will measure the power consumption of any mains appliance with a rating up to three kilowatts. It makes use of a special op amp called an "output transconductance amplifier" or OTA, for sebort. for short.

EA SEPTEMBER 83

CAR ALARM

EA SEPTEMBER 83

\$29.00


This Car Alarm uses the battery earth strap as a sensor to detect when a "courtesy" light or other electrical load occurs when a thief enters a vehicle. The circuitry is simple and immune from false triggering problems. ETI July 81




10-15V **EXPANDED** SCALE V-METER

ETI 159 December 81

\$26.50

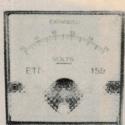

CORE BALANCE RELAY ETI 567

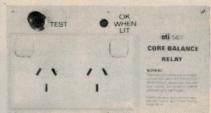

S44.50

WHEATSTONE BRIDGE \$45



Mains-operated equipment that goes faulty is potentially lethal. Electro-mechanical "core-balance relays" which sense earth-fault currents and trip a circuit breaker have been available for house-mains installation for some years. Portable core-balance relay units have obvious advantages. Protect yourself - and your equipment - with this simple, inexpensive project.

VIDEO AMPLIFIER

\$15



FA AUG 83

Bothered by smeary colours, signal beats. and RF interference on your computer display? Throw away that cheap and nasty RF modulator and use a direct video connection instead. It's much better.

The Video Amplifier features adjustable gain and provides both normal and inverted outputs. Power is derived from a 12V DC plugpack supply.

±12V RAILS FOR LAB **POWER SUPPLY**



EA July 1983

\$13

An inexpensive addition to the 50V 5A Lab Power Supply which should prove its worth many times over. It provides additional fixed ±12V outputs for lower power applications.

FRIDGE DOOR ALARM



When the refrigerator door has been left open for about 20 seconds — or, more correctly, when the light has been on for 20 seconds — this EA Fridge Alarm will emit a series of reminder beeps until the culprit closes the door

EA July 1983

S9 FOR PCB VERSION

Portable 31/2 Digit **Heart Rate Monitor**





Here is a new heart rate monitor designed specifically for use by the dedicated fitness seeker. Small enough to carry when jogging or exercising, it features an optical sensor, no electrical connections to the body, an in-built calibration circuit, and direct readout on a large liquid crystal display (LCD).

Driveway Sentry





Activated by your car's headlights, the "Driveway Sentry" will turn on a driveway or garage light so that you can make a safe exit from your car on the darkest of nights. At the end of five minutes, it will automatically turn the light off again.

EA GUITAR BOOSTER

\$17.50



48-50 A'BECKETT ST, MELBOURNE 3000 VIC

PHONE (O3) 347 9251

BETAMOVIE Will this revolutionary

After months of speculation, the new "Betamovie" combination video camera/recorder was unveiled recently at Sydney's Regent Hotel. We were able to inspect it, handle it and also to learn something of its basic technology from an engineering paper made available to us by the Consumer Video Division of the Sony corporation.

While developmental single-unit camera/recorders have been talked about for some time. Betamovie is the first such unit to be released commercially to home video buyers. It went on sale in Japan and the USA in May, and is scheduled for release in Australia in the CCIR (PAL) format during the current month.

The function in Sydney was jointly



home video camera/recorder establish a new trend?

sponsored by Sony, Sanyo and Toshiba, indicating that all three companies see Betamovie as a significant breakthrough and an opportunity to advance the claims of the Beta system as a whole.

While the occasion provided an opportunity for many of those present to see and handle the new cameral recorder for the first time, the actual announcement surprised no one. Over the past year or so, technical journalists around the world have been able to piece together the basic concept of Betamovie from a variety of sources. They already knew that:

It would be a single-unit video camera/recorder, comparable in size and weight to existing high-performance, conventional home video cameras. (At 2.48kg without battery, Betamovie does indeed invite comparison with the WVP-100N discussed elsewhere but, at the same time, it gains portability at the expense of desirable video

production facilities).

It would be completely self-contained and capable of immediate use without external cables or attachments. (It certainly can function independently but provision has also been made to operate it in conjunction with an AC mains adapter, a car battery cord, a high capacity battery belt and an external microphone).

It would use standard Beta cassettes and signal format and offer a maximum recording time of 215 minutes from an L-830. (It does, although the recording time from a single battery in the handle is limited to about 60 minutes. Beyond that, as with other portable systems, recharging, or a back-up battery or other supply is necessary).

It would perform recording only. For playback, the cassette would have to be plugged into a normal Beta domestic VCR. (As demonstrated, Betamovie is indeed a single-function unit. It can record successive scenes without noise breaks but it has no facilities for on-the-spot rewind,

Would the said viewfinder be an electronic type, involving a miniature, high-definition colour picture tube? If so, it would be a breakthrough indeed. In fact, the viewfinder turned out to be a normal optical TTL (through the lens) system, possibly influenced by a consideration that became apparent later.

However, what proved really intriguing was talk of a smaller diameter video drum and a single video head — particularly in view of statements that Betamovie provided a completely standard Beta format signal on the tape. It seemed almost like a self-contradiction and, at the time, Sony executives in Australia appeared to be as much in the dark as we were as to how it had been accomplished.

In all domestic VCRs, to date — Philips, Beta, VHS — the tape has been wrapped obliquely more than half-way round a rotating drum or plate carrying two (or more) record/playback heads, set 180°

apart. (See Fig. 1).

In the Record mode, the heads write alternate magnetic tracks obliquely across the tape, each track containing (nominally) the total information from the respective odd and even fields: 262.5 lines per field in the case of the NTSC system, and 312.5 for CCIR/PAL. In fact, each head remains active for a few extra lines, providing a deliberate overlap, such that line information just ahead of the vertical sync block is fed to both heads and recorded simultaneously — at the end of each field scan and the beginning of the next.

During playback, head switching occurs during this overlap period, minimising the risk of the video system being left even momentarily without

signal due to a timing error.

When trying to envisage a single head system, an obvious difficulty is that no one head, or dual head structure, can be in two places at once — at the finish of one helical scan and the start of the next — let alone provide the overlap required for a standard Beta signal format. Hence the apparent contradiction, which remained unresolved until we sighted the design paper by Seiji Sato, Koichi Takeuchi and Masanobu Yoshida, from the Consumer Video Division of Sony.

In their paper, the three authors begin with the assumption that, to take advantage of the already modest size of the standard Beta cassette, it was




BETAMOVIE

essential to simplify and reduce the overall dimensions of the tape traverse mechanism, beginning with the video drum itself. The whole Betamovie concept really depended on that proposition and it therefore became the starting point for the new design.

Since the length of the helical scan had to conform to the existing standard, the drum size could certainly not be reduced by more than 2:1. But that would not be practical, anyway, because the need for tape feed and take-up guides must limit the tape wrap to less than 360°. To accommodate the necessary wrap length, the new drum would therefore have to be more than half-size.

Calculations suggested that the best mechanical compromise would be a drum circumference (therefore diameter) of about three-fifths of normal, with an active recording/playback traverse of 300° and with the feed and take-up guides located within the remaining 60°. (See Fig. 2).

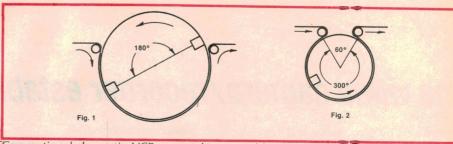But that led to the natural and awkward question: how to cope with the 60° gap and the time interval when the head is not even in contact with the tape? How could the video signal



Conventional domestic VCRs wrap the tape obliquely more than half-way round a rotating drum carrying two record/playback heads set 180° apart (Fig. 1). To reduce the size of the tape transport, Betamovie uses a smaller drum with an active record/playback traverse of 300° (Fig. 2).

possibly be continuous in those circumstances?

Without seeking to explore all the detail set out in the design study, the method which was devised to get around that formidable problem can be summarised as follows:

INCREASE THE LINE RATE: Leaving the frequency of the vertical timebase unchanged, increase that of the line oscillator by a factor of 360/300 (1.2 times). For the NTSC system, this results in 60 fields, each of 315 lines; for the CCIR system, the figures become 50 fields, each of 375 lines.

OVERSCAN THE WANTED IMAGE: Arrange for the camera tube to overscan vertically by the same ratio (1.2 times), such that the number of scanning lines actually involved in the presentation of the wanted scene remains at (nominally)

262.5 per field for NTSC and 312.5 per field for CCIR.

SELECT THE VIDEO DRUM DIAMETER: The video drum spins at 60 or 50 rev/sec, being locked to the field frequency of the particular system. However, the diameter (therefore circumference) of the drum is selected such that the head writes a full-length Beta format track across the tape during the 300° sector. This represents 300/360 or 83% of the vertical scan period and the time required to record just the appropriate number of lines for the respective systems (nominally 262.5 for NTSC, 312.5 for CCIR).

SET THE TIMING: Arrange the timing so that the group of lines retained from each field are those actually involved in the presentation of the wanted scene, as depicted in the viewfinder. The 17% of

STOP WASTING TIME TESTING BOARDS

MD will pin-point microtroubles in seconds. Portable and simple to use by non-technical staff in the REPAIR SHOP or on the PRODUCTION LINE. MD tests ROM, RAM & I/O and prints diagnostic reports. MICRODOCTOR can be plugged into an unknown system to perform a general diagnostic and print a MEMORY-MAP.

The ENGINEER may enter sequences of CHECKSUMS and RAMTESTS. READS and WRITES to specific MEMORY and I/O locations. SHORTING tests on DATA and ADDRESS LINES. PRINT-OUTS of memory in ASCII or HEX. These sequences are retained in CONTINUOUS MEMORY, available always at the push of a key.

* FREE Z80 DISASSEMBLER with each MD (other disassemblers soon to retrofit at low cost). Get a DISASSEMBLER LISTING of ROM in any microsystem!



MICRODOCTOR - \$595.00

Z80 DEVELOPMENT SYSTEM

MENTA puts out a TV PICTURE of memory in hexadecimal. The 40 key keyboard will accept inputs, both in hexadecimal and 280 mnemonics; there is a quick cassette data storage system, a powerful editor which permits program debugging by showing contents of registers and stack. Also there are 24 bits of I/O for external control. A Z80 disassembler is also available which outputs to any RS232 device such as a printer or terminal. MENTA was designed as a low-budget device for teaching microprocessing in schools: professional course-material is available to teachers together with add-on boards for a variety of control functions and robotic applications.



MENTA — \$249.00

INTELLIGENT EPROM PROGRAMMER

Good tools need not be expensive. SOFTY 2 is the latest version of the engineer's favourite EPROM HANDLER for anybody who uses 2516, 2716, 2532 and 2732 EPROMS. SOFTY will program any of these EPROMS or copy any type into another.

SOFTY puts out a TV picture of memory contents, with many code-manipulating and editing facilities. There is also a fast cassette data storage system. SOFTY is also a ROMULATOR (a lead is supplied which may be inserted into a board under development to emulate the ROM using SOFTY's internal RAM. This procedure can also be used on the single-chipper piggy-back type MPL.) SOFTY is complete in itself as a PRODUCT DEVELOPMENT SYSTEM. Code may be entered in HEXADECIMAL via the keyboard also SERIAL and PARALLEL inputs and outputs allow downloading of object code from your computer or printing EPROM contents on your printer.




SOFTY 2 - \$379.00



ELECTRONICS

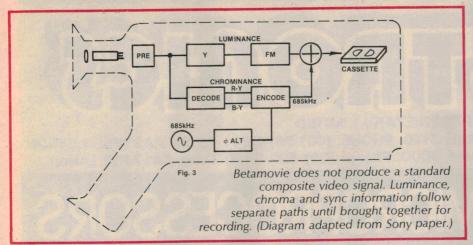P.O. Box 311, Castle Hill NSW 2154. Ph. (02)634 7597.



lines lost during the 60° sector are the overscan lines, not required anyway.

Implicit in the foregoing paragraphs are a number of interdependent calculations involving the precise drum diameter (therefore its peripheral speed relative to the moving tape), the required drum inclination relative to the tape path, the modifying effect of the foreshortened writing period, the head gaps, &c — all essential to ensure that the track as recorded conforms to the system standard.

Just to make things more difficult for themselves, the engineers responsible sought (successfully) a set of figures which would allow them to use the same mechanical components for the NTSC and CCIR version.

Allowing for a few difficulties in Japanese/English expression, the paper by Sato, Takeuchi and Yoshida explains and presents the mathematics behind the foregoing summary and proceeds to further observations about the signal itself.

They point out that, when multiplied by 1.2, the number of lines per frame becomes even and the fields lose the half-line relationship appropriate for an interlaced system. However, the physical distance between the two gaps in the double azimuth head creates a 1.5-line displacement between the alternate fields, anyway, and this can be juggled to the appropriate inter-field relationship by the use of a suitable delay line.

This done, they say, head replacement becomes a relatively simple matter, without the need to adjust two heads critically, relative to each other, on opposite sides of a conventional drum.

They also point out that the amount of signal processing required in a combination camera/recorder is much less than in two separate units: video camera and VCR.

In the latter case, filter and mixer circuits are required in the camera, in order to bring the luminance, chrominance and sync signals together into a composite output signal in the

standard NTSC or CCIR format. Yet, in the VCR, the composite video signal has to be taken apart again, involving the use of comb, low-pass and band-pass filters, plus a delay line, before being modulated on to carriers for recording.

In Betamovie, the need for double, complementary processing is obviated. Luminance and chrominance signals from the camera section, plus sync information can follow separate paths along internal wiring before being finally brought together for recording — a rationalisation that must confer its own advantages. (See Fig. 3).

Against this, however, is the fact that, nowhere inside Betamovie does there exist a standard NTSC (or CCIR) video signal. The scanning circuits operate at line frequencies 1.2 times normal, there is 17% vertical overscan beyond the picture limits and at no stage are the components brought together into a standard composite signal. Only when the cassette is replayed on an entirely separate VCR does a standard NTSC or CCIR signal become available.

This being the case, Betamovie is basically unsuitable for use with any kind of monitor and, as mentioned earlier, it is probably a contributory reason why the designers decided to opt for an optical viewfinder.

But that is, perhaps, beside the point. Betamovie does not pretend to be a general-purpose camera. It has been designed for those who profess not to like general-purpose cameras, with their trailing cables and plugs and gadgetry. They claim to want something that they can simply pick up and point and shoot.

Well, here it is, needing only a Beta VCR, ready and waiting at home, and a spare 2000-odd dollars in your cheque account.

If you fall into that category, Sony, Sanyo or Toshiba would be delighted to hear from you. What's more, you can be quite sure that the other manufacturers will be watching with keen interest also, to see whether Betamovie does look like establishing a new trend!

HOME-VIDEO CAMERAS

Continued from page 16

problem. In tact, it was quite fascinating to note how the auto focus sensed quite accurately a subject as insubstantial as the foliage of a young flowering tea tree — or should we call it a Leptospermum Lambethi? Nor did it find any problem with speeding cars: approaching, passing and disappearing into the distance.

One of the benefits of working around the home like this is that one can take the cassette inside and replay it on the spot, without having to rely on a fading

memory of the original hues.

Under normal blue sky/daylight conditions, and using the auto white balance as per instructions, the colours came up subjectively very close to the original but, with heavy cloud cover, we found it necessary to set the colour balance knob halfway towards "Blue" to keep the whites white and the greens green.

If we had a criticism of the otherwise well set out "Operating Instructions" manual, it would be that it is notably unhelpful in explaining how to cope with likely variations in daylight colour

temperature.

One observation is that, while the auto focus works very well, it keeps right on working while ever it and the camera is left switched on, pictures or no pictures. If the system is operating from an external supply, it would not matter but, for long sessions on the move, it would be essential to conserve battery power by avoiding over-use of the auto focus and power zoom and by switching the camera to standby whenever possible.

We did not actually use the date and timing functions in the practical sense, although we brought them up on the screen to judge their clarity. It is sufficient to say that the on-screen figures are very distinct and clean and the stop watch is quite as professional as you've seen off-air timing major sporting events.

What we did sense was that, after a couple of hours use, the normal shooting routines were becoming quite automatic and one-handed, with the rear of the camera resting on the shoulder. That leaves the other hand free to operate supplementary functions or to provide occasional additional support.

On the assumption that it would do equally as well the things we hadn't tried, we could readily understand why the WVP-100N has become a popular choice by video enthusiasts and a "best seller" for National, despite its "going" price, quoted to us as "around \$1399"

EURSTION GS

PROPRIETARY LIMITED

797 SPRINGVALE RD. MULGRAVE 3170. PHONE: (03) 561 5844 TELEX AA37758 LSTRON 289 Latrobe Street, Melbourne 3000. Phone: (03) 602 3499 Telex AA37758 Lstron

\$7 800K

MICROPROCESSORS

NEW: 16 BIT MICROPROCESSORS

9443 DC 9444 DC P.O.A. 9445-16 DC 141.60 ea 9445-18 DC 141.60 ea 9445-20 DC 176.46 ea 9447 DC P.O.A. 224.00 ea 9448 DC 9449 DC 102.39 ea 9470 DC 117.63 ea The Fairchild F6809 8-bit Microprocessor is an advanced, high performance member of the F6800 family. It offers greater throughput, improved byte efficiency, and increased adaptability to various software disciplines, including position-independent code, reentrancy, recursion, block structuring, and

high level language generation. The F6809 is compatible with all F6800 peripheral devices and is upward source code compatible with F6800-series microprocessors. The device is available in three frequency ranges: 1.0MHz, 1.5MHz and 2.0MHz.

O.E.M. PRICES ON APPLICATION

DEVICE 1-9 PRICE 10-49

THE RESERVE TO STATE OF THE PARTY OF THE PAR		
3850 3851 3852 3853 3854	9.60 12.75 12.00 9.70	7.50 10.90 10.10 7.50
3856 3861A 3861B 3861C	9.95 15.30 12.32 12.32	8.30 12.95 10.94 10.94
3861D 3861E 3871E	12.32 12.32 12.32 12.32	10.94 10.94 10.94 10.94
3871F 3871G 3871H	12.32 12.32 12.32 F3870	10.94 10.94 10.94 P.O.A.
F38E70.2DC F6800 F6802 F6808	55.00 4.68 8.00 4.20	43.00 3.64 6.05 3.26
F6809 F6810 F6820 F6821	12.00 3.20 2.80 2.95	8.95 2.50 2.32 2.10
F6840 F6844 F6845 F6846	5.50 12.80 12.88 35.40	4.25 9.98 9.66 26.60
		20.00

PRICES PLUS SALES TAX

The Fairchild F38E70 is c complete 8-bit micro-computer on a single MOS integrated circuit. The F38E70 is functionally identical to the F3870, except the F38E70 has 2K bytes of EPROM in place of 2K bytes of ROM. The device features 2048 bytes of EPROM, 64 bytes of scratchpad RAM, a programmable binary timer, 32 bits of I/O, and single +5V power supply requirement.




Bankcard Mail Order Welcome Please debit my Bankcard. Bankcard No. Expiry Date

Name
Signature

Prices subject to change without notice. Phone or write for quantity discounts. MAIL ORDERS: To ELLISTRONICS, 797 SPRINGVALE RD MULGRAVE 3170 Minimum pack and post \$2.00. Phone (03) 561 5844

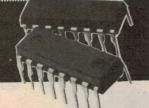797 SPRINGVALE RD. MULGRAVE 3170. PHONE: (03) 561 5844 TELEX AA37758 LSTRON 289 Latrobe Street, Melbourne 3000, Phone: (03) 602 3499 Telex AA37758 Latron



MICROPROCESSORS

The F9445 is a 16-bit microprocessor implemented using Fairchild's Isoplanar Integrated Injection Logic technology. This bipolar technology and a sophisticated pipeline architecture combine to give the F9445 very fast execution times. The processor has eight program-accessible registers and the capability of directly addressing 128K bytes (64K words) of memory. Up to 4M bytes of physical memory may be accessed using the F9444 memory management unit. The F9445 can address 62 I/O devices, handle 16 levels of priority interrupt, and perform fast direct memory access. It has control lines to provide operator-console functions and has an on-chip selftest program.

The F6800 is a monolithic 8-bit microprocessing unit (MPU) forming the central control function for the Fairchild F6800 family. Compatible with TTL, the F6800, as with all F6800 system. parts, require only one +5.0 V power supply and no external TTL devices for bus interface. The F6800 is capable of addressing 65K bytes of memory with its 16-bit address: lines. The 8-bit data bus is bidirectional as well as 3-state, making direct memory addressing and multiprocessing applications realizable.

DEVICE	1-9 PRIC	E 10-49
F6847 F68488 F6850 F6852 F6854 F6856 F6882 F68A00 F68A02 F68A09 F68A10 F68A41 F68A44 F68A45 F68A50 F68A52 F68A52 F68B00 F68B02 F68B02 F68B02 F68B00 F68B10 F68B10 F68B45 F68B50	7.27 7.36 3.10 3.50 7.95 36.00 4.80 5.36 7.39 28.50 3.65 3.20 6.78 18.41 13.35 3.10 3.11 9.07 8.20 10.20 16.57 4.12 3.60 6.95 15.10 4.05 3.54 14.99	5.65 5.72 2.45 2.20 6.15 28.00 3.75 4.17 5.75 19.85 2.67 4.88 13.60 10.36 2.30 2.60 7.05 6.30 7.85 13.80 3.40 2.98 5.50 11.70 3.14 2.95 10.20

ALL PRICES PLUS 20% SALES TAX IF APPLICABLE

PRICES CORRECT AT TIME OF PUBLICATION

PRODUCTS MANUFACTURED BY

FAIRCHILD

A Schlumberger Company

ONE OF THE WORLDS LEADING SEMICONDUCTOR MANUFACTURERS

797 SPRINGVALE RD. MULGRAVE 3170. PHONE: (03) 561 5844 TELEX AA37758 LSTRON 289 Latrobe Street, Melbourne 3000. Phone: (03) 502 3499 Telex AA37758 Latron

MITSUBISHI DISK **DRIVES**



M2896-63

Silmline 8" Disk Drive, Double
Sided, Double Density, No AC
Power Required, 3ms track to
track, 1.6 mbytes unformatted, 3ms t
80 track/side, 10" bit soft error rate.
\$485+ tax. Box & Power
Supply to suit \$95 + tax

Supply \$65.

M2894

Standard size 8" drive, Double sides, double density, 3ms track to track access, 1.6 mbytes unformatted, 77 track/side, 10* bit soft error rate.

\$485+ tax. Box & Power Supply \$95 + tax

Slimline 5¼" disk drive, Double sides, double density, 1 mbyte unformatted, 3ms track to track, 80 track/side, 5922 bits/inch, Steel

\$335 + tax. Box & Power Supply \$65 + tax

M4854

Slimline 51/4" disk drive, Double sides, double density, 96 track/inch, 9521 bits/inch, 1.6 mbytes unformatted, 3ms track to track access, 77 track/side.

\$355 = tax. Box & Power Supply \$65 + tax

MPI DISC DRIVES



B51 \$259+ tax B52 \$365+ tax **B91** \$420+ tax \$525+ tax **B92**

	THEFT
B51	\$520+ tax
B52	\$620+ tax
B91	\$POA+ tax
B92	\$POA+ tay

(to suit Tandy & system 80 etc computers) with Box & Power supplies + 20% TAX

VERBATIM VEREX

12 MONTH WARRANTY 51/4 SOFT SECTORED

\$27.50/10 +20% TAX S-Side Double Density Full Range in Stock

erex AMAZING NEW CP-80 PRINTER

TRIO CS-1560 All

 Simplified circuitry, improved performance and dependability have been successfully realized with the use of ICs throughout A vertical amplifier provides as wide a bandwidth as DC to 15 MHz, as high a sensitivity as 10 mV/div. and a low input capacitance . A sweep rate extends from 0.5 µsec/div to 0.5 sec/div in 19 ranges. Further, TV vertical and horizontal syncs are available for measuring video signals and, its x5 magnified sweep, its range of application is extremely wide • Very easy X-Y operation of high input sensitivity for Lissajous measurements . Dimensions 260(W) x 190(H) x 385(D) mm; Weight: 8.4kg



130mm DUAL-TRACE TRIGGERED SWEEP OSCILLOSCOPE





Connector CON-1 • DIP/IC

Extractor Tool EX-1

• DIP/IC Insertion Tool INS-1416 • PC Card

Guides & Brackets TRS-2

Mini-Shear with Safety Clip MS20 • 14, 16, 24 and 40 DIP PIN Sockets

Terminals WWT-1

 Tri-Color Wire Dispenser WD-30-TRI . Hobby Board H-PCB-1 • Product Catalog

WK-5 WIRE-WRAPPING KIT

Wire-Wrapping Kit WK-8 0

.54 +7.5% TAX

• AWG 30 Wire • 025' Square Posts • Daisy Chain or Point to Point • No

AX Stripping or Slitting Required
JUST WRAP • Built in Cut Off • Easy Loading of Wire
Replacement Wire Spools JUST WRAP

Wire-Wrapping TRADITIONAL Wire-Wrapping T WRAP TOOL COLOUR JUST WRAP JW-1-B (BLUE)

JW-1-W (WHITE) (YELLOW) JW-1-R (RED)

· MOS-1416 14-16 Pin IC inserter 24-28 Pin IC inserter

• EX-2

• MOS-2428 • MOS-40 36-40 Pin IC inserter • WRS-1 ANTI-STATIC Wrist Strap • PRB-1

24-40 Pin IC extractor

Digital Logic Probe Digital Logic Pulsar · PIS-WK-8 CIRCUIT TROUBLE-SHOOTING KIT



wrapping and unwrapping operations

1	Force	Wrap-	Un- wrapp	ing	Size
BW-520 BW-520-BF BW-520-U BW-520-BF-U	No Yes No Yes	Yes Yes Yes Yes	No No Yes Yes	\$196.00 \$209.31 \$225.40 \$239.43	AWG 22 Thru AWG 30



BW-630 BW-2628 RT-2628 L:W2630

BATTERY WIRE WRAPPING TOOL BW-630 and BW-2628

For .025" (0.63mm) sq post "MODIFIED" wrap, positive indexing, anti over wrapping device. Complete with Bit and

FOR AWG 30	\$46.90	+7.5%
FOR AWG 26-28	\$54.54	+7.5%
BIT FOR AWG 30	\$5.33	+7.5%
BIT FOR AWG 26-28	\$10.78	+7.5%
FOR AWG 30 and AWG 26-28	\$22.72	+7.5%
Supplied less bit and sleeve	\$27.89	+7 50/-

SEMI SPECIALS						
	2716-450 NS	S \$3.60 ea	+20% TAX			
	Z80 CPU	\$4.29 ea	+20% TAX			
	Z80A CPU	\$4.56 ea	+20% TAX			
	Z80P10	\$4.29 ea	+20% TAX			
	Z80AP10	\$4.56 ea	+20% TAX			
	Z80 CTC	\$4.29 ea	+20% TAX			
	Z80ACTC	\$4.56 ea	+20% TAX			
	Z80S10	\$12.08 ea	+20% TAX			
	Z80AS10	\$12.35 ea	+20% TAX			
	FULL RANG	GE Z80 SERIES	IN STOCK			
	BD140/139		32.5% TAX			
	BUX 80	\$3.50 ea	+32.5% TAX			
	S	OLE SGS ATES				
	AUSTRA	ALIAN DISTRI	BUTOR			

वपाठना का वि

PROPRIETARY LIMITED

797 SPRINGVALE RD. MULGRAVE 3170. PHONE: (03) 561 5844 TELEX AA37758 LSTRON 289 Latrobe Street, Melbourne 3000. Phone: (03) 602 3499 Telex AA37758 Lstron

NOW FROM



INDUSTRIES



ALSO AVAILABLE

A NEW RANGE OF COMPUTER FANS AT AN AFFORDABLE PRICE!

DESCRIPTION

OK Industries Inc., introduces a new line of Fans and Air movers to meet all applications. These dependable but surprisingly low cost fans are designed to meet any commercial or production application. All of OK's fans are of sturdy all-aluminium die-cast housings. This heavy-duty construction is built for high reliability in all environments.

The RF 180-/230 delivers up to 33 cubic feet of air per minute even with the compact size of 3\%" (79.5mm) square x 1.63" (41.5mm) slim. This compact fan is ideal for all low profile cooling applications where small size but excellent performance is required. Surprisingly light-weight.

The RF 4120-230 is a long-life high performance fan for any general cooling purpose.

Features:

• 80-105 CFM air movement. 4.70" (119.5mm) square x 1.51" (38.5mm) thickness. \$ 16 EACH

\$ 16 EACH

\$1.50 EACH

PRICES PLUS 20% S/TAX



Wire for wire-wrapping, AWG-30 (0.25mm) KYNAR® wire, silver plated, solid conductor, easy stripping.

NEW LOW PRICES

50' SPOOL 100' SPOOL 250' SPOOL 500' SPOOL 1000' SPOOL \$2.20 ea \$3.20 ea \$5.95 ea \$10.50 ea \$19.45 ea

8 colours available ex stock. Red, Black, Blue, Yellow, Green, Purple, White, Brown.

UERSA® IC INSERTION TOOLS

CIT. 820 8 to 20 pin CIT. 2428 24 to 28 pin

4.04

°4.67

22 pin

CIT. 3640 pin 36 to 40 pin \$4 QQ

NOTE PRICES PLUS 7.5% S/TAX IF APPLICABLE.

RESELLER AND QUANTITY DISCOUNTS ON APPLICATION

DESOLDERING PUMPS

DT 900

\$11.51

DT 200

\$8.09

Across the Pacific by helicopter by DON RICHARDS

—a hazardous shipboard landing

A hazardous shipboard landing formed part of Dick Smith's recent around the world solo flight in a helicopter. This is the story of that landing.

On July 22, 1983, Dick Smith landed at Fort Worth, Texas, 50 years to the day after Wiley Post arrived back in the USA to complete the first ever solo flight around the world in a fixed wing aircraft. Dick's landing marked the first ever around the world solo flight in a rotary wing aircraft (or helicopter).

In planning his round the world solo flight, Dick Smith had two main aims: first, to prove that despite the existence of fast commercial airliners there are still worthwhile aviation pioneering goals to be achieved; and second, to demonstrate the range, versatility and dependability of the modern helicopter.

The world circumnavigation was accomplished in three stages. Starting in Fort Worth, Texas, Dick crossed the Atlantic to London in the spring of 1982. The second stage, London to Sydney, was completed later that year. The last stage was set for the Northern Hemisphere summer of this year and Dick sought landing rights for refuelling in many countries: Indonesia, the Philippines, Japan, the USSR, Canada and the USA. Permission to land was granted in all cases except for the USSR. Not only was permission refused, but Dick was warned that infringement of the sensitive boundary zone between the USSR and Japan could mean being shot down without warning.

The subsequent downing of the Korean jetliner by Soviet fighters during September illustrates that last point all too graphically!

The problem was that unless a refuelling stop could be arranged between the northern tip of Japan and the American base at the western end of the Aleutians, Dick could forget about his ambition to circumnavigate the globe. The distance, over 1400 nautical miles, was beyond the range of his

modified Bell Jet Ranger. The distance is, in fact, greater than that between Australia and New Zealand - imagine flying that in a tiny helicopter!

How I got involved

The phone rang one day in early June and Dick asked me how my farm was going. "OK," I answered. "What would you like?"

I soon got my answer. He wanted me to leave the farm, fly to Tokyo, board a container vessel which would then steam to a spot off the Kuril Islands, and supervise a mid-ocean landing and


refuelling operation. He would then complete the leg to the Aleutians and I would continue with the ship to Seattle on the West Coast of the USA (having no other option!). I would also keep continuous contact with the helicopter

by amateur radio. This was essential as Dick anticipated that at times he would be flying at only a few hundred feet above the ocean and would have only a few seconds to give warning of any

failure.

During stages one and two of his around the world attempt, Dick had made contact with many amateurs using his Collins HF 220 SSB set and using the call-sign VK2DIK. These contacts he

found interesting and useful. The container vessel would carry a Yaesu FT-ONE transceiver and I would keep Dick informed of weather conditions in our area before he left Japan and during the course of the flight. The area off the Kurils is prone to heavy fog as warm fronts from the continent meet the cold, moist air over the ocean. If, after passing the point-of-no-return, a shipboard landing was judged impossible because of visibility, wind or

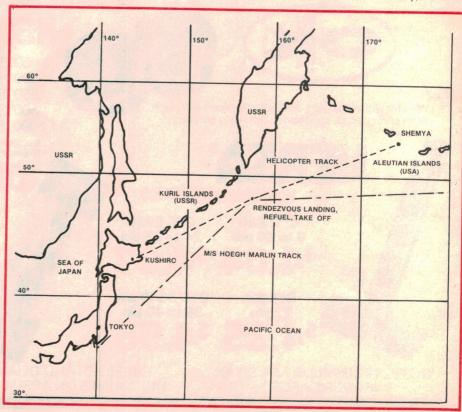




Safely on deck, Dick Smith greets the crew of the M/S Hoegh Marlin. The huge container ship is shown below.

sea conditions, Dick would have to turn to the doubly inhospitable coast of the USSR and hope for the best.

So that was how I came to be on board the M/S Hoegh Marlin on the night of Tuesday, June 21, in my cabin, surrounded by cartons of radio gear, wire dipoles, half a dozen enthusiastic Japanese technicians and not a little confusion. All was eventually sorted out and by 11 o'clock that night we were on the air with the FT-ONE and dipoles that loaded well on the 15-, 20- and 40-metre bands. The technicians from Yaesu departed happily, munching the last of the hamburgers.

Dick had been forced down by bad weather at a small fishing village on the coast of Japan a few hours flying out of Tokyo. The low pressure system that had caused this hold up was to travel with us and haunt us for the next few days. He then had completed the flight to Tokyo and visited the Hoegh Marlin that afternoon to review the plans. We prepared a duplicate chart to the one that Dick would carry in the aircraft so that I could plot his position reports. This work was done in the corridor outside my cabin, head down tail up, subject to the incredulous comments in Norwegian from passing crew members.

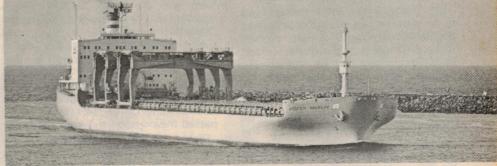The final plan was for Dick to fly the helicopter from Tokyo to Kushiro, a northern airport in Japan, where a ground station would be set up at the shop of the local Yaesu dealer. Meanwhile the Hoegh Marlin would proceed from Tokyo towards the



rendezvous and I would maintain contact with VK2DIK helicopter mobile and, later, the ground station at Kushiro. We would also look for the opportunity to test the radio homing beacon whilst the helicopter was airborne.

On the day of the rendezvous, when the vessel was about seven hours steaming from the proposed meeting place, Dick would leave Kushiro and follow a course that took him along the boundary of the Buffer Zone and then fly east to the vessel with the intention of locating her and making the landing. Once that course of action had been taken, there would be no turning back as insufficient fuel would remain to make the coast of the USSR.

After landing on the *Hoegh Marlin*, VH-DIK would be refuelled and sent on her way to the American base of Shemya in the Aleutians, some 700 nautical miles to the northeast. Radio contact would be maintained throughout, starting on the 40-metre band and changing frequency as necessary.

This was the program:

- Tues June 21 Ship leaves Tokyo for rendezvous.
- Thurs June 23 VH-DIK leaves Tokyo for Kushiro and we conduct test of shipboard beacon.
- Fri June 24 Set up base station Kushiro. Prepare helicopter for departure.
- Sat June 25 VH-DIK to leave Kushiro for shipboard landing and refuelling. Helicopter to then leave ship for Aleutians, and vessel to resume course for Seattle

Amateur contacts

After leaving Tokyo, I made contact at least daily with a group of Australian amateurs, using the frequency of 21.385MHz during daylight and 14.136MHz in the evenings. The group

Across the Pacific by helicopter

consisted of Harry Caldecott VK2DA, Pierce Healy VK2APQ, Mike Barry VK2IH and Ron Payne VK2DBH.

I had also chosen working frequencies for the various bands which I had programmed into the FT-ONE, as Dick had also done with the Collins. I could change frequency with the turn of a switch but I regretted not having a co-axial switch to change dipoles.

After the Hoegh Marlin left Tokyo the weather pattern deteriorated. The low pressure system that had delayed Dick's arrival in Tokyo was still with us and moving at the same speed and in the same direction as we were. It reduced the ship's speed to 13.5 knots and every now and again a bump and shudder would run through the ship as she put her blunt bow into a solid wave.

It looked as though we were going to be south of the rendezvous point for touch-down which would mean a longer leg to the Aleutians and the possibility of the helicopter running out of fuel or daylight, or both! It could also mean head-winds of up to 20 knots, thus further reducing the helicopter's range.

On Friday 24th, good contact was made with the ground station at Kushiro on the 40-metre band. A party seemed to be in progress at the dealer's place. Dick was surrounded by transceivers, switches and ATU's and some 15 Japanese, none of whom appeared to be able to speak English. However it was a good party, as was the one we had on board to mark the longest day. The Norwegians celebrated the day by standing around the bar with drinks on the house. What a pity that some of these quaint customs are not observed in our part of the world!

That afternoon, the captain of the Hoegh Marlin held a final briefing for those who were to take part in the refuelling operation. Several important safety precautions were to be followed: life rings on strong lines were to be attached to both port and starboard sides, a fire team in full reflective clothing was to stand by with pressurised fire hoses and extinguishers laid out on deck, and two men were to stand by a small life raft that could be lowered in seconds. The fuel drums were stored on the foredeck, ready to be rolled aft only after the helicopter had landed.

A hazardous flight

At 0340 Japanese standard time on Saturday, June 25, VH-DIK lifted off from Kushiro Airport in heavy rain and started flying along the coast of Japan for the first turning point about 80 nautical miles out over the ocean and on the edge

of the Japan/USSR buffer zone. Communication was immediately established between the Hoegh Marlin and VK2DIK on 7.060MHz.

By 0445 the rain had cleared and soon after the tops of volcanoes on the chain of islands that make up the Kurils were visible from the aircraft through low cloud. The *Hoegh Marlin* was proceeding on course to the rendezvous in patchy fog and poor visibility. Each time I looked out the window I became more doubtful about our chances of making a rendezvous. The ship was travelling at maximum allowable sustained revs but we were still under the influence of the low pressure system with head winds and swell from the north.

Conditions at the ship gradually improved and by 0700 the fog had lifted and the cloud base was at about 500ft. To our west, Dick was flying above thick cloud with the occasional volcano peak poking through and the height of the cloud base unknown.

To descend through the cloud hoping for a fog-free space between the cloud base and the water could lead to disaster, so I was asked to advise the Department of Civil Aviation and Canberra Operations that the landing may have to be aborted. If that happened, VH-DIK would be forced to fly into USSR air space in an attempt to seek a landing. Harry Caldecott, VK2DA was standing by on 14.146MHz and I passed the message to him for action.

Dick's wife, Pip, and daughters Hayley and Jenny were listening to our radio conversations at the family home in Sydney and, after some prompting, Dick remembered that it was Jenny's birthday. So, despite the forbidding surroundings and the hidden tensions a rich baritone voice floated over the airways: "Happy birthday to you, happy birthday to you, happy birthday dear Jenny . ." and so on. For a moment, I had a vision of hundreds of listeners around the world reaching for the gain control before something horrible happened to the front end of their receivers!

At the Hoegh Marlin conditions were steadily improving. The fog had dispersed completely and the cloud was lifting and looked like breaking up altogether. I had also received a report from Shemya, in the Aleutians, that conditions there were reasonable with high visibility and light winds.

From 9 o'clock that morning onwards I was in continuous contact with the helicopter. Around the ship conditions were almost perfect for a landing; the cloud base was about 1000ft, the wind 5kts from the north, the sea slight and

Just after touch-down, helicopter VH-DIK is dwarfed by its sea-going landing pad. (All photos by the author).

the ship rolling no more than about 3°. At the helicopter things were quite different. Dick could not see the ocean and could only guess at conditions below the cloud base. He could still see the tops of volcanoes on his port side rising through a solid mass of cloud. A decision had to be made within minutes either to penetrate the cloud and search for the ship in unknown conditions or to head west into the USSR looking for a place to land

Dick decided to have a closer look at the islands and see whether a landing would be possible. He came back to me with a report of steep, ice-covered cliffs, small glaciers and a narrow space between the cliffs and the edge of the crater that could be wide and flat enough for a landing ... but not very promising! So we proceeded towards the rendezvous and Dick kept to the buffer zone hoping for an improvement within the short time left.

Tension was rising at both ends of the communication chain! I brought the Master of the Hoegh Marlin to the microphone to reassure Dick of the conditions surrounding the ship, being careful not to apply any pressure that could mar his judgement. I kept on reporting conditions at the ship and Dick kept telling me how impossible the islands looked for a landing.

Then, a break in the clouds, a sight of the ocean and Dick was through; off to the ship, in the narrow space between the cloud base and the water, in good visibility. VH-DIK was now homing in on the beacon, approaching us from about 60 miles away and in direct contact with our skipper on the bridge. The ship swung head to wind and speed reduced for the landing.

"I... well made it!" were Dick's first words as I opened the helicopter door, an obvious release of tension from a man who seldom uses strong language.

The fuel drums were rolled from their position forward and I commenced refuelling. About 170 gallons US were used to bring the aircraft tanks back to "full" and, after a quick lunch, Dick was ready to head for the US Airforce Base at Shemya. Time was important as there could be headwinds and Dick had to find the base and land before dark that evening.

The take-off crew stood by, the deck



was cleared, the fire crew stood ready and the helicopter turbine started. After what seemed minutes the overloaded aircraft lifted from the deck. Maximum overload power could be sustained for only a few seconds. The helicopter nose dipped for forward motion and VH-DIK moved swiftly over the deck, missing the hold-down studs by inches. A quick circuit of the ship and away she went for Shemya. The Hoegh Marlin changed course for Seattle and we all breathed freely.

I maintained contact with the aircraft on the leg to the US base until the airport radio came up and talked Dick down in the gathering dusk.

Champagne

That evening the skipper opened the bar for a champagne celebration and we reviewed the landing and take-off. All had gone well. Good navigation at both the helicopter and the ship meant that

each knew where the other was during the entire flight. Once through the cloud, the beacon guided the aircraft to within visual range. Then it was over to each skipper, one to manoeuvre the boat to minimise pitch and roll and the other to make the landing. The take-off had been successful, but only just. The overloaded helicopter had almost fouled the deck-studs as the ship rolled on lift-

Communications had been excellent throughout, both myself and the ground station plotting each position as reported and, in the later stages, passing each plot to the bridge. We were able to keep VK2DIK informed of our weather and sea conditions as well as alert the authorities that a landing in the USSR would be necessary unless the cloud lifted.

The sole communication from the aircraft during the 15 hours of flying time had been by amateur radio - to the base in Japan and to the Hoegh Marlin.

The most difficult part of the operation, and the most courageous decision, was for Dick Smith to leave his grip, however tenuous, on the half-hidden islands and grope through the overcast to find a vessel 60 miles away. In doing this Dick knew that if he were not successful, a return to the coast for landing would be almost impossible.

Special tribute must also be paid to the skipper and crew of the Hoegh Marlin. They were all vitally concerned that everything should go according to plan and regarded the operation as a test of their seamanship. Without their professionalism, the landing would not have been possible.

Dick, for his part, was delighted with the organisation and success of the operation. He was to comment later on the contrast between sitting in the tiny bubble of the helicopter for seven hours and, within minutes of landing, having a smorgasbord with the skipper in the comfortable dining room of the Hoegh Marlin

The shipboard landing, although important in skill, training and coordination of a number of disciplines, forms only part of a much bigger achievement: that of the first solo circumnavigation of the world by a rotary wing aircraft.



STAR PRINTER DP-8480

SPECIFICATIONS

Printing system -- Impact dot matrix

Interface — Centronics standardised parallel interface (TTL level) built in printer.

Interface — Centronics standardised parallel interface (11 Level) utility interface.

Matrix Character mode 9 x 7 matrix, Graphic mode 6 x 6 matrix.

Printing direction — Character mode Bi-directional printing with logical seeking function, Graphic mode Unit-directional printing from left to right.

Number of characters per line — 80/96/131 (40/48/66 for double-width characters).

Printing speed — 80 characters/sec.

Character set — JIS 160 codes/ASCII 96 codes + International character codes 64

Character set — JIS 160 codes/ASCII 90 codes in the factor of the graphics patterns.

Character size — 2.0 (W) x 2.6 (H) in mm in case of 80 columns/line.

Character space — 2.54mm (1/10 inch) in case of 80 columns/line.

Line space — 1/6. 1/8 or 1/12 inch.

- Friction type Friction feed, Tractor type Variable sprocket feed or friction feed.

Unio feed speed — 7.5 lines/sec at 1/6 inch spacing, 10 lines/sec at 1/8 inch spacing. Buffer capacity — 2K bytes.

Other important functions — Form feed, Diagnostic printing, No-paper detection.



ALPHA-80

unctional specifications unctional specifications with the properties of the propert

Printing format minutes of the control of the contr

inc. tax

(ASK FOR DETAILS) ONLY \$425



649 George St, Sydney, NSW 2000. Phone: 211 0531

CORRESPONDENCE & MAIL **ORDERS:**

Box K21, Haymarket NSW 2000, Australia WRITE, PHONE OR CALL IN! **ALTRONICS**

TOP QUALITY **XTALS**

				*	
				ea.	10+
Y	1000	1.0000 mHz	Parallel	\$11.50	\$10.25
Y	1003	1.8432 mHz	Parallel	9.50	8.75
Y	1006	2.0000 mHz	Parallel	7.50	6.75
Y	1010	3.5875 mHz	Series	3.00	2.75
Y	1012	4.0000 mHz	Parallel	5.00	4.50
Y	1015	4.1940 mHz	Parallel	5.00	4.50
Y	1017	5.0000 mHz	Parallel	5.00	4.50
Y	1018	6.0000 mHz	Series	5.00	4.50
Y	1019	8.0000 mHz	Series	5.00	4.50
Y	1020	10.0000 mHz	Series	5.00	4.50
Y	1025	12.0000 mHz	Series	5.00	4.50
Y	1030	16.0000 mHz	Series	5.00	4.50
_					

HEATSINK COMPOUND

Heat conducting paste facilitates heat transfer from semi to Heatsink. One tube good for up to 30 TO3 package semiconductors.

\$1.20 H 1600...7.5g Pack. New trade pack

\$7.50 H 1610...150g Pack. SAVE UP TO 33%

VELOSTAT



Non-static sheeting for storing CMOS IC's, LSI's etc. 1000 times better than aluminium foil. Will store up to 150 IC's on one 225 x 150mm sheet.

н 0500.... \$3.50 per sheet

DIL SWITCHES

GOLD PLATE SELF WIPING CONTACTS



10Up \$ 3050 \$1.35 4 Way \$1.50 \$ 3060 8 Way \$2.00 \$1.75 ALTRONICS

DAY

NEXT

DELIVERY

JETSERVICE

ANKCARD

ALTRONICS

NEW HITACH SOUARE SCREEN DUAL BEAM

SUPERB NEW MODEL V152F DC TO 15 mHz 1Mv/DIV DUAL TRACE



function)
DC to 15MHz, -3dB lat 4div
DC to 7 MHz, -3dB lat 4div
When using x5 amplifier
24 ns, !for x5i 70 ns typ

600 Vp.p or 300 V IDC + AC peak, at 1 kHz, AC, GND, DC Direct 1M ohm approx 30pF CH1, CH2, DUAL, ADJ, DIFF, CH1 X axis, CH2 Y axis 5 MV div to 5 V div. (when using x5 amplifier 1 mV div.

20 mV div or more fterminated into 5012 50 Hz to 5MHz - 3dB Approx 5012

SPECIFICATIONS

Max input voltage Input Coupling
Input impedance
Operating modes
X Y operation
Sensitivity

Band width Output impedance

CAT Q0152 PRICE ONLY TAX EXEMPT PAID

Features * X-Y Operation * Vertical sensitivity 1mV/div. * 10 x Sweeptime magnification with 1-touch operation * Convenient Ch1 signal DVM output * Z-axis input provided — possible to use as CRT display * 0.2us to 0.2s — wide sweep range setting * Five modes of vertical operation * Panel layout with colour coding of respective functions.

Trigger sensitivity

AUTO low bandwidth Trigger slope External trigger input

Input impedance approx 1M ohm 30 pF or less Max input voltage 100V IDC - AC peak, at 1 kHz) 0 2± (div 15 % 19 calibrated steps Uncalibrated continuous control between steps 1 = 2.5 [provided with click-positioning function] function)
10 times (+7%)
100ns/div (20ns/div and
50ns/div, not calibrated)

Amplitude calibrator
 Waveform

Voltage e Power requirements

Approx. 1kHz - 10% (typ) square wave 0.5V 15% 100/120/220/240V -10% 50 to 60 Hz, apprex. 40W Apprex. 275(W) x 190(H) x 400(D)mm

Approx. 8.5kg

Powerful New 6000 RPM Mini Drill for PC Work Tons of Torque. Just the shot for PCB work.

12V DC operated from external Power Pack 1.2mm chuck capacity Supplied c/w 1mm drill bit.

T2302 \$12.95

Drill Bits: T2320 (0.8mm) . . . \$1.25

T2325 (1.0mm) . . . \$1.25

ALTRONICS JIFFY BOXES

Incredible offer!

Black plastic body with 22 g, aluminium lid and 4 st, screws supplied. Unique horizontal PC Snap In" mounts as well as vertical card guides. Order your PC Boards presized and dispense with costly stand offs, screws etc. These utility boxes are used in dozens of E.T.I. and E.A. projects.

	Board width				
Box	Dimensions	Vertical	Horizontal	Price this month	
H 0101	150 x 90 x 50	90	87	\$1.90	
H 0102	195 x 113 x 60	106	103	\$2.90	
H 0103	130 x 68 x 41	62	60	\$1.80	
H 0105	83 x 54 x 28	50	47	\$1.20	



FOR DESPATCH P&P CHARGES AND ADDRESS DETAILS PLEASE REFER TO OUR AD. ON PAGE 149

MONICS

UNCONDITIONALLY STABLE



The AS-20 is a rugged, reliable general purpose public address amplifier. Designed and manufactured in Australia this amp is suitable for use by schools, sporting clubs, function centres and in professional installations (paging systems, background music).

ALTRONICS

DAY

JETSERVICE

- * Balanced Low Z mic input

 * Unbalanced Low Z mic input

 * Mic muting function (mutes program music with PA announcement)

 * 4-16 OHM output * AUX Treble and Bass controls

 * 100V Balanced line output

 * Full 20 Watts RMS into 8 OHMS

 * Short circuit load protection


 * Less than 1% Distortion.

A2000.....\$149.00

WHY PAY OVER \$200.00 FOR AN INFERIOR UNIT?

35c/m \$34/200m

TOP QUALITY PAGING MIC

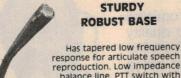

response for articulate speech reproduction. Low impedance balance line. PTT switch with lock facility. Additional switch contacts for remote switching, muting etc. Gooseneck approx. 350mm.

C0166..... \$59.95

SUPER SPECIAL SPEAKER TWIN FLEX

2 x 19/.193

WO204 RED TRACE WO205 BLACK TRACE

PROFESSIONAL HORN SPEAKERS



ALTRONICS

ALTRONICS

DAY

NEX-

DELIVERY

JETSERVICE

BANKCARD

ALTRONICS

NOW IN USE WITH THE WEST AUSTRALIAN EDUCATION DEPT AND PWD

30 WATT WITH LINE TRANSFORMER

Multitap inbuilt line transformer allows taps 330/30W, 660/15W, 1000/10W, 2000/5W. Universal swivel mounting bracket supplied.

\$69.95 4 or more......\$67.80

15 WATT WITH LINE TRANSFORMER

Multitap inbuilt line transformer allows Z taps 660/15W, 1K/10W, 2K/5W, 4K/2.5W. Mounting bracket clears line TX allowing rear wall mounting.


4 or more......\$56.00

8 INCH WIDE RANGE DUAL CONE SPEAKER

200mm (8 in.): 10 Watts Max. power input. Public Address, Background Music. Ideal Hi Fi extension speaker. Includes transformer holes at 51mm. Over 30,000 sold in Australia! Mounting holes 140 x 140mm.

c2000. \$9.50 ea \$8.70

8 INCH CEILING SPEAKER GRILL

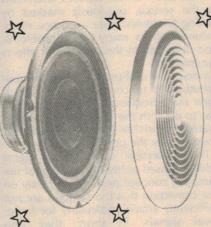

20W HIGH POWER SPEAKER TRANSFORMER

Primary Power Taps (100V Line) 1.25/2.5/5/10/15/20W (Halve these for 70V line) Secondary Taps 4/8/16 OHMS.

M1120....\$10.80 10 or more\$9.90



4W MULTI-PURPOSE SPEAKER TRANSFORMER

Primary: 2.5K, 5K OHMS Secondary: 2, 4, 8, 16 OHMS Frequency Response: 30 Hz -12 KHz. Mounting hole centres 51mm. Ideal for high quality constant voltage PA systems.

M1105..... \$4.95 10 Up each \$4.50



STEEL CORE

THE SET OF TEN B9995 \$79.50 B9995 \$79.50

MOTOROLA CMOS DATA B 1105.....\$11.50

A comprehensive reference covering 40XX, 45XX CMOS family's along with specialty devices such as LCD drivers, telephone and general communication functions and insurficial control. dustrial control.
862 pages essential in all spheres



MOTOROLA MECL DATA В 1100.....\$9.95

Emmiter Collector Logic (ECL) is today's fastest form of digital logic providing the most direct way of improving system performance. This previously hard to get manual provides data on the 10KH, 10K and ill families, MECL memory and PLL CHIPS.

MOTOROLA OPTO DATA

... 58.95 B 1118... Handy reference provides data and application notes on opto couplers, infra red LEDS, Photo transistors and a complete chapter on fibre Optics, a communications system which is fast gaining usage worldwide. VERY EDUCATIONAL.

MOTOROLA POWER DATA

\$12.95 Motoroia are the undisputed world leader in Power Transistors, Renowned for their low cost and reliability, Book includes a 9 page selection guide, application notes and Data Sheets for over 700 Devices, 989 pages, Previously over \$20.00.

TOP SELLING MOTOROLA BOOKS

IF YOU MISSED OUT LAST TIME, ORDER NOW! LATEST EDITIONS JUST ARRIVED

MOTOROLA MASTER SELECTION GUIDE

B 1104.....\$7.95 The most useful book ever printed. Covers MOS IC'S listed by function. LINEAR IC'S listed by function. INTER-FACE IC'S listed by function. LSI, memory. TTI. ECL power products. SCR'S, dlodes, transistors listed by application and ratings. RF, small signal and opto devices listed by application and ratings. Essential Data given for all devices.



MOTOROLA LINEAR IC'S

B 1114.....\$9.95 Popular data manual. At last readily available. Approx. 800 pages, full Data Design proceedures and equivalent listings for 1000's of devices under headings OP AMPS, VOLTAGE REGULATORS, CONSUMER CIRCUITS (eg. TV, AUTOMOTIVE, POWER) HIGH FREQUENCY CIRCUITS and SPECIAL-PURPOSE CIRCUITS.

MOTOROLA LINEAR INTERFACE IC'S

B 1115. \$11.50

Complements the Linear IC Manual. Gives data, design proceedures and equivalent listings for: MEMORY/MICROPROCESSOR SUPPORT LINE DRIVERS/RECEVIERS, TELEPHONY, COMPARATORS, VOLTAGE REFERENCE AND DATA CONVERSION DEVICES. Includes comprehensive selector guide. \$11.50

MOTOROLA MICROPROCESSOR DATA

B 1120.....\$14.95 Over 1200 pages covering all aspects of motorola's microprocessor microcomputer and peripheral components. A clearly written Manual providing all the data necessary to design and build a working computer system from scratch, 100's of circuit examples, flow charts, Truth Tables and programme routines.

MOTOROLA MEMORY DATA

MEMORY DATA

\$ 1113. \$8.95
An absolute must for the microprocessor Buff This is the latest reprint or Microbia's famous
Memory and Manual and includes
in the latest specifications and
ording and microbia and microbia
proof MECL MEMORY. MECL
RAM. MECL PROM. MOS dynamic
RAM. MICRORY AND STATES
MOS SEPROM and MOS ROM.
Worth many dollars more!





SCHOTTIKY TTL DATA ...\$9.95 В 1109....

B 1109. \$9.95
Essential reference for the enthusiast and engineer alike. Designing, building and servicing digital circultry is an absorbing pastime. Data for the LS, ALS and FAST familles along with design considerations and circuit characteristic are logically presented in this manual, making it quick and easy to use.

We mustn't kill CD for the sake of

Compact disc is by far the most promising system so far devised to bring top quality sound reproduction into the home. Yet, like the fabled goose, it is in danger of being fatally mauled by those who are overanxious to get their hands on the golden eggs that it will hopefully lay.



I've had a few uneasy feelings, of late. about the industry's approach to compact disc but what brought the matter to a head and triggered the above title and introduction was a news item in the October issue of the American journal "Stereo Review". I

"Sales of Compact Disc (CD) players in Japan are expected to overtake those of conventional turntables during the fall ... NAD is preparing to launch a CD player this winter . . . Technics will begin selling a \$700 CD player in the US any day now . . . watch for a number of \$599 CD players from various sources by January and some \$399 bare bones

machines next spring or summer."

The first part of the paragraph is interesting but routine. Demand for CD players was expected to escalate rapidly but, even so, it must be particularly keen in Japan to be overtaking that for conventional phono decks, already. Prices were expected to fall with rising production and the announcement of a \$700 CD player from Technics for the US market holds no real surprise. Nor is it surprising that other companies should be looking beyond the Technics release to a figure of \$600 (sorry, \$599).

But the sting in the tail is the throwaway remark about "bare bones machines" next spring or summer.

Just like that ... good grief!

With friends like these...

As I remarked earlier the compact disc is the most promising system yet devised to bring top quality sound reproduction into the home. It has won world-wide acceptance, a unique degree of cooperation and faces no immediate rival. It has presented the world hifi industry with a never-to-be-repeated opportunity to launch and maintain a new standard of quality but, with compact disc commercially less than a year old, a section of the industry is apparently talking blithely about the release of "bare bones" players.

With friends like that, the compact disc doesn't need enemies!

For sure, the compact disc, and digital audio in general, has had its share of "enemies" or - to use a less emotive term - its share of critics who have expressed strong dislike, both for the sound and the theory behind it. However, it is hard to see such opinion prevailing at this late stage.

As for the sound of digital reproduction, there seems to be emerging recognition that much of the dislike is traceable, not to the digital system itself, but to an unaccustomed transparency which exposes limitations at the source, previously masked by analog processes: poor acoustics, multimiking with its many phase problems, and distortion in the mixing and effects equipment.

Indeed, as enthusiasts become more accustomed to compact discs, one of their most frequently heard complaints has to do with the inclusion of program material which has come from an analog source! How the pendulum has swung!

The theoretical objection to digital audio is based partly on rejection of the sampling concept per se, and partly on the conviction that the samples are not sufficiently small, particularly for lower level signals. In short, they (the objectors) dislike the whole idea of reconstructing a waveform from samples but, if it is to be done, then at least the samples should be defined by something more accurate than a linear 14-bit or 16-bit digital system and perhaps should be a logarithmic sampling system.

It is difficult to reject the sampling principle out of hand because, as we have pointed out on previous occasions, AM broadcasting, FM-stereo broadcasting and magnetic tape recording all involve sampling, with the audio contour being recovered from pulses of carrier, sub-carrier or HF bias.

Apprehension about the adequacy of the 16-bit encoding/decoding process is more persistent, as typified by a letter from H. W. Holdaway of Coogee, NSW, which was published in "Letters to the Editor" in the October issue. He feels that distortion due to sampling error of low level signals must surely be as serious as crossover distortion in the early transistor amplifiers, and just as fatiguing to the listener.

He suggests that a modified method of encoding/decoding should be worked out that would deal more effectively with low-level signals. It might conceivably involve the use of dbx encoding. Says Mr Holdaway:

"I believe it is important that such steps be taken quickly, while yet there is only limited software available. Failure to come to grips with the problem will lead to disillusionment and many unhappy customers."

Low level distortion

What Mr Holdaway says is undoubtedly true in principle and is, in fact, confirmed by Technics themselves in the manual for their SL-P10 compact disc player: the level of distortion does rise with decreasing signal level. There is an enormous discrepancy, however, between the level of distortion anticipated by Mr Holdaway and that revealed by Technics' specifications for the D/A conversion process in the

Mr Holdaway mentions (signal) "levels," of about 1.5% of maximum" as an area of concern. It is unclear whether he has in mind a percentage of maximum power (18dB down) or signal voltage (36dB down) but, in both cases, Technics' figures for D/A conversion distortion are very small: 0.01% for -18dB, and 0.08% for -36dB. Both are way below what one might suggest as a level of crossover distortion likely to cause listener fatigue.

Technics show a distortion figure of just over 0.1% for a 1.05kHz test tone 40dB below maximum amplitude. They terminate the curve there, presumably because they believe that the level of distortion products for a fundamental beyond -40dB would be below the threshold of hearing and/or noise ambient.

By projection of what is essentially a linear relationship, one can predict a 1% distortion level at -60dB and 10% at -80dB. But, while the latter figure looks awful at first glance, it is necessary to remember that a listener in any practical listening situation would be hard put to it to hear the fundamental so far down in the dynamic range, let alone spurious

a few easy bucks!

distortion products below that level again!

In any case, while the CD system dynamic range is around 95dB or more, it is hardly likely that normal music programs would be allowed to exceed much more than about 75dB below maximum output level.

While much more could be said on the subject, on both sides, it has been interesting to note the attitude of reviewers for "Gramophone" magazine, who can scarcely be written off as a group of hifi trendies. They accept digital mastering as routine and respectable, and consistently commend CD versions for revealing subtleties of sound and performance that didn't make it through the equivalent analog pressing.

In the face of that sort of reaction, I can't help but feel that our correspondent is likely to be disappointed in his bid to call for a halt and a re-think of the whole digital/CD scene.

But let's get back to those gentlemen who are reportedly planning the release of "bare bones" CD players. How do they imagine that they will be able to strip another \$200 from a budget price that, itself, remains to be achieved?

I would not be greatly concerned if their answer was simply to cut back on the cosmetics and to reduce the control facilities to a basic selection of tracks, start, stop and pause. At least the buyers would be faced with a clear compromise which they could accept or reject.

But I can't see it stopping there. The designers are going to be under strong pressure to save dollars also on the precision spindle and traverse mechanism, the laser tracking circuitry, the error correction system, the D/A conversion, and so on.

I have never ceased to wonder at the ability of the laser system to track that tiny spiral of tracks, but I have also had cause to wonder at the distortion which results when something goes amiss with the tracking. Even though the problem may be a single greasy fingerprint on the surface, it can cause the affected tracks to sound exactly as if they were LP tracks being played by a badly mistracking stylus — one with insufficient playing weight, or suspended on a ball of fluff.

If some manufacturers yield to the temptation to cut back in critical areas, they will invite an increase in basic distortion, plus traumas of a more serious nature if the player fails to cope adequately with minor imperfections in typical discs.

It has been said in the past that, unlike

traditional record players, CD players should all sound substantially similar, with the difference being mainly in finish, appearance and facilities. This should be true of players which are adequately designed but certainly not of those where corners have been cut in vital areas.

I only hope that we are not about to replace a race of cheap and nasty phono decks with cheap and nasty CD players!

CD players for the car

A further area of concern is the widespread assumption that compact disc players belong automatically in the family car.

It is true that the possibility of in-vehicle use was a factor which supported the choice of a 12cm diameter disc, rather than something larger. It is also true that manufacturers expect to be able to mass-produce players capable of coping with in-vehicle vibration levels. But that doesn't mean that the present generation of compact discs is ready for the road.

Amongst other things, in the context of home listening, compact discs offer extra playing time per side, versatile track selection, high quality, low noise and high dynamic range.

On the highway, extra playing time could be handy, and high quality reproduction would be a bonus, within the limitations of what can reasonably be installed in a family car. Very low system noise would not count in the majority of road conditions, while versatile track selection would be subject to what could reasonably be installed and operated in the way of push-buttons.

High dynamic range — already the subject of debate for in-home listening — is clearly out of place in a car. Even with pre-monitored programming, dissension is not uncommon between those who want to belt their ears with music and others who want to talk, or simply to be as quiet as they can under touring conditions. Not many of us own vehicles with partitions between the front and rear seats!

Imagine the problem of bringing into this situation recordings in which neither the producer nor the musicians have been inhibited by the traditional constraints on dynamic range. Or where, perchance, they may be intent on "letting their heads go".

If there's a problem fitting 80dB of dynamic range on top of a 45dB ambient in a domestic lounge room, how much

MEY

When your in the market for a car you head for "Auto Alley" —

"Auto Alley" —
For you, the electronic enthusiast, tradesmen, hobbyist or just an electronic Nut, we've created "Silicon Alley" — better known as York Street. So no matter what you need in electronics, drop your soldering iron and come on in. (OOP'S switch it OFF first)

SINCLAIR SPECTRUM HOME COMPUTER



Sinclair ZX Spectrum-16K RAM Sinclair ZX Spectrum-48K RAM Sinclair ZX Printer 299.00 399.00 169.00

SOFTWARE

Games 1 to 6	19.50
Biorythms	22.50
Space Raider	19.50
Chess	25.00
Raiders	19.50
Planetoids	19.50
Flight Simulation	25.00
Back Gammon	19.50
Vu-File	27.50
Vu-Calc	25.00
Vu-3D	25.00
Scrabble	44.00
Hungry Horace	19.50
Adventure A — Planet of Death	22.50
Adventure B — Inca Curse	22.50
Adventure C — Ship of Doom	22.50
Adventure D — Espionage Island	22.50
Reversi	25.00
The Hobbitt	44.00
Collectors Pack	22.50
Club Record Controller	22.50
Horace Goes Skiing	19.50
Horace & The Spiders	19.50
Embassy Assault	19.50
Cyrus — is — Chess	27.70
ZX — Forth	44.00
Small Business Account	39.00

LOOKING TO BUY A MULTIMETER?

TWO NEW MODELS FROM PARAMATERS

MODEL 7040

Low Cost • 31/2 Digits • 0.1%
Basic DCV Accuracy • 28 Ranges
• 2000 Hour Battery Life • Hi-Lo
Volt Resistance Tests • Overload
Protected on All Ranges • Current
Ranges to 10 Amps.

\$99.00



MODEL 601 Low Cost • 3½ Digits • 0.1%

and 0.25% Basic DCV Accuracy

28 Ranges = 2000 and 200
Hour Battery Life = Hi-Lo Volt
Resistance Tests = 0 verload
Protected on All Ranges = Current
Ranges to 10 Amps = Rugged
construction.

These are just a few of the many 100's of up-todate Electronic items on display at:



DAVID REID ELECTRONICS LIMITED

127 York Street, Sydney, 2000 or Telephone (02) 267 1385

at the leading edge

FIRST 70 MBYTE 51/4" WINCHESTERS ARRIVE.

Vertex Peripherals gave Australia a vote of confidence when they recently shipped us their top-of-the-line high performance V-170 Winchester. Boasting an average access time of 30 millisecs the V-170 offers an excellent, compact central data storage for multi-user systems. Vertex are also shipping 30 and 50 Mbyte product.

MPI LEAPS TO US No 2 IN FLOPPY DRIVES.

In anybody's language that's big. Buoyed up by the industry trend to slimline drives, MPI are delivering both push-button and twist-lock half-height 51/4" drives as well as staunchly supporting their full sized units.

IBM dealers will cheer at the Model 52-SLI, a perfect match for the PC at considerable savings over the OEM installed product.

MINISCRIBE WINCHESTERS SWITCH REPS.

Specializing in 51/4" standard and half-height drives to the ST416 interface, Miniscribe have carved out a reputation for reliable 5, 10 and 20 Mbyte drives at reasonable prices. Daneva Australia now backs the Miniscribe line with their years of mass storage experience.

Miniscribe recently announced that they have successfully negotiated a deal making them a preferred supplier on the IBM PC Programme.

WHISPERING GALLERY.


PSST! 3.3 Mbytes on a half-height 51/4" floppy? Look out for this one early in '84. Incidentally we've heard that the same drive will read standard 48 and 96 TPI media.

A double-sided 3" micro floppy is in the works. Following an agreement between the big three proposers of the 3" standard a US manufacturer is well on the way to launching their own version. We should see product in Australia soon.

daneva australia pty ltd

66 Bay Rd. Sandringham. Vic. 3191. P.O. Box 114. Sandringham. Vic. 3191. Telephone: 598-5622. Telex: AA34439.

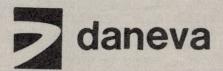Sydney: (02) E&M Electronics 51-5880 Adelaide: (08) DC Electronics 223-6946 Perth: (09) Micro Controls 445-2544 Brisbane: (07) Baltec 369-5900





FORUM — continued

greater would be the problem of trying to do so in a moving vehicle. In that situation, we need more dynamic range like a hole in the roof!

Dynamic range

In short, a great many compact discs, with whispering pianissimos and great, shattering sonic climaxes simply will not translate from the loungeroom to the family car as practical program material, quite apart from any consideration of road safety due to driver distraction. If we are going to travel or even picnic with compact discs, we may have to select them for low — not high — dynamic range.

Who knows: they may have to be produced that way in the first place.

And, just in case you are thinking in terms of car CD players with built-in volume compression, let me sound a word of warning: No matter how it is effected, the end result of compressing dynamic range is to raise the level of those whisper-soft, down-in-the-ambient passages by, say, 20dB.

Reverting to what we said earlier, if we take the low-level passages from a digital recording (say -60 to -80dB) and artificially boost them by 20dB, they come complete with a distortion content

of between 1% and 10%.

I would not go so far as to suggest that volume compression in car CD players will be impractical; rather that it will need to be applied with considerable discretion.

In the meantime, I feel that, if listening conditions in a vehicle tend to nullify the refinements and advantages of compact disc, they must also tend to nullify any undue haste to discard the present car stereo cassette player. Somehow, cars and compact cassettes seem to belong together.

And program content?

Getting away from technicalities, complaint is beginning to mount, overseas, about the program content on some compact discs.

As mentioned earlier, the most frequent complaint is probably the inclusion of material from analog sources, complete with an inherent residual noise and intermodulation distortion that can readily be noticed by keep ears

The important point here, I feel, is not the inclusion of analog sourced material per se, but its inclusion in circumstances which suggest that the producers hoped you wouldn't notice. Analog tracks between digitally sourced tracks on a demonstration disc provide a classic example.

What is necessary, I believe, is a simple, honest notation relating to individual tracks or the work as a whole, which indicates the nature of the original recording, eg,

- * Analog master, 1978.
- † Digital master, 1983.

Such notation would not be a final word on the quality or the merit of the recording but it would be an act of good faith to buyers who are technology conscious.

The fact is that an enormous treasure trove of recorded sound exists in analog form and some of it will inevitably gravitate to compact disc — not as a technical necessity but as a service to those who may ultimately want to standardise on the one player. Suitable endorsement would allow purchasers to understand better what they are buying.

Playing time

No less important is the duration of the program on a compact disc. They will accommodate up to about 73 minutes but the figure that has been most frequently publicised is 60 minutes and this is what purchasers really expect and pay for. However, if software companies take the easy way out and simply remaster the contents of LPs to the one side of a compact disc, the playing time in many cases will end up at 40-45 minutes total.

"Not good enough" say the critics as they recall what happened with some LPs in the bad old days, which played for perhaps 13-14 minutes per side. Compact discs are not cheap to make and not cheap to buy and it is up to manufacturers to ensure that purchasers get their money's worth, even if it means re-grouping tracks and re-writing existing jacket notes.


These days, re-grouping tracks does not present the risk to quality that it once did. If the original masters are copied meticulously on to a digital tape, they can be edited, copied and reassembled under computer control without any cumulative quality loss, before finally being transferred to compact disc.

Over the past two or three years, the world hifi industry has been groggy, not from any lack of product, but as the result of widespread recession and competition from video. Compact disc could provide a basis for recovery — a steady supply of golden eggs — providing they don't kill the goose or inhibit its productivity!

The NEW KEF Constructor Series

A new generation of drive units from KEF is now available to the home constructor. KEF's drive units have been improved in terms of reducing audible colouration as a result of the detailed analysis of speaker vibrational characteristics, using computer aided techniques.

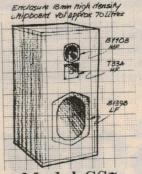Now the improved units and complete technical data on them are available to you to build a system to your own design or to use in any prescribed combinations to complete a system designed by KEF.



Model CS7

A new three way design incorporating the B139, which was the world's first flat diaphragm loudspeaker. The system offers an extended bass response and excellent power handling capability, with the three drive units being combined through a computer designed crossover network to give a very smooth frequency response characteristic with finely detailed reproduction of critical mid-range information.

KEF Making it together Drive Units

Certified mail delivery throughout Australia & New Zealand.

Bankcard, American Express and Diners Club Cards welcome.

For full information, write to: AUDIOKITS, PO BOX 361, BROOKVALE, NSW 2100.

Please send me details of KEF
Systems Designs.
Name:

Address:

.. Postcode:....

Hiff Review

Sony's 701ES PCM adapter is a means of recording audio in digital format on a video cassette recorder.



Sony 701ES PCM Adapter

At present there is only one way to make sound recordings to the same standard as the digital audio disc and that is to use a PCM adapter with a video cassette recorder. We recently tested the latest PCM adapter from Sony, the PCM-701ES and it produces performance figures which beat the best available reel and cassette machines by far.

PCM processors have been developed as a solution to the problem of high distortion levels and low signal to noise ratios found in conventional analog tape recording systems. At present analog tape systems are one of the weaker links in the recording chain, and this processor goes a long way to remedying the situation.

The PCM-701ES works by sampling an audio signal and then digitally coding the level of the signal at each sampling instant. The digital signals representing the audio samples are then combined with error correction and control signals and the whole lot suitably positioned within the standard "lines" of the PAL video format. The signal may then be taped using a standard VCR, giving recording times of up to 130 minutes. The format of the VCR is unimportant and either "Beta" or "VHS" machines may

be used

The digital coding of the audio samples may be switched between a 14-bit format and a 16-bit format. The 14-bit format is an industry standard while the 16-bit format is a non-standard format, offering slightly better noise and distortion figures, worked out by Sony to fit into the 14-bit format. The two formats appear to be compatible in that a tape made using the 16-bit format can by played back on a machine equipped with the 14-bit format only.

As with most things, to get better performance (ie 16-bit resolution) some sort of compromise has to be made this case it is loss of half the error correction capability. This occurs because one of the two error correction words in the 14-bit format is replaced with the 15th and 16th bits of the audio samples in the 16-bit mode.

Because of the reduced error correction in the 16-bit format, recordings using this format should be made on good quality video tapes.

The sampling frequency used in the PCM-701ES is 44.1kHz which gives a theoretical upper limit to the frequency response of 22.05kHz. In practice the response above 20kHz is rolled off by a very sharp filter to prevent "aliasing".

One obvious question regarding the 16-bit format is whether this format is identical to the 16-bit format used in the Compact Disc. If so, this would allow direct digital-to-digital recordings to be made between the two (providing a digital output were fitted to the Compact Disc player).

The answer to this question is no. The reason is that all signals in the PCM-701ES are maintained in a 14-bit word length even when the PCM-701ES is operating in the 16-bit mode. The Compact Disc operates with all 16-bit words and hence the two systems are imcompatible.

Specifications of the PCM-701ES claim a mass of 8.5kg, dimensions of $430 \times 375 \times 80$ mm (W \times D \times H) and a power consumption of 40W.

The front panel of the PCM-701ES is relatively sparse when compared with normal cassette decks since there are no tape transport controls. The front panel has a brush (or scratch) finish which has been black anodised with a matt appearance. In the top left hand corner of the front panel is the power on/off switch, while in the bottom left hand corner is a headphone socket and headphone volume control. The volume control is not continuously variable but

has switched attenuation ranges of 0, 6, 12, 18 and 24dB.

In the centre right of the front panel is a large window housing a fluorescent display. Main feature of the display is the wide range level meters which run almost the full length of the window. The level meters have a calibrated range from -50 to OdB with OdB corresponding to an input of 0.775V. At the right hand end of each level meter are back-lit indicators containing the word "over" which illuminate whenever the recording level reaches +1dB.

The level meters are peak reading and show the instantaneous level of the signal. A peak-hold facility is fitted to the meters and works by indicating the level of the highest peaks with a dot display while displaying transients below the

peak with a bar display.

At either end of the level meters are back-lit indicators which illuminate when appropriate to show the status of the PCM-701ES. "Copy Prohibiting" indicates that the tape being played back carries a digital code which prevents digital copies of the tape being made. "Res 14-bit" and "Res 16-bit" indicate the resolution with which the PCM-701ES is recording a signal. During playback of a tape, the indicators automatically show the resolution with which the tape is recorded, regardless of the resolution setting of the PCM-701ES.

The "Emphasis" indicator illuminates whenever the tape being played back has had emphasis applied. Emphasis is just the boosting of high frequencies (in this case above 1kHz) in a signal before it is placed on tape. When played back, the high frequencies are cut by the same amount as they were originally boosted, reducing any high frequency noise added during the period when the signal was emphasised. All tapes made via the PCM-701ES have emphasis automatically applied to them.

The "PB Muting" (playback muting) indicator lights when the muting circuitry inside the PCM-701ES is investigating dropouts in the signal. The muting circuitry can be disabled via a front panel switch however in this state the muting circuitry is still connected to the signal so the "PB Muting" indicator will light when dropouts occur even though muting is not applied.

On the extreme right of the level meters are two further back lit indicators. The first of these is the "Rec Mute" (record mute) indicator which lights whenever the Rec Mute pushbutton is pressed. The second indicator displays the word "Tracking" whenever the bar graph meters are switched from their usual level meter functions to a tracking meter function to allow optimum adjustment of the VCR heads.

Along the bottom edge of the front panel are eight pushbuttons which control most of the PCM-701ES functions. Included in these pushbuttons are a "Copy" button, a "PB Muting" button, three buttons for controlling the level meters, a "Rec Mute" button and two buttons to select between 14 and 16-bit resolution when recording. When the "Copy" button is pressed, the digital signal from the tape being played is made available at the Copy Out socket on the rear panel of the PCM-701ES. A second VCR may be connected and digital copies of the first tape made.

The "PB Mute" button controls the muting circuitry mentioned earlier and turns it off when not required.

The level meter control buttons switch the meter between three indicating modes. In the auto mode (activated by pressing the "Auto" button), peaks are held for approximately 1.7 seconds while in the manual mode (activated by pressing the "Manual" button) the highest signal peak is held indefinitely or until reset by a second touch on the manual button. When the "Tracking/Level" selector button is pressed, the right channel bar graph display changes to a tracking meter.

The "Rec Mute" button places a blank on the tape for as long as the button is pressed. It does not disable the level meters or the headphone output and these may be used to monitor incoming signals during the muted period. The "14-bit" and "16-bit" resolution buttons select the required resolution for the recording.

In the top right hand corner of the front panel are concentrically mounted right and left channel recording level controls. A friction clutch arrangement between the controls allows them to be used as a single control or as two individual controls as required.

The rear panel of the PCM-701ES contains eight RCA sockets placed in two groups of four. The first group of four are the line inputs and outputs which handle audio frequency signals. The second group of four sockets carry video frequency information. Two of these sockets are labelled video in and video out, and carry the video signal to and from the VCR. The third socket is labelled copy out and produces a digital output when the copy button is pressed. The Monitor Out socket gives a composite video output which may be connected to a television monitor.

If this is done, black and white patterns of bits representing the digitally encoded music will be displayed on the monitor.

Performance results

Record/replay response is the flattest we have ever seen from a piece of recording equipment being within ±0.5dB over the range 10Hz to 20kHz. The response is actually flat from 50Hz to 16kHz except for a slight rise between 7 and 9kHz of +0.2dB. Above 20kHz the response falls very quickly due to the high order, low pass filter included to prevent aliasing.

In both 16-bit and 14-bit modes, the signal to noise ratio was 90dB referenced to the OdB input level. Separation between channels was measured as 88dB at 100Hz, 88dB at 1kHz and 76dB at 10kHz for the 16-bit mode and 88dB at 100Hz, 86dB at 1kHz and 76dB at 10kHz for the 14-bit mode.

Two sets of total harmonic distortion measurments were taken. The first set of measurements were made at OdB for the frequencies 100Hz, 1kHz and 10kHz. Distortion readings in the 16-bit mode for these frequencies were 0.0037%, 0.0045% and 0.01% respectively. In the 14-bit mode the figures worsened slightly to 0.0045%, 0.0045% and 0.012% for the respective frequencies.

The second set of distortion measurements were made at 1kHz for input levels of -20, -10, 0, +1, +2 and +3dB. In the 16-bit mode the respective total harmonic distortion measurements were: 0.026%, 0.0085%, 0.0037%, 0.21%, 3.4% and 7.5%. In 14-bit mode the corresponding measurements were: 0.037%, 0.012%, 0.0045%, 0.21%, 3.4%, and 7.5%.

These distortion figures are typical of

PCM-701ES Specifications

Sampling frequency	44.1kHz
Quantization	14-bit linear of 16-bit linear
Frequency response	10Hz to 20kHz ±0.5dB
Harmonic distortion	Less than 0.007% (14-bit)
Harmonic distortion	Less than 0.005% (16-bit)
Dynamic range	
Dynamo rango	More than 90dB (16-bit)
Channel separation	
Wow and flutter	Below measurable limit
Input level for OdB	0.775V
input level for oub	



GREAT SAVINGS, BUILD YOUR OWN

DICK SMITH SERIES 200

why skimp on sound quality? Build these superb Dick Smith Series 200 hi-fi spea-kers and you'll be amazed at the sound quality that could come from such a tiny package! And you'll be amazed at the savings made over built-up speakers! (See ETI September 1983)

Includes Speaker Grille Cat C-2608 \$31.50 Enclosure Kit Cat C-2636 \$128.50 Speaker Kit Cat C-2046 \$89.50

Complete 200mm D.I.Y. Speaker Kit

will not corrode!

HORN SPEAKER

WEATHER



NEW FROM KAMBROOK!

4 WAY **POWER** BOARD

Get rid of that ugly piggyback double adaptor with this new-look power oard. 4 outlets at P-5612

ONLY

NOW HEAR THIS: FAMOUS SENNHEISER HEADPHONES



Just look at this! Superb head-phones from one of the world leaders in audio products at an unbelievably low price! Check out the quality sound from these

'phones - you won't go elsewhere. Cat C-4120 \$ 95

MOTOROLA

A magnificent new addition to our range of quality speakers. This excellent piezo-ceramic tweeter is an ideal replacement tweeter. Handles up to 40 watts continuous. Add these to your system and you'll notice the difference. Cat C-2006. ONLY

Transistor Checker Multimeter

SAVE \$10



The ideal test instrument for hobbyists, also great for the serviceman – rugged, low profile 25 ranges, highly visible display. And you now save \$10.00! Cat Q-1136 WAS \$79.95



THE POCKET COM II WALKIE TALKIE

Great gift for any child! Full 2-way transmission in a unit so compact it could fit into your pocket! Ideal for construction workers on the job or for mothers who want to know what Johnny is up to in the backyard. Makes an ideal Christmas gift!

Cat D-1101

Complies with spec PEMEO01 of the Australian

REQUIRED! Complies with spec. RFME001 of the Australian Dept. Of Communications.

LICENCE

SAVE A FORTUNE!

At last – a horn speaker you can use anywhere! Until now all horn speakers have suffered a similar problem: corrosion. Now a plastic horn speaker which doesn't

sacrifice any of the acoustic qualities of its aluminium counterparts - but doesn' its aluminium courteins suffer from corrosion! \$10

4 SECTOR ALARM CONTROL INSTALL MODULE

Protect your home and valuables with this alarm control unit. Virtually identical in op. and circuitry to one of the advanced alarm control units you pay \$\$\$ more for! Cat L-5056

ONLY 56950



78

Are you forever sitting with a phone to your ear waiting for the person on the other end of the line to come back to the phone? Well now you can relax because this unit will let you know when there is a person on the other end. Easy to attach via the sucker supplied. Also ideal for conferences or for when those overseas relatives cali—now everone can hear the caller. Cat Y-1174



WHAT A BUY!

Deluxe Slimline TEAC HI FI at a Dick Smith bargain price!

Looking for a great hi fi? Check these out: Teac's new A-505 DC integrated stereo Amplifier and the matching T-303 AM/FM Stereo Tuner. 30W plus per channel, full range of inputs and switching for the most demanding audiophiles. And the new slimline appearance looks a million dollars! AMPLIFIER (Cat A-1305) TUNER (Cat A-1505)

BOOK VALUE

GE OPTO BOOK

Great Value! Cat B-4028

\$0 95

NATIONAL LOGICTTL DATA MANUAL

Contains complete information on the extensive National Semi conductor bi polar logic families. Cat B-4022

Cat B-4023 \$595

AUST'N RADIO

Get into the exciting hobby of scanning with this superb publication. A must for any scanner enthusiast. Cat B-9600

From all of us at Dick Smith to all customers, suppliers and We extend to you the compliments of the season — and we this Christmas

Santa is good to you this summer than 1984 hrives were and 1984 hrives Electronics . Santa is good to you everything you and 1984 brings you everything friends ...





See Page 120 for full address details.

DSE/ABSO/PAI



Convert your car to . . .

Breakerless ignition

Are you one of those hobbyists who would like to have a breakerless ignition system on your car but do not wish to make your own optical system? Then here is your chance to change over to a breakerless system using a Hall Effect device in your distributor.

Our Transistor Assisted Ignition system published in February of this year included details of an optical breakerless system using a phototransistor, LED and a suitable interface circuit but the reader had to solve the mechanical problems. He had to make his own optical breaker plate which requires very precise metalwork and he had to make up a mounting arrangement for the LED and phototransistor.


Now these mechanical problems have been solved with a new Hall Effect distributor kit. Made by EDA Sparkrite of the UK, it is marketed by Jaycar. The kit includes all the hardware necessary for the distributors in most cars sold in Australia. There are a couple of glaring exceptions unfortunately, including the much venerated six-cylinder Holden Kingswood. A crying shame.

Of course, there's nothing to stop you from making your own hardware to match the distributor in your car.

The basic mechanical concept is

simple. A Hall Effect switch is mounted in place of the contact points and a ring magnet is fitted over the distributor cam. The magnet has the same number of poles as the cam has faces and these are equally spaced to provide the appropriate timing pulses from the Hall Effect device to the following electronic ignition circuitry.

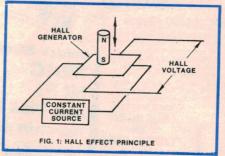
The advantage of using an allelectronic system such as this Hall Effect system rather than a hybrid system utilising the distributor contact set is that,




once set, the ignition timing will always be right. It will not vary due to the gradual wearing down of the contact breaker rubbing block and there will be no "timing scatter" due to distributor cam wobble or wear in the bearings.

Even with a brand new distributor the timing differences from cylinder to cylinder can be as much as 5% and this does contribute to uneven running, particularly at idle speeds. With the Hall Effect system installed the engine will run noticeably smoother and it will stay that way.

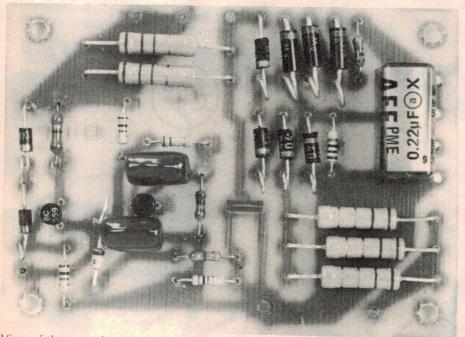One small point to remember is that even an all-electronic ignition system is not completely maintenance free. The spark plugs still have to be checked for fouling and correct gap setting at regular intervals of say 5000 to 10,000 kilometres. And at these times it would probably also be wise to do a routine check of timing, just to satisfy yourself that it is still "spot-on".



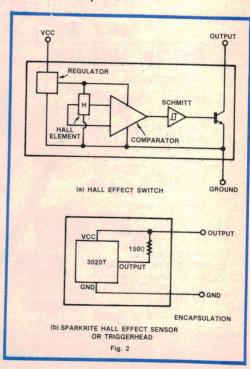View of the assembled PCB. Note the shock relieving loops in the diode leads.





The distributor kit comes packed in a plastic wallet and is suitable for use with most distributors.


What is the Hall Effect?

The Hall Effect sensor principle is shown in Fig. 1. It consists of a thin strip of semiconductor material through which a current is passed. When a magnet is brought near, such that its field is directed at right angles to the face of the semiconductor, a small voltage

appears at the contacts placed across the narrow dimension of the strip. As the magnet is removed the voltage drops to zero.

A practical Hall Effect device is depicted in Fig. 2a. This comprises a voltage regulator, a Hall cell, a comparator connected across the Hall cell and a Schmitt trigger which drives an open-collector transistor. The comparator and Schmitt trigger render the Hall Effect switch characteristics less dependent on the magnetic flux.

Fig. 2b shows how the three-terminal Hall Effect device has been used by Sparkrite in their sensor. Effectively, the

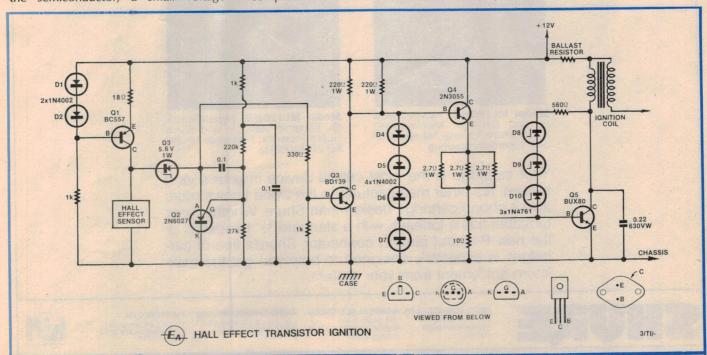

Make your music happen with Shure's new line of stereo cartridges



Models M99E and M92E. Excellent sound on a tight budget. Eliptical stylus, alloy shank. Suits both 1/2" and P-mount tone arms.



Models M105E and M104E. Outstanding performance on a limited budget. Suits both 1/2" and P-mount tone arms.



Model 111E and ML110HE. Unique stylus shank and hyper-elliptical diamond tip. For both 1/2" and P-mount tone arms.



Model ML140HE. Hyperelliptical tip and Beryllium Microwall/Be[™] Stylus Shank for ruler flat response and superlative tracking.



Model ML120HE. Hyperelliptical tip, Dynamic stabilizer and Stylus Guard Protector. Response is ruler flat 20-20,000Hz.

Your cartridge is the most critical device in your sound system. No other manufacturer in the world knows more about phono cartridge design than Shure. Whether your turntable has a tonearm with a standard 1/2" headshell or the new P-mount plug in connector, Shure's line of cartridges is especially designed to help you get the maximum enjoyment from your system.



342 Kent Street Sydney NSW 2000 (02)29 6731

AUDIO ENGINEERS P/L NOMIS ELECTRONICS 689 South Road BLACK FOREST S.A. 5035 (08)293 4896 Cnr. Jane & Buchanan Sts WEST END QLD 4101 (07)448947

AUDIO ENGINEERS (QId)

MARKETEC P/L 18 King William Street Sth Fremantle WA 6162 (09)335 8275



Breakerless

three-terminal device has been converted to a two-terminal device by the connection of a 150Ω resistor between the output and Vcc. By making the GND terminal of the sensor the metal foot, the device has only one lead connection which makes it equivalent to a standard contact breaker, although it is not intended to switch the coil directly or carry heavy currents.

The Sparkrite sensor is actually an epoxy encapsulation of a Sprague UGS-3020T Hall Effect switch (or equivalent) together with the aforementioned 150Ω resistor. The Sprague device is very similar in appearance to a TO-92 plastic transistor, although perhaps a little smaller, and is rated for an operating temperature range from -40 to 125 degrees Celsius.

Sparkrite operate the Hall Effect device

by use of a ring magnet. In fact it consists of a number of radial magnets with all north poles on the inside of the ring and the south poles used to turn on the Hall Effect device.

The circuits

Two circuits are shown, one using the Hall Effect sensor to trigger the Transistor Assisted Ignition first described in December 1979 and subsequently updated in February 1983 and the other showing adaptation for the Capacitor Discharge Ignition first described in August 1970 and updated in July 1975. We shall discuss the modification to the transistor ignition first.

Q1 is a constant current source which feeds the Hall Effect device and zener diode D3. The current from Q1 is set at about 33mA by diodes D1 and D2. Strictly speaking a single resistor could have been used instead of Q1 but the constant current source makes the switching of the Hall Effect device independent of battery voltage fluctuations which would otherwise lead to changes in ignition timing.

+ 12V VIA IGNITION SWITCH HALL EFFECT SENSOR Parts overlay diagram for the new Transistor Assisted Ignition PCB. 1000 *PART OF ORIGINAL CO HALL EFFECT TRIGGERING FOR CDI This circuit shows how to adapt the July 1975 CDI to Hall Effect triggering.

PARTS LIST

TAI Adapter Kit

- 1 Hall Effect distributor kit (EDA. Sparkrite)
- printed circuit board, code 83ti12, 93x69mm
- BC557 PNP transistor
- 5.6V zener diode
- 1N4002 diodes

RESISTORS (1/4W or 1/2W, 5%) $1 \times 220 k\Omega$, $1 \times 27 k\Omega$, $1 \times 1 k\Omega$, $1 \times 330 \Omega$, 1x18Ω.

CDI Adapter Kit

- 1 Hall Effect distributor kit (EDA Sparkrite)
- piece of stripboard (see text)
- BC557 PNP transistor BD139 NPN transistor
- BD140 PNP transistor
- 1N4002 diodes
- 1 5.6V zener diode

RESISTORS

 $1 \times 2.2 k\Omega$, $4 \times 1 k\Omega$, $1 \times 330 \Omega$, $1 \times 47 \Omega$, 1x18Ω.

When one of the south poles of the ring magnet is adjacent to the Hall Effect device it is turned on and so the voltage at the collector is less than 5 volts. This means that no current flows through zener diode D3 and so Q3 is not biased on. In turn, this means that Q4 and Q5 are conducting and current is flowing through the ignition coil.

When the magnet south pole moves away, the Hall Effect device stops conducting and the voltage at the collector of Q1 rises so that D3 conducts, turning on Q3. This turns off Q4 and Q5 which allows the coil to fire the spark plug.

Q3 does not remain in conduction for the whole time that the Hall Effect device is off. This is because of the dwell extension feature provided by the programmable unijunction transistor (PUT) Q2. This operates as follows:

When D3 is not conducting, the anode of Q2 is essentially held at chassis potential by the base resistors of Q3. Then, when the Hall Effect device turns off, D3 conducts and raises the voltage on the anode of Q2. Because of the 0.1µF capacitor connected to the anode, this also jacks up the voltage on the gate of Q2 which would otherwise be held at around 1.3 volts by the $220k\Omega$ and $27k\Omega$ resistors. Subsequently, the voltage at the gate bleeds away until, 0.9ms after the Hall Effect device turned off, the gate voltage has fallen to 0.6V below the anode. This causes Q2 to conduct and so remove the forward bias from Q3. This causes Q4 and Q5 to turn on again and thus current passes through the coil earlier than it otherwise would have without the dwell extension facility.

Breakerless ignition

The rest of the circuit operates the same as the original circuit which was fully described in the February 1983 issue.

The CDI version

As mentioned previously this version suits the CDI circuits described in August 1970 and July 1975 but it could probably be adapted to suit any CDI system which used a similar method for triggering the SCR

As with the version for the Transistor Assisted Ignition, Q1 is a constant current source which supplies around 33 milliamps to the Hall Effect device and D3. When the Hall Effect device is off, D3 is not conducting and so Q2 is biased off as is Q3. When a south pole of the ring magnet moves away from the Hall Effect device it switches off and allows D3 to conduct. This turns on Q2 and Q3 and delivers a pulse of current to the gate of the SCR via the 0.22µF capacitor. This triggers the SCR into conduction.

For further information regarding the CDI circuit refer to the articles as previously mentioned.

Construction

As far as construction of these circuits is concerned, we have developed a PCB (code 83ti12, 93 x 69mm) for adapting the transistor ignition to Hall triggering. For the CDI conversion, we will leave it to readers to add on the extra circuitry using Veroboard or matrix board.

The new Transistor Assisted Ignition PCB is very similar to the previous PCB and is only modified for the input circuitry. Consequently, readers will find it easy to remove the components from

the old PCB and place them on the new PCB without changing the lead spacings. Note the heat expansion and shock relieving loops in the diode leads.

Follow the parts overlay carefully, making sure that the polarity conscious components are oriented correctly. The mounting holes and wiring positions are the same as before so no wiring modifications will be necessary. Mounting details are the same as in the previous article.


Modifying the distributor


The Hall Effect device has been designed by Sparkrite to suit most vehicles with these distributors: Motorcraft or Autolite (4 and 6 cylinders), Bosch (all 4 cylinder), Lucas (4 and 6), AC Delco D202 and D204 (4 cylinder), Toyoto Nippondenso (4 cylinder), and Hitachi Datsun (4 cylinder).

Each kit as supplied from Jaycar includes comprehensive installation instructions. Basically the installation is as follows. First, the contact breaker points and capacitor are removed from the distributor. This also includes a damping rubbing block which is used in some distributors opposing the contact points rubbing block. The grommet or screw connector for the contact points lead should also be removed.

Now the correct cam adapter and adapter plate should be selected, the correct type for the particular distributor being listed in the instructions. The 6-cylinder magnet has four keys to locate it on the cam adapter while the 4 cylinder magnet has three. Place the cam adapter over the cam and then the ring

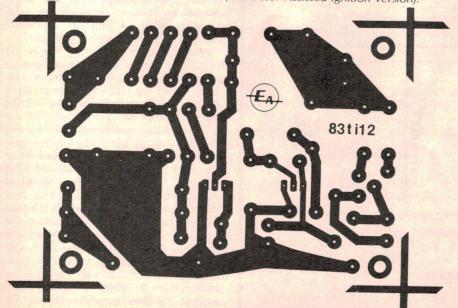Below: actual size artwork for the PCB (Transistor Assisted Ignition version).



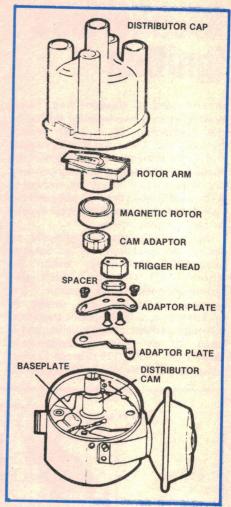

Reproduced from the kit manual, this diagram shows how a typical distributor is adapted to Hall Effect triggering.

magnet, which holds the adapter tightly over the cam.

Note that for clockwise-rotating distributors the painted dot side of the magnet should face upwards. Conversely, the dot should face downward for anticlockwise rotating distributors. This is important since ignition timing will be incorrect if not adhered to.

How the Hall effect sensor is placed into the distributor using the adapter plate and spacers. The spacers are used to adjust the height of the sensor so that the magnet and sensor are centred. The adapter plate allows adjustment of the sensor so that it is tangential to the magnet. Diagrams in the instructions show how this is done. Note also that the air gap between the magnet and sensor face should be around .015 inches or 0.4mm. This adjustment is usually only possible at one point of rotation of the magnet. Just make the gap small but not so small as to cause scraping at the closest point of rotation.

Note that the flexible earth lead must be reconnected.



If Felicity had a better VDU, you'd get better work from Felicity.

In this day and age, productivity and technology go hand in hand – the more advanced the tool, the higher the productivity.

So it is with monitors.

Today there seems to be a belief that because computers are high technology, there's little real difference between the peripherals. So buyers tend to buy on price alone.

But as we all know, lower price is seldom synonymous with higher quality.

Since 1972, Mitsubishi has led the world in video monitor CRT (cathode ray tube) development. In that year, they produced the world's first high resolution colour CRT. The following year, 1973, saw the development of the semitoroidal self-convergence deflection-yoke system, and the long-persistence phosphor colour display screen.

Since then, almost every year has seen further new developments from Mitsubishi – the original internal magnetic shield system; the high-grade broadcasting colour CRT; the Meniscustype projection CRT; the multi-step focus electron gun; the original arc-shield gun; the first anti-reflective coating – the list goes on. Yet despite this massive R & D investment, the price of a top quality Mitsubishi monitor is only a little bit more – and it could save you so much in the

long term.
Mitsubishi monitors, both colour and mono, cased and uncased, are distributed in Australia by Nexus Electronics of Sydney; and Sycom of Melbourne, two companies dedicated to the pursuit of excellence. Their marketing and service support is second to none, anywhere in the world; which


is precisely why they were chosen by Mitsubishi Electric, itself a company devoted to excellence in electronics.

In addition to monitors, Nexus and Sycom also distribute Mitsubishi semi-conductors, and their 51/4" and 8" disk drives – both products of superior Mitsubishi technology

Mitsubishi technology.
For information, on any of our products, simply circle and return the Readers' Service Card, and we'll get full information, including technical specs, to you right away. It's all part of the service, because we do things just that much better.



Mitsubishi semiconductors

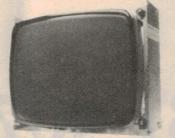

Mitsubishi display monitors



Mitsubishi disk drives

Just that much better

Available throughout Australia. For your nearest distributor contact:

NEXUS

ELECTRONICS PTY LTD. (Inc. in NSW) 339 Pacific Highway, Crows Nest, NSW Australia, 2065. Telephone: (02) 922 1722

SYCOM

Systems and Components Division of SYSTEMS RELIABILITY (AUST) PTY LTD. 49-53 Tope Street, South Melbourne, 3205. Telephone: (03) 699 8433

PANIC

THERE IS NO NEED TO RUSH AROUND AT LUNCHTIME, OR AFTERWORK.

OPEN 7 DAYS

9 am to 5.30 pm (9 pm Thursday)

BIRHERHEAD ELECTRONICS

THE ONE STOP ELECTRONICS SHOP

81 4077

SHOP 71 BIRKENHEAD POINT, Harbourside, Drummoyne 2047

Breakerless ignition

Now the lead from the Hall Effect device can be fed through a suitable grommet to the electronic ignition. In most cases, it should be possible to use the original grommet used with the points lead. The lead from the Hall Effect sensor can either be soldered directly onto the electronic ignition input, or you may prefer to use suitable plug-in connectors. Make sure that the lead from the sensor to the grommet has sufficient slack to allow for full vacuum advance.

Timing the engine initially can be difficult so we recommend this method. Simply connect the lead from the Hall sensor to the positive of the battery via a 220Ω resistor. Now connect a multimeter between ground and the Hall sensor lead. Rotate the distributor by rotating the engine by hand and watch the voltage reading on the meter. It should read about 4V when the south pole is activating the sensor and about 11 to 12 volts when the magnet has passed. This transition from low (4V) to high (11V) is the firing point.

Loosen the distributor and rotate it so that the transition from high to low occurs at the correct static ignition timing point for your vehicle. Note that the engine should always be fully rotated in the correct direction and not reversed when performing this timing. This is important since there is considerable hysteresis in the Hall Effect sensor and you are likely to find the wrong firing point if you reverse the engine and then bring it forward again.


When the firing point is correct, check that the rotor arm is facing the relevant cylinder position (usually cylinder 1) on the distributor cap, or the timing mark for number 1 cylinder on the distributor body. The distributor should only have to be moved slightly from its original position. The rotor arm should now be located so that, at maximum and minimum settings of vacuum and centrifugal advance, the distributor cap contact is always located within the range of the rotor arm.

If this is not the case and you find the rotor arm positioned between two adjacent distributor cap contacts, then

the Hall adapter plate will have to be modified so that firing occurs at the correct point. Clamp the sensor with a small G-clamp and position the distributor so that the centre of the rotor arm is opposite the appropriate distributor cup contact. Now move the Hall sensor so that the device goes from low to high at this firing point.

A bracket can now be made to support the sensor in this position. Alternatively, holes can be directly drilled in the advance plate to locate the sensor.

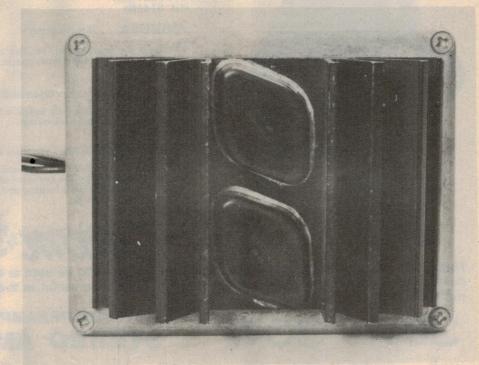Finally, the engine should be dynamically timed according to the procedure in the workshop manual.



This circuitry is all mounted in a metal diecast case measuring $118 \times 93 \times 56$ mm. A finned heatsink is essential for transistors Q4 and Q5.


3 FROM AMERICA IN YOUR HOME, EVERY MONTH, FOR LESS THAN \$29! Now, 73: Amateur Radio's Technical Journal has a special offer for Electronics Australia readers. For a special introductory price of under A\$29, get 73 magazine, a leader in the electronics field for over 23 years. Microcomputing applications. Enjoy 146 pages of: • Construction projects. Certificates and awards. · Satellite news. · Operating tips. International reporting. · Contest rules. Product reviews. Subscribe today and enjoy our special rate! Amateur Radio's Technical Journal 73: Amateur Radios's Technical Journal. OK! I want a subscription to 73: Amateur Radio's Technical Journal. ☐ Please send me 12 issues of 73 for US\$25 (that's less than \$29 a year!), ☐ I have enclosed a check or money order. US funds drawn on US bank. surface delivery ☐ Please send me 12 issues of 73 for US\$55, airmail delivery. ☐ Please charge my credit card. ☐ Please bill me. ☐ American Express ☐ Master Card ☐ VISA Exp. Date -Card # Name Address_ Post Code 73: Amateur Radio's Technical Journal PO Box 931, Farmingdale, NY 11737, USA. Offer expires on February 29, 1984.

Special Annoucement

Jaycar Electronics is proud to announce a range of very low cost "Turtle" like robot kits. Don't let the low prices fool you - they are not toys.

The units feature solderless connections with explicit illustrations to ease assembly. Only simple tools (i.e.

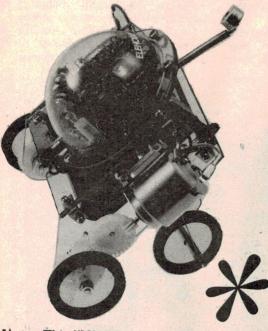screwdriver, pliers etc.) are needed to assemble.



PIPER MOUSE

This "microbot" is powered by 2 DC motors that drive wheels. When a special ultrasonic whistle is blown, the unit goes left, right, straight ahead according to your command. Complete, including perspex dome cover! Be a Pied Piper! Cat. KJ-6680

ONLY \$39.95

AVOIDER (not illustrated)

Similar to the Piper Mouse, but this unit travels on its own. It avoids objects because it has an infra-red beam system. Very clever! Cat. KJ-6682

\$44.95

LINE TRACER (not illustrated)

This robot will automatically follow a black line drawn onto a sheet of paper. It uses an infra-red feed back system. Cat. KJ-6684

\$39.95

MEMOCON CRAWLER (not illustrated)


This robot is controlled by a keyboard which is supplied. The operation of the unit is programmed by the keyboard and stored in RAM. All movements can be controlled as well by lights (beams) and sound (buzzer). A very sophisticated unit. Cat. KJ-6686

\$79.95

Note: The "Microbots" work well on their own but can also be used as a platform for robotic development. If you are a robot experimenter you will find them useful as they help resolve the mechanical parts problem.

W+30V

STEREO PREAMPLIFIER EREO AMPLIFIER

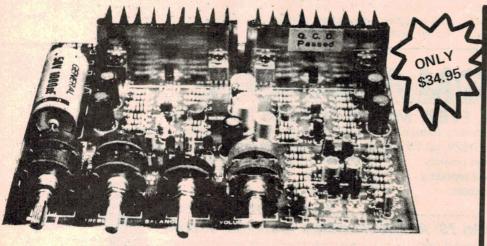

- Fully built and tested
- Separate bass, treble, balance and volume controls
- Less than 0.1% distortion
- Mic, phono and aux. inputs (line)
- Power supply components on board

Back at last! No hassle amplifiers. Just connect a transformer, speakers a signal and you're away!

STAGGERING VALUE

\$34.95!!

MICRO COMPUTER POWER SUPPLY

All multi-polarity D.C. supply problems solved! This fully built and tested unit provides you with REGULATED power as follows: -

- -5V @ 0.5A, +5V @ 6A,
- -12V @ 0.5A and
- +12V @ 2.5A!!

(You can modify it to give $\pm/-15V$

- Current limit on all outputs
- Heavy duty Darlington Transistors used
- Only power transformer(s) needed

A price breakthrough at -\$39.95!!

(Suitable transformers commonly available)

31DIGITAL



Low cost unit. Completely self-contained. No longer an expensive proposition! This easy-to-build kit (takes about 1 hour) is self-contained, compact and even comes with a front panel filter/bezel. It can be battery 6V or IC powered.

200mV. Full scale (+/- 199.9mV)

Input impedance 10 to the twelvth ohms Required DC 5-6V @ 150mA

Guaranteed to reset to zero at zero input voltage

Automatic reverse polarity indication

Assembly instructions include notes on using your DPM for: Amp-meter, AC-Voltmter, Anmeter, Thermometer, Frequency Counter, Capacitance Meter (circuits supplied) \$29.95

STAGGERING VALUE

Cat. KJ-6670

MN3001 BUCKET BRIGADE

used in many projects lately and has been very hard to get. available from us at a lower-than-normal price. They are now available from us at a lower-than-nor NORMALLY \$22.50

ONLY \$19.50 each — Cat. ZK-8001



GOLD PLATED WIRE WRAP SOCKETS Incredible



Value!



IEC Cable Connectors



Most imported equipment these days now uses IEC-320 style AC power inlet connectors. Indeed, the electronics mags will soon be specifying these connectors on many of their mains powered projects to simplify (and therefore make safer) mains wiring. Jaycar now stocks a range of ELECTRICITY AUTHORITY APPROVED mains line cords. We have them in straight entry, left and right entry with and without standard 240V mains moulded plug. Each cord is a generous 2 metres long and is rated at 7.5 amp continuous.

Cat. No	Description	Price
PS4302	LINE CORD STRAIGHT ENTRY 2M	\$3.95
PS4304	LINE CORD R/HAND ENTRY - 2M	\$3.95
PS4305	LINE CORD L/HAND - 2M	\$3.95
PS4306	LINE CORD STRAIGHT ENTRY WITH	
	240V PLUG - 2M	\$4.95
PP2302	IEC 320 CHASSIS PLUG	\$2.95
WM4530	2 PIN 240V PLUG MOULDED TO 2M FIG. 8	
	7.5 AMP CORD - BLACK IN COLOUR	\$2.95
	(Ninter the first E items are grow in colour)	

True proportional control with this kit. Includes recommended joystick unit.

Following the spectacular success of the DP2010 Digital Multimeter kit, we now have an ENGINE ANALYSER KIT! But the spectacular thing is the price! It is ACTUALLY CHEAPER than the DPM-05 Display and Case!! The Minitune will measure voltage, resistance (down to a very low range), RPM and Dwell Angle.

S42.95

TEST LEADS TO SUIT ONLY \$2.95

FERGUSON TRANSFORMERS

ı	MF-1000	PL9/5VA PCB	\$7.90
ı	MF-1002	PL12/5VA PCB	\$7.90
l	MF-1004	PL 15/5VA PCB	\$7.90
ľ	MF-1006	PL 18/5VA PCB	\$7.90
ı	MF-1009	PL24/5VA PCB	\$7.90
ı	MF-1012	PL30/5VA PCB	\$7.90
ŀ	MF-1015	PL40/5VA PCB	\$7.90
ı	MF-1018	PL18/12VA PCB	\$8.95
ı	MF-1021	PL24/12VA PCB	\$8.95
ı	MF-1024	PL30/12VA PCB	\$8.95
ı	MF-1027	PL1.5-18/20VA LP	\$17.95
ı	MF-1030	PL12/20VA LP	\$14.50
ı	MF-1033	PL15/20VA LP	\$14.50
ı	MF-1036	PL18/20VA LP	\$14.50
ı	MF-1039	PL24/20VA LP	\$14.50
ı	MF-1042	PL30/20VA LP	\$14.50
ı	MF-1045	PL40/20VA LP	\$14.50
ı	MF-1048	PL12/40VA LP	\$17.95
ı	MF-1051	PL15/40VA LP	\$17.95
ı	MF-1054	PL18/40VA LP	\$17.99
ı	MF-1057	PL24/40VA LP	\$17.9
ı	MF-1060	PL30/40VA LP	\$17.9
ı	MF-1063	PL40/40VA LP	\$17.9
ı	MF-1066	PL30-9/60VA LP	\$20.9
1	MF-1069	PL12/60VA LP	\$20.9
ı	MF-1072	PL15/60VA LP	\$20.9
١	MF-1075	PL18/60VA LP	\$20.9
1	MF-1078	PL24/60VA LP	\$20.9
1	MF-1081	PL30/60VA LP	\$20.0
	MF-1082	PL40/60VA LP	\$20.9
	MF-1087	PPB8/1000 Bell transformer	\$13.9
	MF-1092	TS115/125B 115V STEPDOWN	\$79.5
	MF-1095	PF3577/JT144 56VCT 2 amp	\$34.5
	MF-1098	OP590 Line output transformer	\$45.0
	MM-2015	PF4361	\$39.5
	MM-2016	PF4362	\$49.5
ı	MM-2017	PF4363	\$49.5

VIDEO SENSATION AT LAST

A Video Enhancer/ Distribution Amplifier designed **EXCLUSIVELY** for AUSTRALIA

12 Volt AC Adaptor only \$12.95



NOT A KIT BUILT, TESTED AND GUARANTEED KIT VERSION ONLY \$39.50

Cat. AV6501

Jaycar has had designed a high quality, high performance Video Enhancer which is specifically for the Australian 625 line 50 frame

PAL-D system.
As far as we know it is the ONLY Australian designed, Australian built unit available!
But, guess what? The Jaycar AV6501 Enhancer is CHEAPER than

its inferior imported Asian counterparts!! This unit is professionally designed and University tested! It works

SPECIFICATIONS

SPECIFICATIONS

a1 Maximum enhancement, not less then +8.3dB © 2MHz

21 Enhance dissibled (Bypess) response, DC to BMHz, -0.5+1.0dB,

a3 Colour Subcernier 0BB notch frequency, tunable to 4.43 MHz,
0.5dB, all settings.

a49 Colour Subcernier 0BB notch frequency, tunable to 4.43 MHz,
0.5dB, all settings.

a50 Enpirifer group delay, less than 0.0750 S

a50 Enpirifer group delay, less than 0.15 volts p-p. (Sync. is clipped first.

a60 Power 12V AC © 100mA

7 Controls, DN/OFF, ENHANCE, ENHANCE/BYPASS SWITCH,

CORE/GAMMA CONTROL

81 Input connector, RCA socket

99 Output connector, RCA socket x 3

DESIGN FEATURES

9 Output connector, RCA socket x 3
DESIGN FEATURES

1 A unity gain notch at the colour subcarrier frequency, whose purports to prevent the colour subcarrier frequency, whose purports to prevent thornimance to luminance errors at high enhance levels.

2 A closed loop configuration with lead tag compensation to achie stable, well defined gain

3 DC coupling, eliminating large capacitors in series with the visignal and achieving DC response for applications requiring it.

44 Low output impedance prior to termination resistors, enabling up three outputs to exist and be used or left unterminated.

5 A level dependant closed loop response or Gamma control ("Core")

6 Clip on negative going signals at –67 volts into 75 ohms to preve sync errors owing to overshoot.



DP400

MINITUNE

\$42.95

CX-230 ELECTRONIC CROSSOVER

ONLY \$257 Cat. AZ-5030

See previous ad for technical data

Incorporating

ELECTRONIC AGENCIES

SYDNEY

R.P.M 20.000r p

Ref: ETI Dec. '83

F.S.D

SHOWROOMS

117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614 TELEX: 72293

CARLINGFORD RD & PENNANT HILLS ROAD - PHONE: (02) 872 4444

CONCORD ARRAMATTA ROAD - PHONE: (02) 745 3077

HURSTVILLE 121 FOREST ROAD - PHONE: (02) 570 7000

NUMBER 1 FOR KITS

POST AND PACKING CHARGES
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)
\$100 - \$198 (\$8.00) Over \$199 (\$10)
"Free INSURANCE for Road & Registered Post over \$200"
All heavy or bulky items (over 20kg.) sent Comet Road Freight \$12.00 any in Australia.

SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE
Mon - Fri 9am - 5.30pm: Sat - 9am - 12pm: Thurs night 8.30pm
Mon - Fri 8.30am - 5.30pm. Sat - 8.30am - 12pm: Thurs night 8.30pm

MAIL ORDERS AND CORRESPONDENCE: BOX K 39 HAYMARKET, SYDNEY 2000



Easy-to-build electronic game

Chase 'N' Chomp

Emulating a popular gobble-em-up video game, Chase 'N' Chomp is a hand-held electronic version that will bring hours of enjoyment. Using novel bi-colour LEDs and simple sound effects, the game should prove popular with young and old alike.

No game is valued if it represents little challenge, is predictable and takes no account of a skilful player. With this game you can expect to lose. "Chase 'N' Chomp" is not easy to play. It requires considerable skill, quick reflexes, cunning and a degree of luck. The game also contains an element of surprise due to the unpredictable movements of the game opponent.

Physical layout of the game can be seen in the photographs. Eight bi-colour LEDs are arranged in the maze pattern and, in addition, three LEDs are located in the top right hand corner. Two indicate a win or loss of the game while the third indicates "chomp". Four switches are used: an on/off switch, a start switch which restarts play after each game is completed, and two chase switches which allow opponent attack in either the clockwise or anticlockwise direction.

Upon pressing the start switch, one of the bi-colour LEDs will appear red in one position on the playing field. This is the opponent. A second bi-colour LED will also appear in a different position and this will alternate between green and red at about a one second rate. This is the player.


The object of the game is to "chomp" your opponent before it chomps you. This involves landing on your opponent; in other words occupying the same LED space. It is possible to chomp your opponent while your playing LED is either green or red, but to win, as indicated by a flashing win LED, the player LED must be green at the time of chomping. Accordingly, it is necessary to coordinate your move to chomp your opponent when the player LED is green or a "lose" will be indicated. In other words, don't try to chomp your opponent while it has its little red mouth open!


The chase control switches allow movement of the player LED. The clockwise chase switch moves the player in a clockwise direction through the



maze pattern. Similarly, the anticlockwise chase switch moves the player in an anticlockwise direction through the maze. To increase player difficulty, the chase switches are rendered ineffective unless the chomp LED is lit. Pressing a chase switch before the chomp LED lights will only delay your chance to move.

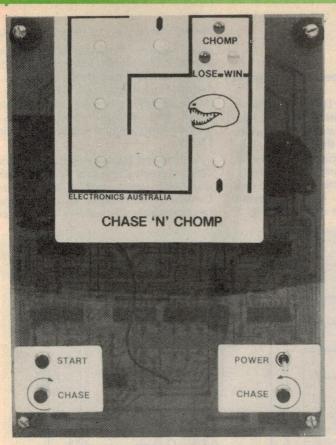
While you are moving your player, the opponent is not idle. In fact the opponent is quite crafty and, although restricted to moving within the maze, can move rather spasmodically. Sometimes, he will even reverse direction to pounce upon and chomp the player. The game is over and a flashing lose LED indicates the player's



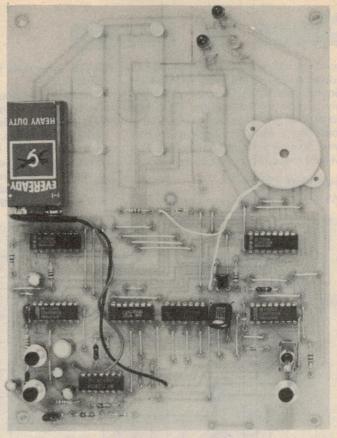

Two stages of construction: completed unit (left) and view of assembled PCB (right).


Fig. 1 (right) shows several different ways of driving the bicolour LEDs while Fig. 2 (below, right) shows the basic scheme for the Chase 'N' Chomp circuit.

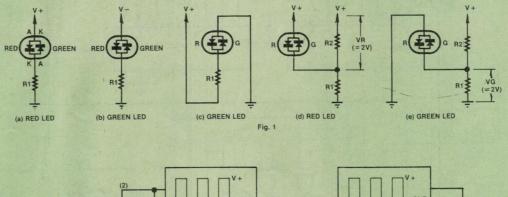


We estimate the current cost of components for this project to be approximately

\$30

This includes sales tax.

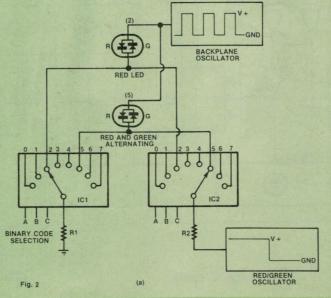

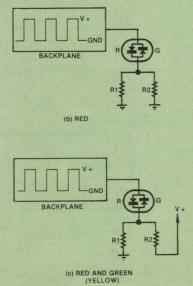

Chase 'N' Chomp

doom. In all cases, if the opponent is allowed to attack, the game will be lost.

Sound effects are simple, providing only a tone for the playing LED. The sound is similar to an ambulance siren, promoting a sense of urgency to the game. Scoring has not been included as it would make the game too expensive.

Bi-colour LEDs

Well that describes how the game is


played. Now let's see how the game operates.

Externally, bi-colour LEDs are similar in appearance to a normal single-colour LED, with two leads and a frosty white package. Internally, they contain two reverse connected LEDs of contrasting colours. Applying a current of between 5 to 30mA in one direction will light one LED while current in the reverse direction will light the other LED. Fig. 1

shows several ways of driving the LEDs.

Fig. 1a shows the circuit for lighting the red LED. This simple circuit can also light the green LED if its cathode is taken to a negative supply as shown in Fig. 1b. For a single supply, it is necessary to swap both the ground and positive connections to light the green LED as in Fig. 1c.

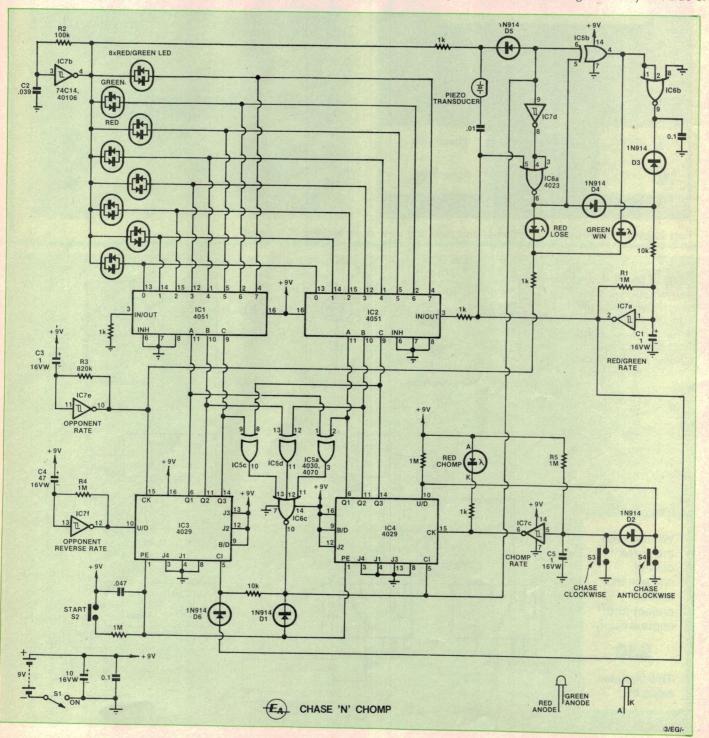Another technique for lighting both the red and green LEDs using a single supply is shown in Figs. 1d and 1e. This requires the use of two resistors, R1 and R2, and has the advantage that only one side of



the LED package must be connected to the ground or positive supply. When the red LED is lit (Fig. 1d), the current is limited by R1, while the voltage drop across R2 will be the voltage drop across the red LED (typically around 2V).

A similar situation applies to Fig. 1e except that, in this case, the current is limited by R2, a voltage drop of around 2V is developed across R1, and the green LED is lit.

Note that a yellow light can be obtained by applying AC to the device. This lights both the red and green LEDs alternately so that the two colours are mixed in the eye to give yellow.

Fig. 2a is a simplified block diagram of the bi-colour LED driving circuit for our game. Note that only two of the eight LEDs used are shown for clarity. IC1 and IC2 are 8-channel multiplexers and these are shown as single pole 8-position switches. A three bit binary code applied to inputs on the multiplexers allows selection of each switch position. For IC1, the common or pole connection is permanently tied to ground via R1. The common of IC2, however, is tied to the red/green oscillator which alternately connects R2 to ground and the positive supply rail.

The backplane oscillator produces a 150Hz signal swinging from the positive supply rail to ground. When it is at the positive rail, LED 2 will be red. LED 5 will also light red when the red/green oscillator is at ground. When the backplane oscillator is at ground, LED 5 will light green provided the red/green oscillator is at the positive rail. LED 2 will be off.

Since the backplane oscillator is relatively fast, and due to the persistence of vision, LED 2 will appear to be continuously on and glowing red. LED 5 will alternate between red and green at the red/green oscillator rate.

To light other LEDs, all that is required is a differing code applied to the multiplexers to access the new switch position.

Circuit details

Although the circuit may at first appear daunting, it can be made simple by dividing it into subsections. IC1 and IC2 are the two central ICs depicted in Fig. 2. These have A, B and C inputs to select the switched outputs from 0 to 7. If, for example, inputs A, B and C are grounded, then output 0 is selected. If


they are all taken to the positive rail then output 7 is selected.

IC7b forms the backplane oscillator, which is also depicted in Fig. 2. This oscillator is formed by a 74C14 Schmitt trigger, a 100k Ω resistor (R2) and a .039 μ F timing capacitor (C2). Operation of the Schmitt trigger is as follows.

Initially, C2 is discharged and so the output of IC7b is high. C2 now charges via R2 until the voltage reaches the upper threshold point of the Schmitt trigger. The output of IC7b then goes low and C2 discharges via R2. When the voltage on C2 reaches the lower threshold of the Schmitt, the output goes high again and the cycle repeats.

Incidentally, some readers may question our use of the term "backplane" which is usually confined to the common electrode in a liquid crystal display. Plainly there is no equivalent in the Chase 'N' Chomp circuit but the backplane oscillator performs a similar function in providing a common line upon which is superimposed an AC signal.

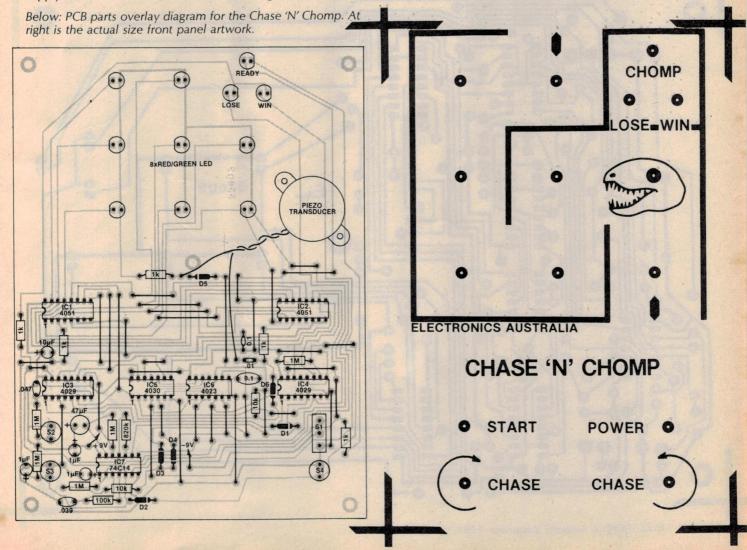The in/out common connection of IC2 is connected to the output of the red/green rate oscillator via a $1k\Omega$ resistor. This oscillator is formed by



Chase 'N' Chomp

Schmitt trigger IC7a and its associated $1M\Omega$ feedback resistor (R1) and $1\mu F$ timing capacitor (C1). Frequency of operation is approximately 1Hz.

Two up/down presettable counters, IC3 and IC4, are used to control the IC1 and IC2 multiplexers. These provide binary codes to the A, B and C inputs and thus determine which of the multiplexer outputs are internally connected to the in/out pin (pin 3). The up/down capability of the counters allows us to direct the LEDs to turn on in the up sequence (clockwise from 0-7) or turn on in the down sequence (anticlockwise from 7-0).

At each positive-going clock input to a counter, its binary outputs, Q1 to Q3, increment or decrement to the next count number. This is decoded by the corresponding multiplexer to light the adjacent LED. IC1 and IC3 form the opponent section of the LED circuit with

IC3 clocked at a 1Hz rate by Schmitt trigger oscillator IC7e. This opponent rate oscillator increments the count of IC3 only when the pin 5 carry-in (CI) input is low. The carry-in signal can thus be regarded as a clock enabling signal.

The output of the red/green oscillator (IC7a) is fed to the Cl input of IC3 via diode D6. When the Cl input is high, the player LED is green and no clocking can occur in IC3. This ensures that the opponent LED can only move when the player LED is red (ie, when the red/green oscillator is low). Two results flow from this: (1) because clocking of IC3 depends on the phase relationship between IC7a and IC7e, the opponent LED moves spasmodically; and (2) the opponent always loses if the opponent moves to chomp.


IC7f, also a Schmitt trigger oscillator, oscillates very slowly and determines whether IC3 counts up or down. This

reverses the direction of the opponent LED. When the output of IC7f is high the counter counts up and consequently the red opponent LED travels clockwise. When the output is low the counter counts down and the LED travels anticlockwise.

Clocking and up/down operation of IC4 is carried out manually and is considerably different to that for IC3. Under normal conditions, capacitor C5 at the input to Schmitt trigger IC7c is charged to the positive rail via R5 and so the output, pin 6, of IC7c is low. The chomp LED is therefore lit. The up/down input is tied high via a $1\text{M}\Omega$ resistor. When the chase clockwise switch is pressed, C5 is discharged and the clock input of IC4 goes high, incrementing the counter. The chomp LED is now off since the Schmitt output is high.

When the switch is released, C5 begins to charge. After about one second the capacitor voltage reaches the upper trigger point for IC7c and the output goes low, relighting the Chomp LED. The

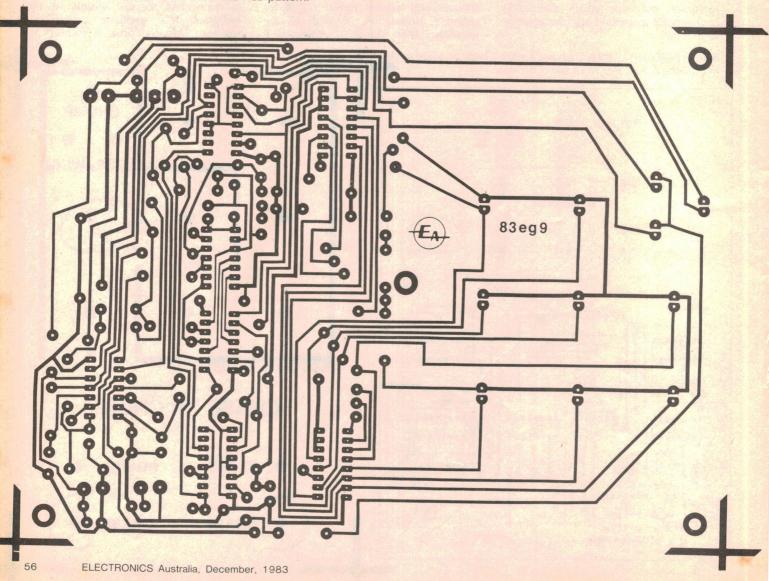Below is an actual size artwork for the PCB pattern.



JUST OPENED THESE AND LOOK AT THESE SPECIALS!

Geoff Wood is well known on the retail electronics scene in Sydney. Now he's opened his own store in a brand new location and he's stocking the broadest range of prime quality National Semiconductor product ever stocked at a retail level in Sydney. The specials listed will be available only while stocks last - so get your orders in early. Many other specials for personal shoppers only.

MEMORY MM2114N	1.95	LINEAR DEVICES LM349N HIDE BAND UNCOMP QUAD 741 OF	0.95
MM2114N-055	0.95	LM309K SV TO-3 REGULATOR	1.80
CMOS		LM338K	8.80
CD4007C	0.40 s inv.	LM381N LOW NOISE DUAL PREAMPLIFIER	1.45
CD4008C	0.85	LM386N-1	0.55
CD4015C	0.75	LM565CN EVER POPULAR PHASE LOCK LOOK	0.95
CD4028B BCD-DECIMAL DECODER	0.85	LM723CN	0.45
CD4050B HEX NON INVERTING BUFFER	0.45	UA741HC METAL CAN VERSION	0.95
CD4069	0.35	UA741PC MOST POPULAR OP AMP EVER MA	0.35 DE
CD4070	0.35	LM7805CT	0.75
CD4160B	0.95	LM7812CT TO-220 12 VOLT POSTIVE REGU	0.75
CD4175B	0.95	LM7815CT TO-228 15 VOLT POSTIVE REGU	0.75
CD4584B	0.85	LM7905CT	0.85
CD4724B	0.85	LM7912CT TO-220 12 VOLT NEGATIVE REG	0:85
MM74C04	0.35	LM7915CT TO-220 15 VOLT NEGATIVE REG	0.85
MM74C86	0.35	LM78L05ACZ	0.35
MM74C150	3.80	LM78L12ACZ	0.35
MM74C160	0.95	LM78L15ACZ	0.35
MM74C162 DECADE COUNTER, SYNCHRONOUS	0.95	LM79L05ACZ	0.70
MM74C175	0.95	LM79L12ACZ	0.70
MM80C97	0.70	LM79L15ACZ	
			/

ODEO		
OPTO MA1026ALR time/temperature module	27.00]
DL1416 4 DIGIT ALPHA NUMERIC D	36.00	,
WITH INBUILT DECODER/DR	IVER.	
NSM39152 10 SEGMENT BARGRAPH MOD		
WITH INBUILT LOGARITHM	C DRIVER.	
NSL4855 RED 5 MM	0.15	
NSL4955 GREEN 5 MM	0.20	
NSL5086 RED 3 MM	0.15	
TIL313	1.50	
DECIMAL POINT.		
RED BEZEL	1.95	
BLACK SURROUND.		9 18
OTHER BEZE AVAILABLE ASK.		
SOCKETS S100-S TRUE \$100 BUS EDGE CON		10
MOTHER BOARD WITHOUT M		
AXR-3-11 FEMALE	3.95	
AXR-3-12	2.05	
AXR-3-31 FEMALE	4.40	
AXR-3-32 MALE	2.40	

	AXR-LNE-11	6	25
	AXR-LNE-12	6	10
	AXR-LNE-31	6	25
	AXR-LNE-32	3	45
	DB25P D TYPE PLUG SOLDER	2	35
	DB25S D TYPE SOCKET SOLDER	3	45
	DISCRETE 1N914 OLD OLD FAVOURITE SIGNAL DIG	0	05
	2N222A NPN GENERAL PURPOSE TO-18	0	48
	2N2904 PNP GENERAL PURPOSE TO-18	0	40
	2N3019 NPN MEDIUM POMER TO-5	0	69
	2N3053 NPN MEDIUM POMER TO-5	0	64
	2N4032 NPN MEDIUM POWER TO-5	0	64
	2N4360 VERY POPULAR FET	0	60
	2N5485	0	70
	2N5656 NPN POWER TO-126	0	92
	2N6707 NPN MEDIUM POMER TO-92 PLUS	0	49
	PN3563 NPN UHF TO-92	0	18
	PN3643 NPN MEDIUM POWER TO-92	0	18
-	TIP3055 NPN POMER TO-220	1	20
1	The second secon		

NATIONAL
SEMICONDUCTOR
DATA BOOKS
AUDIO/RADIO 9.25
CONTAINS WEALTH OF INFORMATION ON
PREAMPS, AM/FM/STEREO, POWER AMPS AND
FLOOBYDUST.
ADV. LOGIC 9.25
COVERS ADVANCED LOGIC FAMILIES
(74ALS AND 74AS).
CMOS 10.95
CONTAINS DETAILS ON 74C AND CD4000
SERIES. INCLUDES SPECIAL FUNCTION
LOGIC, MEMORY AND APPLICATION NOTES.
LIN APPLIC 17.00
FROM NATIONAL SEMICONDUCTOR, THE BEST
APPLICATION BOOK AVAILABLE.
LINEAR DATA 2 VOLS
PER PAIR 20.00
THE FINEST COLLECTION OF DATA AND
TYPICAL APPLICATIONS ON OP AMPS, REGS
COMPARATORS, REFERENCES, INSTRUMENT
AMPS, ANALOG SHITCHES, SAMPLE & HOLD,
BUFFERS, SPECIAL FUNCTION, AUDIO AND
SPEECH DEVICES EVER PUBLISHED.
LOGIC 9.95
COVERS 7400,741,74H,74LS,74S PLUS A
WIDE RANGE OF PROPRIETARY PARTS.
TRANSISTOR 7.00
MHO NEEDS TRANSISTORS? APPARENTLY
ENERVANE THE BOOK PHOLINES ON PH.

MJ, TIP, FETS ALL IN ONE HANDY VOLUME.

TEXT ON POWER SUPPLY CONSIDERATIONS,

AD/DA ADD3501

DAC0808

12.00


2.25



National Semiconductor

8.30 to 5 Monday to Friday, 8.30 to 12 Sat. Mail Orders add \$3.00 to cover postal charges. Next day delivery in Sydney add \$5.00. All prices INCLUDE sales tax. Tax exemption certificates accepted if line value exceeds \$10.00.

\$10.00 minimum Bankcard Orders.

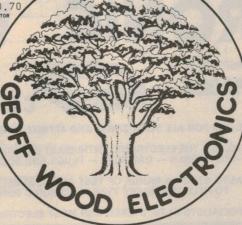

FREE DATA BOOK of our choice to the first 50 purchasers mentioning this advertisement.

GEOFF WOOD ELECTRONICS

PTY LTD Incorporated in N.S.W.

656A Darling St, Rozelle 2039 (One door from National Street) Tel: 810 6845

Chase 'N' Chomp

chase anticlockwise switch operates in a similar manner to the chase clockwise switch with the exception that the up/down input of the counter is pulled low with the closing of the switch. This decrements the counter. Diode D2 isolates this pull-down function of the up/down input from the chase clockwise switch.

There will always be a wait of about one second after release of a chase switch before the chomp LED lights and counter IC4 can be reclocked. Pressing a chase switch before the IC7c Schmitt trigger goes low again will discharge C5 without clocking IC4.

Detection of the end of game, whether it be a win or lose, is carried out by exclusive OR (XOR) gates IC5a c, and d, and by a three-input NOR gate IC6c. End of game occurs when both the player and opponent LEDs occupy the same position. This means that there will be the same binary count on both IC3 and IC4. XOR gate IC5a checks for the same logic level from the Q1 outputs of IC3 and IC4, while IC5d and IC5c check the Q2 and Q3 outputs respectively.

XOR gates operate such that the output is high when the inputs are different and low when they are the same. Consequently, when the same count is on both IC3 and IC4, all XOR gate outputs will be low, but at least one will be high if IC3 and IC4 have different counts.

The NOR gate (IC6c) operates such that its output will be high only when all inputs are low. Consequently, pin 10 of IC6c goes high only when IC3 and IC4 have the same count.

This high from IC6c brings the carry in, CI, high on both counters which then

stop counting clock pulses. As a result, the game remains latched with both the opponent and player LEDs at the same position at the end of a game.

It is now necessary to detect either the "win" (green LED, IC7a high) or "lose". (red LED, IC7a low) situations so that we know who won the game.

Since we know that a "lose" occurs when the red/green oscillator is low and that a win occurs when the oscillator is high, we can determine the win or lose condition after IC6c goes high. IC7d inverts the high from IC6c and this sets the output of IC6a, wired as a two-input NOR gate, high if IC7a is low and low if IC7a is high. Consequently, when high, the lose LED will light. When low, the output of XOR gate IC5b will be high and the win LED will light.

The cathodes of the win and lose LEDs are connected to the opponent rate oscillator, IC7e, via a $1k\Omega$ resistor. The win and lose LED will thus flash at a 1Hz rate.

At the end of the game, it is necessary to halt the red/green oscillator so that the win or lose state will remain. This is done using diode D4 if the game is lost and diode D3 if the game is won. As explained previously, when the game is lost the output of IC7a (pin 2) will be low while the output of IC6a will be high. At the same time, diode D4 pulls the input to IC7a high via a $10k\Omega$ resistor, thus stopping the red/green oscillator in the low state at which the game ended.

For the win situation, the outputs of IC7a and IC5b are both high. In this case, however, the output of IC5b is inverted by IC6b and IC7a is stopped by pulling its pin 1 input low via diode D3.

The game is now left in a state where

PARTS LIST

- 1 PCB, code 83eg9, 138x186mm
- 1 Perspex sheet, 138x186mm
- 1 Scotchcal label
- 8 bi-coloured LEDs (Soanar SPRG511 red/green)
- 2 5mm red LEDs
- 1 5mm green LED
- 3 momentary contact pushbutton switches
- 1 SPDT toggle switch
- 1 9V battery (type 216)
- 1 battery clip for 216 9V battery
- 1 piezoelectric transducer (Toko PB-2720 or equivalent)
- 4 15mm standoffs
- 4 25mm machine screws and nuts
- 4 rubber feet

SEMICONDUCTORS

- 2 4051 8-channel analog multiplexers
- 2 4029 presettable up/down counters
- 1 4030, 4070 quad 2-input exclusive OR gate
- 1 4023 triple 3-input NAND gate
- 1 74C14, 40106 hex Schmitt trigger
- 6 1N914, 1N4148 diodes

CAPACITORS

- 1 47μF/16VW PC electrolytic
- 1 10μF/16VW PC electrolytic
- 3 1μF/16VW PC electrolytic
- 2 0.1μF metallised polyester
- 1 .047μF metallised polyester
- 1 .039μF metallised polyester
- 1 .01μF metallised polyester

RESISTORS (5%, $\frac{1}{4}$ W) 5×1M Ω , 1×820k Ω , 1×100k Ω , 2×10k Ω , 5×1k Ω

the win or lose LED is flashing on and off and the player and opponent LED remains in the position where the game

(O3) 723 386O

IAN J. TRUSCOTT'S

CORNER BAYSWATER AND EASTFIELD ROADS, CROYDON, VICTORIA, 3136.

ELECTRONIC

SPECIALISING IN SALES AND SERVICE TO -







CONTACT US FOR ALL YOUR 27MHZ AND 477MHZ REQUIREMENTS

OUR VAST RANGE OF COMPONENTS TO SUIT THE ELECTRONIC ENTHUSIAST INCLUDES: RESISTORS — CAPACITORS — IC's — POTENTIOMETERS —HEAT SINKS — CABINETS — PLUGS AND SOCKETS OF MOST KINDS.


WE ALSO STOCK A RANGE OF TEST AND ASSEMBLY GEAR TO HELP THE HOBBY TYPE ELECTRONIC BUFF

WE ARE SPECIALISTS IN TV, STEREO AND MOST ELECTRICAL REPAIRS.

was won or lost. In the case of a win, both red and green LEDs will light and appear yellow. For a lose, only the red LED will light.

To restart the game, the start switch is pressed to bring the preset enable (PE) pins of IC3 and IC4 high. The preset enable allows the binary code set by the jam inputs, J1 to J4, of IC3 and IC4 to be loaded into the Q1 to Q3 outputs of the counters. For IC3, J1 and J4 are low and J2 and J3 are high. This sets multiplexer IC1 to the 6 output. For IC4, only J2 is high and IC2 is set to the 4 output.

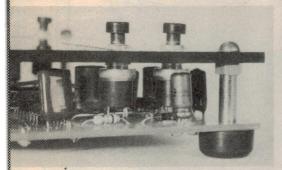Upon pressing the start switch, the voltage at the PE input does not rise immediately but is delayed by the $1M\Omega$ resistor and $.047\mu$ F capacitor. Due to slight differences in the characteristics of IC3 and IC4, one IC will preset the jam



View showing how the pushbutton switches are mounted.

inputs before the other. As soon as this happens, IC6c goes low (since the player and opponent LEDs now occupy differing locations) and pulls the PE inputs low via D1. This prevents the slower IC from preloading.

This racing effect provides some randomness in the positioning of the LEDs at the beginning of the game. Note that since the PE pins are only held low at the end of the game via the charge on the $.047\,\mu\text{F}$ capacitor, the game will eventually restart itself when the capacitor discharges due to leakage.

Sound effects are provided by a piezoelectric transducer, one side of which is connected to the output of the backplane oscillator (IC7b). The other side of the transducer is connected to the red/green oscillator (IC7a) so that a slightly different tone occurs for the red and green LEDs. Diode D5 turns off the sound effects at the end of the game by shunting the signal from the backplane oscillator to the positive rail.

The reason for the change in tone is that the red and green LEDs draw different currents and this affects the supply to the backplane oscillator and hence its frequency. In addition, the voltage swing across the transducer will vary slightly, depending upon which section of the LED is on.

Power for the circuit is derived from a

9V type 216 battery with on/off switching provided by S1. A 10μ F electrolytic capacitor and a 0.1μ F metallised polyester capacitor provide supply rail decoupling.

Construction

All components for the game are mounted on a printed circuit board (PCB) coded 83eg9 and measuring 138x186mm. We used a 138x186mm perspex sheet supported on 15mm standoffs to cover the PCB, and this supports the LEDs and switches. A Scotchcal label is used to depict the maze and the switch and LED functions.

Begin construction by marking out and drilling the various holes for the LEDs, switches and corner mounting screws in the perspex sheet. The locations for these holes can be easily found — just use the PCB as a template. Holes for the LEDs are drilled to 5mm, while the corner holes and switch holes are drilled to 3mm and 7mm respectively.

The Scotchcal label can now be attached to the perspex panel. Cut the label into three sections as shown in the photographs and drill small pilot holes (1mm) at the positions indicated. Peel away the backing paper and carefully attach the label to the perspex, making sure that the various holes are correctly aligned. Finally, use a sharp knife or reamer to enlarge the holes in the Scotchcal material to the correct size.

Attention can now be turned to the PCB assembly. Follow the layout diagram when mounting the parts and take particular care with polarised components. Install the wire links first, then the resistors, diodes, capacitors and ICs in that order. Note that the ICs are CMOS devices, so the usual precautions apply: earth the barrel of your soldering iron to the earth track on the PCB using a small clip lead, and solder the power supply pins (7 and 14 or 8 and 16) first.

Next, the battery clip and the transducer can be wired into circuit, but make sure that you get the battery clip leads the right way round. The transducer is non-polarised so it does not matter which way you connect it. We used double-side tape to secure the battery and transducer to the PCB.

The switches are installed directly on the PCB and are soldered right at the ends of their leads. This done, insert (but do not solder) all the LEDs into their respective mounting holes and attach the perspex panel to the PCB using 15mm spacers and machine screws and nuts. These same machine screws are also used to secure a rubber mounting foot at each corner of the PCB.

Finally, position the LEDs so that they protrude slightly through the front panel and solder their respective leads.

S-100

AND **STD** BUS CARDS — PARTS COMPUTERS

Australia's IEEE — 696 S100 Specialists

Complete systems or all the parts you need to build or extend your own!

We supply products from:

AED ● GODBOUT

MORROW ● SSM

QT ● JADE

PULSAR ● WARNER

S100 & STD Products:
CPU ● Memory ● I/O ●
Video ● BUS Cards ●
Disk Controllers ● Custom
Designs etc ★ etc ★ etc

ALSO: CABINETS ● POWER SUPPLIES ● CABLES ● CONNECTORS

Complete Systems:
PULSAED COMPUTER
BASED ON STD BUS
UNIVERSE: THE MOST
ADVANCED S100
SYSTEM IN THE WORLD

Send an A4 stamped addressed envelope for free catalogue or indicate particular interest for further details.



MICROCOMPUTER PRODUCTS

Sydney: AED Computers, 24 Darcy St, Parrmatta, NSW 2150. Phone (02) 689 1744. Telex AA70664 GIRFRI.

"I'm certainly going to buy one." EDITOR, Australian Personal Computer

The brilliant Dick Smith VZ-200 Personal Computer



AMAZING VALUE!

\$199

Cat X-7200

LIMITED STOCK-HURRY DON'T MISS OUT.

Here it is — the breakthrough you've been waiting for! A personal computer with all the right features: colour graphics, sound, standard Microsoft BASIC for easy

programming, a whopping 8K bytes of RAM memory, the ability to work with a standard TV set, and much more. Yet thanks to modern electronics and our buying power, the Dick Smith VZ-200 will cost you only \$199 — far less than any comparable computer (and you get our 7-

day money back satisfaction guarantee!). There'll never be a better time to invest in your family's future....

What the experts say:

"...this is a great machine, and one that is likely to change the face of Australian personal computing." — Editor, APC.

"We are impressed with the excellent implementation of Microsoft BASIC, full on-screen editing, repeat keys and easy-to-use graphics features." — Creative Computing, May 1983.

"If....you want a computer for playing games, for self-education, for learning about BASIC and perhaps for writing your own programs, the VZ-200 has one overwhelming advantage — the number of features for its price." — EA, July 1983.

Now every family can afford their own personal computer!

Yes, for just \$199, the Dick Smith VZ-200 gives you amazing computing power — far more than many machines two, three or even four times the price. Now you can find out what computers are all about. The kids can use it with their school work. It can keep track of your home budget. It can even help you in your business!

DICK SMITH Electronics

See page 120 for address details





Technological Breakthrough!

Colour Printer/Plotter at an amazingly low price!

Don't buy just a printer – here's a fantastic NEW 4 colour printer that is an X-Y plotter as well! Use it to produce graphs, pie charts, printing in many different sizes and lots more – all in four colours. Thanks to its built-in microprocessor, all of this can be done easily using simple commands in your BASIC programs.

commands in your BASIC programs.

Look at some of the features:

4 colours! (black, green, red, blue [uses ball pen inserts]) * A PLOTTER as well as a printer * Standard Centronics-type parallel interface * 10 chars. persec. printing speed * Software switching between printing and plotting * 40/80 columns per line * Resolution0.2mm * Stepsize0.2mm min. * Full 96 char. ASCII set (caps and lower case) * Inbuilt microprocessor provides 'intelligence' - plots lines, etc in response to simple commands * Plotting speed 52 mm/sec max vertical and horizontal, 73 mm/sec for 45 plotting.

* & the best feature of all is THE PRICE!

AVAILABLE ONLY \$ 7

Use any Centronics type printer with this

Printer Interface

Now get a printed 'hard copy' of both your programs and your data with this low cost Printer Interface. This superb compact module simply plugs into the back of your VZ200 alongside the memory expansion module, and lets you connect it to any standard Centronics-type printer, (like the X-7208 above). Includes printer cable.

16K MEMORY MODULE

WANT MORE MEMORY?

SIMPLY PLUG IT IN!

Want to write your own programs but find the memory of your computer unable to handle it? This happens with almost every computer, no matter how large its memory! But with the VZ200 the answer is simple - just plug in the memory expansion module and now your VZ200 has a whopping 24K of total RAM! Cat X-7205

A great range of games software

POKER Straight draw poker – just you and the computer. You can bet, raise, call, bluff and fold, just like the real thing. Cat X-7232. MATCHBOX

MATCHBOX
A great memory tester! Behind the letters on the grid are pairs of symbols, but you can only see one at a time. Which letters have which pairs behind them? Good colour graphics and sound effects. Cat X-7231

BLACKJACK

Ever wanted to visit Las Vegas? This is the next best thing—OR a good way to practice if you're planning a trip there. Blackjack or '21' is the game and the screen shows all the cards. Cat X-7235

HANGMAN

If you can't guess the mystery word (8 letters) the figure on the screen is hanged you lose! Based on the popular children's game, this program helps kids with spelling and vocabulary. Cat X-7233

NOTE: Some programs may require 16K memory module.



EXCITING **NEW GAMES AVAILABLE**

SLOT MACHINE/KNOCK OFF/ RUSSIAN ROULETTE Cat X-7234 CIRCUS Cat X-7236 BIORHYTHYM/PAIR MATCHING/ CALENDAR Cat X-7237 HORSE RACING Cat X-7238 INVADERS Cat X-7239 DYNASTY DERBY Cat X-7240 GHOST HUNT Cat X-7242 HOPPY Cat X-7243

ALL ONE PRICE! \$12.50 ea.

WE'VE GOT NEW BOOKS TOO!

VZ-200 Technical Manual

Want to get the most from your VZ-200? This technical manual explains all the ins and outs, ups and downs. For the real computer enthusiast or the beginner who wants to know more! Cat B-7204

Introduction to Computing

Are you a 'babe in the woods' when it comes to computing?
Try this one out: written just for YOU! In a language you can
understand, it will have you a VZ-200 expert in just a few
days! Cat B-7200

First Book Of Programs

Tried, trusted and true programs for your VZ-200. There's something for everyone- and remember, they're all written in BASIC so you can save these on cassette so you only have to key them in once! Cat B-7202

Plus these great financial & educational

A great introduction to the basic principles of statistical analysis. Explains about the Mean, Variance Standard Deviation, different types of Distribution etc. Gives you the opportunity to test your knowledge by working out examples. Cat X-7251

examples. Cat X-7251 STATISTICS 2 Following on from Stat. 1, this program deals with more advanced concepts. Tests of sta-tistical significances. Students T-test, the Chi Square test and so on. Cat X-7252

MATRIX
Working out mathematical matrices can be a real chore. This program gives you more skill in handling them by practice. Cat X-7253
TENNIS LESSON/GOLF LESSON

you can learn a quite a lot about the game. Cat X-7254

PORTFOLIO MANAGEMENT


Like to invest in the share market? This program will help you to analyse and manage your portfolio for max, profit and min, risk It requires your working model from models. gives you a working model of your portfolio, so you can see the likely effects of any changes. Cat X-7261

changes. Cat X-7261
DISCOUNTED CASH FLOW ANALYSIS
An ideal working tool for executives, accountants etc, providing a model for market capital budgeting decisions and minimising an investment without prejudicing a project's liquidity. Cat X-7262.

real crore. This program gives you more skill liquidity. Cat X-7263
In handling them by practice. Cat X-7263
FINANCIAL RATIO ANALYSIS
A program for the professional accountant, investment advisor, or small business owner or golf. It plays by the rules so even if don't win who doesn't want to stay small! Cat X-7263

ONE LOW PRICE \$12.50 ea

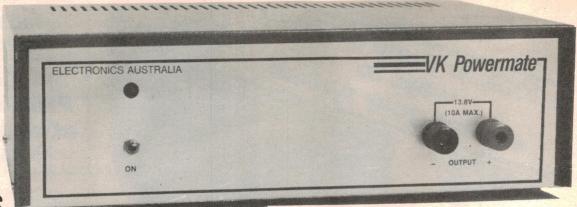The VK Powermate supplies 13.8V DC at currents of up to 10 amps.



Build this 13.8V supply and retire that messy battery

VK Powermate


by COLIN DAWSON


One of the most consistently requested projects would have to be a regulated 12V power supply to run amateur band transceivers. Five years ago we presented the VK Powermate to satisfy this demand. Now, following in its footsteps, comes the Powermate Mk II — able to deliver more than 8A and using only a few extra components.

Typical amateur equipment likely to need a power supply such as described here would be higher output — 25 to 30 watt — two-metre transceivers, or one of

the lower output – 10 watt – models driving an "afterburner" (RF power amplifier) possibly designed to deliver 40 to 50 watts. This latter arrangement can be particularly demanding.

Faced with the need to power such equipment, many an amateur resorts to a 12V battery discarded from the family car, connected across some form of "trickle" charger. There are a number of disadvantages to this method. The battery requires periodic maintenance, poses a hazard to other equipment by virtue of its acid electrolyte, has a limited life expectancy, and will not maintain an output of 13.8V under load. There is also a very real risk of introducing significant hum into the signal — and being chipped

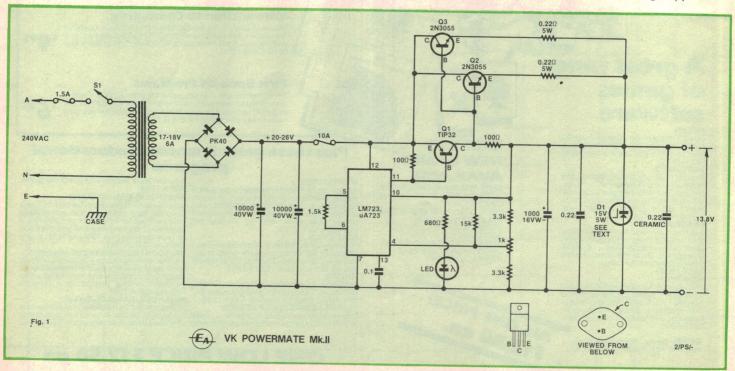

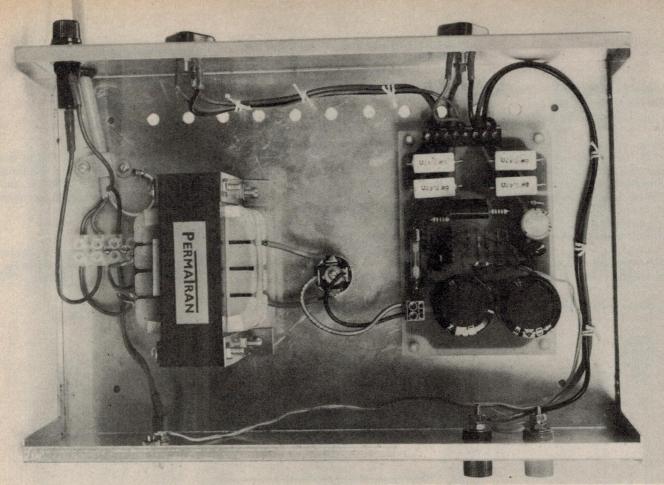

View inside the prototype. Note the row of holes drilled in the chassis to promote air flow.

about it by one's fellow amateurs! This project overcomes those problems.

A voltage of 13.8V is now a well established design figure, the majority of transceivers being rated to give maximum RF output at this figure. Originally, transceivers of this type were designed primarily for use in cars where a nominal 12V supply is available from the battery.

However, since the electrical system in a car normally runs at between 13 and 14 volts, the transceiver manufacturers long ago decided to rate all their equipment for about 13.8V. This enables considerably more power to be achieved, as much as 20% more, than would be available if the rating was exactly 12V.

Design details

This design is an upgraded version of the May 1978 unit, the main aim being greater current capability. The previous design had a current limit of about 5A continuous, the main limiting factor being the 2N3055 output transistor.

In this version we have duplicated the output stage, ie, two 2N3055s in parallel, providing up to twice the current rating with suitable heatsinking. But that is not the same as saving that we automatically get 10A out of the system. Other factors now limit the current rating.

FREQUENCY ERROR SERIES PASS CURRENT FIG. 2

One is the transformer. This is the same model as used in the original, and has a continuous rating of 6A, so this must be regarded as the maximum continuous rating. But the transformer can deliver more on an intermittent basis - such as when used in an amateur role - and it should be guite practical to run it up to about 8.5A under typical 50% duty cycle conditions.

If it was desired to run 8.5A continuously, two changes would have to be made: a transformer with at least this continuous rating and more substantial heatsinking, such as moderately large finned heatsinks, for the output transistors.

Beyond 8.5A, even assuming the above modifications, the circuit will cease to regulate, due mainly to the limitations of the power transformer, rectifier, and filters, and their inability to maintain enough input voltage to overcome the losses in the rest of the system. Thus the output voltage would fall, though not significantly up to about 10A. But this must be regarded as the absolute maximum for this circuit.

As already implied, we can avoid the need for "add-on" heatsinks for current up to about 6A continuous. The metal K&W case has a large enough surface area to dissipate most of the heat generated by the output transistors. The ventilated cabinet also allows heat from

VK Powermate

other components to escape (this case is available from several retailers).

As a further refinement to the original design, we have used PC board-mounting terminal blocks. These connectors have only recently become available and are used to replace PCB pins. Previously, we have used solder lugs bolted to the board for heavy current connections, the main reason being to avoid the use of PCB pins — they are not really adequate to support heavy wiring.

The new terminal blocks are available in even multiples from 2 to 12. We have

used a two-way and an eight-way and this takes care of all the wiring to the printed circuit board. Four and eight-way blocks are available from Jaycar, and Avtek sell the full range.

Apart from the provision of fuses, the VK Powermate does not have short-circuit protection. Our first prototype did have a "foldback" current-limiting characteristic, which gives reduced power dissipation under short-circuit conditions, compared with a simple current-limit characteristic. Unfortunately, the line regulation was found to be inadequate so we discarded the current limiting feature.

The circuit is based on the 723 regulator integrated circuit. This was

We estimate that the current cost of parts for this project is approximately

\$90


This includes sales tax.

originally introduced by Fairchild as the uA723, second-sourced by National Semiconductor as the LM723 and produced by other manufacturers with similar "723" designations.

How it works

Fig. 1 shows the complete circuit diagram of the VK Powermate while Fig. 2 shows the schematic of the 723

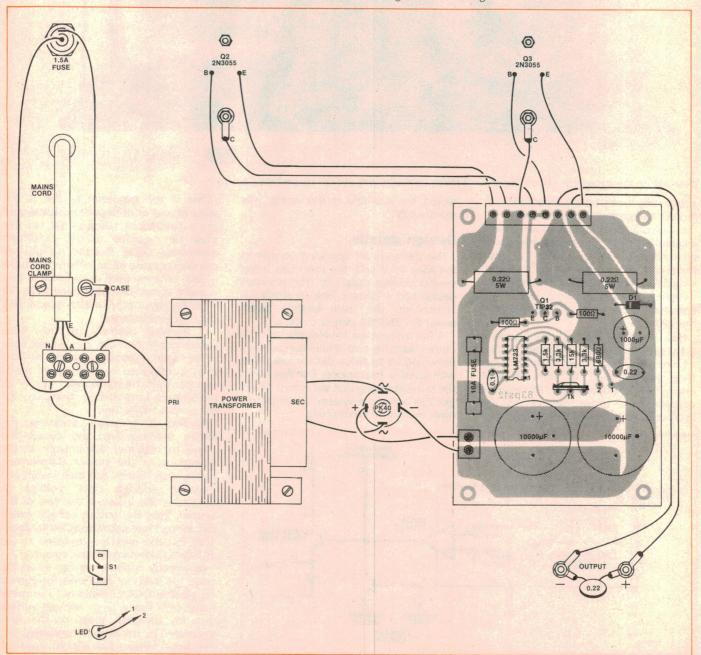Below: parts overlay and wiring diagram. Use 4mm auto cable for the high-current wiring.



regulator. The latter figure shows the 723 regulator as comprising a series pass transistor, error amplifier and reference voltage source. The error amplifier compares a proportion of the output voltage with the internal reference voltage source and makes continual adjustment to the base current of the series pass transistor.

Low dropout voltage

Maximum current rating of the series pass transistor in the 723 regulator is 150mA. This must be amplified by external power transistors to provide a supply capable of several amps. In this circuit the series pass transistor is used to drive a PNP power transistor (TIP32) which in turn provides current drive to two NPN power transistors (2N3055).

This arrangement has a low dropout of about 3V, which is equal to that of the 723 when used alone. Consequently, this circuit has very good line regulation without having excessive power dissipation.

The TIP32 transistor has a 100Ω resistor connected between its base and emitter, and the two 2N3055s have similar resistors connected between their base and emitter circuits, though not directly to their emitters, which are isolated by the 0.22Ω resistors. These 100Ω resistors avoid the possibility of high temperature leakage degrading the regulation

characteristic of the power supply.

A problem which can arise through using parallel output transistors — as we have done — is unequal load sharing. Due to slightly differing characteristics, one transistor may tend to conduct more heavily than the other. This is prevented by the inclusion of current sharing resistors in the emitter circuit of each transistor, which forces the transistors to accept an equal share of the load.

Alternative resistors

The value of these resistors is given as 0.22Ω , but we realise there may be some difficulty in obtaining these in the 5W range. For this reason we have designed a printed circuit board which will accept two parallel 5W resistors in each position. This would allow 0.47Ω resistors to be used and these are in plentiful supply.

A $1.5k\Omega$ resistor is connected between pins 5 and 6 of the 723. This is included to make the source impedance feeding the non-inverting input of the error amplifier approximately equal to the source impedance of the output voltage divider which drives the inverting input. Adding this single component makes quite a worthwhile improvement to the temperature stability of the output voltage.

The output of the regulator is heavily

bypassed to give a low output impedance at radio frequencies and to ensure good transient response.

A crude but effective method of overvoltage protection is used in this circuit. It consists of a zener diode, of appropriate voltage rating, and 5W or higher power rating, wired directly across the output terminals. If, for any reason, the regulator circuit malfunctions and the output voltage tends to rise above the selected voltage, the zener will draw very heavy current and blow the 10 amp fuse.

The zener voltage selected will depend on the tolerance of the transceiver or other equipment to excessive voltage. Most service manuals specify an absolute maximum voltage, typically 15 for a nominal 13.8V unit. Thus a 15V zener would be appropriate.

In blowing the fuse the zener itself will most probably be sacrificed, but this is a small price to pay in order to protect a valuable piece of equipment. There are more elegant methods of protecting transceivers against over-voltage, but this method is simple and reliable.


Construction

Most of the circuit components are mounted on the printed circuit board (PCB) which is coded 83ps12 and measures 82 x 119mm. Dominating the PCB are the two 10,000µF/40V electrolytics (Elna) which have a combined ripple rating of 10.4A at 120Hz. Substitution of smaller electrolytics is not really recommended as their lower ripple ratings may lead to reduced service life.

Do not substitute a less rugged transistor for the TIP32, which has a collector current rating of 4 amps. Other transistors (such as 2N3053 or BD140) will work, but on overloads they will "punch through" before the 10 amp fuse blows. And if that happens, the 723 IC will blow too.

A small flag heatsink should be fitted to the TIP32. This can be either a commercial unit or a piece of light gauge aluminium about 20 x 30mm.

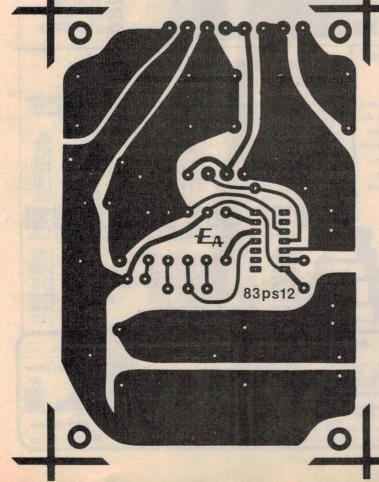Do not try to increase the output rating of the Powermate by increasing the fuse rating. This will only lead to the possibility of damage to the 3055s, and quite possibly to other parts of the



Left; actual size PCB artwork. Ready etched boards are available from kit retailers.

Below: this graph plots the line output as a function of load. Regulation is maintained for loads up to 8.44A.

JAYCAR FOR VALUE!



Incredible but true, Some plays a tune!
Each card is fitted with an electronic watch module, battery and flat transducer. An appropriate seasonal tune plays when the card is opened. Now no more expensive than ordinary high

EASY TO USE

Apply solder to the tip of soldering iron and then press the temperature



SOLDERING IRON TEMP. TESTER

Temperature is the most important factor for soldering!

Prevent precision parts from burning intermittent connection.

When you solder electronic parts to the printed circuit board, you should know

the proper temperature. Improper temperature can cause damage

to parts or cold soldering.

e ou tex

DEGREES CENTIGRADE!

READS TEMP IN

Ideal for all temperature controlled irons







NEW only \$395

UNIDIRECTIONAL ELECTRET MICROPHONE INSERT

Just out in time for the new EA Parabolic Microphone project! (Ref: EA Nov. '83). This brand-new direct import unit has an average sensitivity around 7dB BETTER than the common low cost Electret insert.

The unit (Cat. AM-4012) has a front-to-back ratio of 1.5:1. The power requirements are the same as for the low cost mic. insert.

Each insert is supplied with a comprehensive data sheet which includes connection details, specs, and frequency response graph.

Be early as they may be in short supply around Xmas.

Cat. AM-4012

Amazing Value

PROFESSIONAL COMPUTERISED \$69.95 CAR ALARM WITH FLASHING LIGHT



- This alarm has all the features of those expensive types. These include: * Flashing light for visible protection
 * Automatically switches on when ignition key is in off position and switched off with same key no
- switches
 * Exit and entry delay and unit chirps
- when exit delay begins
 * Sounds for one minute, then resets
 * Pulsating or steady alarm tone selectable
- * Can be used with optional N.O. Motion
- * Bonnet, boot, car stereo and CB protected

 * All hardware, wire and two warning
- Cat. LE-8600 \$69.95

16 bit computer KIT





THE ALL SINGING ALL DANCING MULTIMETER

Scoop purchase of quality "KAISE" Japan-ese 3½ digit LCD digital multimeter.

— Manual range override (Normally auto-ranging)

- ranging)
 A must Zero adjust button. Calibrates meter if you change test probes
 Virtually "open circuit" input impedance Magnificent clear LCD readout
 Most significant digit flashes if out of range.

- range
 Ton Ton Eeper for status identification
 +/- 100V DC, 600V AC
 Resistance & Current ranges (AC & DC)
 Lo ohms range for checking semis
 4mm banana plug leads on industry
 standard 19mm centres
 High current shunt available



PI-6452 PI-6456 PI-6458 PI-6460 PI-6462 PI-6464 PI-6466 PI-6468

MACHINED PIN GOLD CONTACT IC SOCKETS...

Expensive. But the best for professional work. Each pin is machined out of solid material (not punched out of a flimsy sheet). High quality heavily gold plated inserts form the socket end of the pin. The pins are then precision moulded into a high quality plastic housing, Ideal for use in equipment where high field service costs are a distinct possibility or where high reliability is essential.

Description	ALL THE PROPERTY OF THE PARTY O	1-9
8 WAY SOCKET		\$0.90
14 WAY SOCKET	The secretary	\$1.15
16 WAY SOCKET	mannin	\$1.25
18 WAY SOCKET		\$1.45
20 WAY SOCKET		\$1.60
22 WAY SOCKET	Amazina	\$1.75
24 WAY SOCKET	Amazina	\$1.95
28 WAY SOCKET	/ 11110121119	\$2.25
40 WAY SOCKET		62.05

Cat. No HE-1452 HE-1454 HE-1457 HE-1458 Description
84/6V 203(D) x 102(H) x 153(W)
84/8V 203(D) x 102(H) x 203(W)
84/8V 203(D) x 102(H) x 203(W)
84/10V 203(D) x 102(H) x 254(W)
84/12V 203(D) x 102(H) x 305(W)
84/17V 203(D) x 102(H) x 305(W)
84/17V 203(D) x 102(H) x 305(W)
93/8V 28(D) x 76(H) x 150(W)
93/8V 28(D) x 76(H) x 150(W)
93/10V 28(D) x 76(H) x 203(W)
93/12V 282(D) x 76(H) x 305(W)
93/17V 228(D) x 76(H) x 432(W) HE-1459 HE-1461

Horwood Instrument Cases

\$22.00 \$25.50

\$1.50

Incorporating

ELECTRONIC AGENCIES

117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614

TELEX: 72293 CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444 CONCORD

SHOWROOMS

117 PARRAMATTA ROAD - PHONE: (02) 745 3077

HURSTVILLE 121 FOREST ROAD - PHONE: (02) 570 7000

NUMBER 1 FOR KITS

POST AND PACKING CHARGES
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20) \$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50) \$100 - \$198 (\$8.00) Over \$199 (\$10) Over \$199 (\$10) Over \$199 (\$10) Over \$199 (\$10) Over \$100 - \$199 (\$10) Over \$100 - \$100 (\$100 Over \$100 Over \$100

MAIL ORDERS AND CORRESPONDENCE: BOX K-39 HAYMARKET, SYDNEY 2000



VK Powermate

circuit. The specified 10A fuse will take surges of up to 14A before it blows, which is well above the regulator drop out current.

At 305 x 205 x 90mm, the K&W case can easily accommodate all the components and allows some free space for cooling. Between the transistors, bridge rectifier, transformer and power resistors, there is a lot of heat generated when the supply is working hard. In addition to the slotted lid, we would recommend drilling a series of holes across the bottom of the chassis to promote air flow.

If the planned use of the power supply suggests that additional heatsinks should be fitted, there are a number of types available. Two small heatsinks will probably be a more convenient arrangement than one large one and two types listed in the Dick Smith catalog would seem to be suitable. One is listed as H-3422 and the other, slightly larger, as H-3460. They should be mounted with the fins vertical.

The transformer used is known as the "M2000" and has a rating of 18VAC at 6A (ours was supplied by Jaycar, but other kit sellers have an equivalent). Virtually any transformer with a secondary voltage of 17 to 18V at a current of 6A is suitable. Lower current ratings could be used if the inferior load regulation is acceptable.

In the other direction there is at least one transformer available with an 8A rating. This is the model JT 266, made by Jones Transformers Pty Ltd, and available from Ace Radio, 136 Victoria Rd, Marrickville, NSW.

When mounting the output transistors, use a mica washer, two insulating bushes and heatsink compound. Most of these are available in TO-3 mounting kits. The connection to the collectors of these transistors is made by means of solder lugs to one of the mounting screws for each transistor (the case is the collector for this type of transistor). Later, when the Powermate has been tested, plastic covers should be fitted to the 3055s.

An EDI Minibridge, type PK40F, is used as the bridge rectifier. It has an average current rating of 8 amps. As with the transistors, the PK40 heatsinks to the chassis, but no mica washer need be used here — the metal face of the rectifier is not an electrical connection. Alternatively, the bridge rectifier could be the higher rated PB40 which is widely available.

A pair of binding post/jack sockets are used for the ouptut connections. Don't forget to use heavy duty insulated wire for all the high current wiring. The type

known as "4mm auto cable" is suitable.

The $0.22\mu F$ ceramic capacitor is connected across the back of the output terminals. This provides RF bypassing of the output. The negative output terminal may also be connected to the case to minimise the effects of radiated RF signals. This could be a consideration when the antenna of high power equipment is very close to the power supply, although we were not able to

PARTS LIST

- 1 K&W case, 306 x 204 x 90mm or similar metal project case.
- 1 Scotchcal front panel, 305 x 90mm 1 PCB, 82 x 119mm, code 83ps12
- 1 transformer with secondary 17 to 18V at 6A
- 1 SPST mains toggle switch
- 1 4-way insulated mains terminal block
- 1 2-way PC-mounting terminal block
- 1 8-way PC-mounting terminal block
- 2 heavy-duty binding posts, 1 red, 1 black
- 1 3AG panel mounting bayonet fuse holder and 1.5A fuse
- 2 fuse clips, Swann FC1
- 1 3AG 10A fuse
- 2 solder lugs
- 1 flag heatsink (for TIP32)

SEMICONDUCTORS

- 1 LM723 or µA723 IC regulator
- 1 TIP32 PNP transistor
- 2 2N3055 NPN transistors
- 1 PK40 or equivalent bridge rectifier
- 1 15V 5W zener diode
- 1 LED and bezel

CAPACITORS

- 2 10,000 μF/40V electrolytic (PCB mounting)
- 1 1000μF/16V electrolytic (PCB mounting)
- 1 0.22μF ceramic
- 1 0.22μF metallised polyester (greencap)
- 1 0.1 µF greencap

RESISTORS (1/4W, 5%)

1 x 15k Ω , 2 x 3.3k Ω , 1 x 1.5k Ω , 1 x 680 Ω , 2 x 100 Ω , 2 x 0.22 Ω /5W (see text), 1 x 1k Ω trimpot (large vertical)

MISCELLANEOUS

4 rubber feet, 4 nylon PCB stand offs, 1 grommet, mounting hardware for TO-3 transistor, heatsink compound, 2 TO-3 plastic covers, mains cord and three-pin plug, mains cord clamp, heatshrink tubing, 4mm auto cable, hook-up wire, screws, nuts, lockwashers, solder.

NOTE: Component substitutions are not recommended. See text.

induce any anomalies with the antenna of a 2-metre set only a metre away.

Take care with the mains wiring. The three-core mains cord should be passed through a grommetted hole in the rear of the case and anchored with a cord clamp. Mechanically terminate and solder the earth wire to a solder lug secured under one of the transformer mounting screws. The rest of the circuit is not earthed.

Terminate the active and neutral conductors plus the wires to the transformer primary and the mains switch to a three-way insulated terminal block. Make sure that the soldered connections to the mains switch and transformer primary fuse are insulated with heatshrink tubing or "spaghetti".

When construction is complete, check all wiring carefully. To protect the overvoltage zener diode, it is important that the $1k\Omega$ trimpot be set initially for minimum output voltage. This is with the wiper closest to the positive rail or, in physical terms, fully anticlockwise as seen from the rear of the case.

Test the supply with a dummy load before it is used with a transceiver. A piece of jug element cut to a length would be suitable. Make sure that the output voltage does not change by more than 200mV between the loaded and unloaded conditions. This is a far more valid test than operating the power supply with a transceiver because your voltmeter is quite likely to be upset by the transmitted signal.

In this regard, analog meters are likely to be less affected than their digital counterparts. We found a digital meter to have an error of 1V during transmit, a cheap analog to have an error of 0.5V and an expensive analog to have no error. To test whether an indicated change in voltage is genuine, short the test leads of the meter together and transmit. Obviously, any reading on the meter is an induced error — but don't be surprised if this does happen.

(Note that the suggested dummy load will get very hot, and may even burn out, if used for more than a few seconds at a time. This should be long enough to set the voltage but, if prolonged testing is necessary, it would be necessary to immerse it in water.)

During normal operation, the output transistors will become quite hot, especially if the supply is running at 6A continuously. This is quite normal. All components are within ratings.

So there it is; a rugged power supply with excellent filtering and regulation which should be large enough for all but the very large transceivers. It would also serve as a bench supply for any service organisation handling car radios and similar equipment. It should have a long and useful life.



\$699 will buy you the newest and most exciting educational, home and business computer available on the market today!

BGR COMPUTERS PTY LTD ARE PROUD TO ANNOUNCE THE LAUNCH OF THE FULLY AUSTRALIAN MANUFACTURED EXCALIBUR 64 PERSONAL HOME COMPUTER.

- 64K RAM
- EXTENDED MICROSOFT BASIC
- RF, VIDEO AND RGB OUTPUT
- DISPLAY 40 x 24 OR 80 x 24
- CENTRONICS PARALLEL PORT
- FULL RS232C PORT

- 16 COLOURS VIDEO OR RE
- 27 COLOURS RGB
- RUNS CP/M 2.2
- 640 x 288 RESOLUTION
- 300 OR 1200 BAUD CASS INTERFACE
- FULL SIZE QWERTY KEYBOARD

COMPARE THE EXCALIBUR 64 FEATURE FOR FEATURE WITH ANY OTHER COMPUTER ON THE MARKET. YOU WILL BE CONVINCED THAT IT OFFERS UNPARALLED VALUE FOR MONEY.

COMPARISON CHART

FERTURES	EXCALIBUR 64	MICROBEE IC 32K	RPPLE II	ATARI 800	COMMODORE 64
BAM	64K	32K	48K	48K	64K -
ROM Microsoft BASIC Colours	16K Yes 27	16K No No	12K Yes 15	10K No 16	20K No 16
Screen display	40 x 24 or 80 x 24	64 x 16 or 80 x 24	40 x 24	40 x 24	40 x 24
Resolution	640 x 288	512 x 256	280 x 160	320 x 192	320 x 200
RF, Video and RGB	Yes	No	No	No	No
Runs CP/M 2.2	Yes	No	No	No	No
RS232C	Yes	Yes	No	No	No
Centronics/Parallel Port	Yes	No	No	No	No
Power supply built in	Yes	No	Yes	No	No

The EXCALIBUR 64 is a fully complete computer. Unlike most other computers there are no hidden extras, no expensive options to add to a low base price. The EXCALIBUR 64 was designed with the user in mind, offering a massive 64K RAM with actual 48K user RAM — extended Microsoft BASIC, an

industry standard — CP/M 2.2 compatability allowing you access to thousands of currently available programs. Highly functional two piece case offering flexibility and professional operation — Full size raked QWERTY keyboard — fully expandable to a complete business system.

THE EXCALIBUR 64.

THE COMPUTER YOU HAVE BEEN WAITING FOR HAS FINALLY ARRIVED

And what's more it's fully Australian designed and developed.


THE MOST POWERFUL COMPUTER AND THE LOWEST COST CP/M BASED SYSTEM AVAILABLE TODAY.

Your EXCALIBUR 64 can be expanded into a fully fledged business machine with performance and price that will leave you and your accountant jumping for joy. Just add our optional disc controller board and add drives of your choice.

There's never been a computer available before with the sophistication of the new EXCALIBUR 64.

For the serious personal computer user, it offers truly outstanding performance. For the first time computer

user, the EXCALIBUR 64 allows you access to play games with spectacular graphics and colours. The graphics and colour capabilities of the EXCALIBUR 64 are unmatched by any other computer under \$1500. For business use the EXCALIBUR 64 allows you access to accounting packages, time management, business systems and statistical analysis. For the family you can have fun with action games, adventure games and educational programs, which you can plug directly into your home television set

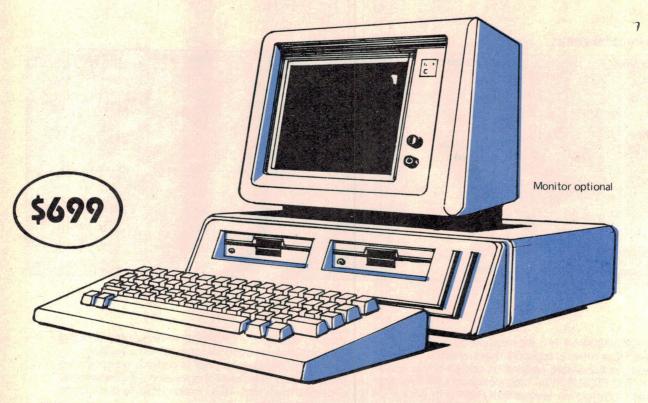

DISK CONTROLLER BOARD: \$299

Plugs on board the EXCALIBUR 64. $5\frac{1}{4}$ or 8 inch drives. Will run up to four drives single sided

single density or double sided double density under software control.

EXCALIBUR 64

THE MOST POWERFUL, FLEXIBLE AND BUSINESSLIKE MACHINE IN ITS CLASS

EXCALIBUR 64

TECHNICAL SPECIFICATIONS

Z80A CPU Clock speed 3.5 Mhz Total RAM 70K Screen Mem 2K Colour Mem 2K PCG Mem 2K User RAM under Disk

Actual user RAM under

drives

BASIC

48K

Language Extended Microsoft BASIC Similar to Tandy Level II Disc Basic but also includes

colour commands

Colour 16 foreground colours

64K

8 background colours using video or RF 27 foreground colours using RGB with monitor

Graphics mode 128 programmable

characters

128 graphic characters 96 ASCII characters (includes lowercase)

Video Resolution RF, video and RGB OUTPUT Low res 320 x 288 pixels Hi res 640 x 288 pixels

Video display

24 lines x 40 characters 7 x 12 dot matrix

(TV or monitor)

24 lines x 80 characters 7 x 12 dot matrix (monitor preferred)

Cursor Keyboard Flashing block full size 60 key QWERTY layout

4 programmable function

keys - 8 functions

Cossette Built in interface

software controlled at 1200 and 300 baud - Kansas City

(counter timer circuit)

Serial. full RS 232C I/O Ports

Parallel. 8 bit centronics

compatable

Expansion 2 expansion ports on

board each providing all major control and data lines


Single channel 3 octaves Audio

programmable under BASIC

Power supply On board


Disc controller board **Options**

Direct connect Modem

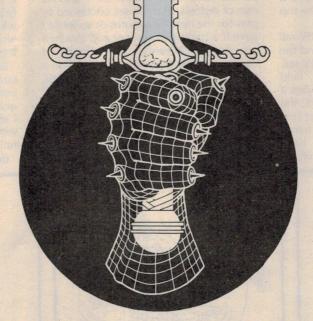


EXCALIBUR 64.




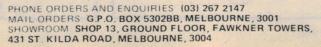





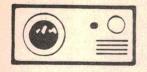

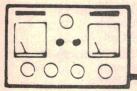

The Serviceman

A tricky intermittent & more on TV fires

My main story this month concerns a simple case of frame collapse; simple, that is, in the sense that it is a common fault and usually not hard to trace. But it seems that there is always room for variation on a theme. And, in this case, it led me guite a dance.

The set involved was a Philips K9, and one which I had serviced a number of times over the years, mainly for routine faults. On this occasion the customer rang to say that the set had developed a bright line across the centre of the screen; the typical symptom and description for a frame collapse condition.

I duly called at the house, switched the set on, and observed the effect exactly as the owner had described it. Nor did it take much effort to find the immediate cause of problem. Swinging out the larger of the two boards, carrying the scan circuits, my attention was immediately drawn to two 5W resistors, fitted with thermal cutouts, near the top left hand corner of the board.

One, R483, 22Ω , supplies the +20V rail for the vertical deflection circuit, and the other, R487, 33Ω , supplies the -20V rail. These are spring loaded devices, held closed with solder, which spring open if the resistor overheats and melts the solder. It is not unusual to find that one of these has tripped in the case of frame collapse, either because they have sensed a fault elsewhere in the circuit, or

because they sometimes develop a fault themselves.

And so it was in this case; R483 had tripped, though for what reason was not immediately obvious. All I could do was reset it and see what happened. However, I did take the precaution of using 50-50 type solder in place of the usual 60-40 type. This is in line with a recommendation issued by the makers, following a tendency on the part of the original units to open unnecessarily in hot weather, or because repeated heating and cooling apparently caused a form of metal fatigue in the solder.

Then I switched on and waited. The picture came up normally, there was no sign of distress, and the set continued to play for the next 10 minutes or so while I gave it a routine once over and touched up height, linearity, etc. Finally, I concluded that it had most likely been a simple solder failure and that nothing more was needed. However, I warned the customer to call me immediately in the event of trouble.

I heard nothing for the next couple of weeks, and I had assumed that my diagnosis was correct. Then the


customer was on the phone, with the news that the set was playing up again. When I enquired as to whether it was the same fault the owner said no, it wasn't exactly the same. As he described it, the set would run for long periods and then would develop a series of horizontal streaks, followed by frame collapse, but with a white line at the top of the screen rather than in the centre.

Then he added that, by switching the set off for a few minutes and switching it on again, it would perform perfectly, usually for several hours. These symptoms didn't fit any pattern I had encountered before and, because of the intermittent aspect, I decided that the set would have to come into the workshop. I advised the customer accordingly, and arranged to pick the set up in a couple of days when I had another call in the same area.


In fact, by the time I did call for the set it had reverted to the original fault; a bright line in the centre of the screen which no amount of on-off switching would cure. This wasn't surprising, since R483 had flipped again.

Back at the workshop I cleared a corner of the bench for the set, swung out the board where I could get at it quickly, reset R483, and switched on. As I expected, the set came up normally, with no signs of distress, and kept on running for the rest of the day.

But what I didn't expect was that the

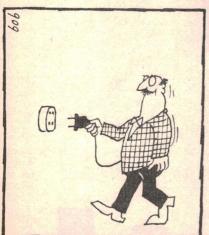



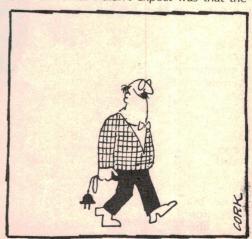

set would keep on like that, day after day, for over a week. According to the owner it would seldom run for more than a day without giving trouble, and never more than two days. So why wouldn't it play up on my bench.

At this stage I suddenly had a horrible thought. Had I unwittingly deceived myself with the bench set-up? I swung the board back inside the cabinet, refitted the back, switched on and waited. All went well for an hour or so, then I happened to glance at the screen and, lo and behold, there were the streaks across the screen just as the customer had described them.

A few minutes later the picture collapsed, leaving a bright line across the screen about 25mm from the top, again just as the customer had described it. There was no doubt in my mind now; the fault - whatever it was - was markedly temperature sensitive. And, by leaving the cabinet open, and the board swung out for easy access, I had completely nullified the test.

What was more, the weather had been quite cool over the previous week, whereas now, after I had closed the cabinet, it had turned much warmer. Mentally kicking myself for being deceived so easily, I tried to work out what was the best way to tackle the fault from here.

THE OLD BLANKET TRICK

Quite obviously, the cabinet had to be opened and the board swung out for me to work on it, so I resorted to the old blanket trick, draping it over the board and the open back of cabinet. I switched on again and the set, which had cooled by now, came up normally. I sat and waited.

Sure enough, after about 15 minutes, the frame collapsed as before. I lifted the blanket clear and turned around to reach for a can of freezer on the bench, intending to spray the most likely components and, hopefully, pick out the faulty one. But as I turned back to the set I realised it wasn't going to be that easy; in the few seconds that the blanket had been off the set had come good.

I tried this blanket-on, blanket-off routine a couple more times and confirmed that the whole set-up was extremely critical but, also, that I could create either condition virtually at will. At this stage I brought the CRO into action. The main deflection circuit, which is direct coupled, consists of some eight transistors, TS540, 545, 550, 560, 565, 568, 570 and 580, more or less in that order from input to output.

I connected the CRO to the input of the first stage, TS540, and, by juggling the blanket, confirmed that the waveforms at this point did not change with the fault condition. That ruled out the circuitry ahead of this point and made the remainder of the chain the prime suspect.

At this point I had intended to follow through with the CRO to pinpoint the faulty stage, but I found that trying to work with the blanket draped over the set extremely awkward. Instead, I rigged up a small radiator to direct heat onto one side of the board.

And that was where I allowed myself to be sidetracked. I started by heating the component side of the board, but found that it seemed to take inordinately long for the heat to work, even though the components were quite hot. So I tried heating the other side, whereupon the set reacted in only a fraction of the time. This convinced me that I probably had a pattern fault; a hairline crack or something similar.

I went over that side of the board with a fine tooth comb. I examined it under a glass, I bridged likely tracks, I prodded and probed; all to no avail. Finally, I was forced to the conclusion that, in spite of my observations with the radiator, there was nothing wrong with the pattern and that it had to be component fault.

Leaving the radiator directed on the pattern side I was about to start probing with the CRO again when, on impulse, I picked up the can of freezer and squirted several transistors. This restored performance, but it was hard to tell which transistor was responsible, if any, because other components, and the board, also copped some of the freezer.

But I did narrow the area down to that around TS540, 545, and 560, where the briefest burst was enough to cure the fault. And of these three, I fancied that TS545 seemed to be marginally the more sensitive. It was quite easy to change this, which I did, but drew a blank; the fault was as much in evidence as before.

Next I changed TS540 and that was it. No amount of heating and cooling would produce the fault. But was the transistor faulty, or had I cured a subtle dry joint in replacing it? Remembering the sensitivity of the pattern side of the board to heat, I still had my doubts.

Determined to settle the matter once and for all, I put the old transistor back in the board, whereupon the fault returned, exactly as it had been before. So that proved that point, but why did the fault respond more readily to heat on the pattern side of the board?

I even tried heating the body of the transistor directly, with the soldering iron, and even this required a considerable time to create the fault, compared with heating the pattern side of the board.

I finally concluded that the transistor fault probably involved one of the leads, such as a faulty joint to the lead, and that



POKER MACHINE SIMULATION:

This simulated poker machine keeps a record of your winnings and unlike the real ones, you can set a limit on your losses. CALENDAR CALCULATOR:

This program displays or prints out a calendar for any year of the 20th century — and keeps track of paydays!

OTHELLO GAME:

The game of Othello, or Reversi, is played on an 8 × 8 grid with counters of two This one has a "help" option.

INVESTMENT ANALYSIS: How much money can you make investing for a fixed term of years at current interest

rates? Find out with this program. **GUESSING GAME:**

Is it animal, vegetable or mineral, a place, name or a car? Play against your friends, guess the object.

LIST AND SORT: This program lets you compile lists of up to

500 items, arrange them in alphabetical order and save them on cassette tape. FRED THE SHRINK:

Got a problem? Perhaps Fred can help. Talk things over with your computer — it may give you a new perspective on life!

SIMPLE MATHS DRILL:

A great one for the kids — or to test your own arithmetic skills. It tells you the right with comments if you goof.

LOTTO NUMBER SELECTOR:

We don't guarantee you'll win your fortune, but this program makes picking Lotto It's fun to use, too. numbers easy. It's fur TRIANGLE SOLUTIONS:

Computerised trigonometry at your service. If you think you know all the angles, try this program for size

MORTAR ATTACK GAME:

Match wits with the computer! See how long you can hold out in this challenging game of mortar bombardment.

CAVES & MONSTERS:

Go adventuring in the maze. You must fight monsters and find the treasure, but be careful - the monsters get tougher as you

AMATEUR Q CODE TUTORIAL:

If you're thinking of going for your amateur radio licence, or just want to find out what all those "Q" codes mean, try this.

DIRECTORY FOR CARAVAN PARKS:

Owners of caravan parks can keep track of who's where with this program. It can be adapted to other applications too.

SUPER-POKEY GAME:

Another poker machine game, but this one has graphics. For the budget conscious, you can set an upper limit on your stake.

TATTSLOTTO NUMBERS:

For those south of the border we present a program to select numbers for Tattslotto entries. Good luck.

Note: this book is exclusive to, and available only from, Electronics Australia, 57 Regent St, Chippendale 2008, PRICE: \$4 or by mail order from Electronics Australia, PO Box 163, Chippendale, NSW 2008. PRICE: \$5.

NAGREALDUUN

Replace your existing speakers or "ADD ON" to enjoy superb stereo sound in other rooms in your home.

The Dick Smith



build yourself at a large saving on comparable speakers

Designed in Australia by our own technical staff, the Series 200 speakers can actually be built by you in just a few hours. The result is a superbly handsome pair of speakers which sound like you spent a fortune

Dick's worldwide buying power, coupled with new sound technology and the fact that you build these speakers yourself enables you to enjoy the sound quality of big home speakers at a fraction of the cost!

Compare the quality features and specifications:

- Fine Woodgrain Finish
- Fully Imported Contoured Grilles
- Top Quality Speakers

Peak power handling - 40W, Impedance -80hms, Freq response - 45Hz to 20kHz, Speakers - 200mm woofer, 125mm midrange & 64mm tweeter, Crossover - 3 way, at 15kHz & 5kHz, Dimensions: (cm) 64x38x29.6 (26 litres)

Included in the Series 200 kit are:

Speaker Grilles (Cat C-2608) Enclosure Kit (Cat C-2636) \$31.50 \$128.50 Speaker Kit (Čat C-2046) \$89.50

Complete Series 200 Kit

per pair

Haven't time to build them yourself? The Dick Smith Series 200 Speakers are also available in built-up form for only.

> **AMAZING** VALUE

100

Cat A-2370

Per. Pair

As featured in September ETI. EXCLUSIVELY FROM

DICKSMITH Electronics

See our other ads this issue for full address details

THE SERVICEMAN — Continued

heat applied to the lead, via the copper pattern, raised the temperature at the fault site much more rapidly than heat applied to the body, where it would encounter much more thermal resistance.

Which is a nice neat explanation in hindsight, but the situation completely confused me on the workbench, and sent me off on a time wasting wild goose chase. The lesson to be learned, I think, is not to switch horses in mid-stream. Or, in other words, when you start out on a test sequence, follow it through.

MORE ON TV FIRES

To change the subject, here is another story about the possible cause of fires in TV sets. I dealt with this at some length in the October notes, featuring a story from Mr J. L. of Tasmania, with photographs of a particular switch found in a Blaupunkt receiver which was all set to burst into flames. Following that I received a letter from another serviceman, Mr J. M. of Warwick, Queensland, describing a completely different potential fire cause. He writes:

The job commenced in the usual fashion; a phone call. The customer told me his TV set had caught fire, and could he bring it into the workshop for repairs. The statement "My TV set has caught fire" is usually an exaggeration. In most cases the customer has seen a thin wisp of smoke from the back of the set, or has smelt a burning odour, as when a fusible

resistor burns up.

In this case, however, I was told that the flames were put out with a small extinguisher. I asked him where the flames had appeared, and he told me the plastic front of the set, just under the controls. I arranged for him to bring the set into the workshop the next morning. Meanwhile I puzzled over what could have happened. I have been in the TV service industry for 16 years and the number of fires I have encountered in TV sets would come to less than a handful.

Next morning the set arrived and was placed on the workbench. It was a 63cm Philips, with a K11 chassis. Looking at the front escutcheon of the set, a 5cm x 2cm melted hole was clearly visible. The odd thing was its location; right in front of

speaker.

Closer investigation showed that there was no speaker cone to be seen and, on removing the speaker frame, the only thing remaining was the burnt wiring of the voice coil winding. Quite obviously the speaker had caught fire - but why?

My first thought was that perhaps a spark had dropped from the power switch and had ignited the speaker cone, but closer investigation showed that the location of the power switch made this impossible. A high DC voltage across the voice coil winding would certainly cause it to overheat, even get red hot before going open circuit. Could this be the

A check of the circuit diagram revealed that transformer coupling was used between speaker and output transistors, which made this possibility remote. A check was made of the wiring and everything was found to be as per the circuit diagram.

A new speaker was installed and the set tested. Sound came on normally and no irregular DC voltages were found. The only conclusion I could reach was that the voice coil had developed a shorted turn which had caused a high current to be drawn through the remaining turns. This would have caused them to ignite the paper voice coil former and, in turn, the cone.

Careful questioning of the customer revealed no new clues. Apparently the family had been watching the program with the sound at its normal level, and no distortion was heard before smoke and flame appeared at the front panel. The only other damage arising from the incident was a slight distortion of the plastic channel selector switch bank, which was replaced.

This most unusual fault raises the following questions: has a house fire been caused by a speaker which has ignited? And are speakers the safe devices we thought they were?

After completion of this job I recalled an incident which took place a few years earlier. I had sold an inexpensive pair of car speakers to a young chap, who installed them on the back parcel shelf of his car. A couple of weeks later he complained he saw smoke coming from one of the speakers, followed by distortion in that speaker.

I replaced the speaker under warranty, and then carried out a post mortem on the faulty speaker. When audio was applied the sound was heavily distorted and an ohmmeter across the winding showed a lower than normal reading. On removal of the cone and voice coil assembly I observed that the central windings had turned black with heat and that the coil was burnt nearly in half.

I wonder if others have had similar experiences.

Thank you J. M. Your experiences certainly do raise some pertinent questions; particularly the ones you pose yourself. Until the exact reason for such incidents can be determined, it is unlikely that the questions can be answered, or suitable precautions taken.



300 WATTS

These great inverter kits enable you to power 240V appliances from a 12V DC power source. Tremendous for camping, fishing etc. install into your Car, Boat or Caravan.

A fully regulated and overload protected design, featuring XTAL locked frequency. Use to power hi-fi, TV sets, even electric drills for short time

periods.

MANY OF THESE KITS ARE NOW IN USE FOR EMERGENCY LICHTING PURPOSES.

ALTRONICS' KIT features & Gold plated edge connector and PCB huss & Low age rate XTAL & Sockets for all IC's & High Efficiency Transformer.

K6750.... (EA JUNE '82) ... \$199.50

(\$10 DELIVERY AUSTRALIA WIDE)

TWO GREAT 40 WATT MODELS




GENERAL PURPOSE

Suits small appliances, ie. Turntables, Tape Decks, Shavers etc. Variable frequency adjustment enables speed control of turntables. Works as a trickle charger when mains power is available. EASY CONSTRUCTION VALUE PLUS

BANKCARD JETSERVICE DELIVERY NEXT DAY

ALTRONICS

K6700.....\$55.00

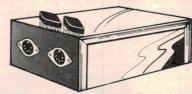

FLUORESCENT LIGHTING

Operates above the audible frequency range and is capable of driving one 40 watt or two 20 watt fluorescent tubes to 150% of their normal 240V efficiency. Install permanently into caravans. COMPLETE BOXED KIT, INCLUDING ALL WINDING WIRE.

K6505..... \$37.50

ALCOHOL BREATH TESTER K1583 ONLY

(SEE EA

ALTRONICS

DAY

NEXT

ELIVERY

6

JETSERVICE

BANKCARD

ALTRONICS

MAY 1983)

This Great new Kit from EA will be a smash hit with all the smashed people at your next party. Fun to build, Fun to calibrate and Fun to use. More seriously, this unit could save lives.

MICROWAVE OVEN LEAK DETECTOR



ETI PROJECT


Completely passive project receives microwaves via an antenna which develops a voltage across a detector diode driving the meter.

Monitor your microwave oven with this easy to build kit. All components mount on single PCB, including the meter.

Genuine Hewlett Packard Hot Carrier Diode supplied.

K1724..... (still only) \$14.50

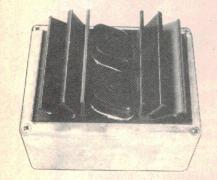TRANSISTOR ASSISTED IGNITION WITH DWELL EXTENSION



The Altronics Kit includes all components for the modifications, detailed by Electronics Australia Feb. 1983.

Yes, it's bad enough paying \$2.00 a gallon for petrol without wasting a fortune on an out of tune engine. Fit this transistor assisted ignition kit in minutes and start saving money from the very next petrol stop. Easy to build!

K4010..... \$35.00

POWER DOWN MAINS APPLIANCE TIMER

(ETI JULY '82)



Clever new design from ETI, mains appliance is turned on at the press of a button and automatically turned off some preset time later.
Use for electric blankets, bathroom heaters, patio light. If your inclined to fall asleep while watching TV late at night — this is the kit for you.

SEC Approved Transformer — Screened Front-Panel — Complete Kit as per ETI article, includes every last part.

K6265.....only \$32.50

See EA November, 1982

A MUST **FOR YOUR** COMPUTER

SYSTEM

This great new Project from EA is the answer to a Maidens Prayer.
What Does it Do?

A single 240v mains plug and lead feeds one unswitched master 240v outlet plus 4 switched 240v outlets. With say a hi-fi system, plug your main equipment item (e.g. Amp) into the master outlet and whenever you "switch on" your amp — presto — mains power is on" your amp — presto — mains power is applied to the other 4 outlets i.e. simply "turning on" your amp turns on your tape cassette, tuner, turntable, graphic equaliser without mains spikes, plops etc.

Just the shot for your Computer System. The Altronics Kit includes case and all outlets.

K6000..... \$39.50

FOR DESPATCH P&P CHARGES AND ADDRESS DETAILS PLEASE REFER TO OUR AD. ON PAGE 149

POWER SUPPLIES

ALTRONICS

BANKCARD JETSERVICE DELIVERY NEXT DAY

ALTRONICS

ALTRONICS

QUALITY VIDEO KITS

Video has been booming for quite a while finally a range of video accessories in kit form

form.

Two video amplifiers for both VCR and Computer use, a brand new Video Enhancer and our popular VCR Stereo Synthesizer. All four represent outstanding value for money and all are assembled with Altronic's Extra Care.

VIDEO AMPLIFIERS



DISTRIBUTION TYPE Simple, low-cost project will allow you to drive five video monitors from one source, such as a video cassette a video cassette recorder or a computer. Great for piping video around the house, or for clubs meetings when screening lectures etd, or for computer demonstrations.

THE ALTRONICS KIT includes all components as specified by ETI **plus all** power supply components.

K5830..... Only..... \$45.00



SINGLE OUTPUT

INVERSE AND NORMAL OUTPUT

Brilliant new kit from EA, Super cheap and Super Effective. Whilst our K5830 is suitable primarily for VCR use this video amplifier is best suited to use with computers. The EA documentation supplied is extremely well written and provides details for installation into television sets.

NO MORE SMEARY COLOURS, SIGNAL BEATS OR RF INTERFERENCE NOTE * NOT SUITABLE FOR USE WITH LIVE CHASSIS

TV SETS.

K5850.....\$14.95



VIDEO ENHANCER

Here's a **simple** but **effective** Video Enhancer that is super **easy to build** at a fraction of the cost of commercial models

Unit sharpens picture detail, and can actually improve the quality of a copy by amplifying the top end of the video signal.

AT LAST A VIDEO ENHANCER KIT

\$35.00

ENJOY THE PLEASURES OF STEREO SOUND

(See EA Sept. 1982)



STEREO SYNTHESIZER FOR VCR'S AND TUNERS

Synthesize realistic stereo from virtually any monophomic source by simply connecting this unit between the source and your stereo amplifier. * Quality Phillips MN3001 (not second source

- dropout)
- Provision for 2 different signal sources. Selection of either source via front panel switch
- Normal or stereo sound selection.
 Complete kit includes all hardwear, cables etc., even solar.

Important ★ beware of Kitset suppliers who sell this kit for less ★ you get less!

K5810.....\$**55.00**

If you're thinking of buying a power supply then buy from us, we are the experts on power supply kits and carry a supply to suit most enthusiast and professional requirements......READ ON.



BENCH STANDARD

- 3-30v Output @ 1 Amp. Fully Regulated, Fully Protected from Thermal Overload and Short Circuits.
- Based on EA Design

\$42.50 K3200.....

- * All the features of above PLUS Current Limit * ETI Design.
- \$49.50 K3205.... (PICTURED).....

DUAL TRACKING

- 1.3 to ± 22v Output @ 2 Amps.: + 5v @ 0.9 Amps Fully protected.
- 10 turn pot enables Voltage adj. to within 10mV. EA Design (March '82).
- \$89.50 K3220.....

HIGH CURRENT

MICROCOMPUTER PS

5 Volts @ 3 Amps. * + 12 Volts @ 2 Amps. 12 Volts @ 200 milliamps.

This universal design has enough grunt to power most disk drives.

\$59.50 13.8 VOLTS @ 10 AMPS HAM'S & CBER'S

Save the expense of a Mains Powered Rig

\$89.50

HIGH CURRENT — DUAL METERING

EA SWITCH MODE DESIGN

- 2-50 Volts at massive 175 Watts. CLEVER DESIGN a fully mains isolated supply with a "Switchmode" low voltage circuit.
- * Easy to build


K3300... (EA MAY, JUNE '83).. \$139.00 K3301... CONTROL OPTION)... \$10.00 K3302... (± 12V OPTION) ... \$12.50

ETI SERIES REGULATOR DESIGN

- 0-40 Volts @ 5 Amps **thats 200 Watts.**Current limiting 0-5 Amps variable.
 Specifications Second to None.
 Free from the hum and noise sometimes associated with other techniques.

A PROFESSIONAL SUPPLY

K3325.... (PICTURED).... \$175.00

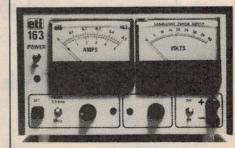

All Altronics prices include Sales Tax Don't be conned by other advertisers whose seemingly low prices are "plus Tax in fine print". You could well pay up to 321/2% more.

FUNCTION GENERATOR



The most essential piece of test gear (second only to a good multimeter) on any hobbyist's bench is some kind of audio signal generator. This design utilizes the latest circuit techniques to produce stable, low distortion waveforms.

A truly versatile unit at a bargain price.

** 4 digit frequency readout (eliminates tiresome dial calibration) — typical accuracy ± 2% ± 3 overlapping ranges x1, x10, x100 ± 600 OHM Nominal Output — continuously variable 3MV — 2.5V P-P Distortion — sinewave : less than 0.7% @ 1KHz ± Linearity — triangle wave: better than 1% @ 1KHz ± Squarewave rise time — 6V/Uz maximum output ± Amplitude stability — better than 0.1dB on all ranges.

With the exception of the display all components mount on a single PCB making this kit suitable for all constructors.

\$85.00

DIGITAL CAPACITANCE METER



NEW DELUXE FINISH

NEW DELUXE FINISH

We are pleased to announce the release of the Digital Capacitance Kit housed in our Deluxe H0480 ABS instrument Case. This superb Test Instrument Kit now compliments our top selling Digital Frequency Counter and Function Generator Project Kit. Electronics Australia Project. Measures capacitance of both polarized and non-polarized capacitors from 1 picofarad to 99.99 microfarads in 3 ranges. Check values of unmarked capacitors, especially those little trimmers that are never coded. Select precise values for filters and timing networks within ease.

EXCLUSIVE TO ALTRONICS Each kit includes precision measured capacitors for accurate calibration of each range.

FOR DESPATCH P&P CHARGES AND ADDRESS DETAILS PLEASE REFER TO OUR AD. ON PAGE 149

Design Techniques for

In Part 1 of this article we discussed basic rhythm structures and established the principles of rhythm generation using clock oscillators, counters and instrument simulators. From this theoretical discussion we now move on to practical circuits which can exploit these ideas and serve as a basis for further experimentation.

As we established in part 1, the basis for every rhythm unit is a device that generates pulses sequentially on separate output lines. One can obtain rhythm effects with as few as three or four output lines but to allow for more interesting variations 16 lines must be considered the minimum and for very fancy rhythm patterns one may need 32

lines to allow for 1/32 beats. Rather than just give one circuit, we shall discuss several approaches; a basic 16 line version, a 32 line version, and a scanning multi-pass circuit. We shall also give some diode matrix rhythm pattern examples.

One word of warning. If you decide to start experimenting with pulse

OUTPUT TO INSTRUMENT SIMULATOR H DIODE IN MATRIX

generating circuits, make sure you have an oscilloscope. Without this instrument it is almost impossible to track down faults in the circuit if it does not work.

The complete circuit of a basic single pass 16 beat pulse counter is shown in Fig. 14. The heart of the circuit is the combination of IC2, 3 and 4 which together form a counter with one clock requency input and 16 output lines. IC2 and 3 are dual D-type flipflops (4013) which together form four flipflop stages in cascade. The Q output of each stage is used to provide the four input lines to IC4.

Depending on the state of each flipflop, the four lines carry a code of high and low voltages. These codes are accepted by IC4, a 4-to-16-line decoder, type 4515. Each input code results in one of the 16 output lines being activated. We shall therefore require a sequentially changing code to obtain the required effect of the 16 output lines to be activated in sequence.

The outputs of IC4 are normally high and will go low one by one when the ap-


TARIE 4

A SECTION OF THE SECT	+12V
	\$1
R1 \$ 22k\$	10001
22k\$ 1 11	14 + + 11 11 14
1 IC1a	13
	9
1 IC2 4013	9 IC3 4013 12
₹vB1	12 4
R2 470k	8 2 5 10 6 7 8 2 5
C1 +12V +12V	
STOP	
A R3 ★ C2 →	
10k 3 .047	
STARTO S2 1 1 1	
3/4	2 3 21 22
\$3	1 + 12V
IC4 CONNECTIONS	IC4 4515
COUNT PIN	24
1 15 IC1b 5	15 19 12 23 16
2 11 40 1	
3 9	
4 10	.047
5 8 6 7	B
7 6	
8 5	33k\$ 33k\$ 33k\$
9 4	+ + + +
10 18	TO INSTRUMENT
11 17	SIMULATOR
12 20	
14 14	
15 12	IE 1 LINE 13 LINE 16
16 16	E 1 LINE 13 LINÉ 16
+12V OPTIONS	12 IC1d
	1001
(♣\) START	(REPLACES S2)
\vee	3.3M
470Ω	
BC108	
FROM POINT 47k STOP	100k 8 IC1c 3.3M≹
B STOP.	W 10 10 10
÷ +	9
DOWNBEAT INDICATOR	START/STOP TOUCH SWITCH Fig. 14
一个人,但是一个人,他们也是一个人,他们也是一个人,他们也是一个人,他们也是一个人,他们也是一个人,他们也是一个人,他们也是一个人,他们也是一个人,他们也是一个	

	TABLE 1											
Input	O	IC4										
pulse number	stage 1	stage 2	stage 3	stage 4	pin low							
1 2 3 4 5 6 7 8 9		L L H H L L H H L .	L L L H H H H L .	LLLLLLLH	11 9 10 8 7 6 5 4 18							
10 11 12 13 14 15	HLHLHLH				17 20 19 14 13 16 15							

Rhythm Generators Part 2

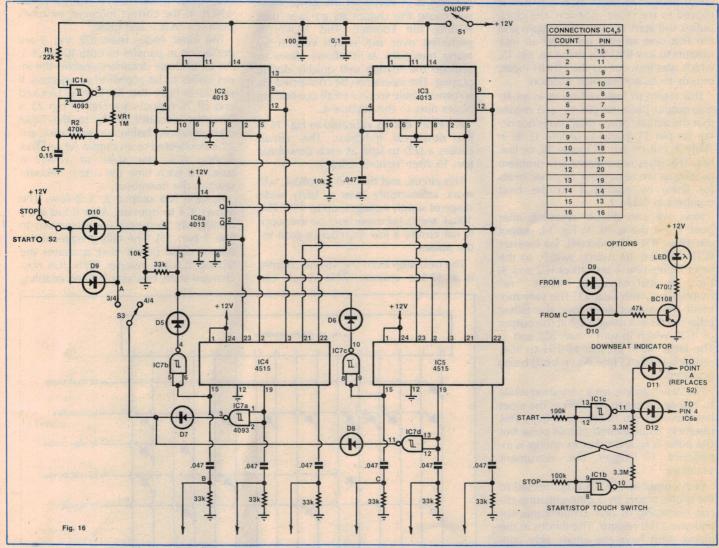by NICK LABORDUS 5/3 Durham Close, North Ryde NSW 2113



propriate input code is presented. As we shall see later, the instrument simulators require a sharp pulse at their input. This means that the output signals of IC4 must be differentiated (Fig. 15). Differentiation of a square wave by an R/C network results in two pulses, a negative one on the falling edge of the square wave and a positive one on the rising edge. Only one of these two can be used to activate the instrument simulator and a decision must be taken before the counter circuit can be designed.

Either version is possible but as there is a time shift between the positive and the negative pulse, the choice has some effect on certain reset connections in the counter circuit. In our example we have selected instrument simulators with a positive input pulse. In Fig. 14, IC1a and its associated components form the clock pulse generator, the frequency of which is determined by the values of C1, R2 and VR1. The clock produces square wave pulses which are fed into four flipflop circuits in cascade. Both IC2 and IC3 consist of two flipflops each. Each flipflop stage divides its input pulse frequency by two. At a clock frequency f, the respective output frequencies of the stages 1 to 4 are: Stage 1 (pins 2, 5 IC2) f/2; stage 2 (pins 9, 12 IC2) f/4; stage 3 (pins 2,5 IC3) f/8; stage 4 (pins 9, 12 IC3) f/16.

Table 1 shows the behaviour of the four output lines as new pulses from the clock generator arrive at the input of flipflop 1. Table 1 also shows which of the 16 output lines of IC4 (indicated by pin number) goes from high to low at

what input code. Note that the flipflops return automatically to the first code after having reached the 16th. This suits our aim perfectly for all non-waltzrhythm patterns. For waltz pattern we need only 12 lines and we shall have to reset the counter after it has produced the 12th output pulse.

But before considering this function in detail we will have to modify the beat (input pulse) numbers of Table 1. This is due to the need to always start the rhythm generator on beat 1.

Using the "on-off" switch to start the unit will result in the counter starting in a random fashion rather than on beat 1 (the down beat). This can be overcome by introducing a separate switch for the "start-stop" action, leaving the "on-off" switch in the "on" position so that all cir-

Design Techniques for Rhythm Generators

cuits are functional.

In the "stop" position, S2 connects a high to reset pins 4 and 10 of IC2 and 3. This forces the four selected outputs to show HHHH, independent of the arriving clock pulses. As soon as the switch is moved to the "start" position, the clock pulses will start to take effect again and the first one arriving will send all four outputs to low (LLLL). In doing so, pin 15, which was low due to the HHHH input, returns to its normal high position.

This return to high will result in an active output pulse on pin 15, and means that the actual "down beat" does not occur on pin 11 (pulse 1, or line 1), as in Table 1, but on pin 15 (pulse 16, or line 16). This does not present any problem as long as we re-number all other beats (or lines) by adding 1 to the beat numbers in Table 1.

Now we can discuss resetting after beat 12 for the waltz. In Fig. 14, output pin 19 of IC4 is connected, via inverter IC1b and the 3/4 (waltz) switch, to the reset inputs pins 4 and 10 of IC2 and 3. Pin 19 corresponds, after "renumbering", with beat 13. The very moment this output goes low, the falling edge results in a rising edge at the output of IC1b which in turn resets IC2 and 3. The latter now present HHHH to IC4, resulting in pin 15 (the down beat) being activated.

Pin 19 will go low for a very short while to initiate the reset. As soon as the reset has occurred, pin 19 returns to high. This results in an unwanted output pulse but this pulse is so short that its energy is insufficient to trigger the instrument simulator.

Each output line of IC4 is connected to the diode matrix by a differentiating circuit consisting of one .047 μ F capacitor and one 33kΩ resistor. The diodes in the matrix must have the anode side connected to the output lines so that only the positive pulses will arrive at the instrument simulators.

Having two spare gates in IC1, we can add a touch control to our rhythm unit without much effort. Touching one of the inputs with the finger will produce a high output, acting as "stop" by resetting IC2 and 3. A touch on the other input will cause the output to go low, thus starting the counter. This facility is perferred over the switch version by many musicians as it allows them to activate the rhythm unit quickly during playing. The inputs can be connected via screened cable to two small conducting plates next to the keyboard.

A further option indicated in Fig. 14 is the downbeat indicator. This circuit causes a LED to light at each downbeat (pin 15 after "re-numbering").


This circuit, and the one to follow, will work satisfactorily over a fairly wide range of supply voltages, up to 15V. The 100µF and 0.1µF capacitors on the supply rail ensure a low impedance path for the pulses.


The next step from the 16-line counter is a 32-line counter. This circuit can

create fancy rhythm patterns with 1/32 beats or act as a double-pass 16-beat counter, allowing some reduction of monotony. The full circuit is shown in Fig. 16. The heart of the circuit is the same as that of the 16 beat counter. In this case there are two 4-to-16-line decoders to obtain 32 output lines. The only other addition is a flipflop (IC6a) which, at the correct moment, switches from IC4 to IC5 and back.

The input codes from IC2 and 3 are presented in parallel to both IC4 and 5. Pin 23 of these decoders enables the input codes to be accepted or rejected. If pin 23 is high, the decoder is blocked and all 16 outputs are high. If pin 23 is low, the decoder reacts to the input code in normal fashion. In each case, pin 23 is connected to an output (Q or Q) of flipflop IC6, the state of which is switched each time the active decoder reaches the downbeat.

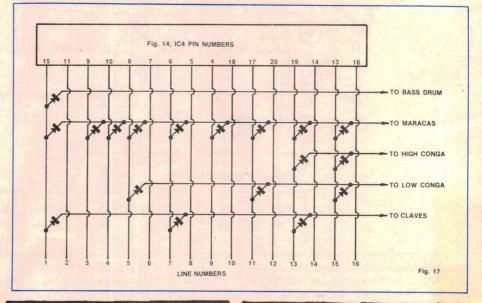Assume IC6 output 2, 5 is low. This allows IC4 to operate. After it has gone through its 16 output lines it returns to line 1 (pin 15). The falling edge of this output pulse (going low), activates the flipflop IC6 via inverter IC7b. IC6 now changes state, blocking IC4 and enabling



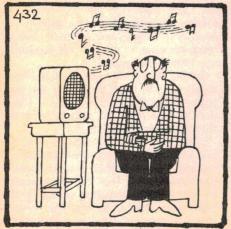





This is the revolutionary Sanyo Betamovie. It records a standard Beta cassette inside the camera itself.

Just pop in the cassette and you can shoot for up to 3 hours 40 minutes with sound.

That's 3 hours longer than you can shoot

with any similar VHS camera.

By wrapping the tape around the circular recording head 300 degrees instead of the conventional 180 degrees, Betamovie's recording head has been reduced in size by 40%.

So everything is self-contained in one

lightweight unit.

No external recorders and cables. The small Betamovie is big on other features too.

It has an F1.2 6x power zoom lens with a 9-54 mm focal length, so it covers everything

including macro.

The minimum light requirement is just 28 lux – a little more than one candlelight.

The through-the-lens viewfinder features LED indicators with all the relevant information vou need.

There's automatic white balance adjustment. And a built-in uni-directional microphone.

Of course if you're considering buying a video cassette recorder, Sanyo Betamovie is a great reason for choosing the Beta format.

But soon there'll be another.


Sanyo Beta Hi-Fi; VCR's with Hi-Fi sound approaching the quality of digital audio disc.

Sanyo Betamovie and Beta Hi-Fi.

Giant breakthroughs that make Beta the better format.

Available soon from selected retailers.

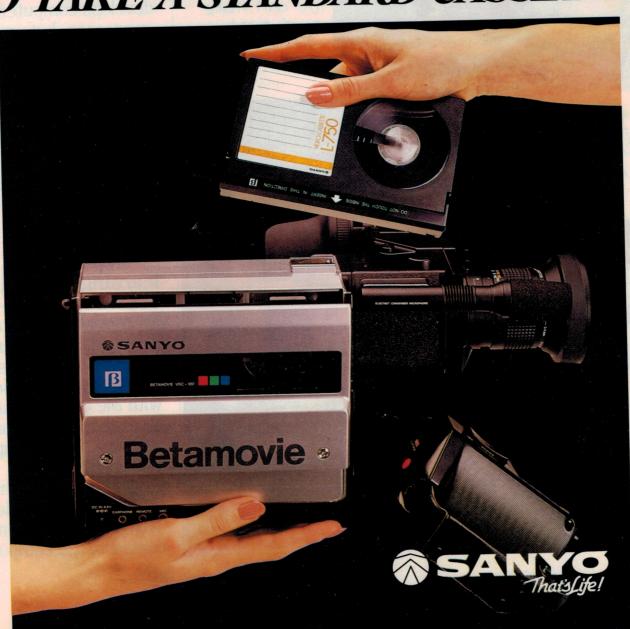THE FIRST VIDEO CAMERA TO TAKE A STANDARD CASSETTE.



TIIOGO

Giving your children the Educational Edge.

A lesson in Educational Software from Texas Instruments.

The natural way to

innovative approach to

education that not only

awareness, but enriches

a child's math, logic and communication skills in a

develops computer

natural step-by-step

TI LOGO is the

learn



"I like TILOGO
because you
can make any
shape you want.
You can make
ots of neat
procedures"

"I wish I could do the computer every day"



"I WISH EVERY SCHOOL HAD TI LOGO" "about 6 weeks
ago I made a
procedure
Called "LIKE."
IT Lists all
the names of
the people | Like
over and over
that's why I like
TI LOTO!"

WHAT THE EXPERTS SAY
ABOUT
TILOGO

Stepby-step learning

TI LOGO is a childappropriate computer
language. This means
students of all levels of
ability can communicate
with the computer using
an easy-to-understand
language. To accomplish
a specific task the
student must "teach" the
computer what to do.
This puts the student in
control of the computer

and so can set his or her level of achievement. Learning is therefore fun and rewarding. **Exploring** increasingly complex learning TI LOGO can teach

students on a personal level helping them to discover the importance of skills like spelling, communication and sequential thinking. With the help of "Turtle Graphics" students can

learn a computational style of geometry by "acting out" the role of the turtle, from simple to advanced stages. The procedure can be saved on a diskette, or cassette and re-used as required. Animated "Sprites" can also be used to create designs already known to the computer, or any shape the student designs. In the home or classroom, a Texas Instruments Home Computer with TI LOGO programme plays a special role in today's teaching and learning.





TEXAS INSTRUMEN

"Everyone should have his own GENIE"

THE VERSATILE, AFFORDABLE COLOUR COMPUTER AT YOUR FINGERTIPS.



Brilliantly simple, ideal for business, home or educational applications, the Colour Genie has all the wanted features and more, including: • Affordable price • 16K RAM Standard capacity • Sharp, colourful graphics in 8 colours • Built-in interfaces • Fully expandable with "off the shelf" peripherals • No commitment to one brand for interfacing compatability • Huge range of software packages available • Keyboard, cassette recorder and 2 manuals included in the low price • Will play video games of all types – or create your own!

Enter the exciting world of computing with the low priced and simple to use Colour Genie!

With many practical applications for use in small businesses, word processing, home accounting and leisure uses, the Colour Genie is packed with features and

For further information and brochure contact: Skarbek Trading and Services

P.O. Box 103, Doncaster East, Victoria 3109 or

value.
All this for only \$499 (including Cassette Recorder)

Telephone (03) 842 1251 Bankcard or Mail Orders Welcomed. (Dealer enquiries invited)

COLOUR GENIE

The Versatile Computer.

Adgroup STS 624

Design Techniques for Rhythm Generators

IC5. The latter now reacts to the available HHHH input by sending pin 15 low, this pulse becoming the down beat for the IC5 cycle of line pulses.

(Note that there is an active output pulse on pin 15 of IC4 at this moment, as this pin returns to high. This pulse is so short, however, that the energy content is insufficient to activate the instrument simulator.)

This low pulse on pin 15, IC5, also appears, inverted by IC7c, at the input to IC6a (pin 3), but does not have any additional effect because it appears at this point simply as a continuation of the pulse which began on pin 15 of IC4. After IC5 has been through a full cycle of 16 beats and pin 15 goes low again, IC6

switches again and enables IC4.

The "start-stop" and "3/4" actions are the same as described before but require more connections to control more ICs. The circuit also shows the options suggested for the previous circuit, the down beat indicator and the start-stop touch switch.

The diode matrix represents the "recipe book" of the rhythm unit. It is not the intention of this article to provide the reader with a complete list of recipes. The reason for experimenting with rhythm units is to develop new and interesting patterns. The way to do this is to listen to a record, analyse the rhythm and to try to simulate it in the diode matrix. This takes time and patience but


is great fun, especially when one plays an instrument like a piano or an organ.


In order to set up the rhythm unit with some test patterns, Table 2 gives some recipes for a 16-beat counter. Fig. 17 shows the actual diode matrix for the "rhumba" pattern in Table 2.

Rhythm selector switches are required to connect certain diode matrices to instrument simulators. For each rhythm, one multi-pole switch is needed. As explained in Part 1, such switches are difficult to buy, and expensive. For that reason it was decided to use single pole switches which control type 4016 quadruple bilateral switches. These ICs are readily available and as the four CMOS gates in each IC are individually accessible, total freedom is obtained in determination of the number of poles per selector switch.

Fig. 18 shows the "waltz" selector switch. The number of switch elements is equal to the number of instrument simulators to be activated (plus one acting as the 3/4 switch in this case). With the selector switch in the "off" position, the control inputs of the CMOS switches are kept low, causing them to be turned off. In the "on" position, the control inputs go high and each CMOS switch element now connects the appropriate diode pattern to the instrument simulators.

Continued next month

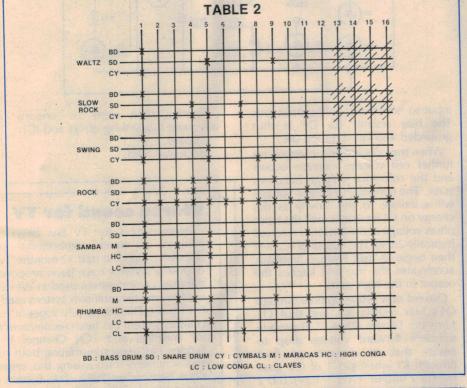

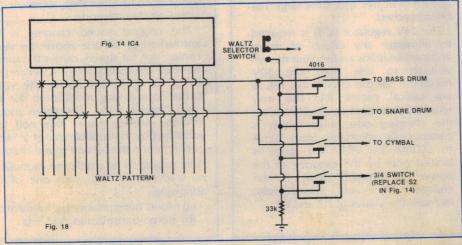



1920's style vintage wireless set as described in Nov. E.A.

This vintage style Unidyne wireless kit may be your last chance to bring an ancient circuit to life and at the same time gain a valuable momento of the "golden era" of valve radio. All parts are provided, including a spare valve, and the coils and wiring techniques faithfully duplicate the methods of the radio pioneers of the 1920s. The set features a solid mahogany base, gold

The set features a solid mahogany base, gold lettered bakelite panel and early phones. It really works well and has the appearance and feel of a genuine museum piece.


feel of a genuine museum piece. Price is \$79.50 plus \$5 postage and packing. An excellent gift idea. Send payment with your order now to ensure delivery before Christmas.

To: Technicraft

338 Katoomba Street, Katoomba N.S.W. 2780 Telephone: (O47) 82 3418

Circuit & Design Ideas

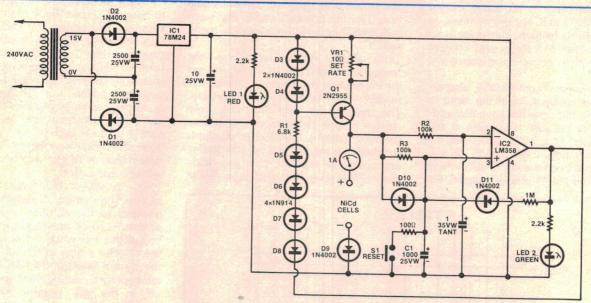Interesting circuit ideas from readers and technical literature. While this material has been checked as far as possible for feasibility, the circuits have not been built and tested by us. As a consequence, we cannot accept responsibility, enter into correspondence or provide constructional details.



Constant current NiCd charger with automatic shut-off

During the charging cycle of NiCd cells, the voltage increase across them follows an upward monotonic curve. When the cells are fully charged, the voltage across them remains constant. This NiCd charger circuit detects when no further change occurs in cell voltage and automatically turns off the charger at the end of the charging cycle.

A bonus of this scheme is that the charger can automatically accommodate from one to 12 cells, since specific voltages are not detected. Only the charging rate requires manual setting.

The circuit shows a conventional constant-current charger (Q1 et al) configured so that the cell voltage to be detected is ground-referenced. Any constant-current charger could be adapted to this design.

The full-charge detector circuit employs an LM358 op amp (IC2) as a comparator in which the cell voltage is applied to the inverting input (pin 2) as a reference voltage whilst the same source applied to the non-inverting input (pin 3) is delayed by the time-constant R3.C1. As long as the reference (cell) voltage continues to increase, the non-inverting input will lag sufficiently behind the inverting

input to hold the LM358 output low. The bias resistor for Q1 is thus grounded and Q1 is turned on.

When the cells are fully charged, no further cell voltage increase occurs and the reference voltage becomes static. The non-inverting input voltage will continue to rise slowly as the charge on C1 increases until the input offset voltage of the LM358 is reached (typically 2mV). The output of IC2 will then begin to rise. Positive feedback accelerates the rise and latches the output in the high state.

Current now ceases to flow through Q1's bias resistor R1, and thus Q1 turns off. Diodes D5, 6, 7, 8 provide sufficient forward voltage drop to ensure that no current can flow through R1 when pin 1 of IC2 goes high (IC2 output = Vcc - 1.5V). LED 2 (green) indicates that full-charge has been reached.

The 24V regulator (IC1) is required to eliminate any effects of mains voltage variations and to limit the rail voltage to less than the 30V maximum for the LM358. No values are critical except R1. This may require adjustment to accommodate the charging rate range which is continuously adjustable from 50mA to 500mA by VR1. The range is limited only by the capacity of the power transformer used. If the charger shuts off prematurely, increase the values of R2 and R3.


Finally, take care to ensure adequate heatsinking of Q1 and IC1. I. Board, McDowall, Qld.

Stereo sound for TV

Stereo sound for TV has been the subject of much experiment and discussion over the past 12 months. Two opposing systems have been proposed: the dual carrier system used in Western Europe, and the multiplex system used in FM stereo. The technically superior two channel system has been recommended for Australia and TCN Channel 9 in Sydney has been transmitting both real and simulated stereo using this system since September 1982. The system is designed to handle mono, stereo or dual language transmissions.

The original sound channel is left untouched at 5.5MHz above the vision carrier, but, for stereo, carries the sum of the two channels (L + R). A second FM carrier at 5.742MHz above the vision carrier carries the modulation for the right channel only. The three modes (mono, stereo, dual channel) are identified by the modulation of a 54kHz subcarrier on the second sound channel. This subcarrier is amplitude modulated to a depth of 50%, with one of the following:

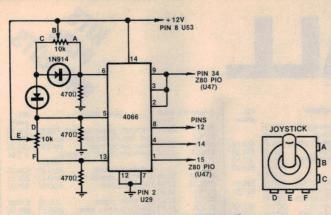- (a) Mono transmission: no modulation
- (b) Stereo transmission: 117.5Hz



Super-80 joystick and interface

If you need a joystick for the Super 80 Computer costing around \$7.00, here is a simple circuit to interface the Tandy Electronics 40k Joystick (Cat No. 271-1706).

The circuit uses a 4066 quad bilateral switch IC. This IC has four analog switches which close when the control pin voltage is 70% of the rail voltage, and open when the pin is grounded. Pins 5, 6 an 13 are the control pins and are normally tied low by 470Ω resistors.

When the resistance of the joystick decreases, additional current flows though the 470Ω resistor(s) to ground and this, in turn, activates the analog switches. The switches are connected to the Z80 PIO in the same manner as the keyboard switches so, when using the keyboard, it is essential to have the joystick-pole centred.

For this joystick to be used with the Super 80, you will have to poke the following numbers and also set up the following USR commands.

FOR A=0 to 23:READ B:POKE A,B:NEXT A DATA 62,247,24,6,62,253,24,2,62,254,1,0 DATA 0,211,248,219,250,254,127,192,1,1,0,201

USR COMMANDS

IF (USR(0)=1) AND (USR(4)=1) THEN...: REM JOYSTICK POLE IS IN THE DOWN POSITION

IF USR(0)=1 THEN...: REM JOYSTICK-POLE IS IN UP

IF USR(4)=1 THEN.... :REM JOYSTICK-POLE IS TO THE

IF USR(8)=1 THEN.... : REM JOYSTICK-POLE IS TO THE LEFT

Here is a program to make the character "X", draw a picture on the screen with the use of the joystick.

10 CLS:W=271

20 FOR A=0 TO 23:READ B:POKE A,B:NEXT A

30 DATA 62,247,24,6,62,253,24,2,62,254,1

40 DATA 0,0,211,248,219,250,254,127,192,1,1,0,201

50 IF (USR(0)=1) AND (USR(4)=1) THEN 100

60 IF USR(0)=1 THEN 110

70 IF USR (4)=1 THEN 120

80 IF USR(8)=1 THEN 130

90 GOTO 50

100 L=32:GOTO 140

110 L=-32:GOTO 140

120 L=1:GOTO 140

130 L=-1

140 W=W+L

145 IF (W>511)OR(W(0) THEN W=271

150 CURS W:PRINT "X"

160 GOTO 50

D. Milic, Knoxfield, Vic.

(c) Dual language: 274.1Hz

Tone decoders are normally provided to detect these tones and switch the outputs appropriately. However, readers may like to experiment with stereo reception using manual switching.

This circuit shows a simple method of obtaining stereo sound from a Philips K9 or K11 receiver. The method consists of duplicating the FM demodulator section and dematrixing the resulting (Right) output to yield Left and Right channels.

A simple demodulator is the Philips U240 module which can easily be retuned to 5.742MHz. When added to a Philips K9 or K11 receiver, the module outputs are then suitable for direct connection into a summing amplifier. The outputs of the two op-amps are Left and Right directly, and can drive line level inputs on your stereo or VCR. The prototype used an 8-pin dual MC1458 op amp IC but two 741s would be just as good.

Note that pins 2 and 3 of the U240 module provide a balanced audio output at constant level. Pin 5, however, provides an audio output that varies with the remote control setting.

A standard TV IF response is designed to handle an FM sound signal at


31.375MHz, and the response includes a minimum at this frequency. Some frame buzz may be evident in the output of the second channel, and the setting of the sound IF trap may need to be changed to a frequency between the old (31.375MHz) and new (31.133MHz) sound carriers.

The alignment procedure for the additional U240 module is as follows:

- Connect an FM signal generator to pin 17. Set generator to $100\mu V$ out at 5.5MHz, modulated with 1kHz;
- Observe demodulated audio on pin 3 of module (preferably using a CRO);

- Adjust L11 and L12 for maximum audio output (see Fig.1). Adjust L10 for lowest noise/distortion;
- Retune signal generator to 5.6MHz, 5.7MHz and, finally, 5.742MHz. Adjust L11, L12 and L10 as above for each new frequency;
- Check that limiting occurs at IF input at $100-130\mu V$;
- Set generator to 5.742MHz and 50% AM and adjust L10 for minimum demoduated audio. (Note: he shield should be fitted for this adjustment.)

A. Wyatt, Turramurra, NSW.

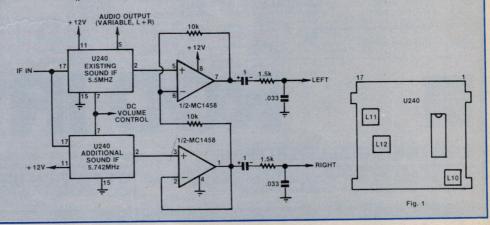



WALL

Board N	o PCB Price			Kit	Board No				Kit	Board No	PCB	Description		V:A
EA6800	\$15.50	6800 Micro computer		price \$119.00	81UA6	Pric	e		price		Price	9		Kit price
EA6802	\$15.50	6802 Micro computer		\$119.00	81MC7	\$2.90	Benchmate power supply Moving coil preamp	JUN 8		79TI11 83FC2	\$3.90	Trans.ass. ignition update	ed FEB 8	3 \$34.50
		Power supply to suit Hex keypad 19 keys		\$35.00 \$39.50	81OR7 81P6	\$9.50	Electrochume (electr. orga	n) JUL 81	1 \$59.00	83BP3	\$3.90	Fuel consumption meter) Brown out protector	MAR 83	
75L11	\$2.50				81SW7	\$4.90	Pools/lotto selector Electronic steam whistle	JUL 81	\$22.50	83MS4	\$3.90	Stereo simulator PCB ver	sion	\$12.00
78UP10 79FE11	\$9.50	2650 extra ram Photo flash exposure mtr.	OCT 78		81MC8	\$10.90) Musicolor IV	AUG 81	\$84.00			Self contained unit	APR 83	\$ \$20.00
79PC9	\$3.90	Pulse generator	NOV 79 SEP 79		81SM7 81CL9	\$3.90) Bagatelle) Digital clock/thermometer	AUG 81		83PC3A	\$3.90	Touch lamp dimmer	APR 83	\$20.00
79SE3 79TI11	\$4.90	Train model sound	MAR 79		81GA9	\$4.90	Photon torpedo game	SEP 81 SEP 81	\$80.00 \$24.50	83PC3B 83PS5	\$3.50	Touch lamp timer	AUG 83	\$21.00
79PS11	\$2.90	Transistor assisted Ign. Experimenters power sup	NOV 79	\$34.50	81UC8 81WS10	\$4.50	Universal timer & stpwatch Wind universal indicator	SEP 81		83SC7	\$3.90	LCD event counter	JUL 83	\$ \$32.00
79PC12 79SF10	\$2.90	Fan speed control	DEC 79		.81AO10	\$3.50	Audio test unit cass. deck	OCT 81	\$52.50 \$47.50	83SC8 83VA8	\$3.50	2MHZ digital freq. meter	AUG 83	\$60.00
79SF10 79SF9	\$2.50	Photo slave flash Photo sound trigger	OCT 79 SEP 79		81SS11 81SG9	\$8.90	Slide cross fader	NOV 81	\$99.50	83EG5	\$4.90	Video amplifier Electronic roulette wheel	AUG 83 MAY 83	\$15.00 \$24.00
79UPS6	\$3.90	Universal power supply	JUN 79	\$34.50	81AU11	\$3.90	Led sandglass Audible turn indicator	NOV 81 NOV 81		83PS5		Electronic breath tester	MAY 83	\$25.00
80ST10A 80ST10B	\$3.90 \$3.50	Stylus timer	OCT 80		81FM10A	\$5.90	500MHZ digital freq. mtr.	DEC 81	\$135.00	83GA6	\$7.90	50V/5A power supply Effects unit	JUNE 83 JUNE 83	\$140.00
80TC12	\$3.90	Bipolar train controller	OCT 80 DEC 80	\$34.50	81FM10B 81CH12	\$3.90 \$3.50	Christmas decoration	DEC 81		83PP5	\$5.90	Overload indicator	ILINE 83	\$20.00
80CM3A 80CM3B	\$4.90 \$3.90	Digital capacitance mtr.	MAR 80	\$49.50	81LD12	\$4.50	Led bar graph display	DEC 81		83PS7 83AL6	\$3.50	±12V for lab power supply Fridge door alarm	JULY 83 JULY 83	
80PG6	\$7.90	TV pattern generator	MAR 80 JUN 80	\$67.50	81MI11 81WD12A	\$3.90	Metronome (low current) Wind direction indicator	JAN 82		83MS4	\$3.90	Compumuse	AUG 83	\$20.00
80TV8 80F3	\$4.50	TV CRO adapter inc. p/pag	ck AUG 80	\$39.90	81WD12B	\$3.50	will direction indicator	JAN 82 JAN 82	\$24.50	83WM8 83TT8	\$6.95	Electronic watt meter Transistor tester	SEPT 83 SEPT 83	\$65.00
80PP3	\$2.50	Audio prescaler	MAR 80 MAR 80		81P19 82EP1	\$6.90	Construction of the constr			83MS8	\$4.90	Soil heating unit	SEPT 83	
80LL7 80B7	\$3.90	Leds & ladders	JUL 80	\$19.50	OZEFI	\$12.50	Free standing eprom prog with '24 pin' textool socket	JAN 82	\$45.00 \$55.00	83VE10 83MD9	\$4.90	Video enhancer Nail finder	OCT 83	\$35.00
80BM10	\$3.90	Beat frequency oscillator Car battery monitor	JUL 80 OCT 80	\$11.50	007110		and AC plugpack		\$69.50	83SS9	\$3.90	Speed sentry	OCT 83 OCT 83	\$10.00 \$11.00
80DC10	\$6.50	Digital storage CRO ad.	NOV 80	\$89.90	82TH2 82CR1	\$3.90	Digital thermometer Lge. scrn. storage CRO Add	FEB 82		ET014 ET043	\$4.90	Dual voltage power supply	DEC 71	
80HLA5 80LS12	\$2.90	Car headlight alarm Selectalott	MAY 80	000.00				FEB 82	\$119.00	ET044	\$2.50	Heads or tails Two tone doorbell	OCT 76 OCT 76	\$3.90 \$4.90
80LBR12	\$2.90	I ight heam relay	DEC 80 NOV 80	\$22.00 \$13.00	82EG2 82PS2	\$3.90	Cudlip Dual tracking power supply	FEB 82	\$12.95	ET047	\$2.50	Morse practice set	DEC 76	\$3.90
80PC4 80PC7	\$2.90	Power heat controller	APR 80		82LF2	\$3.90	Low fuel indicator	MAR 82 MAR 82	\$87.50 \$16.50	ET048 ET061	\$2.50	Buzz boards Simple audio amp	DEC 76	\$4.50
80G6	\$5.90	Power saver induc mtr Musical tone gen.	JUL 80 JUN 80		82CM3 82AO3A	\$3.90	LCD capacitance meter	MAR 82	\$79.00	ET062	22.90	Simple AM funer	OCT 76 MAR 77	\$5.90 \$6.90
80GPS3 80AU3	\$2.90	Voltage regulator multi	MAR 80		82AO3B	\$3.90	Function generator	APR 82 APR 82	\$79.50	ET063 ET064	\$2.90	Electronic bongos Simple intercom	NOV 79	\$5.90
80AW4	\$4.50	Hifi auto turn off Receiver all wave	MAR 80 APR 80		82VC3	\$3.50	Voice canceller	APR 82	\$22.50			Electronic siren	OCT 83 DEC 79	\$5.90
80TM8A	\$6.90	Digital engine analyser	AUG 80	\$49.50	82VX4 82VS10	\$3.50	Vox	APR 82	\$15.00	ET066	\$2.50	Temp alarm	DEC 79	\$5.50
80TM8B 80PP7A	\$2.90	Eprom programmer	AUG 80		82PT4	\$3.90	Photographic timer	APR 82	\$48.00	ET067 ET068	\$2.90	Singin moisture Led dice	OCT 76	\$7.95
80PP7B	\$3.90		JUL 80 JUL 80	\$79.50	82IV5 82P5	\$5.40	12-240V inverter 40 watt Universal preamp MM/MC	MAY 82	\$49.50	ET071	\$2.50	Tape noise limiter	JUN 79	\$6.90
80RF5 80SA3	\$2.90	Rumble filter Playmaster stereo amp.	MAY 80		82TO5	\$3.90	Tacho/dwell meter	MAY 82 MAY 82	\$35.00 \$72.50	ET072 ET081	\$2.50	Two octave organ Tachometer	JUN 78	\$9.50
80CH7	\$8.50	24UV ac light chaser	MAR 80 JUL 80		82TS3 82GA5	\$3.90	Low cost touch switch Guitar booster	MAY 82	\$12.00	ET083	\$2.50	Train controller	OCT 83 DEC 79	
80RAM12 80PA6	\$5.90	Ram expansion for dream	DEC. 80	\$39.00	82EM6A	\$4.90	Theremin	JUN 82 JUN 82	\$17.50 \$34.50			Car alarm Car over rev. alarm	JAN 77	\$13.50
		Playmaster 300W amp mod	JUN 80	\$63.00	82EM6B 82IV6	\$3.90 \$8.90	12 240V inverter 200			ET130	\$2.50	Temp/volts converter	OCT 79 FEB 76	
80CL4 80TRS11	\$3.50	Timer controller	APR 80				12-240V inverter 300 watt Power monitor	JUN 82 JUL 82	\$195.00 \$18.00	E1132	\$3.90	Experimenters power suppl R.M.S. voltmeter	yFEB 77	
80SA10	\$9.90	RS 80 printer serial in. Playmaster mosfet stereo a	NOV 80	\$17.50	82HB6	\$3.90	LDC heart rate monitor	JUL 82	\$79.00	ET135	\$3.50	Digital panel meter	AUG 77 OCT 77	
90AD10			JAN 81		82CC7A 8	\$4.00	Car computer to	JUL 82 SEP 82	\$109.00	ET136	\$2.90	Linear scale cap meter	MAR 78	
80AD12 80RM12	\$3.00 /	Autodim light dimmer Cylon voice simulator	JAN 81 JAN 81	\$32.00 \$19.95	82DP6 82PA7	\$4.90	Decimal point for D.G. meter	JUL 82	\$70.00	EIIO/D	53.90 /	Frequency meter LCD Audio oscillator	MAY 78 MAY 78	
80FB12	\$3.90 (Buitar fuzz box	FEB 81	\$19.90	82PA7 82UR8	\$9.50	Sub woofer amp Ultrasonic rule	JUL 82 AUG 82	\$85.00 \$49.00	E1139	\$2.50 I	Power meter	MAY 78	
81SW1 81SP1	\$3.90 (Osc. switch dual trace RS 80/SYS 80Serial interf	FEB 81	\$60.00	82MS8	\$6.50	Stereo synthesizer	SEP 82	\$55.00		3.50 B	Electronic dummy load Two tone generator	OCT 80 JUL 80	\$99.00
81GA3	\$11.50 (olor graphic analyser	MAR 81 S	\$109.00	82EF9 82PC8	\$4.90	Electric fence Fluorescent starter	SEP 82	\$19.50	ET152	52.90 (Capacitance meter	FEB 80	\$34.90
80GA12 81DC2	\$6.50 2	5W guitar amplifier e Gong doorbell	MAR 81		82FC8A	\$6.50 1	Digital readout	OCT 82 OCT 82	\$5.00 \$72.00	ET153 S	3.50	Temperature adaptor Crystal marker	MAY 83	\$19.95
81DC3B	\$8.50 L	ligital and	MAR 81 S	\$14.95	82FC8B	\$3.90 F	For short wave	OCT 82		ET158 9	3.50 L	ow Ohms meter	OCT 81 NOV 81	\$37.50 \$36.50
81DC3A 81IR4	\$9.50 A	nalogue storage CRO	MAR 81		82TA10	\$3.90 F	Freezer alarm	OCT 82 OCT 82	\$21.00	ET159 ET160	2.90 1	0-15V exp. scale voltmeter	DEC 81	\$26.50
81RC4C	\$2.90 Ir	nfra-red relay receiver nfra-red relay transmitter	APR 81 APR 81	\$39.00	82VS10	\$7.90 9	Speech Synthesizer	OCT 82		ET161 . 9	4.90 E	3.8V 10 amp power supply valuation meter	JUL 82	
81HB4A	\$7.50 H	eart rate monitor	APR 81	\$82.00	82PC10 82AL11	\$3.90 F	Power up Super siren	NOV 82 NOV 82	\$36.00 \$23.50	E1162 \$	64.50 C	0-30V var. power supply	DEC 82	\$47.50
81HB4B 81MA4	\$3.50 \$4.50 T	ouch sensitive alarm	APR 81 APR 81		82PC11	\$3.90 [Driveway sentry		\$32.00		8.00 2	0-40V/5A alb power supply Zener diode tester	MAY 83 MAY 83	
81VM2	\$2.90 H	igh impedance DC voltmete	er		82QR12A 82QR12B	\$9.95 F \$9.95	Playmaster AM tuner	DEC 82 \$		ET166	F	requency counter	AUG 83	\$9.00 \$16.00
81SI3	\$7.90 T	RS 80/SYS serial interf.	APR 81 APR 81		82PH12	\$4.90 [Digital PH meter	DEC 82 9	\$135.00		4.90			
81RC4A	\$4.90 2	channel (receiver)		\$72.00	82EG12 82FD5	\$2.90 E \$4.90	Boggle goggles (short form)	DEC 82	\$9.60	ET166D \$	4.90 F	ower supply	AUG 83	\$24.00
81RC4B	\$2.50 In	fra-red remote (preamp)	MAY 81		82DP6	\$3.90				E1165 \$	7.50 T	acho calibrator	NOV 82	\$39.50
81SP5	\$2.90 S	ound pressure meter	MAY 81 MAY 81	\$37.00	83TV1A 83TV1B	\$4.90 F		JAN 83	\$39.50	E1255 \$	2.90 T	hermometer	NOV 77 NOV 80	
81CC5	\$2.90 P	C birdies	MAY 81	\$14.50	83TV1C	\$2.90		JAN 83 JAN 83		ET256 \$	3.50 H	lumidity meter	OCT 83	\$29.50
81DT5	\$3.00 D	ream tape controller	MAY 81 MAY 81		83PS1 S	3.90 F	Plugpack regulator	JAN 83	\$14.00	ET257 \$	2.90 U	Iniversal relay board	OCT 83 MAY 81	\$19.95 \$13.50
81MP6	\$3.90 M	icroprocessor power suppl	ly		83EG1 S	3.50 L	vith plugpack ed head light chaser	JAN 83	\$29.50 \$12.00	E1230 \$	2.50 N	ini drill speed controller	JUI 81	\$9.50
		udio oscillator	MAY 81 JUN 81 5	\$59.00	82WB1 5	52.90 V	Vheatstone bridge	FEB 83	\$45.00	ET259B \$	3.90	'ersatile 'incremental' timer	JAN 82	\$39.00
			301101	00.00	82AO2 \$	2.90 A		FEB 83 FEB 83	\$8.00	ET260 \$	2.60 P	hoto lamp flasher	DEC 79	A. Carlot
	Y	STATE OF STA					P(C) 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	2000	100000000000000000000000000000000000000				S. Carre	



ROD IRVING

ROD IRVING ELECTRONICS

425 High St., Northcote, Vic. 48-50 A'Beckett St., Melb., Vic. Phone (03) 489 8866, (03) 489 8131, Mail Order Hotline (03) 481 1436
Mail orders to P.O. Box 235 Northcote 3070 Vic.

Minimum P & P \$3.00. Errors & omissions excepted.

Telex AA 38897

CHART WAY

		1		The state of the s	THE PARTY			Via.	1	1	FL		Kit
Board No					PCB	Description		Kit price	Board No	o PCB Price	Description		price
	Price	DEC 70	price		Price	Series 5000 preamp comple		\$259.00	ET650A	\$4.90 S	Stac timer	NOV 78	Name of Street
ET261 ET263	\$2.90 Fog horn \$2.90 Simple egg timer	DEC 79 DEC 79			5	Series 5000 preamp front pa	panel	2200.00	ET650B	\$4.50			
ET263 ET264		MAR 80		THE REAL PROPERTY.	- 5	Series 5000 preamp metal v	work		ET650C	\$4.50	200	1	0.00
ET265	\$3.90 Power down	JUL 83 \$	\$37.00	ET480	\$4.50 1	100 watt amp module	30 AP	\$25.50	ET653		16 Channel comp output driv	iver	\$45.00
ET268	\$2.50 Nicad float charger	MAR 83	\$9.50		\$4.50	50-100W amp module pwr s	supply	\$22.50				NOV 82	\$169.00
ET316	\$3.50 Transistor assisted ignition	MAY 77 \$	\$34.00				30 AP		ET654	\$69.00 €	Gen. purp. interfce. for Appl	MAR 83	\$109.00
ET317	\$3.90 Car rev monitor	JUL 77	\$34.00	ET481M	\$3.95	Hi-power p.a./guitar amp mo	nod. 30 AP	1	ET660	\$19.00	Learners microcomputer	OCT 81	\$99.00
ET324		AUG 80 S MAY 83 S	\$34.00 \$17.50	ET481PS	\$4 90	12V/100 p.a. inverter	30 AP	1	21000	K	Key set (18) to suit ET660		\$30.00
ET323 ET325	\$3.90 Headlight delay \$2.50 Car auto electric probe	WIA 1 03	¥17.50	ET481PS ET483	\$4.50	Sound level meter	FEB 78			C	Colour option kit to suit 660		\$16.50
ET326	\$2.50 Exp. scale led voltmeter		\$12.50	ET484	\$5.90 1	Expander compressor 30 A	APJUL 77	The state of the s	ET668		Microbee eprom programm	mer	\$38.00
ET327	\$3.50 Turn/Hazard indicator	OCT 80 \$	\$22.00	ET485	\$5.25	Graphic equaliser	JUN 77	250.00				FEB 83	\$47.50
ET328	\$2.90 Led oil temp meter	JAN 81 S	\$19.00	ET486	\$4.90	Howl round stabilizer	NOV 77	\$59.00	ET670		With textool socket Low cost micro keyboard	MAY 82	ψ 4 7.50
ET329	\$2.50 Exp. scale vehicle ammeter		\$19.00	ET488 ET489A		60W amp module Audio spectrum analyser no	JAN 83	1	ET670 ET682	\$79.00 V	Versatile eprom card	MAY 81	\$115.00
ET330 ET332	\$3.90 Car alarm \$3.90 Electronic stethoscope		\$29.00				APR 78	THE REAL PROPERTY.	ET686	\$9.50 p	ppi-based eprom programm	mer	\$48.00
ET332 ET333	\$3.90 Electronic stethoscope \$3.90 Reversing alarm	JAN 82 5	\$10.00	ET489B	\$3.50			1	200			OCT 82	
ET334	\$3.90 Auto tester	JAN 83		ET492	\$3.90	Sound bender	FEB 82	\$29.00	ET688A	\$3.50 L	Bipolar prom programmer		\$48.50
ET335	\$4.50 Windscreen wiper controller	erMAR 83	004.01	ET494		Loud speaker protector	OCT 82	\$24.50	ET688B	\$3.50	Aerial amp	MAR 76	
ET336	\$3.90 Low cost tacho dwell	AUG 83	\$24.00	ET496		Speakers & crossovers		\$749.00	ET708 ET713	\$4.90	Aerial amp FM tuner add on	SEP 77	
ET363 ET417	\$3.50 \$2.90 Overload indicator	AUG 73	1			Speakers & crossovers Crossover kits		\$199.00	ET717	\$4.90 0	Crosshatch generator	MAY 78	L. York
ET417 ET421	\$2.90 Overload indicator Three way (Dick Smith)	SEPT 83				Speaker boxes (prices per p	pair)	\$269.00	ET724	\$3.90 N	Microwave leak detector		\$16.50
ET421 ET438	\$3.90 Led level meter		\$12.95	ET499	\$4.95	5 50W mosfet amp 75-85	MAR 82	\$79.00	ET726	\$3.50 F	R.F. amp 70W 6/10 meter	FEB 80	
ET440	\$8.50 25 Watt stereo amp	MAR 75		27 TV 74	AL TENA	Transformer	The state of the s	\$43.50	ET729	\$3.90 (UHF TV masthead amp	APR 81	\$36.00
ET445	\$2.90 General purpose preamp	JUL 76	\$8.25	ETER	64.0-	Anodised heatsink		\$42.50	ET730 ET731		UHF TV converter Teletype modulator	MAY 81 OCT 79	
ET446	\$3.90 Stereo limiter	JUL 76 MAY 77	The same of	ET525 ET527	\$4.90 \$5.90			22/10/20	ET731 ET733	\$4.50	RTTY computer decoder	APR 83	\$20.00
ET449 ET450A	\$3.90 Mike preamp \$4.90 Bucket brigade	MAY 77 DEC 77	The state of the s	ET527 ET528) Intruder alarm	JAN 75		ET734	\$7.90 F	Phoney patch	MAY 83	\$65.00
ET450A ET450B	\$4.90 Bucket brigade \$4.90	DLOTT	WEEK	ET539	\$3.90) Touch switch	MAR 76		ET735	\$4.90 (UHF to VHF convertor	MAY 81	
ET452	Guitar practice amplifier	JAN 80	100000	ET541	\$3.90) Train controller	MAY 76		ET736		Radio facs pict-comp deco	oder	\$25.00
ET453	\$2.90 Amp class B gen purpose	APR 80	The same of	ET547	\$3.50	Telephone bell extension	JUN 77	177 19114	ETTO	92.00	Video mod to suit con	SEPT 83	
ET454	\$3.90 Fuzz box	APR 80	\$20.50	ET549A		Metal detector	MAY 77 MAY 80	HOUSE STREET	ET760 ET824		Video mod. to suit 660 micro Slot car power supply	DEC 81	\$15.50
ET455	\$4.50 Loud speaker protector		\$32.50 \$49.50	ET560 ET561		240V mains locator Metal Detector	MAY 80 MAR 80		ET825	\$5.90	Slot car contr. (no case)	DEC 81	\$59.00
ET457 ET458	\$3.90 Scratch & rumble filter \$4.90 Led level meter		\$49.50 \$27.00	ET562	\$3.90	Geiger counter	APR 80		ET905	\$16.00	Polyphonic organ	JAN 83	
	\$4.90 Led level meter \$16.50 Series 5000 1/3 oct graph e	equ \$	\$189.00	ET563	\$4.50	Nicad fast charger	JUL 80	\$59.95	ET918	\$3.90	A SHARE OF SHARE		
		NOV 82		ET566A	\$2.90	O Pipe & cable locator	APR 80		ET1501A	\$2.90 1	Negative ion generator	APR 81	\$39.00
ET459B	\$16.50			ET566B	\$4.90	0			ET1501B	\$2.90	A CONTRACTOR OF THE PARTY OF TH		
MARKE	Graphic equ. front panel		WHAT I	ET567	\$4.50	O Core balance relay	APR 81 OCT 80		ET1501C ET1503		Battery charger	AUG 81	
ETIE	Graphic equ. metal work	DECO	\$20.00	ET568 ET570A	\$2.90	0 Photo flash trigger 0 Infrared 'trip' relay TX	JAN 82	\$24.50	ET1505	\$5.90	12V fluoro. inverter	AUG 81 AUG 82	
ET461 FT464	\$3.90 Balanced input preamp \$2.90 IC audio amplifier	DEC 82 JUL 83	\$20.00 \$8.00	ET570A ET570B	\$3.20	0 Infrared 'trip' relay RX	JAN 82		ET1506	\$2.90			
ET464 ET465	\$2.90 IC audio amplifier \$4.50 Loud Hailer	JUL 83	\$50.00	ET572	\$4.90	O Digital pH meter with probe	pe DEC 80	\$109.00	ET1509	\$4.90	D.CD.C. inverter	SEP 82	
ET466	\$8.50 300W amp module	FEB 80	\$67.50	ET573	\$4.50	0 Universal timer	OCT 79		ET1510A	\$3.90	Model railway points	JAN 83	1000
ET467	\$6.90 4 input mike preamp	JUL 80	\$29.50	ET575	\$2.90	0			ET1510B		Controller and indicators Immersible temp, controlle	ler FEB 83	3 \$19.50
ET470	\$4.50 60 watt amp module series	s 4000	\$26.00	ET576	\$8.90	Electromygram General purpose power su	TPV 6	\$95.00	ET1511 ET1512		Immersible temp. controlle Electric fence tester	FEB 83	\$24.50
ET471	\$9.90 Audio preamp series 4000	TPV 6	\$49.50	ET577	φ3.5L	Electromygram General purpose power su	TPV	100.00	ET1515	\$3.95	Motor speed controller	APR 83	3 \$27.50
E14/1	\$9.90 Audio preamp series 4000 Series 4000 front panel	1176	\$49.50	ET578	\$3.90	Simple nicad charger	JUN 80		ET1516	\$3.90) Model engine ignition syst	tem	\$41.50
ON THE REAL PROPERTY.	Series 4000 metal work			ET581	\$3.25	5 15V dual power supply	JUN 76	\$17.50	ET1517	\$3.75	Video distribution amp	SEP 83	3 \$45.00
ET472	\$4.50 Power supply for series 400	100 TPV 6	\$24.00	ET583	\$2.90	Marine gas alarm	AUG 77	7	ET1520	\$3.90) Wideboard amp	JUL 83	3 \$37.00
ET473	\$5.90 Moving coil preamp series	s 4000	\$54.00	ET585R	\$2.90	Ultrasonic receiver	TPV 6			lectronics		STATE OF THE PARTY	Mary Control
A STATE OF THE PARTY OF THE PAR		TPV 6	Control of the	ET585T ET586	\$2.90	Ultrasonic transmitter	TPV 6	5 \$10.95	HE102		Guitar phaser	JUN 81	1 \$25.00
ET474 ET475	\$2.90 Interface 60W amp	JAN 80 SEP 80	\$99.00	ET596		0 White noise generator	NOV 81		HE103		Transistor tester	MAY 81	\$9.40 1 \$7.50
ET475	\$6.90 AM tuner Set of three pot cores	JEY 80	\$29.50	ET598A	\$3.90	0 Touch switch	FEB 81		HE104 HE105		A.M. tuner Basic amplifier	MAY 81	1 \$9.50
ET476	\$7.90 Series 3000 amp 25W steri	reo	\$84.00	ET598B	\$3.50	0			HE106	\$3.90	F.M. radio microphone	MAY 81	\$8.50
		NOV 80		ET599A	\$3.50	0 Infra red remote control	MAY 80	0 \$76.00	HE107	\$3.90	D Electronic dice	JUN 81	\$5.95
ET477	\$7.90 Series 5000 pwr. amp mod	d 150W	\$63.50	ET599B	\$3.50	0			HE108		O Power supply	19972	\$11.95
1		JAN 81		ET599C ET599D	\$4.90		vpply		HE110		Unmistakabell		\$6.90
100000	Series 5000 power amp co	omplete kit	Ф299.00	E1599D	\$3.21	0 I.R. remote cntrl power su	MAY 80	1	HE111	of Links	Ohmeter		\$19.90 \$11.90
	Series 5000 pwr amp front Series 5000 pwr amp meta	nt panel	THE REAL PROPERTY.	ET603	\$4.90	00 Music synthesizer sequen	ncer		HE112 HE113	\$3.20	0 Micromixer 0 Water alarm		\$11.90 \$9.45
ET479NE	B\$13.90 Series 5000 preamp r		THE REAL PROPERTY.	Marie Land		The second second second	AUG 77	The state of the s	HE113 HE114		0 Water alarm 0 Digital counter	OCT 81	
	OCT 81		THE STATE OF	ET604		Metronome	SEP 77	7	HE115	\$2.90	0 Reaction timer	2016	
ET478MC	C \$4.90 Moving coil preamp (5000)) SEP 81		ET606	\$3.90	90 Electronic tuning fork	NOV 79		HE116	\$3.90	0		中心节息
ET478MM		5000)	\$18.50	ET607A ET607nf	\$2.90	90 Sound Effects generator	AUG 81 AUG 81		HE117	\$3.90	0 House and car alarm		\$16.90
Held Jack	Some Agent Library P. St.	SEP 81	THE PERSON NAMED IN	ET607nf ET631-2		90 60 Keyboard encoder	AUG 81 APR 77		HE121		0 Scratch and hiss filter		\$9.00
ET478SA	\$2.90 Series 5000 preamp switch	oct 81	THE PERSON NAMED IN	ET631-2 ET635		O Computer power supply	APR 81		HE122	01	Alien invadore		
ET478SB	3 \$1.90 Series 5000 preamp switch		The state of the s	ET636	\$19.9	30 7 slott s100 mother board	d MAY 80	0 \$89.50	HE123 HE126		0 Alien invaders 0 Nicad charger (P/Pac	ick ex \$9.95	5)
-14/05B	The Series South prearing swit	OCT 81	THE REAL PROPERTY.	ET638A	\$5.90	00 Eprom programmer	JUL 78	8	HE126 HE127	\$3.51	Siren	υA φσ.σί	\$3.90
ET478SC	\$1.90 Series 5000 preamp switch	ch brd		ET640	\$69.00	00 Memory mapped VDU		\$129.00	HE128	2000	Fog horn		30.00
		OCT 81	The same of the sa	ET644	\$69.00	00 Direct connect modem	OCT 82		HE129	\$3.50	0 Simple tuner		
ET478SD	D \$1.90 Series 5000 preamp switc	ch brd.		ET646A ET646B	\$3.75					The state of			
		OCT 81	\$12.90	ET646B ET647	\$3.75	Speech synthesizer	OCT 82		The state of the s				
ET479	\$3.50 Series 5000 bridging adap	ptor MAR 82	φ1Z.9U	ET647 ET649		Microbee light pen	AUG 83		The same				
图 是不		MAIN 02	AND DESCRIPTION OF THE PERSON	010					100/100		THE REAL PROPERTY.	September 1	

ECTRONC



ROD IRVING ELECTRONICS

425 High St., Northcote, Vic. 48-50 A'Beckett St., Melb., Vic. Phone (03) 489 8866, (03) 489 8131, Mail Order Hotline (03) 481 1436 Mail orders to P.O. Box 235 Northcote 3070 Vic.

Please address tax exempt, school, wholesale a RITRONICS WHOLESALE 1st floor 425 High St. Northcote 3070 (03) 489 70 (03) 489

Minimum P & P \$3.00. Errors & omissions excepted. Please address tax exempt, school, wholesale and dealer enquiries

1st floor 425 High St. Northcote 3070 (03) 489 7099 (03) 481 1923 Telex AA 38897

Electronic ballast for

Electronic ballast circuits
for fluorescent lamps have
recently become widely
used in Europe and a
similar trend is expected
in Australia in the future.
Siemens Ltd, a German
company, have supplied
us with a working
prototype module for
evalution. What advantage
does it have over the
conventional circuit and
how does it work?


Features of electronic ballasts are many and impressive. They offer instant tube starting, and absence of flicker due to the high operating frequency. Also they will drive more than one tube, produce no audible hum, and do not require power factor correction. Their efficiency is also greatly increased. Losses are up to 60% lower than the ballast losses of a conventional system, while the higher operating frequency increases light output of the fluorescent lamp by up to 15%. By using Siemens' new, more efficient "Lumilux" fluorescent tubes even further power savings can be obtained.

They do have one drawback, however, and that is a much higher initial cost when compared to conventional ballast/starter systems. For this reason this article is presented as one of general interest only. It should not be regarded as a constructional article, as the cost to hobbyists of mains-rated power FETs is currently too high to make the circuit an economic proposition.

Basically, the electronic system comprises a DC power supply derived by rectifying and filtering the AC mains waveform and a solid state high frequency oscillator driving the tubes via small chokes. High voltage Metal Oxide Semiconductor Field Effect Transistors, MOSFETs, are used as the oscillator drivers

Before delving into this electronic ballast circuitry, a discussion of the conventional ballast and starter circuit will enable us to compare the advantages and disadvantages of each system. Fig. 1

For instant starting, higher

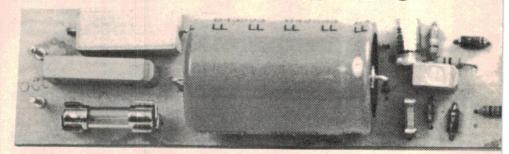

shows the circuit for a conventional fluorescent starter circuit. This basically consists of the ballast and starter. We shall ignore the capacitor connected across the mains for the present.


When power is first applied, a small current flows through the ballast, tube filaments, and starter. The starter is filled with an inert gas. This ionises and the resultant heating of the gas causes the bimetallic contact within the starter to close. A heavier current then flows through the tube filaments and ballast.

The tube filaments heat and begin to emit electrons. At the same time the starter cools and the bimetallic contact opens and interrupts the filament current. The resulting back EMF from the ballast generates a large peak voltage which ignites the tube. When the electric discharge is established in the fluorescent tube, it has a very low resistance and the ballast inductance is needed to limit the maximum current supplied to the tube.

In normal operation, the tube ignites and extinguishes during every mains half cycle so that it actually flashes at 100Hz. Note that the .005 μ F capacitor across the starter suppresses RF interference caused by the starter contact opening and the discharge within in the tube itself

The advantages of this system are simplicity, economy and ready availability. Now for the disadvantages: Firstly there is the starting characteristic. Typically at first turn on, the starter needs several attempts to ignite the tube resulting in a slow and flickering start. The second disadvantage occurs when the tube approaches the end of its life when lamp-end flicker becomes a problem. Thirdly, there is the need to replace the starter periodically since it has a limited life.

Other disadvantages concern the

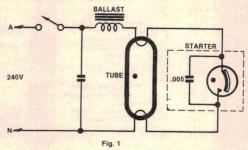

The conventional fluorescent starter circuit is simple and economical but also has disadvantages, including high power consumption.

choke. Due to iron core losses and the resistive (I²R) losses in the windings, power is consumed by the choke. Iron core losses are very small compared to these I²R losses and can be neglected. A typical low loss choke for a 40W fluorescent tube dissipates between 5 and 8W. This means that about 11% of a fluorescent light power bill is used in heating the choke.


Power factor


In general a 40W fluorescent tube is supplied with about 416mA and has 96V RMS across it. This same current passes through the choke but, due to its inductance, the current lags behind the voltage. At the active and neutral terminals the power factor (the cosine of the angle between the current and voltage) is typically 0.48. Now we can calculate the power dissipated by the combination of tube and choke. The formula is $E \times I \times P$ power factor. So we have $240V \times 0.416A \times 0.48 = 47.9W$. Since 40W is consumed in the tube, the choke dissipates the remaining 7.9W.

By connecting a capacitor across the active and neutral terminals the power factor is improved since the capacitor provides a current leading the voltage. If the capacitor were made large enough

fluorescent lamps

efficiency and greater light output

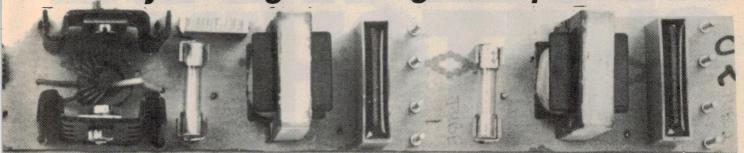

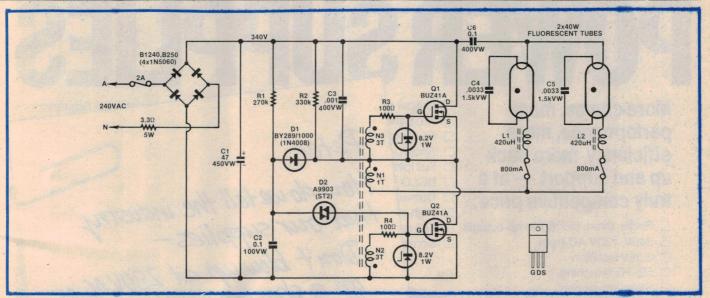

the lagging current of the inductor would be cancelled by the leading current of the capacitor. A $3.5\mu F$ capacitor improves the power factor to 0.85. Now the line current reduces to 235mA, and the phase between the current and voltage is much closer than without the capacitor.

Recalculating the power dissipated in the choke and tube, we obtain, $240V \times 0.235A \times 0.85 = 47.9W$. Again 40W is consumed in the tube and 7.9W dissipated in the choke, but the significant point is that the line current is reduced to 235mA.

This reduction in the line current may not at first appear important since after all the same power is used regardless of power factor. However, the line current contributes to I²R losses in the incoming supply lines. Consequently the lower the line current the lower these losses become. (And remember this is a square law.) These losses do not affect the consumer directly, although, the electricity

supply authorities are interested in keeping the power factor as close to unity as possible. This reduces losses within their alternators, transformers and supply lines.

By contrast, the electronic ballast appears to solve every problem inherent in the conventional ballast system but with a few advantages and disadvantages of its own. Because of the very high frequency of operation, the electronic ballast provides virtually instant starting and complete freedom from visible lamp flicker. The high operating frequency also allows the use of smaller and more efficient chokes which reduce circuit losses and allow a more compact lamp housing.

The very much higher operating frequency (around 120kHz) should also minimise strobing effects which, in the past, have prevented the use of fluorescent lights in some factory situations. Strobing effects can make rapidly rotating machinery appear to be sta-

tionary or rotating very slowly, and thus create a safety hazard. While strobing can still theoretically occur, even at 120kHz, the risk of it matching typical machine speeds would seem to be minimal.

The lack of audible hum will probably also mean that recording studios which previously would not use fluorescent lights can now install them and obtain energy savings.

Electronic starter circuit

Circuitry for the electronic ballast consists of a DC power supply, an oscillator comprising MOSFETs, Q1 and Q2 and associated components, and the current limiting chokes, L1 and L2, for the tubes. This circuit is for driving two 40W fluorescent tubes.

A 340V DC power supply is derived by full wave rectifying the mains voltage and filtering with the $47\mu\text{F}/450\text{VW}$ capacitor, C1. A 3.3 Ω resistor connected in series with the AC supply limits the

More choice, more performance, more efficiency, more back up and support — at a truly competitive price.

- ☐ Single, three, four & five rail outputs ☐ Fan ov
- ☐ 240V/120V AC input
- ☐ 3.5kV isolation
- ☐ 50KHz switching
- ☐ Standard models
- ☐ Custom design available

☐ Output o

Australia ☐ 5 year g

☐ Short ci ☐ Full loca

□ DCLO \$ ☐ Conver

☐ High ef

□ Comp

Peter,

How do we tell the industry

that our supplies - T Don't blow up at 280VAC or on a short circuit

data call Scientific

Don't self-destruct
Dou't need a fan over 25°C. That our specs are real and

our supplies don't look like

Kevin



6 Holloway Drive, Bayswater,

Victoria, 3153 Tel. (03) 762 5777 Telex AA 36308

Scientific Electronics

MADE IN AUSTRALIA Distributors: S.A., Graphic Electronic Industries 42 6655. W.A., W.J. Moncrieff Pty. Ltd. 325 5722

Electronic ballast for fluorescent lamps

surge current through the diodes when power is first switched on.

At first switch on, C2 begins to charge via R1. When the voltage across C2 reaches about 32V (after about 3ms), Diac D2 breaks down and conducts current from C2 into the gate of Q2. Q2 then turns on and generates a current pulse through the N1 coil of the transformer, L1 and L2, the heater windings of the tubes, C4 and C5, and finally C6.

Back EMF

Once C2 is discharged, gate current no longer flows and Q2 turns off. L1 and L2 now produce a high voltage back EMF due to the interruption of current flow. Provided the heaters are sufficiently warm to support continuous ionisation, the tubes will ignite. If not then the cycle will begin again to further raise the heater temperature. Capacitor C2 charges and dumps current into the gate of Q2 which again turns on, pulsing current through the tube heaters and L1 and L2.

This process continues until the tubes light. The resultant heavier current flowing through N1 of the transformer induces voltages in both N2 and N3 windings sufficient to trigger the gates of Q2 and Q1 respectively. N2 and N3 are connected out of phase and the negative voltage from N2 to the gate of Q2 switches Q2 off. The positive voltage from N3 switches Q1 on. Current now flows in the opposite direction through C6, the tubes, L1 and L2, the coil N1 and MOSFET Q1. Capacitor C6 now begins to discharge.

This reversed current flow through N1 induces positive gate voltage at N2, turning Q2 on again. The negative gate voltage at N3 turns Q1 off. C6 now begins to charge since the current through N1 is once again reversed.

High frequency oscillator

The circuit now operates as a high frequency 120kHz oscillator with L1, L2 and C4 and C5 controlling the free running frequency. L1 and L2 also are used to limit the current supplied to each fluorescent tube. Each time Q2 is on, C2 is discharged via diode D1 so that the Diac, D2, is kept from firing.

The zener diodes between the gate and source of each MOSFET, Q1 and Q2, limit the maximum Vgs voltage while the 100Ω resistor in series with each transformer winding limits the zener current

If the tubes are removed from the circuit, R2 and C3 are used as the load for Q2. This keeps the circuit operating with D2 triggering Q2 and Q1 remaining

off. The circuit is ready to start the tubes should the power be on while the tubes are installed.

Note that the chokes are quite small. These are iron cored with a 2.5mm air gap which prevents the core saturating. A 10mm diameter ferrite toroid is used for the transformer core to support the N1, N2 and N3 windings. The MOSFETs used are SIPMOS (Siemens Power MOS) BUZ41A, and these are mounted on small heatsinks to aid heat dissipation.

Performance of the electronic ballast is quite impressive. The instant start of the fluorescent tube and the lack of flicker are immediately obvious. When power is switched off, the brightness of the tube gradually dims until it extinguishes. This is due to storage in the DC power supply

Some of the efficiency can be credited to the slightly increased light output from a fluorescent tube when operated at a high frequency. Power savings are also had by the use of the small chokes. These are low loss due to the large wire diameter and small number of turns around a small core. They can be small and still provide the necessary current limiting since operation is at a high frequency.

The high frequency of operation can

cause problems with electromagnetic interference (EMI). We made comparisons of the interference caused to medium and shortwave radio reception by electronic and conventionally ballasted fluorescent lamps in the near vicinity to a receiver. While not rigorous, these tests showed that the levels of radiated interference were comparable.

Current waveform

A related problem is the shape of the current waveform for the electronic ballast circuit. While the electronic ballast does not require a power factor correction capacitor as does the conventional ballast there is still a problem for the energy supply authorities in that the rectifier uses a capacitive-input filter. This means that the current waveform is in the form of a short duration pulse at the peak of each mains half-cycle. The result is distortion of the mains waveform and the generation of unwanted harmonics.

For commercial users though, the large scale use of electronic ballasts will lead to large savings in annual office and factory lighting bills.

Anyone requiring further information should direct their enquiries to Siemens Ltd, 383 Pacific Highway, Artarmon, NSW, 2064, or 544 Church St, Richmond, Victoria, 3121.



ESA0040A



All new, All mode, All powerful . . . **Computer Aided Transceiver**

Wow! What a transceiver. Everything you could EVER want... and then some! Even before its release, Yaesu have over 5000 on back order: that's just from the brochure!

It's the absolute latest state-of-the-art in design - in fact, its CAD/CAM (computer aided design, computer aided manufacture) ensures unbelievable standards of reliability.

Features:

LOOK AT THESE

FEATURES:

STOCKS DUE IN MID TO LATE DECENIZER BUT WILL THERE BE BUT WILL THERE BE ANY LEFT FOR YOU?

All mode-including FM with no optional extras All HF bands from 160 to 10m including WARC

General Coverage Receive - 500 to 29.999MHz Computer Aided - use with your micro for external control

Full 100W PEP/DC at 100% duty cycle

Tiny 238 x 93 x 238mm (smaller than some 2m rigs!)

Cat D-2940 All this for only

Neat! Fits under your FT 757 and you'd hardly notice it was there! Designed just for the FT757. makes your base station really look the part. 240V input. Cat D-2941

FC 757 AT Antenna Coupler

The very latest auto coupler for your 757. Great for mobile & contest use - you can almost work into a piece of wet string! Cat D-2942

FIF 232 C RS-232C Interface

Run your transceiver via your micro. Allows external control of VFO, memory functions, etc. 4800 Baud - so it's fast! Cat D-2943

> Due in stock next month!

Before buying elsewhere check the Dick Smith 'Invisible Extras

We honour Yaesu's 12 month guarantee: beware of others who may only offer you a 90 day warranty!

We have the largest service centre to back that guarantee. If anything does go wrong with your Yaesu, we can fix it fastest!

Dick Smith Electronics: Australia's largest supplier and Yaesu factory approved distributor and service centre.

Dick Smith Electronics have over 40 stores throughout Australia (with more to come!) plus over 200 approved re-sellers. You're never far from friendly help and service!

lome Brew' UHF Transceivei

Remember the good old days' of amateur radio? When an amateur built his own gear and was so proud of it! Sadly those days passed! With incredible advances in technology, it became economically and technically impossible to compete with commercially built equipment. NOW home brewing is here again! And what's more with the all new Dick Smith UHF Explorer, you'll end up with a transceiver less than the cost of a commercial unit—and not just as goodbetter! YES! A completely up-to-the-minute design featuring obase locked-loop frequency synthesis. featuring phase locked-loop frequency synthesis



Cat K-6300

SPECIFICATIONS: Freq. Cov.

No. of Channels Mode of Operation Supply

13.8v DC. Receiver 340mA with full audio output and all options. Transmitter 2A more (5 watt output). (5 watt output).
Dual Conversion Superhet
0.4uV for 20dB quieting
+/-7.5kHz - 6dB
+/-15kHz - 60dB
Better than 80dB

438.025 - 439.000MHz ir 25kHz steps.

Receiver Sensitivity Selectivity

Adj. Chan. Reject Transmitter Power Output

5W (typical) +/-5kHz Deviation Spurious Emissions Better than -60dB

OPTIONS AVAILABLE

Upgrade Kit (Cat K-6302) (Repenter, Simeter, additional xtal filter & new front

ONLY \$24.50

UHF Antenna

Just for your UHF transceiver. Includes deluxe gutter gripper base, UHF co-ax and whip with cutting details. suitable for UHF CB.

Cat D-4014 \$

NEW 70cmH/held

YAESU

Superb hand-held transceiver for those people constantly on the go! Covers full 438-439MHz band in 25kHz steps, with simplex AND standard 5MHz repeater split.

Look at these features:

● 10 memories ● Low 720g weight Switchable 200mW/ 1W output.NiCad battery (and charger!) and rubber duckie whip are included! Cat D-2930

and it's only





THAT'S THE DIRECTLY IMPORTED

DICK SMITH SS105S HF TRANSCEIVER

Last chance for a real bargain! All band HF transceiver now reduced to clear - and look at the incredible specs. Where else could you get a transceiver of this type for under \$500? And with optional pcb, it will even do FM (great for 10m and for transverting!). Quick - before they all disappear!

WAS \$549 AMAZING VALUE ONLY

ACCESSORIES FOR THE SS105S

Noise Blanker

That really works! Minimise most types of pulse noise. Highly recommended for maximum transceiver capability. \$9095 Cat D-2901

FM receive IF unit
FM receive circuit to convert 9MHz to 455kHz and amplify and detect signals; equipped with a built-in squelch circuit. \$5995 Cat D-2902

FM transmit IF unit

Build your own

Phone Patch

IF circuit for FM transmit, consisting of \$3495 a modulation circuit & IF amplifier. Cat D-2903

25 kHz monitor

Plug-in pcb to g... accurate calibration. \$2.495 Plug-in pcb to give 25kHz for

100W Linear Amp

100W Linear Amplifier. when you've got that big ticket! Work the world - and more (more?) Cat D-2905 \$245

Phone patching is legal from November 1st! Build your own phone patch and save a fortune . . . very simple kit, suits most transceivers. Compare our price from Compare our price from built-up units!

Cat K-3054

Not Telecom Permitted

WHY NOT USE



Dick Smith Ham Shacks are located in the Dick Smith Stores listed below. You'll find a licensed amateur at each Shack


below. You'll find a licensed amateur at each Shack.

Sydney 125 York St'267 9111 ● Sydney 6 Bridge St 27 5051 ● Gore Hill 162 Pacific Hwy 439 5311 ● North Ryde Lane Cove & Waterloo Rds 88 3855 ● Gosford 315 Mann St 25 0235 ● Melbourne 399 Lonsdale St 67 9834 ● Richmond Bridge Rd 428 1614 ● Springvale Springvale & Dandenong Rds 547 0522 ● Brisbane: Buranda 166 Logan Rd 391 6233 ● Townsville Ingham Rd & Cowley St West End 72 5722 ● Toowoomba Bowen & Ruthven Sts 38 4300 ● Adelaide Wright & Market Sts 212 1962 ● Perth William St & Robinson Ave 328 6944 ● Cannington Wharf St & Albany Hwy 451 8666 ● Hobart 25 Barrack St 31 0800 ●

bankcard

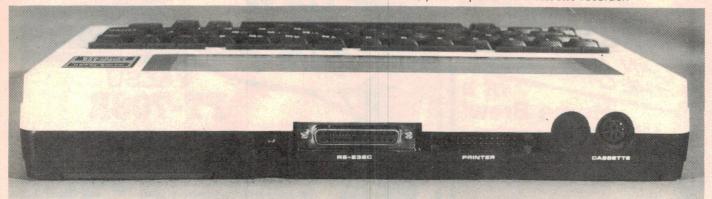DICK SMITH Electronics See Page 120 for full address details





TANDY MODEL 100 PORTABLE COMPUTER First of the new generation

The TRS-80 Model 100 is one of a new breed of portable computers — significant not so much for what they offer (although that is considerable) as for the possibilities they foreshadow.

by PETER VERNON

Not many years ago Isaac Asimov wrote science fiction stories about portable "information processors" which were all things to all users. While the advent of the wristwatch computer is still some time away, portables such as the Model 100 are pointing the way.

Not much bigger than a slim encyclopaedia volume (300 x 215 x 40mm W x D x H) and weighing 1.7kg, the Model 100 comes with a full-size typewriter style keyboard and a 40-column by 8-line liquid crystal display. Software is built-in, with a powerful Microsoft Basic interpreter, word processing, appointments file, communications and address filing programs. Four penlight batteries provide sufficient power for around 20 hours of operation, with a red LED indicator on the top right of the console which lights to show that the batteries should be changed. Alternatively, when the Model 100 is not used "on the go" power can be supplied by a 6VDC plugpack adapter.

The 56-key keyboard is easy to use thanks to its size and clearly labelled black and white keytops. While it is flat,

rather than stepped (with the rows of keys on different levels), it is both comfortable and compact, a rare combination.


Above the main keyboard are 16 smaller keys, comprising eight programmable function keys, four special purpose word processing functions and four cursor control keys.

Above these is the 8-line by 40 character LCD screen, capable of displaying both upper and lower case alphanumeric characters plus graphics. A control on the right side of the console adjusts the display for optimum contrast from a specific viewing angle, although overhead lighting can still cause problems in this respect. There is an advantage however — with the display adjusted for best viewing by a user seated in front of the machine, so no one can read over your shoulder.

The 40 column display is more readable than most LCDs because of the large, fully-formed characters. It also

TRS-80 Model 100 Basic statements and functions

ABS, ASC, ATN, BEEP, CALL, CDBL, CHR\$, CINT, CLEAR, CLOAD, CLOAD?, CLOADM, CLS, CLOSE, CONT, COS, CSAVE, CSAVEM, CSNG, CSRLIN, DATA, DATE\$, DAY\$, DEFDBL, DEFINT, DEFSNG, DEFSTR, DIM, EDIT, END, EOF, ERL, ERR, ERROR, EXP, FIX, FOR. . .NEXT, FRE, GOSUB, GOTO, HIMEN, IF. . .THEN, INKEY\$, INP, INPUT, INPUT#, INPUT\$, INSTR, INT, IPL, KEY, KEY LIST, KEY ON; OFF, KEY STOP, KILL, LCOPY, LEFT\$, LEN, LET, LINE, LINE INPUT, LIST, LLIST, LOAD, LOADM, LPOS, LPRINT, LPRINT USING, LOG, MAXFILES, MENU, MERGE, MID\$, MID\$=, MOTOR, NAME, NEW, ON ERROR GOTO, ON KEY GOSUB, ON TIME\$ GOSUB, ON . . .GOTO, ON . .GOSUB, OPEN, OUT, PEEK, POKE, POWER, POS, POWER, CONT, POWER OFF, PRESET, PRINT, PRINT@, PRINT#, PRINT.USING, PSET, RESUME, READ, REM, RESTORE, RESUME, RETURN, RIGHT\$, RND, RUN, RUNM, SAVE, SAVEM, SCREEN, SGN, SIN, SOUND, SPACE\$, SQR, STOP, STR\$, STRING\$, TAB, TAN, TIME\$, TIME ON; OFF; STOP, VAL, VARPTR.

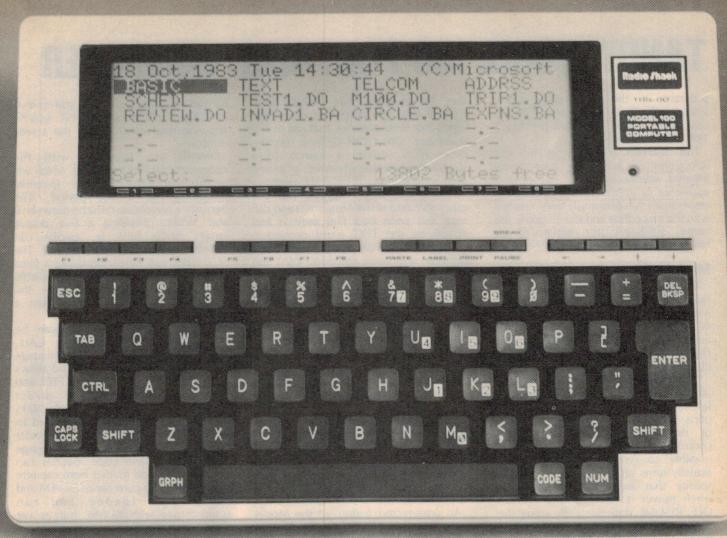

Tandy's Model 100 portable computer comes with five built-in programs and the capacity to store many more files.

seems to suffer less from "access flicker" than the 80 column displays now becoming available. Naturally it is not as fast as a video display, and in fact typing at moderate speed can outrun the display (although not the keyboard buffer). It is a strange experience at first to finish typing a line and then watch as the letters appear one by one across the screen.

The Model 100 has an array of graphics symbols, Greek characters and special mathematical and typesetting symbols which can be accessed from the keyboard using the GRPH key in conjunction with the standard keys. In addition the full ASCII character set and control codes to be produced from the keyboard using the CODE key, and for those who prefer a numeric keypad a locking NUM key converts letter keys on the right side of the keyboard to allow fast entry of numeric data.

On the right side of the Model 100 console is a power switch, the display control mentioned above and an input for 6V DC from a plugpack adapter. A socket for the connection of a bar-code scanner is on the left, while the rear has a reset button, RS232C connector, a Centronics standard parallel printer

connection and a connection for a cassette recorder. The serial interface is a standard 25-pin D-type connector while the printer port connection consists of two rows of pins on 2.54mm centres and requires a special purpose printer cable. Underneath the console is a plastic cover which conceals a 40-pin expansion connector and a socket for additional ROM, the battery compartment and a power switch for the separate Nicad batteries which power the memory of the Model 100. Normally this switch is in the On position, even when changing the main batteries. Switching it off will clear the entire memory.

Processor and memory

The Model 100 is based on the 80C85, a CMOS (low power) version of the Intel 8085. Except for differences in interrupt handling, the machine language for this processor is identical to that of the 8080 so additional software should quickly become available. Clock speed is 2.4MHz, giving the Model 100 a respectable performance, and memory can be expanded in increments of 8K to a maximum of 32K available to the programmer.

To conserve the batteries an automatic power-down feature will switch the computer off after 10 minutes without a keyboard entry, unless a program is running. Ten minutes is the default — from Basic the period can be set anywhere from one minute to around 22 minutes.

When first switched on, the Model 100 displays a menu of built-in software and existing user files (if any), the date and time and the amount of memory remaining. Files may be of one of three types, identified by two letter extensions following the six character file name. Basic programs are suffixed with a .BA. data and word processor files with .DO and machine language programs with .CO. A particular file is activated by moving the cursor over the file name and pressing Enter, or by typing the name of the required file in response to a prompt on the bottom line of the menu display.

If the user has previously stored a file in memory two options are available. To activate a Basic program, for example, the user can activate Basic and load the file in the normal way, or move the cursor over the file name of the program and press Enter. Initiating a Basic

TANDY MODEL 100 PORTABLE COMPUTER

program in this way automatically activates the Basic interpreter, while if a data file is selected the word processor. TEXT, will be activated.

The address filing program and appointments scheduler cannot be entered unless a file of names and addresses or appointments information respectively has previously been created with the text editor and stored under the name ADRS.DO (for addresses) or NOTE.DO (for appointments).

Model 100 Basic

The Basic of the Model 100 has some similarities to that of other TRS-80 machines - not surprising, since all are from the Microsoft stable – but includes additional capabilities in keeping with the special requirements of the integrated software system.

Model 100 Basic is especially strong on interrupt handling and input/output, with full support for the serial and parallel ports, function keys and clock/calendar of the portable. Other statements control the power supply, and it is possible to write a program which actually turns off the computer, and to specify that execution will continue when power is restored (the POWER OFF, RESUME statement). By using the statement IPL a program can also be made to run automatically when the computer is switched on.

The function keys of the Model 100 are supported by statements which allow each programmable key to be associated with a string of up to 15 characters, as in:

KEY1,"?DATE\$"+CHR\$(13)

Once this statement has been executed, pressing function key F1 is equivalent to typing the definition and will display the current date. The question mark is equivalent to the PRINT statement and CHR\$(13) is the carriage return character which activates the definition. The statement KEY LIST will display the current definitions of all eight function keys.

The function keys can also be used to create a processor interrupt and re-direct the flow of program control. Key interrupts are enabled by the statement KEY ON and associated with particular subroutines by the ON KEY GOSUB statement, which is followed by up to eight line numbers. Function key F1 will direct the program to the first line number, F2 to the second line number and so on.

The clock and communications ports can use interrupts in the same way, so

that, for example, ON TIME\$="time" GOSUB (line) will jump to a subroutine when the time matches that set in the statement. ON COM GOSUB, on the other hand, causes a branch to a specified subroutine whenever incoming data is detected at the RS232C port.

Basic is also fully integrated with the other software of the Model 100 and can read and write data files created and edited by the TEXT word processor. Input and output can also be re-directed between a cassette recorder, RAM and the communications port or output sent to the parallel printer under program control. The default for I/O operations is the battery-backed up RAM of the machine, so that, for example, SAVE "Prog1" will store a Basic program in memory, adding its name to the menu which appears on start-up. SAVE"CAS:Prog1" will store a program on the external cassette recorder, and SAVE"LPT:Prog1" will send the program to the parallel printer. Other options are LCD (for the screen) and COM (send a program via the RS232C communications port).

At any time the Basic statement MENU will return the user to the initial menu of options shown on power up.

An unexpected feature of the Model 100 is its support for graphics and sound effects. The LCD screen can be considered as a matrix of 240 x 64 points and individual pixels turned on and off with the statements PSET and PRESET. The LINE statement is also available to allow lines to be drawn between specified points, or with the options B and F, to draw boxes on a specified diagonal with an optional fill. In addition to graphics there is an array of screen

formatting and PRINT statements including PRINT@ and PRINT USING. allowing total control over the screen display.

Sounds are specified with the statement SOUND freq, time, which will produce a tone of the specified frequency for a set period. The frequency parameter must be between 0 and 16383, providing a five octave range, while time is specified in increments of 1/50th of a second. The BEEP statement simply produces a fixed tone, while SOUND ON/OFF is available to activate a tone to indicate the progress of program loading from a cassette recorder.

Machine language routines can be executed with the statement CALL, which jumps to a machine language routine at a specified address and allows two parameters to be passed. PEEK and POKE are available for direct manipulation of the Model 100's memory, and VARPTR can be used to locate the address of a particular variable for use with machine language programs. Machine code routines can also be saved and loaded from cassette or RAM with the commands SAVEM and LOADM, or loaded and run automatically with RUNM, but as yet there is no monitor program to allow easy entry of hexadecimal codes.

Error-trapping is provided with the statements ERL (returns the number of a line in which an error appears), ERR (returns the error code), ON ERROR GOTO and ERROR (which allows an error to be simulated when testing a program).

Program editing is not as straightforward as in previous TRS-80

TRS-80 Model 100 specifications

Processor 80C85

Up to 32K in 8K increments

Cassette recorder Bar code scanner Expansion interface


56 keys, typewriter style Liquid crystal

40 x 8 lines text 240 x 64 graphics Single voice

Five octave range Microsoft Basic

Text editor Communications Address filing Schedule filing

Documentation Excellent

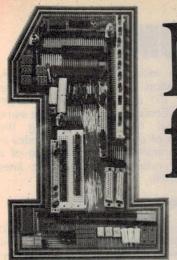

No.


SOME AT COST! SOME BELOW COST! While stocks last



6 Volt Rechargeable 1 Ampere Hour lead acid gel batteries


10 way bit Switches 3 AT COST



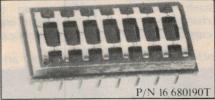

16 Pin Programmable header

> cents each

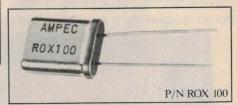

10 MHZ Crystals BELOW COST


Mail order welcome. Add 10% for postage.

Sales tax not included

The Ampec Trade Shop

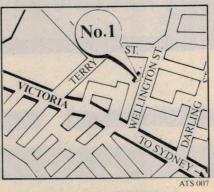No. 1 Wellington Street, Rozelle, N.S.W. 2039 PHONE: 818 1166





95

TANDY MODEL 100 PORTABLE COMPUTER

computers. First of all, typing EDIT (line number) puts the user in the word processing mode, with the specified line appearing at the top of the screen. Editing is then performed by using the word processing functions to insert and delete characters etc. Pressing ENTER however will not return the user to Basic but simply inserts a carriage return in the line being edited. To return to Basic it is necessary to press F8, the function key normally defined as "menu". If the edited line is now acceptable to Basic all is well and programming can continue. If the line is still in error the message "TEXT ILL-FORMED" will be displayed.

Unless otherwise specified arithmetic on the Model 100 is double precision with values ranging from 10⁻⁶⁴ to 10⁺⁶² and 14 significant digits. Single precision (six significant digits) and integer arithmetic can also be specified.

Word processing with the Model 100

The text editor built into the Model 100 is one of the machine's best features. While 40 columns by eight lines of text may seem to be a limited display, in practice it works quite well on a paragraph by paragraph basis while the cursor control keys allow speedy access to other parts of a large document. Normally the cursor control keys move one character space at a time, but can be used in conjunction with the SHIFT keys to move word by word and to the top or bottom of a particular screen of text or with the Control key to move to the

beginning or end of a line, or vertically to the beginning or end of an entire file.

The Backspace key by itself will delete the character to the left of the cursor and DEL (Shift-BKSP) deletes the character under the cursor. All keys (including the cursor controls) automatically repeat after being held down for a fraction of a second.

Large alterations of text are assisted by the "cut and paste" features of the editor. To move a section of text from one location to another, for example, the procedure is to mark the start of the text with the SELECT key (F7) and then move the cursor to the end of the passage to be selected. Text between the selected start and the cursor position is displayed in inverse to verify the operation. After a section of text has been marked it can be copied (F5) or transferred (F6) into a "paste buffer" and reinserted in the text at any location by moving the cursor and pressing the function key labelled "PASTE". The difference between a copy and a transfer (called CUT in the manual) is that COPY leaves the original text undisturbed while CUT deletes the originally selected text from the document. Text from the paste buffer can be used repeatedly throughout a document until it is overwritten by a subsequent CUT or COPY operation.

Also available is the FIND command, activated by pressing F1, which prompts for a text string and searches the file for each occurrence of that group of characters. As with all function and cursor control keys the operation can

also be initiated with a Control-key combination, a useful feature when the Model 100 is connected to a larger system. Control keys also activate some additional functions, allowing the insertion of printer command codes in text (Control-P) and the addition of a carriage return/linefeed to text lines (Control-M).

Limited print formats

The one limitation of the Model 100 text editor is the narrow range of print formatting commands. One function key, labelled PRINT, serves either to print the contents of the screen on a parallel printer or (used with SHIFT) prints the entire file. Screens are printed exactly as they appear, in eight lines of 40 characters each while SHIFT/PRINT first prompts for a line length and formats the text accordingly. There is no way of printing part of a file which crosses two screens — printing is all or nothing.

Text files can however take advantage of I/O redirection and can be saved and loaded from RAM or a cassette recorder or sent via the RS232C port to a larger system, using either a modem or a direct serial link. Once transferred to a large computer the full range of print formatting commands of that system could of course be used on the file.

Since Model 100 Basic can also read and write data files it would also be possible to create text formatting programs in Basic and overcome the limitations of this aspect of TEXT.

The 40 character by 8 line LCD screen displays large, clearly readable upper and lower case characters.

The Basic of the Model 100 shows some similarities to that of other TRS-80 machines - not surprising, since both are from the Microsoft stable. That of the Model 100 however has additional capabilities in keeping with the special requirements of a portable system.



As well as word processing and program editing, TEXT must be used to create ADRS.DO and NOTE.DO files required by the address list and scheduling programs.

Using the address filing program (called ADDRSS) requires the creation of a data file with the name ADRS.DO with the text editor. Once the file is created it can be searched with the commands Find and Lfnd (F1 and F5). Find searches the entire file for a match to the string specified and displays the result.

ADDRSS is a rudimentary program. The data file is searched from the position of the cursor to the end of the file in its entirety rather than field by field, so that for example, "Mr Jones" and "Jones Street" both match the string "Jones". Capitalisation does not seem to matter—"smith" and "SMITH" are reported as matching strings—but this is unimportant in this application.

The SCHEDL program works in exactly the same way as the address organiser, using a file called NOTE-DO and the command Find and Lfnd to search for a specified string. In spite of the name the program does not take advantage of the clock/calendar feature of the Model 100 and while useful as a general-purpose filing program will be disappointing to those expecting an appointments manager or reminders of important dates. Any competent programmer could do a better job, given the power and features of the system and no doubt many will.

Communications

The Model 100 communications program, TELCOM is both versatile and easy to use. TELCOM is entered from the menu and operates in one of two modes; an "entry" level which allows communications parameters to be specified, and the terminal mode itself, activated by pressing F4.

The entry mode allows the selection of data transmission rate (nine standard baud rates from 75 to 19,200bps), word length (6, 7 or 8 bits), parity, number of stop bits and handshaking status. The default mode is 300 baud, 7 bits, no parity and one stop bit, as used by the majority of bulletin boards and dial-up services.

In the terminal mode operations are selected by pressing various function keys. Full or half-duplex operation can be selected and data displayed as it is received or stored in a RAM file for later use. Optionally, incoming data can be echoed to a parallel printer, and files can also be transferred to the host system. Some users of this feature have reported problems caused by the fact that the Model 100 does not transmit a line feed character with a carriage return. Many bulletin boards expect each line of data

to be terminated by a line feed/carriage return pair, and special formatting programs would be required to use the Model 100 successfully with such services.

This difficulty aside, TELCOM makes the Model 100 a simple, compact terminal for communication via a modem or an RS232C link. Apart from use as a portable computer terminal the communications capability also makes the machine ideal for transferring data between otherwise incompatible systems and other users have discovered the advantage of entering data in the field and later transferring it to a larger computer for storage, formatting, and printing.

In conclusion

Who will use the Model 100? First of all, it must be said that for mathematical calculations and other applications where the large text display and full-sized keyboard is not required the Sharp PC-1500 or similar Tandy pocket computers are quite sufficient. Using the Model 100 solely for these applications would represent "overkill".


Where the Model 100 really shines is in text processing and communications. The full keyboard, 40 character by eight line display and integrated software really come into their own here, while the availability of a terminal mode makes

the Model 100 an ideal mobile adjunct to a larger computer system.

At the moment however the features of the Model 100 are under-utilised by the existing software. The TIME and DATE functions could be put to much more extensive use and print formatting is limited, but in spite of this the Model 100 may be the wave of the future. Programs from Tandy and independent software suppliers will become available as the Model 100 comes into wider use but already the potential is evident. Tandy has gone a long way towards translating the writer's dream into reality.

Prices and expansion

Compared to "pocket computers" the Model 100 is an expensive machine. Considering the wealth of features though, and comparing the price with portables such as the Epson HX-20 and the NEC PC-8201 gives a truer perspective on the price. A Model 100 portable computer with 8K of RAM costs \$1099. Memory expansion is relatively expensive at \$169.95 per additional 8K of RAM, but a second version with 24K of RAM already installed is priced at \$1399. Adding the memory to bring the Model 100 up to its full 32K means that the machine reviewed here costs \$1568.95. A parallel printer cable to suit costs \$24.95.

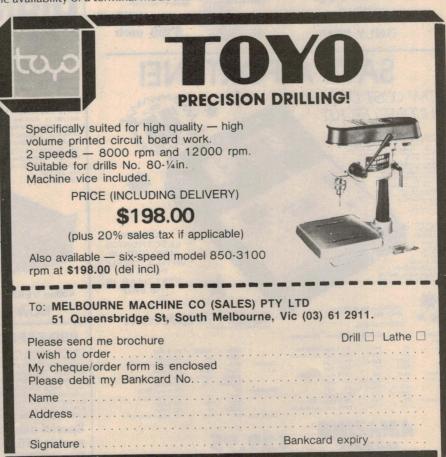

UNBEATABLE KIT VALUE Jaycar & Electronic Agencies

"Blueprint" 5000 preamp | Lyrebird Piano Kit



- FUNCTIONS
- MOVING COIL INPUT
 MOVING MAGNET (DYNAMIC)

- ONOVING MAGNET (D'CART)

 INPUTS (2 OFF)

 TUNER INPUT

 AUX INPUTS (2 OFF)

 TAPE INPUTS (2 OFF)

 TAPE OUTPUTS (2 OFF)

 TAPE OUTPUTS (2 OFF)

 AUDIT CALIBRATION
 OSCILLATOR

 LED AVERAGE (VUI) & P.

 LED A
- OLED AVERAGE (VU) & PEAK

 LEVEL METERS -48dB TO +9dB

FEATURES •EXTREMELY CLOSE TRACKING TO RIAA PHONO EQ.

- TO RIAA PHONO EO.

 GOLD PLATED CONNECTORS
 ON ALL INPUTS
 ON ALL INPUTS
 ENGLISH 'LORLIN' LOW NOISE
 SELECTOR SWITCHES
 LOW NOISE 1% 'SOppom BETAL
 FILM RESISTORS USED
 TINNED FIBREGLASS PCB's
 LOW CAPACITANCE SCREENED
 CABLE USED THROUGHOUT
 OUALITY LC SOCKETS

OUALITY I.C. SOCKETS

SPECIAL REAR PANEL

MULTICOLOURED RECTANGULAR LEDS USED

5000 POWER 5000 SERIES GRAPHIC



BLACK MONOLITH

unbeatable value **ONLY \$319**



Cat. KE4204

\$199 each

2%:5 digit 2%:5 digit 2%:5 digit 1A/250V 2%:5 digit 4%:5 digit 7%:5 digit 1%:1 digit 260V 1%:1 digit r.m.s. 1%:1 digit 1%:1 digit 1%:1 digit 1%:1 digit 260V r.m.s.

SAVE A FORTUNE



DP2010 kit Cat. KJ7010 ONLY \$45 SPECIFICATIONS

Resolution Accuracy Protection 1%:1 digit 500V for 1%:1 digit one minu 1%:1 digit 1%:1 digit 1%:1 digit 1A/250V 1%:1 digit 3%:1 digit 1mV 10mV 100mV 1V 1uA 10uA 100uA 1mA 1mV 500V for

> AMAZING VALUE

GREAT NEW FEATURES!!

- FREE! A stand flike the one illustrated but not exactly the same). Worth around \$50 but yours at no extra charge with each 73 or 88 note kit.

- FREE! A soldering iron (worth around \$19). Yours to keep to give years of faithful service after you have completed your Lyrebird. (88 note only)

- FREE! A 200g roll of solder. You will need some to build the Lyrebird but there, will be plenty left over for other projects. (73 & 88 note versions).

- FREE! Quality IC sockets provided in both kits.

REF: EA 11/81-1/82

VERSION \$589



REMEMBER!! THE LYREBIRD OUTPERFORMS READY BUILT PIANOS COSTING UP TO THOUSANDS OF DOLLARS MORE, WHY PAY MORE WHEN YOUR CONSTRUCTION KNOWLEDGE CAN SAVE YOU A FORTUNE?



The stand that we provide for the piano kit is not the same as the one shown in the illustration.

88 NOTE VERSION \$589 73 NOTE VERSION \$475



Musicolor IV

KE3025 \$89.90

JAYCAR KITS ARE THE BEST AND COST NO MORE

The Digital Delay Line is designed to produce a huge variety of electronic effects. It works very well but the amazing thing is the low low price! The effects depend on the time delay selected and some of those included are: Phasing, Flanging, Chorous, ADT (Automatic Double Tracking), Echo, and Vibrato. The delay time can be varied form 0.32ms to 1.6 seconds! Because the signal is stored in digital form there is, unlike analog systems, no degeneration of the signal with time and unlimited repetition is provided by use of the freeze

control.

All the controls mount directly upon PCB's to eliminate wiring and to further simplify construction the main board is 'plated-through' i.e. there are no wire links or link-through pins. The whole of the memory whether for the basic 400ms machine or the fully expanded 1.5 second model all fits on the main board. The cabinet which is free standing but also suitable for 19" rack mounting, is fully finished to a very high standard. The panel is deep blue whilst the cover is prayed with a durable black enamel. The kit is avail-able for only \$449 — compare that with inferior uints that can cost over \$2,000!

ONLY



BBD EFFECTS BOX

Fantastic low-cost instrument using the versatile MN3001 Bucket-Brigade Delay Line to achieve brilliant sonic effects. Now you can emulate the commercial rock groups with Phasing, Flanging' Reverb and Echo. The Jaycar kit includes all components INCLUDING IC sockets and the TU-04 box. (Not cut down but this is easily done). Jaycar has a specially built cabinet for this kit with all holes prepunched etc., at only \$10 extra but only if you buy the original kit from us. Available as a separate item for \$29.50. WHEN THE KIT IS PURCHASED WITH THE DE-LUXE CASE THE TU-04 CASE WILL NOT BE SUPPLIED.

Special cabinet to suit \$10.00 Cat. HB6445

COMPLETE KIT



Cat. KE1522 \$79.00

METAL TUNING

A scarce commodity now! Made in Australia, 2 gangs (OSC & RF) gangs can be paralled. (Total approx. 160pF). High quality with ¼" brass shaft. Measures 30 x 40 x 30mm. Worth well over \$4.00 Cat. RV-5740

ONLY \$1.00

QUALITY PHILIPS (?) 6" ROUND SPEAKER

It says Philips on the back but we're not sure: 8 ohm 4 watt. A bargain whether Philips or not. Cat. AE-8156

NORMALLY \$6.95 THIS MONTH ONLY \$3.95 SAVE \$3.00

DEFINITELY FOSTER **BRAND 8" SPEAKER**

This widerange unit is ideal for replacement purposes. Features large magnet. 8 ohm imp. Cat. AE-8146

NORMALLY \$4.95 THIS MONTH ONLY \$2.9 ONLY 100 UNITS IN STO

INLINE IGNITION SUPPRESSOR

ne ignition suppressor. Simply cut HT lead

and screw into place.

NORMALLY \$0.75 each
THIS MONTH \$0.40 each High quality unit made for the RAAF!! Cat. AE-8905

MATCHING SPARK PLUG ADAPTOR

Matching spark plug suppressor also made for the RAAF.

NORMALLY \$1.00
THIS MONTH \$0.50 each
Cat. AE-8909
QTY LIMITED

MAINS ROTARY SWITCH

WERE \$0.95 EACH NOW \$0.50 EACH

Quality Australian made SPDT Cat. SR-1280



QUALITY ENGLISH MADE ARCO TOGGLE SWITCH

GENUINE 250V @ 3A with uncommon (but Cat. SE-0660

NORMALLY \$1.95 each
THIS MONTH ONLY \$1.00 each

GLASS BREAKAGE DETECTOR

High quality unit can be configured either N.O. or N.C. Self adhesive pad attaches to glass. Only 30mm diameter! NORMALLY \$9.95 each THIS MONTH ONLY \$8.95 each

ALARM STICKERS NORMALLY \$1.00 each window in your house or car. Cat LE-8500 1.9 – \$1.00 each 10 + – \$0.75 each sh

Cat. LE-8500

1. 9 – \$1.00 each

10 + – \$0.75 each

Note: No specific alarm system is shown –

further confusing potential theft.

10" ELECTRIC **GUITAR SPEAKER**



Quality Pioneer brand check the specs! Check the price!!

HURRY

Impedance Voice Coil Dia. Power Rating

Response Total Flux

Flux Density

Net Weight

Resonant Frequency Sensitivity Response

8 ohm 1½ (inch) 60 WATT (RMS) 98 (dB/W) 80Hz - 7,000Hz 61,100 Maxwell 8,300 Gauss 1,540 gm

WARNING ELECTRONIC ALARM FITTED

8

CHANNEL

MIXER

KIT

LICEPETZ rysta Clock



- Very compact and reliable Self-starting one-second stepping motor has strong torque Powered by 1.5V AA battery that lasts for a year Supplied with two sets of hands, one short and one long ±15 second/month accuracy
- 56mm square, 15mm deep omplete with data sheet, instructions and wall hanger bracket.

low cost IC inserters AND **EXTRACTORS** Up until now these have cost a fortune!!

Features:

- CMOS SAFE conductive plastic
- Exclusive bent pin alignment guides in handle . 8 to 40 pins.
- Ground strap can be connected.
- One hand operation.

INSERTERS

Description 8 - 20 pin 22 pin 24 - 28 pin 36 - 40 pin Normally NOW Cat. No Model \$4.16 GIT820 TH1810 CIT22 CIT2428 CIT3640 TH1812 \$6.50 \$4.86 \$6.95 TH1814 \$6.26 \$8.95 TH1816 EXTRACTOR TH1818 ET480 \$2.95

Deceptively simple looking device. One piece metal construction. 8-40 pins

NOW \$2.06



115 VOLT COMPUTER FANS

> GREAT VALUE

4 95

We have made a scoop purchase of computer grade Box Fans.
They measure a standard 80 x 80 x 40mm. But there's a catch!
They are only available in 115V!
Great if you are making equipment for export to the USA — or
use 2 in series! No problem!
ONLY \$14.95

Ref: EA March/April 1983 This great 8 channel 'live' mixer is perfect for bands, churches, theatre groups, home

for bands, churches, theatre groups, home recording, disco etc.

Each input channel accepts either microphone (balanced) or line (1V) levels. Powerful equalisation foldback effects facilities are provided. The left and right master channels can drive balanced or unbalanced lines with 5 band "graphic" equalisation. Separate foldback and "effects" are provided.

The unit can be rack mounted or housed in a

The unit can be rack mounted or housed in a console chassis (which accommodates the power supply). Attractive wooden end-pieces finish the console to form a professional looking unit. si onal looking unit.
Complete 8 channel mixer

(19" fack mount) Cat. KJ6504 \$495.00 Console mount chassis, power supply and wooden end pieces

\$98.00 Cat. KJ6505 You end up with a \$1500+ unit for under \$600

WHAT'S UP DOC?

Are the "rabbit ear" antennas on the back of your portable TV broken? You know those ones that are telescopic and have ball-swivel joints. We have genuine 'HMV' factory spares that will fit other TV's

Apparently they are almost industry-standard components. Each unit comes with a short length of lug-terminated 300

We have a small job lot available at only \$7.95 each. ONLY 220 SETS AVAILABLE. \$695 Cat. AA 2005

\$7.95

Incorporating

ELECTRONIC AGENCIES

SHOWROOMS

117 YORK STREET - PHONE: (02) 264 6688 and (02) 267 1614 TELEX: 72293

CARLINGFORD GFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444 CONCORD

ARRAMATTA ROAD - PHONE: (02) 745 3077

HURSTVILLE 121 FOREST ROAD - PHONE: (02) 570 7000

NUMBER 1 FOR KITS

POST AND PACKING CHARGES
\$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20)
\$25 - \$49.99 (\$4.50) \$50 - \$99.99 (\$6.50)
\$100 - \$198 (\$8.00) Over \$199 (\$10)
"Free INSURANCE for Road & Registered Post over \$200"
All heavy or bulky items (over 20kg.) sent Comet Road Freight \$12.00 anywhere in Australia.

in Australia.
SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE
Mon — Fri 9am — 5.30pm: Sat — 9am — 12pm: Thurs night 8.30pm
SHOP HOURS SYDNEY
Mon — Fri 8.30am — 5,30pm. Sat — 8.30am — 12pm: Thurs night 8.30pm

MAIL ORDERS AND CORRESPONDENCE: BOX K-39 HAYMARKET, SYDNEY 2000



Making PGBs in small

Making printed circuit boards for your own designs or for projects described in this and other magazines can be very satisfying. With new techniques and products the process is simple, clean and efficient.

There are a number of methods available to the constructor who wishes to make his own printed circuit boards (PCBs) but this article will focus on the methods used at Electronics Australia to produce project prototypes. Except for the scale of production the techniques involved are essentially the same as those used in commercial electronics manufacture, using photographic processes.

Although the materials described here cost more than etch-resistant inks and paints, the higher cost can be justified by the advantages of the dry resist process. Artwork processed as a photographic film can be used repeatedly, producing consistent results with a minimum of mess and fuss. No special skills are required once the initial PCB pattern has been created, making the method ideal for small manufacturers and hobbyists.

After the design of a circuit has been finalised the first step in making a printed circuit board is to create the artwork representing the PCB pattern. For this purpose we use actual size adhesive tapes and IC pads, such as those made by Bishop Graphics and the Japanese Izumiya company. These are rubbed down in the required pattern on a sheet of transparent plastic to produce a positive image, with areas of copper represented by tapes over the clear plastic.

The next step is to transfer the circuit board image to film to create a permanent copy of the artwork. Artwork created with tapes and adhesive materials are not suitable for multiple use or permanent storage as the tapes tend to come adrift in time.

To create a film copy of the artwork, UV sensitive photographic material is used. When the taped copy is clamped together with a suitably-sized piece of 3M Reversal Film type 8007 and exposed to ultraviolet light a negative image is created, with areas of copper represented by clear film and areas of opaque, film representing those parts which must be etched clear of copper.

In researching this article we used a UV light box from Kalex. This professionally produced box uses four UV tubes and is

fitted with a slide-out drawer and shelving to permit exposures to be made on one of two levels to cater for the different properties of photosensitive films, copper-clad board and 3M "Scotchcal" materials.

An exposure time of 10 seconds is all that is required to transfer the artwork image to the sensitised film, although if in doubt it is best to over-expose rather than under-expose the material. Following developing in a chemical bath the film produces a high contrast negative ready for use in exposing a sensitised copper-clad board. Of course, before the image is developed, futher exposure to UV light can mar the image. For this reason the film must not be exposed to sunlight or fluorescent tubes, although a low-wattage incandescent lamp can be used in the work-room as dark-room conditions are not required. The black plastic bags used for shipping the sensitised films are ideal for temporary storage and transport of films between exposure and developing.

Once transferred to film the artwork can be usd to create as many printed circuit boards as are required. A special type of copper-clad board coated with UV light-sensitive etch resist is used here. Called "Riston" (trade name) board, this material is exposed to ultra-violet light through the negative produced in the previous stage. Again the Kalex light box can be used, although the optimum exposure time for the Riston board is slightly longer at around 90 seconds.

When treated with the developer, areas of the resist exposed to ultraviolet harden and become impervious to the effects of the etching chemicals while unexposed areas are not affected.

As supplied the Riston board is covered by a protective plastic film which should be left in place during exposure and removed before the board is developed. For best results the board should be left for around 15 minutes between exposure and developing to allow the chemical coating to stabilise.

A pool of developer sufficient to cover the board is all that is required (say about a dessertspoonful for an average board), although additional developer can be added during the process. Kalex supply their own brand, either in a concentrate ready-to-use 25% solution.

When developed the copper areas of the board take on a dark blue colour. This is the etch resist which will prevent these areas from being affected by the etchant solution. A properly exposed and developed board should have copper areas which are hard and resistant to scratches. If the exposed area is soft it is most likely that the exposure time was insufficient and there will be a loss of definition in the finished board. Over-exposure, on the other hand, will enlarge the PCB tracks and close up small hole patterns, leading to problems when the board is etched.

After treatment in the developer bath the board should be washed in running water to remove all traces of the developer. Etching is the next step. Any of the commonly available etchants can be used, including ferric chloride or ammonium persulphate, can be used here. Both are poisonous and corrosive, and in addition ferric chloride will discolour fabrics and other materials it contacts.

Etchants are usually sold in powder form and mixed as required. Plastic containers should be used for etching as the chemicals will attack metal. Between uses all solutions should be stored in clearly labelled bottles. Warming the solution or mixing the powder with hot water will reduce the etching time.

Commercially available etching tanks use racks to hold the boards and a pump to circulate the etchant to reduce the time taken for the etching process. Kalex make two models, one a full-featured version for mass production and the other a simple two-compartment tray with supports for PCBs. Vertical mounting in this model restricts the size of PCBs to approximately 15cm ×9.5cm, although boards up to 19cm square can be etched if they are laid flat in the tank.

For home and hobbyist use a plastic tray is perfectly adequate as long as it is sufficiently large to allow the full immersion of the required board.

After etching the board should be washed in clear running water to remove all traces of the etching solution and the hardened etch-resist removed with steel wool and methylated spirits. Once the bare copper is exposed the board can be trimmed to size and drilled, ready to form the basis of an electronic masterpiece!

quantities

by PETER VERNON



The Kalex UV light box

The Kalex UV light-box is intended for use in the commercial application of the PCB techniques described in the accompanying article. It has been designed to process 3M Scotchcal, 3M I.N.T. labelling materials, 3M exposure film and Riston 3000 boards.

Four Philips T1 03T UV tubes with a peak wavelength of 420 nanometres are built into the top of the box for this purpose, although the box can also be used in other applications where UV light exposure is required by fitting tubes which peak at lower wavelengths if necessary. An "instant start" feature ensures that the tubes come on immediately, without flickering, as Kalex have eliminated the starters and provided transformers to preheat the tube filaments.

The light box measures 42.8 × 78.8 × 29cm (W × D × H) and is finished in wood grain veneer. The artwork or PCB to be exposed is placed in a drawer which slides in and out of the box and held in place by a plate of glass on a foam rubber backing surface. Materials with dimensions of up to 55 by 26cm fit comfortably in the box.

Two intensities of exposure are available since the sliding drawer can be fitted on one of two levels created by internal shelving in the box. The upper level places the artwork about 10cm from the UV tubes, but requires

the sliding drawer to be fully removed from the box and turned upside down before re-installation. Both sides of the bottom surface carry foam backing, but the removable glass sheet must be relocated, a process that would be simplified if it was fitted with some sort of lifting handle.

On the front panel of the drawer is a dial for setting the mechanical exposure timer, a toggle switch controlling power to the tube filaments and two indicator lights; "power on" and "exposure in progress". Mains power is controlled by the switch on the wall socket as there is no mains power switch on the light box. A microswitch in the cabinet ensures that the UV lights cannot be switched on with the drawer open.

The timer is a mechanical type with the dial marked with numbers from 0 to 6 and graduated in tenths. A separate timming control sets the overall range of the timer from one of three ranges; 0-3.6 seconds, 3-60 seconds and 36-720 seconds. A small screw-driver is needed to make this adjustment. although we found that once set on the 60 second range further adjustment was not required when exposing UV sensitive films. With the tray on the lower level however, from one to two minutes is required to correctly expose Riston copper clad board, making the 12 minute range necessary.

KALEX

UV MATERIALS

- Riston™ PCB
- 3M Scotchcal
- · 3M INT

UV PROCESSING EQUIPMENT

KALEX LIGHT BOX

- Autoreset Timer
- 2 Level Exposure
- Timing Light
- Instant Light Up
- Safety Micro Switch
- Exposure to 22in x 11in

\$395.00 + ST

KALEX "PORTU-VEE"

- UV Light Box
- Fully Portable
- Exposure to 10in x 6in

175.UU + ST

KALEX ETCH TANK

- Two Compartment
- Heater
- Recirculation (by Magnetic Pump)
- Two Level Rack
- e Lid

\$595.00 + ST

KALEX "PORTETCH"

- Two Compartment
- PCB Rack
- \$29.95 STI

DELIVERED

With 200mg Aerosol can

Positive 20 Photo resist



\$39.95 STI



101 Burgundy St, Heidelberg 3084 (03) 458 2976 Telex AA 37678 MELTON (03) 743 1011

SPECIALIST SCHOOL SUPPLIERS





See page 120 for full address details.





The box is 100% light-proof when the sliding drawer is closed but the mechanical timer and exposure indicator light provide confirmation that the light box is in operation. Once the selected exposure time is set on the timer dial, closing the drawer activates the microswitch and turns the lights on for the set period. Opening the box or switching off the power to the tube filaments instantly turns off the lights and sets the timer back to the start of the specified period, ready to be activated again when the drawer is closed.

This arrangement is ideal for exposure of multiple boards or artwork, as the timer need only be set once, at the start of the process. It also means, however, that when the box is first switched on the timer comes up with whatever setting was last used.

Kalex also make a smaller light box, the "Portu-vee", designed to the same high standard and suitable for exposure of materials with dimensions of up to 25 × 18cm. Unlike the larger unit this is a fully portable device, somewhat similar to a suit-case with four UV tubes mounted in the lid and a carrying handle on one side.

A commercial etching tank is also available, fitted with a 10W magnetic pump to circulate the etchant or developer. The pump is mounted externally and pumps through two tubes mounted vertically at diagonally

opposite corners of the tank. The tubes are drilled to produce a series of jets in the liquid, augmented by liquid circulation to the pump input across the bottom of the tank


A heater is mounted at the same corner as the tank outlet where suction from the pump prevents the warmer solution from rising to the top of the tank, ensuring a more uniform bath temperature. Racks for mounting printed circuit boards are also included, and the tank is compartmentalised to allow etched or developed boards to be rinsed by the circulation of fresh water through a hose connection from the

This etching tank includes mounting racks, a heater and pump circulation of etching fluid.

water supply. An outlet hose allows waste water to be channelled away from the work in progress.

Kalex can also supply a full range of 3M and Riston materials, developers and etchants and all requirements for manufacturers and hobbyists wishing to produce their own professional standard PCBs. For further information contact the company at 101 Burgundy St, Heidelberg, 3084 or their branches in Yarraville and Melton, Victoria. Phone (03) 458 2976.

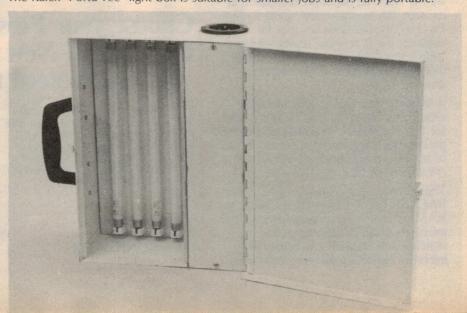The Kalex "Portu-vee" light box is suitable for smaller jobs and is fully portable.



microbee se

microbee Series 2 EDUCATOR

The microbee Series 2 was specifically designed to serve the needs of the EDUCATION MARKET. Let's face it, the primary non-business use for most personal microcomputers is to increase our learning capabilities either about computers (computer awareness) or about life itself. microbee Series 2 has now been officially approved by Education Departments in NSW, WA and Queensland and is being carefully considered in virtually all other states and by the National Schools Commission at the time this magazine was going to press. Over 5,000 microbees are now in constant use in schools, universities and technical colleges throughout Australia and New Zealand and the number is growing daily.

A large and increasing body of highly creative software has now been written for the microbee by students, teachers and professional programmers. We are aware of up to 6 new programs a day so you are assured of long term support.

The microbee Educator uses BATTERY BACKED NON-VOLATILE CMOS RAM so your programs are saved in the microbee Series 2 after the power is switched off. Students can bring the microbee Series 2 Educator home from

school to complete assignments ready for class the next day. With the optional BEEMODEM you can use your microbee Series 2 Educator to talk to other computers or information networks.

For school classroom use BEENET 1 is available to connect up to 16 or even more microbees on the same classroom network so that the teacher is able to co-ordinate the class with maximum efficiency.

Specifications:

PROCESSOR: Z80A running at 3.375 MHZ **KEYBOARD:** 60 key FULL SIZED QWER-TY layout with full travel.

MEMORY: 44K comprising of 16K user RAM (expandable on-board to 32K), 20K ROM software, 4K character ROM, 4K graphics and screen memory.

DISPLAY: Direct video to external monitor or modified TV. 80 by 24 and 64 by 16 character display modes, high resolution PCG graphics to 512 by 256 pixels. Upper and lower case with full programmability at any screen location.

SOFTWARE: MICROWORLD 16K BASIC V5.22 in ROM, MICROWORLD Z80 machine code monitor, built-in diagnostics, NETWORK-ING with programmable baud rates from 110 to 4800 Baud, 7,8 bit formats, half, full duplex transmission and complete file transfer using the 'HOBBY' standard Christensen protocol.

INPUT/OUTPUT: Programmable 8 bit input/output parallel port, programmable RS232 port, cassette interface, direct video, 50 way Z80 expansion bus.



microbee Series 2 \$449 EDUCATOR

Recommended Options:

microbee HIGH RESOLUTION
MONITOR\$199.00
BEEMODEM\$149.50
RGB COLOUR MODULE \$125.00
microbee PRINTER\$449.00
BEENET 1 (recommended for school classroom use only).

Choose your Personal Computer from the all New microbee Series 2 with Guaranteed E-X-P-A-N-D-A-B-I-L-I-T-Y

If your needs are for POWER PACKED computer for the home then the Personal Communicator with its generous 68K Memory comprising of 32K user RAM, 28K ROM Software, 4K Character Rom, 4K Graphics and Screen Memory is the computer for you.

microbee Series 2
PERSONAL
COMMUNICATOR
\$499

For serious use you can select the microbee Advanced Personal Computer (APC) which can be used with 1, 2 or even more disk drives to provide computing power unmatched by other computers in its class.

microbee Series 2 ADVANCED PERSONAL COMPUTER WITH SINGLE 400K DISK DRIVE \$1495 WITH DUAL 400K DISK DRIVE \$1795



microbee Series 2 EXPERIMENTER

By popular request, the low cost microbee Series 2 Experimenter has been designed for those who are starting out in the fascinating world of computers or those who want to share the fascination of exploring the exciting developments in the fast moving MICRO WORLD.

Demand for projects using the microbee is so great that 'Electronics Today' are now planning to run a microbee project every month during 1984. So far ETI has described the light pen, EPROM programmer, a radio TTY printer, the World's first home facsimile receiver and ROM expander board for the microbee. Virtually every local computer magazine has run reviews and/or columns devoted entirely to the microbee. If you want to be part of the MICRO-COMPUTER GENERATION in 1984 then microbee Series 2 Experimenter is the ideal starting point.

Specifications:

PROCESSOR: Z80A running at 3.375 MHZ. KEYBOARD: 60 key FULL SIZED QWER-TY layout with full travel.

MEMORY: 36K comprising of 8K user RAM (expandable on-board to 16K), 20K ROM software, 4K character ROM, 4K graphics and screen memory.

DISPLAY: Direct video to external monitor or modified TV. 80 by 24 and 64 by 16 character display modes, high resolution PCG graphics to 512 by 256 pixels. Upper and lower case with full programmability at any screen location.

SOFTWARE: MICROWORLD 16K BASIC V5.22 in ROM, MICROWORLD Z80 machine code monitor, built-in diagnostics, NETWORK-ING with programmable baud rates from 110 to 4800 Baud, 7,8 bit formats, half, full duplex transmission and complete file transfer using the 'HOBBY' standard Christensen protocol.

INPUT/OUTPUT: Programmable 8 bit input/output parallel port, programmable RS232 port, cassette interface, direct video, 50 way Z80 expansion bus.



Recommended Options:

microbee HIGH RESOLUTION
MONITOR\$199.00
BEEMODEM\$149.50
RGB COLOUR MODULE \$125.00
microbee PRINTER\$449.00
microbee EXPERIMENTER'S
'PROJECT BOARD' (Coming

microbee computer shops



1 Pattison Ave, Waitara 2077. Phone (02) 487 2711



729 Glenferrie Rd, Hawthorn 3122. Phone (03) 818 2244



Cooleman Court, Weston A.C.T. 2611. Phone (062) 88 6384



Soon)

141 Stirling Highway, Nedlands, Perth. Phone (09) 386 8250



welcome here

DIRECT ORDERS PHONE (02) 487 2711

> APPLIED TECHNOLOGY RETAIL PTY LTD



Authorised Dealers:

NSW: Jaycar, (inc. Electronic Agencies) 117 York Street, Sydney. 115 Parramatta Road, Concord.

113 Parramatta Road, Concord. 121 Forest Road, Hurstville. Cnr Carlingford and Pennant Hills Road, Carlingford.

Compu-K, 7 Casino Street, Lismore. Comput/Ed, 8 Park Arcade, Park Avenue, Coffs Harbour. ACT: Computech, Belconnen Churches Centre, Benjamin Way, Belconnen.

VIC: Computerland South Melbourne, 37 Albert Road, Melbourne.

S.A.: Key Computers, 1061 South Road, Edwardstown. 77 Grenfell Street, Adelaide.

W.A.: Altronics, 105 Stirling Street,

QLD: Software 80, 105 Milton Road, Milton.

Electrographic Office Systems, 25 Grafton Street, Cairns.

Town and Country Computers, CTL Centre, Anne Street, Aitkenvale, Townsville.

TAS: Central Data, 14A Goodwin Street, Launceston.

New Products... Product reviews, releases & services




Electric cleaner for soldering iron tips

C & K of Australia has recently acquired the Australian agency for Elvo Electronics Ltd of Switzerland. Included in this new range is the Elvo soldering iron tip cleaning instrument, the "Clean-o-point", a self-contained unit which uses motor driven sponge rollers to provide fast and reliable tip cleaning on the production line or work bench.

Features of the Clean-o-point include a quick, positive cleaning action and the provision of a removable tray which collects excess solder — which can be recycled. In a manufacturing plant the elimination of this wastage plus the extension of life of soldering iron tips made possible by regular cleaning can pay for the cost of the cleaning unit in a very short time.

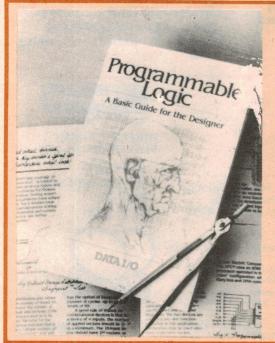For further information contact C & K Australia Pty Ltd, 15 Cowper St, Parramatta, or PO Box 229, Parramatta, 2150. Phone (02) 635 0799.



Warburton-Franki data on PLAs

Warburton Franki now has available a 32-page guide book which explains programmable logic arrays and the advantages offered over fixed function LSI and custom circuits.

Published by Data I/O, the book describes an actual design problem, showing how design equations were generated and translated into fuse tables to program the logic arrays. Functional testing is also covered.

The book, "Programmable Logic – A Basic Guide for the Designer" is available free of charge from your local Warburton Franki office or the head office at 199 Parramatta Rd, Auburn, NSW, 2144.



Discolighting for the home

New from Arlec Pty Ltd is "The Discolite System", described as "a complete portable lighting set for your very own disco effects at home".

The set consists of six lamps and holders, cable, two reflectors with brackets and the Discolite control unit. Assembly requires no wire cutting or joining, so the complete system can be set up or dismantled in minutes.

The six coloured lamps have a mirror coating on the inside of the globe to concentrate the light output while the reflector units are free-standing but with provision for fixing to walls and ceilings etc.

Rated at 500W and connected directly to any 240V mains outlet, the Discolite control unit functions either to flash the lights in time with music, as a strobe light controller, or a light dimmer. In the music mode an internal microphone picks up the beat of the music to allow control of the lights without direct connection to audio equipment.

In the strobe mode, the Discolite will flash the lights at a selected rate independently of the sound source. In the "Dim" mode the Discolite becomes a light dimmer, allowing continuously variable adjustment of light intensity.

Arlec products are available from their dealers throughout Australia, including their new agencies in Canberra, [24 Geelong Street, Fyshwick, ACT (062) 805 519] and Wagga [7 Norton St, Wagga Wagga, NSW, 2650 (069) 212 735].

Arlec Pty Ltd also has outlets in Victoria, 30-32 Lexton Rd Box Hill; NSW, 47 Drummond St, Belmore; Queensland, Cnr Vernon Terrace and Ethel St, Newstead; South Australia, 30 Beulah Rd, Norwood; and Western Australia, 611 Hay St, Jolimont, 6014.

Video tapes on electronic tools and techniques

Educational Video Productions, of Melbourne, has available a series of four instructional video tapes covering tools and techniques for electronic assembly, PCB production and soldering.

The tapes are intended for use in schools, TAFE colleges, technical institutions and industrial training programs, and are the result of extensive research by educationalists and industry engineers from leading Australian companies.


The four titles — the first of the series — are "PCB Artwork Design", "PCB Fabrication", "PCB Assembly — Tools" and "Soldering". The third title is actually a double presentation, the first on component mounting, handling and board assembly and the second on tools for electronic work, including a review of the Xcelite range of tool kits.

Tools are divided into "essential" and "optional" categories and the selection criteria for each type explained along with illustrations of their use.

Each tape concludes with a series of multiple choice questions designed to reinforce the material presented and each provides a very good introduction to the topics at a high school level.

Running time of the tapes varies, but the tape on soldering techniques, for example, is 22 minutes long. Topics include the reasons for soldering, solder composition and the role of flux, the varieties of soldering irons available and handling precautions for sensitive components. Continuous heat and variable temperature irons are described and illustrated with explanations of the advantages and disadvantages of each type and the various defects of soldered joints are detailed. Multiple choice questions conclude the tape.

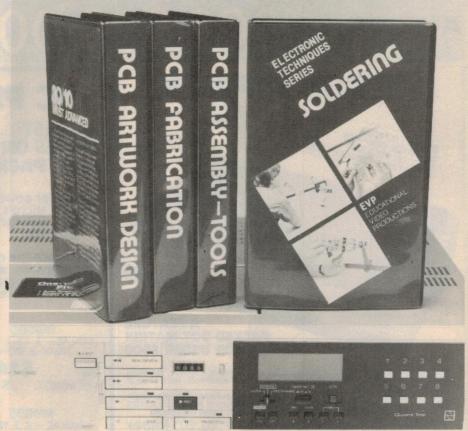The tape on artwork design runs for 20 minutes and is a complete explanation of the steps from a circuit diagram to the production of a PCB artwork master,




presented in a simple, understandable way. It in turn leads into "PCB Fabrication", which covers the making of artwork negatives, the use of photoresists, board exposure and etching, concentrating on the use of Riston materials. Again a series of questions at the end of the presentation reinforces the material and adds to the usefullness of the tapes for teachers in a classroom situation.

We have viewed the tapes and were impressed by the clear presentation and quality production standards. According to EVP, professional studio facilities, presenters and directors have been used throughout, and the final production

reflects this attention.

The original material has been produced on one inch master tapes to broadcast specifications and are individually duplicated onto video cassette for distribution. Both Beta and VHS formats are available.

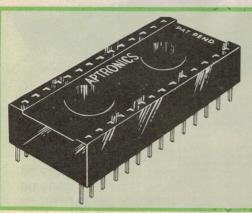With the increasing emphasis placed on electronics and contruction techniques, particularly in the TAFE curriculum and secondary schools, the EVP tapes should play a valuable role. They are available at \$39.95 (plus sales tax where applicable) from Educational Video Productions, 57 Burwood Rd, Hawthorn, Vic, 3122. Phone (03) 819 4983 (10am-4pm only).



"Programmable" IC sockets simplify prototypes

Rifa Pty Ltd has announced the release of a new "programmable" IC socket that allows the pins of integrated circuits to be selectively connected to different pins of the socket

The main application is seen as matching different IC pin-outs to existing circuit board layouts, a need which occasionally arises when using devices from a number of different

manufacturers.

Installation of the socket allows all sources of a particular IC to be used regardless of pin configuration, facilitates evaluation of new devices and speeds up-grading and testing in the field.

For further information on the new socket contact Rifa Pty Ltd, 202 Bell St, Preston, Vic, 3072. Phone (03) 480 1211.

ALTRONICS

NEXT DAY

DELIVERY

BANKCARD JETSERVICE

ALTRONICS

MICRON SUPER 80



Your "Super 80" printer will enable you to print letters, reports, graphics generated pictures, etc and importantly for the programmer, Hard Copy of

program listings.

Operating under software control from any general purpose micro-computer the Super 80 features 13 different print types including emphasizd (LETTER QUALITY). Bidirectional print action ensures smooth, quiet operation.

228 ASCII Characters, Handles 4" to 10" Paper STANDARD CENTRONICS INTERFACE

VALUE PACKED AT D1174	\$499.50
INTERFACE CABLE TO SUIT MICROBEE D1190	
SPARE RIBBON D1175	The second secon

TOP QUALITY LINED PRINTER PAPER TRACTOR FEED AT LAST AT AFFORDABLE PRICE TO SUIT SUPER 80 240mm WIDE D1160. \$39.50 380mm \$47.50 2000 SHEETS PER BOX

CENTRONICS PLUG

36 WAY D1192 \$14.95

When you buy one of our printers you'll need a centronics plug. If you are **MICROBEE USER**, have a look at our **INTERFACE KITS** on the opposing page.

UK MADE, GOLD PLATED D RANGE CONNECTORS SAVE 25% ON BULK QUANTITIES!



	ea.	10 +	25
0880 DB9 Male 9 Pin	2.50	2.20	1.5
0881 DB9 Female 9 Pin	2.95	2.70	2.
0885 DB9 Backshell	2.85	2.50	2.3
0890 DB15 Male 15 Pin	2.95	2.50	2.3
0891 DB15 Female 15 Pin	3.50	3.00	2.8
0895 DB15 Backshell	2.85	2.50	2.3
0900 DB25 Male 25 Pin	4.50	3.95	3.6
0901 DB25 Female 25 Pin	4.95	4.50	3.9
0905 DB25 Backshell	2.85	2.50	2.3



JUST PHONE OR WRITE & ASK
WE'LL SEND YOU OUR SOFTWARE CATALOGUE
HONEYSOFT ● MYTEK ● DREAMCARDS

DC PLUG PACKS

AT LAST . . . DIRECT IMPORT PRICES ON FULLY APPROVED **PLUG PACKS**

Great for powering small Micro's, TV Games, Slot Car Sets. etc.

Eliminate the need for batteries, when testing or operating new projects.

M9000 240v AC — 3, 4.5, 6, 7.5, 9, 12v DC @ 300mA

ONLY......\$14.95 4 OR MORE......\$13.50

M9005

240v AC — 6, 9, 12v DC @ 500mA

ONLY...... \$14.95 4 OR MORE......\$13.50

Both Plug packs come with instructions and a 4 way multiplug 1.6m lead.



ASC 126

DELIVERY

JETSERVICE

CARD

THE SENSATIONAL MICROBEE IC



The all new Microbee IC has got to be the most value packed ROM based personal computer available today. **New enhanced basic** enables 64 x 16 or 80 x 24 screen format while networking and the clock speed is now a zippy 3.375 MHz and over \$110 worth of software integrated in ROM i.e. the absolutely delightful **Wordbee** word processor package or Editor Assembler

plus all the other exciting features that have made the Microbee famous.

D1020.....16K IC..... \$499.00 D1035.....\$599.00 ARCADE GAMES, PERSONAL, BUSINESS AND EDUCATIONAL APPLICATIONS.

64K on board RAM, Z80A based running at 4mHz (Top speed) Floppy disk controller, Real time clock.

time clock.

That's right! A fully configured 280 computer running at maximum capacity, on a single PCB. On board disk controller drives up to four double sided, double density drives either 8 or 5 2 by RS232 1/0 Ports, both may be software configured, use one for a terminal the other for a printer or modem etc. Battery backed real time clock software accessible for automatic dating of documents, timing during games. Fully STD buss compatible — choose from thousands of ready available plug in card options Bootstrap Monitor on board — boots to CP/M. Choose from the worlds largest range of software.

Altronic KIT FEATURES

Two versions of the bootstrap monitor supplied. One set for 1200 baud operation enables connection to MICROBEE 16 & 32K ICS utilizing their terminal emulation facilities. The other set for 9600 baud operation. Complete set of IC sockets.

Double sided plated through PCB — solder masked and pretinned.

56 Pin STD connector.

2 x DB25P's and ribbon cable for peripheral connections.

Quality components used throughout including solder and full documentation.

K9690 \$499 Diskettes 8 9600 Bau 9600 Baud \$150 1200 Baud \$150 K9692 1200 Baud \$150

ALTRONICS

ALTRONICS

DAY

NEX

DELIVERY

JETSERVICE

BANKCARD

ALTRONICS

\$24.50



computer music synthesizer that is easy to build and easy to use, connects to any computer with a Centronics-style parallel port and provdes music over a five octave range and a wide variety


* EXPERIMENTAL KIT - PCB, COMPONENTS & SOFTWARE.

K9834.....

MULTIPROM INTERFACE FOR THE MICROBEE

(ETI NOV. '83)

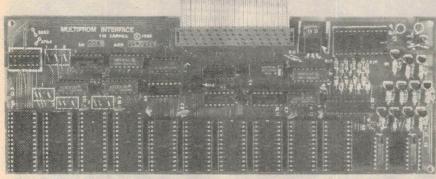44K OF PROGRAM STORAGE * FULLY SOFTWARE SELECTABLE * SUITS BOTH IC AND PLUS MACHINES * 8 OUTPUTS FOR CONTROL APPLICATIONS *



A sensational new kit for the MICROBEE, requires no modification to the computer except for the fitting of a 50 pin expansion socket. This project is easy to build and will allow you to store and software select up to 44K of eprom storage — acts like a mini disk drive system with the speed of RAM. Extra units may be added to further increase storage

The Altronics Kit comes complete in every way * Full set of IC sockets. * Double sided, plated through board.

Assembled connection lead to Microbee Fully documented.

* Cassette monitor included (plus sourcefile).

\$99.50 K9673....


50 PIN EXPANSION SÓCKETS

Right angle type to suit Microbee, floppy disk controllers etc Mounts on PCB and mates with IDC sockets.

D1196...\$8.50 EA...10 +...\$7.50

PRINTER INTERFACE KITS FOR THE MICROBEE

PARALLEL TYPE

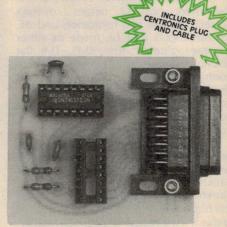

BUILD YOUR OWN INTERFACE AND SAVE \$\$\$

A simple kit to build — takes about 20 minutes, save on the cost of a built interface and save the cost of a serial printer.

.....\$29.95 К9671.....

TTY TYPE

Teleprinters are cheap, so is this kit. If you've got an old Teleprinter this is for your.

K9672..... (Only)..... \$17.50

SUPPORT FOR THE MICROB



BANKCARD JETSERVICE DELIVERY NEXT


ALTRONICS



\$55.00 K9668

Versatile, low cost and easy to build. Plug straight into the microbee I/O port. Suitable fo 2716, 2732, 2532, 2732A and 2764 Eproms. Burr your games programmes and eliminate cassetti

(See Review ETI AUGUST 1983)

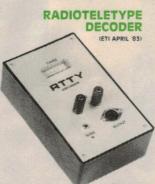

\$19.50 K9733 Display RTTY encoded messages on your Video Monitor. Receive up to date weather information, international News before the Papers, all sorts of coded military info. Simple circuit uses PLL techniques Single PBE Construction Kit includes DB15 Plug and backshell for connection to microbee Shelded pretinned PCB.




PROVIDES DIRECT PERSONAL CONTACT WITH YOUR BEE!

K9649

\$19.95

AT LAST — a light pen for the Bee. This pen works in the low-resolution graphics mode and connects directly to the I/O port. * Complete kit including DB15, 2m CORD * Fully documented with software example.

FAX-DECODER

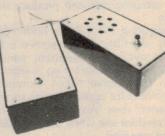

This project allows you to decode the signals of shortwave stations transmitting radio facsimile weather maps, safellite pictures etc and then reproduce them on your dot-matrix printer . Complete kit of parts includes DB15_Ribbon_Coble.

* SOFTWARE LISTING

New Products...

Combined multimeter/ oscilloscope from Kent Instruments

A new device from Kent Instruments (Australia) combines the functions of a digital multimeter, an oscilloscope and a transient recorder in one portable, battery-powered package.

Called the Metrawatt M2050 Digital Scope Multimeter, the instrument combines a 3½-digital multimeter and a liquid crystal oscilloscope display with a resolution of 128 × 64 points.

The digital multimeter section of the instrument has 32 ranges covering current, voltage and resistance, and AC measurements may be made as either average value or true RMS. The flat screen LCD oscilloscope provides a high contrast image and a range of 30 input levels and eight timebases. Trigger capabilities include internal and external sources and AUTO trigger with a continuously variable trigger level.


The digital oscilloscope section uses a successive approximation technique with a maximum sampling rate of 512kHz and a resolution of eight bits. Timebases for display of the full storage memory range from 1ms to 60 minutes and a ×4 expansion facility is available.

When configured as a transient recorder the M2050 uses two separate memories to store random transient events, with a maximum sampling rate of 500kHz. Once triggered by a transient event the recorder can display the memory contents on the LCD screen. The triggered position can be set to in steps of 25% from the start to the end of memory, allowing the user to view events before, at, or after the trigger event.

A chart recorder interface is also included to allow the stored waveform to be plotted. Signals to the plotter are interpolated to eliminate the effect of the sampling rate and produce smooth plots.

Measuring 257 × 169 × 88mm (W × D × H) when the display screen is folded down over the instrument panel, the M2050 will operate for up to eight hours from its internal Nicad batteries and retain data for approximately six months between uses. An AC adapter is also included for use when battery operation is not required.

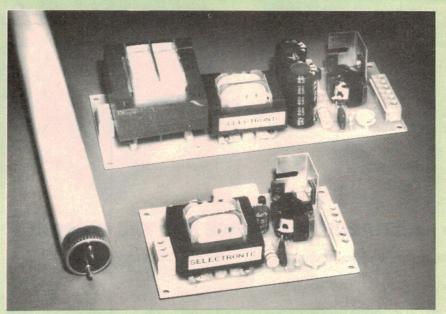For further information on the M2050 contact Kent Instruments (Australia) Pty Ltd, 70/78 Box Rd, Caringbah, NSW, 2229. Phone (02) 525 2811.



Selectronic's emergency lighting system

Selectronics has released details of new 8W and 10W emergency lighting systems for use in fluorescent fittings. The solid-state modules do not require a starter or ballast and are powered by three D-type Nicad cells.

The emergency lighting units are designed and manufactured by Selectronics, who claim that they are more than competitive with imported equipment.

Selectronics also manufacture a wide range of transformers and power supplies, including a new 350W five rail unit designed primarily for computer applications. The SM350AE1 is an open frame switch mode supply with five regulated outputs: +5.2V at 25A, +24V at 6A, +12V at 6A, -5V at 2A and -12V at 2A. Total output power is 350W

continuous with a peak of 460W for 30 seconds.

Output ripple and noise is quoted as less than 2% p-p up to 20MHz and efficiency as greater than 65% at full load. Over-voltage protection is provided on the +5V, +12V and +24V rails and two 110V outputs are provided for powering cooling fans. Other features include reset and power fault signals, a remote on-off facility and remote selection of input voltage.

As with all power supplies from Selectronics the SM350AE1 is backed by a five year guarantee and complete technical back-up.

For further information, contact Selectronic Components Pty Ltd, 25 Holloway Drive, Bayswater, Vic, 3153. Phone (03) 762 4822.



MULTIPROM INTERFACE

The Multiprom board is an extension of the Microbees memory in ROM. It simply plugs into the fifty way bus expansion port on the core board. It fits either neatly inside the Microbee or behind it, using the Microbee's own power supply.

power supply.

The board takes the EDASM and NET eprom normally residing inside the Microbee, but allows several different sets to fit in: Editor-Assembler, Wordbee, Logo, MiniPascal, Networkrom, Bemon or your own program. It has room for 4 sets of eproms in the EDASM location and 3 sets of eproms in the NET location, a total of 44K of eprom. The board can be simply daisy chained with up to 6 slave boards using an outside power supply in this case, allowing a maximum total of 308K in ROM. The EDASM locations accept either type 2532 or 2764 eproms and they can be mixed. Another powerful feature of the board is the input/output system. 11 outputs, open collector transistor driven, Each can turn ON or OFF a relay under program control. 8 inputs, buffered and protected can read 8 switch status ideal for coimputer controlling of model trains, alarm systems, tape recorders, machinery etc.

The Avtek kit includes a plated through board plus all components to make this exciting project. There is also provision on the board to change the address of the ports used for eprom selection and input output.




MUITI ROM BOARD

XM-1 - This is a totally new product developed EXCLUSIVELY for AVTEK. It takes two sets of EPROMs (e.g. WORDBEE and EDASM) and allows you to choose between them by simple KEYBOARD COMMANDS. It will take a short time to assemble and is simply installed inside the MICROBEE with one DIP plug (supplied) and two solder connections XM-1 suits early model MICROBEE plus models using 2532 type EPROMs.

These have serial numbers starting with 8 ONLY \$19.95

XM-2 same as XM-1 but suits the "MICROBEE IC" and is even simpler to fit. Also responds to PAK1 and PAK2 commands.

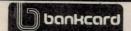These have serial number starting with 9 - ONLY \$16.95



S-100 SOCKETS High quality, gold plated \$6.95 ea or 10 for \$65

Power-on automatic bootstrap to CP M system in on-board EPROM

SEE ETI OCTOBER 1983 FOR FULL DETAILS

Real time clock chip with battery backed supply Bus Interface All signals meet STD Bus electrical spees. External Connections

50 way edge connector provided for 8" floppy

disc connections
1 16 pin RS232C for terminal connection
1 16 pin RS232C for printer connection
FULL KIT PHONE FOR FINAL PRICE
PCB - MANUAL & ROM ONLY \$149.00



172 LIVERPOOL ROAD, ENFIELD Phone: (02) 745 2122

> DON'T FORGET WE ARE PROBABLY THE LARGEST SELLER OF IC'S, COMPONENTS, IDC CONNECTORS, ALTRONICS KITS ETC. IN SYDNEY

ASHED

That's our price Dec Only \$10 P&P - NO Bankcard Check the opposition!!

COMING SOON! Disc Controller & C/PM to suit 32K MicroBee - WATCH OUR ADS!! CAR ALARM - WAS \$69.50 SAVE \$10 Dec. Only NOW \$59.50 - full featured - easy to install. Logic & Voltage testers SAVE nearly 20% \$7.95 Dec. Only

Reach the FOR AROUND



Limited Stock

THIS KIT WILL 'KILL' ALL OTHER KITS AVAILABLE IN IT'S TOTAL COMMUNICATION Modulation Frequency shift keying. Digital Interface RS-232C Auto answer and disconnect. Data communication to basic Bell or CCTTT specifications giving a world data communications capability. Operates with your normal phone: 300BPS or 1200 BPS with backward channel 75 BPS. Indicators and nets which. Auto answer or namual connect. Backward channel standard on 1200 BPS indicators and nets which. Auto answer or namual connect. Backward channel standard on 1200 BPS. Bell 103 answer 300 BPS, Bell 202 equalised 1200 BPS. Bell 202 equalised 1200 BPS. CTTT V23 mode 2 equalised 1200 BPS. CTTT V23 mode 2 equalised 1200 BPS. CTTT V21 answer 300 BPS.

AND IT'S COMING SOON:

THE PRICE? AROUND \$200. THAT'S HUNDREDS LESS THAN THE NEAREST EQUIVALENT!





(ELECTRONICS) Pty. Ltd.

TWO GREAT LOCATIONS

119 YORK STREET, SYDNEY 2000

PHONE: (02) 267 8777

(Above Charlie Browns Place)
172 LIVERPOOL ROAD (HUME HIGHWAY), ENFIELD

PHONE: (02) 745 2122

All Correspondence to:
P.O. BOX (3302, QUEEN VICTORIA BUILDING,
SYDNEY 2000

POST AND RACKETS

POST AND PACKING

Divide the value of your order by 20 (5%) to get post and packing value and then add \$2.00 it's that simple!

All Bankcard orders can only be sent to a normal address (NOT a P.O. Box). All Bankcard orders will be sent by registered mail (add \$3 to P&P charges).

ENFIELD OPEN ON SUNDAY

EASTERN

COMMUNICATION CENTRE

COMMUNICATIONS, ELECTRONICS AND COMPUTERS

168 ELGAR ROAD, BOX HILL SOUTH, 3128 Phone enquiries: 288 3107

CONTACT Keith VK3ACE or David VK3UD HOURS: Mon.-Fri. 9-5.30, Sat. 9-12 BANKCARD WELCOME OR WE CAN ARRANGE FINANCE

FULLY EQUIPPED SERVICE CENTRE ALTRONICS DISTRIBUTOR

7 DIGIT FREQUENCY COUNTER



UNBELIEVABLE 0.005% ACCURACY

GENERATOR



CAPACITANCE METER



with Deluxe Instrument Case

COLOUR GE



WIDE RANGE OF SOFTWARE AVAILABLE

- 16K Rom 16K Ram on board
- Expandable to 32K on board
- Extended microsoft basic
- RS232C & parallel ports built in
- RF & video built in
- Loads at 1200 baud
- 24 × 40 screen display
- Programmable characters
- 8 function keys

\$499 (incl. tax)

50U 5A LABORATORY POWER SUPPLY




New switchmode supply can deliver anywhere from three to 50V DC and currents of 5A at 35V or lower. Highly efficient design.

EA May, June 1983

EASTERN CONVERTER! CW/RTTY/COMPUTER

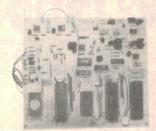Hooks straight up to your RS232 Terminal or Teletype via 20mA loop.



RTTY COMPUTER Connect to terminal and modem. See EA November, 1982



POWER

A MUST FOR YOUR COMPUTER SYSTEM

This great new Project from EA is the answer to a Majden's Prayer

What Does It Do?

A single 24Ov mains plug and lead feeds one unswitched master 24Ov outlets but 4 switched 24Ov outlets. With say a hi-fl system, plug your main equipment Item (eg Amp) into the master outlet and whenever you. "switch on" your amp – presto – mains power is applied to the other 4 outlets ie simply "turning on" your amp turns on your tage; cassette, tuner, turntable, graphic equaliser without mains spikes, plops, etc.

Just the shot for your Computer System.

The Altronics Kit includes case and all outlets.

Cat K6000......\$39.50

LABORATORY



Q 1040 Multimeter Q 1041 Carry Case \$72.50 \$14.50

From Tokyo Laboratories, Japan

Remember the days when high grade precision laboratory multimeters were available only from Uk and then they cost a King's Remember Well throw the Health of the Health of

FAX-80



plus Tax

80 column printer. Bi-directional graphics printer.

Plugs into APPLE® or compatible computers. Software and documentation for instant CW BAUDOT, ASCII transmissions.

Can be adapted for Commodore



ORDER NOW - LIMITED STOCKS

COPIED AND PROGRAMMED PCB's MANUFACTURED TO ORDER.

APPLE. COMMODORE & TRS 80

New Products...

New Loftek audio test set

The Loftek Audio Test Set simplifies the alignment and calibration of virtually all types of audio systems. Level calibration of tape recorders and mixing consoles, frequency response measurements and verification of signal strength throughout an audio circuit are just some of the applications of the TS-1

The LofTech TS-1 audio test set combines an audio sine wave generator with a digital meter. The generator's range extends from 15Hz to 30kHz and the meter can be switched to read either frequency or decibels. The oscillator section has an output for feeding test signals to external equipment and the meter can accept signals from the equipment under test. When a plug is inserted in the meter input socket the internal connection between the oscillator and the meter is broken, allowing the TS-1 to be used simultaneously as a signal generator and a measuring device.

When switched for signal level the

New SC7000 scanner from Imark Pty Ltd

Imark Pty Ltd now has available the Saiko SC7000 scanning receiver, a compact unit which provides coverage of the VHF low band (60-90MHz), the VHF high band (140-180MHz), the UHF band (380-520MHz) and the air band. Channel steps for VHF and air bands are 2.5kHz, and 25kHz for the UHF band.

A Z80 microprocessor controls scanning functions, allowing the operator to scan between pre-set frequency limits, store up to 70 frequencies in memory and monitor and store frequencies for later recall. Two scanning speeds and a digital display of frequency and operating



modes are provided together with an output for a tape recorder, a 24 hour clock and memory battery back-up.

Dimensions of the Saiko SC7000 are $270 \times 90 \times 30$ mm (W × D × H) $270 \times 230 \times 90$ (W × D × H) and mass is 3.1kg. A telescopic whip antenna, mounting brackets for vehicle installation and an operator's manual are provided with each receiver.

Further information is available from the importers, Imark Pty Ltd, 167 Roden Street, West Melbourne, Vic, 3003. Phone (03) 329 5433.


meter reads whole decibels over the range of -50 to +24dB, with 0dB representing 0.775V. This reference point may be adjusted from the rear panel.

In the frequency display mode the meter responds from 1Hz to 99.99kHz.

LEDs are provided to indicate Hz, kHz and dB ranges.

For additional information contact distributors, Hilotek International Pty Ltd, Miles St, Mulgrave, Vic, 3170. Phone (613) 561 2888.

Plug into 'Eveready' rechargeables.

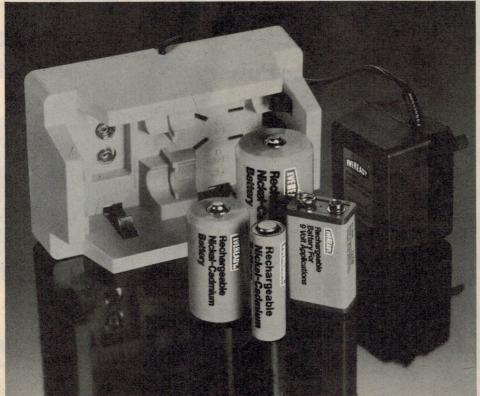

Our rechargeable range, in popular sizes, can be charged up to 1000 times on the new model ACC50E Charger, thus offering an extremely economical power source to the heavy-battery user. Especially ideal for photo-flash, movie cameras, tape recorders, transceivers and electronic games and toys.

Please don't hesitate to call for further information.

EVEREADY.

Rechargeable Nickel-Cadmium Batteries.

Union Carbide Australia Limited, Battery Products Division, 157-167 Liver.pool Street, Sydney. Phone: 269 0656 SALES OFFICES: Brisbane: 47-49 Sherwood Road, Toowong. Phone: 3716877. Adelaide: 121 Greenhill Road, Unley. Phone: 272 0611 Melbourne: 14 Queens Road. Phone: 26 1241, 26 2332. Perth: 901 Hay Street. Phone: 321 2926.

UNION

veready and 'Union Carbide' are registered trade marks.

085.P.834A





Top quality EPROMs at rock bottom prices.

2716 EPROM \$4.00 each \$3.70 10+ 2532 EPROM \$7.00 each \$6.30 10+ 2732 EPROM \$7.00 each \$6.30 10+ 2764 EPROM \$11.00 each \$10.00 10+

Hitachi 2114AP2

Fantastic price on brand new Hitachi 2114AP2. These are low power 200nS devices going for a song!! But stocks are limited so you'll have to be quick. \$1.30 10up

Microprocessor Tick Tocks

Enthusiasts, get out your soldering irons. Santa Sheridan has got these amazing OKI MSM5832RS microprocessor controlled clock, calendar ICs in stock. You'll spend hours learning about all its functions. And look at this tiny price.

only \$800

Fantastic 14 page applications and technical manual:

Pushbutton Telephone

We've sold thousands of these superb phones from PYE/TMC. With 10 memories and 'try again' facility its not surprising!! But we're clearing them out at massively reduced prices. You re the benefit!!

were \$5900 50 only. First come, first served!!

14 and 16 pin IC sockets

Never again at these prices. High quality AMP low profile sockets at a fraction of their

10 for \$1 100 for \$9

Colorburst Crystals

Going for a song!! These crystals are used in many projects and timing circuits. at these prices you can use them for experimenting etc. Solder type 4.43619MHz

only \$2

LEDs at Very Light prices!!

Scoop purchase of high quality Stanley 3mm red LEDs. Packs of 200 only at this price!!

200 for only \$1600

Centronics

This is the most common plug of all on Centronics printers, computers etc. Amphenol type 57/303/60. Most of our opposition are charging around \$18.00 for these connectors. Look at our Knockout Price!!

ONLY 1,000 available

The Pulsar


Little Big Board at a

You've seen the specs (or see October ETI for the full article). So you know its fantastic value. Now buy at a better Sheridan price!!

> Kit 1: PC Board, MP7A Monitor PROM, Users Manual and setup sheet. List price is \$149.00

Kit 2: As above but with full component set and LB00T6 boot PROM. List price is \$499.00

Sheridan

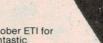


Sheridan





Books & Literature

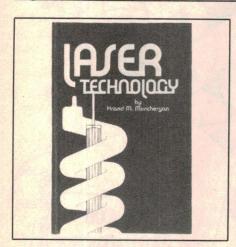

Light on lasers

LASER TECHNOLOGY by Hrand M. Muncheryan. Published 1979 by Howard W. Sams & Co, Inc. Hard covers, 145 x 223mm, 285 pages. Illustrated with many photographs and diagrams. ISBN 0 672 21588 8. Price in Australia \$21.95.


Not very many books are published on this subject so this text is very welcome as it treats the subject comprehensively and is quite up to date. Inevitably though it does miss out on the laser technology used in the latest compact disc players. Apart from that it can be thoroughly recommended.

There are fifteen chapters and five appendices. Some chapter headings are as follows: Applied Laser Principles; Laser Holography; Laser Waveguide Principles; Laser Instrumentation in Medical Surgery; Laser Instrumentation in Dentistry; Laser Systems for the Military and Security Surveillance Laser Systems. Our copy came from Jaycar Electronics Pty Ltd, 380 Sussex Street, Sydney. (LDS)

Terminology explained

DICTIONARY OF AUDIO, RADIO AND VIDEO by R. S. Roberts. Published by Butterworths & Co Ltd, London, 1981. Hard covers, 140 x 220mm, 248 pages, illustrated with diagrams and circuits. ISBN 0 408 00339 1. Recommended price \$42.00.

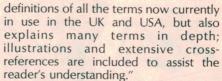According to the jacket description, "This dictionary not only provides clear



And that is a fairly accurate description of the book. One might quibble over the word "all" but it is fair description. More important, perhaps, is the extent to which various terms are defined. This can vary from one or two lines to more than half a page, plus diagrams and cross references. In this respect the book tends to be more of an encyclopaedia than a dictionary, though the author does not claim this.

On the other hand, the author points out that there has been no attempt at a "textbook" approach to these definitions; merely an attempt to point the way to more detailed study, if needed. Nevertheless, where desirable to assist the explanation, appropriate formulas have been included.

By their very nature, books of this kind tend to be of limited value to the individual, but would be appropriate in technical education and other libraries.

Our copy from Butterworths Pty Ltd, Box 345, North Ryde, NSW. (PGW)




TRS-80 Color Computer

MAKING THE MOST OF YOUR TRS-80 COLOR COMPUTER by Peter Vernon. Published by Prentice-Hall of Australia, 1983. Soft covers, 152 x 230mm, 192 pages. ISBN 0-13-547647-X. Price in Australia \$14.95.

Since this book is written by one of our

staff, we are not really in a position to give a truly objective review. However, in nine chapters the author gives readers a good introduction to the TRS-80 Color Computer. He deals at some length with Color Basic statements and functions and gives valuable insights into the graphic and sound features of Color Basic with over a 100 sample programs.

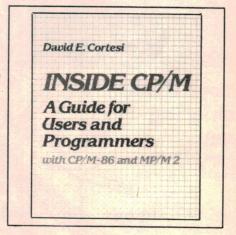There are also appendices for the Color Computer character codes, musical notation, machine language and Hexadecimal. (LDS)



A detailed guide to CP/M

INSIDE CP/M: A Guide for Users and Programmers by David E. Cortesi. Published by CBS College Publishing, NY, 1982. Soft covers, 188 × 236mm, 570 pages ISBN 0 03 059558 4. Price \$41.95.

This perhaps the most detailed and comprehensive book on CP/M available. In coverage and detail it sets a standard which other writers would do well to emulate, and although written for newcomers to computing as well as the more experienced it truly does have something to say to everyone.

The text is divided into two sections; a tutorial which presents the fundamentals of using and programming a small computer with CP/M, and a reference guide for programmers, organised and indexed for ready reference.

The tutorial section is further subdivided into four parts. The first four chapters introduce the newcomer to computers and CP/M, explaining the components of a computer system and defining systems and application programs. Valuable guides to drives and printers are provided, and in addition there are section on shopping for a computer system, organising the computer workplace and insuring against the loss of the system or valuable data.

Chapters five to eight introduce the new user to the CP/M operating system. The keyboard and the process of bringing CP/M up on a computer are discussed first, followed by descriptions of the most commonly used commands and the file system. Separate chapters are included on the use of PIP, (Peripheral Interchange Program) for file transfer, and on ED, the CP/M line editor. Organisation of disk libraries, hard disks and the use of the SYSGEN and SUBMIT utility also receives a separate chapter.

Chapters 9 to 12 address the facilities provided by CP/M. Starting with binary data and number systems and the representation of data, this section takes the reader step by step through some of the intricacies of the operating system, including the organisation of disks and files. Chapter 11 describes some of the languages available under CP/M, and discusses the merits of compilers and interpreters, while Chapter 12 describes the use of assembly language and DDT, the Designer's Debugging Tool.

Section Four of the tutorial system is for experienced programmers who wish to learn how to access the Disk Operating System of CP/M using assembly language. Again the coverage is complete and detailed, including service requests, opening and writing files, format of directory entries and the use of program libraries. Interfacing to the Input/Output System is also covered in detail for CP/M, MP/M and the 16-bit CP/M-86 versions of the operating system.

Section one of the book, occupying perhaps half of the 570 pages, has its own index and a glossary. It is followed by the reference guide, which consists largely of summaries and charts of instructions, I/O assignments, ASCII and hex values and the 8080 and Z80 microprocessor instruction sets. A separate section covers the use of the assembler, and further summaries are provided of all features of the BDOS and BIOS components of CP/M.

Detailed summaries and maps of CP/M memory use, directory format and the configuration of the CP/NET networking system conclude this section.

Considering the amount of material covered and the detail provided, "Inside CP/M" will be a valuable addition to the library of anyone using or considering using CP/M. It is clearly written and well organised and has something for everyone, from the beginner to the advanced programmer. Highly recommended.

"Inside CP/M" is available from Altronic Distributors and their re-sellers throughout Australia. (PV)

LIKE TO GET AN AMATEUR RADIO CERTIFICATE? IT'S MUCH EASIER WITH PROFESSIONAL HELP.




If something's worth doing, it's worth doing well. So don't waste your valuable spare time finding your own way through the Amateur Radio maze. Ask Stott's instead. We have top professional instructors, who'll make sure your time is well spent on your way to an operator's certificate. You'll have individual attention, working at your own speed, in the comfort of your own home. Any queries will be answered personally, and promptly.

So don't delay. Mail the coupon for full details.

Over and out.

	Melbourne, 159 Flinders Lane, 3000. Tel: 63 6212
Stotts	Sydney, 383 George Street, 2000. Tel: 29 2445 Brisbane, Suite 3, 65 Mary Street, 4000. Tel: 221 3972 Adelaide, 85 Pirie Street, 5000. Tel: 223 3700 Control of the Street Stre
The name to trust in correspondence education.	W. Perth, 25 Richardson Street, 6005. Tel: 322 5481 Hobart, 150 Collins Street, 7000. Tel: 34 2399 New Zealand, Box No. 30-990, Lower Hutt. Tel: 676 592
Please send me free, and without obligation, full details of the following courses:	The Stott's range of courses in Amateur Radio is:
(PLEASE PI	Novice Amateur Operator's Certificate of Proficiency.
MR. MRS. MISSAGE	Amateur Operator's Certificate of Proficiency.
ADDRESS	Amateur Operator's Limited Certificate of Proficiency.
Stott's undertake that no sales counsellor will visit you.	Radio for Amateurs ALA/ST4467/EA1283

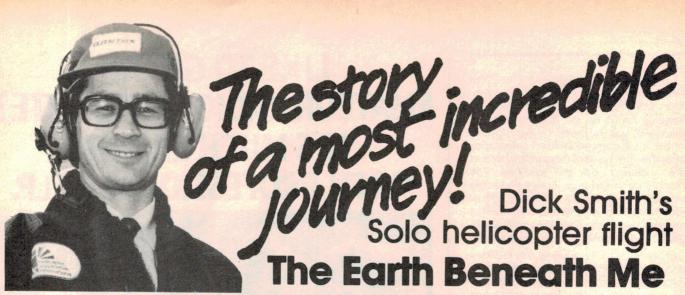



In a word ... magnificent! See the world as it's never been seen before in this day-by-day account of one of the aviation events of our time.

From the scorching deserts of the Middle East to the frozen wastes of the Arctic, Dick has captured every incredible moment for all to share and enjoy.

And even more: a 'guided tour' of Dick's helicopter VH-DIK, showing all the controls, what they do – even how to fly it! A beautifuly hard-bound edition for years of enjoyment - you must read The Earth Beneath Me'. Cat B-9105


A wonderful collector's item and gift idea! \$

Also Available on Video Cassette Contains three one hour commercial documentaries of the flight, as seen on John Laws' World. Available in either VHS of BETA \$6950 formats. (Mail order only)

STORES THROUGHOUT AUSTRALIA OR USE THIS EASY MAIL ORDER FORM

Yes! I would like to order
copies of "The Earth Beneath Me" book (Cat B-9105) @ \$24.50 ea.
☐ Video VHS cassette(s) @ \$69.50 ea.
Video Beta cassette(s) @ \$69.50 ea.

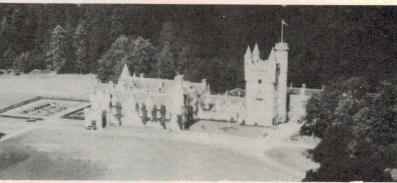enclose cheque/postal order for \$.... Or please charge to my Bankcard



Over 100 magnificent full colour plates. 256 pages, including sections on how the helicopter operates and flies

POSTAGE & Signature DICK SMITH MAIL

CARD NO.

ORDER CENTRE P.O. Box 321 North Ryde, N.S.W.

50 & 25 YEARS AGO

"Electronics Australia" is one of the longest running technical publications in the world. We started as "Wireless Weekly" in August 1922 and became "Radio and Hobbies in Australia" in April 1939. The title was changed to "Radio, Television and Hobbies" in February 1955 and finally, to "Electronics Australia" in April 1965. Below we feature some items from past issues.



December 1933

Radio City: New York's "Radio City", which opened on November 15, has a central tower 836 feet or 70 storeys high; the closely-placed upright steel pillars needed for such a tall building make it impossible to put wide studios there, so they have put the studios at the foot of the tower, in a building only 12 stories high. The 35 studios cover about 400,000 square feet.

The ninth floor claims the largest studio in the world -78×132 feet, and 35 feet high. On part of the 10th floor are four studios arranged like a clover-leaf around a control room; the floor of the control room moves round, so that television apparatus of the future may be quickly focussed into any of the studios through sound-proof glass.

Pedal wireless and the flying doctor: A feature article in the December 15 issue described the Australian Inland Mission flying doctor service which was then about five years old, a station having been established at Cloncurry in 1928.

☆ ☆ ☆

The system consisted of base stations transmitting voice messages to the outstations, with the outstations replying in Morse code. The outstation transmitters were powered by pedal driven generators and the Morse code characters were generated by a typewriter-like keyboard, to permit operation by unskilled persons.

Looking still further back: The December 1, 1933 issue reminded readers that this was the 10th anniversary of broadcasting in Australia. It reproduced the diagrams of two crystal sets and two one valve sets which had been presented in "Wireless Weekly" 10 years previously.

Two hundred metres and down: The British RAF is abandoning the long waves for the 20 to 100 metre band, especially for long-distance work in the East, using a special three-valve receiver with an amplifier employing two stages of screen grids in push-pull.

☆ ☆

Patent problems: As we go to press we learn unofficially that the STC-Philips-AWA patent-holding group is going to make a charge of 3/6 per valve socket, with slight reductions in certain cases. For the home builder a licence will be issued at half this figure - 1/9 per socket. So far it is not clear how this amount is to be collected, and at a glance it appears as though the collectors of the amount will have great difficulty in deciding whether a homebuilt set is being worked upon by an experimenter "with a view to furthering or improving the art". If a home builder can prove that he is an experimenter working in this manner, then it appears that he will be justified in refusing to pay any royalty at all.



December 1958

Birth of atomic timekeeping: Main exhibit at the recent "Pendulum To Atom" exhibition at the Goldsmiths Hall in London was the Caesium Atomic Clock.

Developed by scientists at the National Physical Laboratory, the atomic clock is so accurate that it loses only one second every 300 years and needs one gallon of water every minute to keep it cool.

It is possible to achieve this degree of precision because of the extreme stability of the fundamental properties of the atom, which are also independent of all external parameters, such as temperature, with the exception of magnetic field.

The National Physical Laboratory use the clock to calibrate the standard quartz oscillators.

So it's not new after all: A new radio broadcasting system that provides full stereophonic sound through a single receiver and dual speakers on the regular AM broadcast band was unveiled recently by the Radio Corporation of

The experimental system was demonstrated for the first time to an audience of broadcast station executives at RCA's David Sarnoff Research Centre at Princeton, New Jersey.

A standard AM signal is made up of a carrier wave and two symmetrical sidebands of slightly higher and lower frequencies to either side of the carrier. In the stereo system demonstrated to the broadcasters, each of the stereo channels is carried by one of these sidebands.

In the stereophonic AM receiver, the two sidebands are separated and fed to two speakers, left and right, to reproduce the stereo effect picked up at the studio.

The stereophonic receiver also can pick up non-stereo broadcasts and play them through either speaker or both, without any stereophonic effect.

(Editor's note: this would appear to be very similar to the present day Kahn system which uses upper and lower sidebands.)

TV relay satellite: A soviet satellite for relaying TV broadcasts appears to be in the planning stages. Such a scheme was recently described by scientist Druzhkin and engineer Sorin in the magazine "Knowledge Is Strength". They envision for Moscow a future audience taking in Europe, Asia, Africa and Australia.

Druzhkin and Sorin say a relay satllite should be fired to a height of 36,000 kilometres (22,350 miles), at which it would move at a speed equal to that of the earth's rotation around its axis; it would, in effect, hang over a given spot on the earth's surface.

They estimate two kilowatts are needed to power the transmitting apparatus. They propose to use solar batteries at first and switch later to small nuclear reactors.

Project Plowshare: Atom bombs for war will eventually give way to atom bombs for peace as we learn to use the huge explosive power to perform useful

It may be possible to rejuvenate old oil fields, open up vast deposits of low grade ores, and create huge underground water reservoirs for arid regions, all with atomic bombs.

This is the opinion of American scientists who are studying the results of deep underground atomic blasts that they touched off this year and last at their Nevada test site.

STORE LOCATIONS

	STURE LUC	AIIUN	9
NSW	Cnr. Swift & Young Sts	ALBURY	21 8399
	Parramatta Rd & Melton St	AUBURN	648 0558
	T55 Terrace Level	BANKSTOWN SQ	707 4888
	613 Princess Hwy	BLAKEHURST	546 7744
The state of	Oxford and Adelaide Sts	BONDI JCT.	387 1444
	531 Pittwater Rd	BROOKVALE	93 0441
	147 Hume Hwy	CHULLORA	642 8922
	162 Pacific Hwy	GORE HILL	439 5311
	315 Mann St	GOSFORD	25 0235
	4 Florence St	HORNSBY	477 6633
	Elizabeth Dr & Bathurst St	LIVERPOOL	600 9888
and the		NORTH RYDE	88 3855
		PARRAMATTA	689 2188
	The Gateway, High & Henry Sts		32 3400
	818 George St. 6 Bridge St	RAILWAY SQ.	211 3777
	125 York St	SYDNEY	27 5051
	Tamworth Arc & Kable Ave	SYDNEY	267 9111
	173 Maitland Rd	TIGHES HILL	66 1961 61 1896
200	263 Kiera St	WOLLONGONG	
ACT	96 Gladstone St.	FYSHWICK	28 3800 80 4944
VIC	260 Sydney Rd.	COBURG	383 4455
VIC	Nepean Hwy & Ross Smith Ave	FRANKSTON	783 9144
	205 Melbourne Rd.	GEELONG	78 6766
	399 Lonsdale St	MELBOURNE	67 9834
	Bridge Rd & The Boulevarde	RICHMOND	428 1614
	Springvale & Dandenong Rds.	SPRINGVALE	547 0522
QLD	293 Adelaide St.	BRISBANE	229 9377
		BURANDA	391 6233
	Gympie & Hamilton Rds	CHERMSIDE	359 6255
	Bowen & Ruthven Sts	TOOWOOMBA	38 4300
	Ingham Rd & Cowley St West End		72 5722
SA	Wright & Market Sts	ADELAIDE	212 1962
		DARLINGTON	298 8977
	Main North Rd & Darlington St		260 6088
WA	Wharf St & Albany Hwy		451 8666
		PERTH	328 6944
1		PERTH	321 4357
	TAS 25 Barrack St	HOBART	31 0800
1			



HOURS

All Dick Smith Stores are open for trading during the normal trading hours for their particular area (either 9-5.30 or 8.30-5). Many stores are also open for late night trading. Please ring the store concerned for their particular hours.



Terms available to approved applicants through.



MAJOR RESELLERS

SPEEDY PHONE/BANKCARD ORDER SERVICE

Just phone your order and Ba details - it's so simple!

(02) 888 2105

ORDER ONLY ON THIS NUMBER ENQUIRIES: (02) 888 3200


HEAD OFFICE AND MAIL ORDER CENTER: P.O. Box 321, NORTH RYDE, NSW 2113. TEL. (02) 888 3200

POST & PACKING CHARGES

ORDER VALUE	CHARGE	ORDER VALUE	CHARGE
\$5.00-\$9.99	\$2.00	\$50.00-\$99.99	\$5.00
\$10.00-\$24.99	\$3.00	\$100.00 or more	\$6.50
\$25.00-\$49.99	\$4.00		
Charges are for goods	sent by post in Austr	also only not aumail austra	on as soud femals

Dear Customers.

Quite often, the products we advertise are so popular they run out within a few days, Or unforseer circumstances might hold up shipments so that advertised lines are not in the stores by the time the advert appears. And very occasionally, an error might slip through our checks and appear in the advert after all, we're human too!). Please don't blame the store manager of staff, they cannot solve a dock strike on the other side of the world, or fix an error that's appeared in print. If you're about to drive across town to pick up an advertised line, why not play it safe and give the store a call first.....just in case.

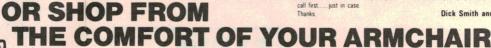

with our lightning fast fully computerised new mail order system.

Yes! Our mail order service has 'gone computer' offering you even faster, more efficient service than ever before—and (we believe!) much better than anyone else can offer.

Whether you choose to shop by mail, by our phone-in Bankcard order line (see above) or even by telex (No. 20036) you'll find it receives the personal attention that only our friendly, expert staff can give—plus the incredible speed and accuracy of our computer.

When you place your next order you'll find a special note enclosed telling you all about our amazing new system. We think you'll agree....it's pretty special!

MAKE YOUR XMAS DOLLAR GO FURTHER - USE DICK'S 'DON'T BE CONNED' CHECKLIST!

DICK'S 'DON'T BE CONNED' CHECK LIST

Watch out for the sneaky little 'plus sales tax' message hidden somewhere in the advert. All Dick Smith's prices

INCLUDE sales tax!

Watch out for hidden extras. Some people don't tell you the whole story - the extra (essentiall) bits you'll need. If any of our kits, etc, are 'short form' - we tell you so!

Watch out for guarantees - or lack of them! If there is one, can it be backed up? Dick Smith has a large, well equipped

3.

Service centre – just in case you have any problems!
Watch out for fly-by-nighters. There's always someone out to make a quick buck and disappear! Dick Smith Electronics is now in its sixteenth year... you can trust Dick Smith.

Dick Smith Electronics





Serious about soldering? Do it the right way with a temperature controlled soldering iron! Dick Smith Auto Temp!

Fully variable temprature control (approx 200C to 500C!)

● Lightweight iron ● Instruction manual ● Full Energy Authority approval Cat T-2000



SOLDER

1.25mm (18g) 200

0.71mm (22g) 200

grams Cat N-1619 \$550 grams Cat N-1623 \$550

Semi Automatic **Belt Drive Turntable**

Complete with base, perspex lid and quality magnetic cartridge. Belt drive for superb speed control, low 0.06% WRMS wow and flutter. Suits all modern hi fi amplifiers.

w 0 0 5

I A C V B W W C I D EXE

Cat A-3080 ONLY

D

0 W 1 D 1



[AM)



The last word in pocket calculators CASIO

FX-602 P PROGRAMMABLE

WAS

CALCULATOR 88 memories - 512 steps - full memory retension. An amazing 33 parenthetical levels, up to 9 sub-routines

and nestings. Cat Q-3110 NEW LOW PRICE!

\$199.00

NOW ONLY



QUALITY IC SOCKETS



For circuits that need top reliability (and isn't that all of them??) Use these deluxe gold plated IC sockets. As used in top computer systems, space shuttles, missiles etc.

10 or more:

Cat P-4314 Cat P-4316 \$1.50 \$1.30 16pin 22pin 40pin Cat P-4322 Cat P-4340 \$3.95 \$3.50

240V Lead & Plug \$4

Fantastic value for project builders: 1.8m 3-core cable complete w moulded plug save \$\$\$ ov with / save \$\$\$ over separate bits. Cat W-2057

QUALITY HSS DRILL SET \$4 550

At last! A high speed at last: A fligh speed steel drill set for all uses. Famous Frost brand (13 pieces) in handy plastic pack. A must for the hobbyist. Cat T-4801





Microwave Detector

alarm sensor that doesn't rely on opening doors, broken beams etc. It traps thieves in the act - as soon as they move, they're gone!! A brilliant 21 st century alarm system that's almost impossible to beat. Cat L-5000

ONLY

500

Bosch Digtimeter Unbelievable

Microprocessor controlled flexibility for all timing and switching functions like burglar alarms. industrial processors even swimming pool filters! Cat Y-1121

DON'T MISS 500 OUT IT'S JUST

Balanced Mic Cable Complete

NEW


Huge 20m length of quality mic cable fitted with Cannon-type plugs & sockets. Intended for sockets. Intended for balanced-type micro-phones, ideal for other types too. Cat W-1100

TOP \$0095 VALUE

AC DEL STOP

7 8 9

15 6

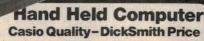

A brand new hand held computer from one of the world's leading manufacturers. The Casio PB100-learn as you go computer with VLSI CPU equivalent to 150,000 transisors! With 544 program steps and 94 data memories (expandable). 5 x 7 dot matrix 12 digit display and a standard 53 key keyboard

NEW WEN MODEL ONLY

1K RAM PACK Expands the PB100's \$40 memory to 1K, programming to 1,568 steps. A must for the serious user. Cat X-5112

WEDGE' SPEAKERS

Latest wedge-style speakers for the ultimate in car hi-fi sound. 3-way system, 4 ohms impedance (suits most car systems), handle a huge 50 watts max. Ideal for vans, trucks, 4WD's, etc tooreal home hi fi quality as you drive.

PAIR 7095



DICK SMITH WELLER Cordless Soldering Iron

ANNWHERE At Last! A portable Soldering iron. Comes with a built-in Ni-Cad battery that can be recharged from supplied charger, and a built-in light for those jobs that are in dark corners

Cat T-1050

\$5245

240V CANNON **PLUG & SOCKET**

Mains rated! Don't take chances with mains! If you haven't got room for normal 3 pin plugs and sockets, these genuine Cannon brand fittings are the

Line Plug Panel Socket Cat P-1627 Cat P-1630

\$695

\$595

FOR THOSE WITH LIMITED SPACE

ADHESIVE BACKED L

ONLY \$ 95

Invisible Speaker Cable System

Huge scoop purchase of unique home speaker wiring system. Under carpet, wallpaper, etc - 10m cable tape plus four plugs & sockets. Cat W-1288

IN LINE **FUSE HOLDER** (3AG)

90¢ Suits 3AG fuses, complete with 600mm ead at no extra charge. Spring loaded for sure

Extra High Grade **Ferrite** Rods 60¢

Cat S-4277

Small (40mm) lengths top grade ferrite. As used in Playmaster Amplifiers, suitable for huge range of







Will the real Murphy please stand up!

I was just re-reading some old numbers of EA, and on p107 of March 1975 EA I noticed another reference to Murphy's Law. I get the impression that most people think it is some kind of a joke; but now it seems that Murphy is a real person. He is Air Force Captain Edward A. Murphy Jr. who had a hand in designing the harness that held Major John Paul Stapp when they were trying to find the limits of human endurance to acceleration.

There were 16 sensors on the harness, and after one test they had all read zero. Someone had connected them all the wrong way round. This was the occasion for Murphy to state: "If there are two or more ways to do something, and one of these ways can result in a catastrophe, then someone will do it." The aim of Murphy's Law is that equipment should be so designed that it will be difficult, or impossible, to connect it wrongly.

The humorous popular version, with its fatalistic acceptance of the inevitable, perverts his original concept of a sort of moral to help prevent accidents.

The above information is taken, in some cases verbatim, from p78 of the Jan./Feb. issue of "Science 83".

Quite possibly others may have written to you about this, but there is also the possibility that they may not have done so. I think that not only is this an interesting piece of information, in view of the popular expression of Murphy's Law, but in its original form it is an adage worthy of being taken seriously by those who are concerned with the design of modern technical equipment. Maybe it would be good if Edward A. Murphy Jr. went down in history as more than just a joke.

Ronald W. Fiegert, Finschhafen, Papua New Guinea.

Valves resurrected...

So "Valves are Dead"! Then so must I be (see article on p94 of EA, September 1983). In the last year or two I have constructed eight or ten projects for myself and others. Of this number the following were valve devices: a communications receiver (10 tubes); a hifi tuner (10 tubes); an AF equaliser (3 tubes) (tubes are heated by DC, fed from a 2N3055 regulator); a regulated power supply (4 tubes); an 8MHz oscilloscope (11 tubes); and a 250W VHF amplifier (14 tubes).

Valves are not dead – all the foregoing things work! What is dead, of course, is the supply of coils for AM valve receivers.

Transformers can be arranged along the lines you have described — though there are other ways. Valves can be obtained too — there are several Australian suppliers, two in particular, who stock most of the major usage types of the last 50 years.

Might I comment on the Reinartz mode receiver – the old "three band two". Getting one of these to run

nicely is akin to learning digital electronics using a 6800 chip as a starting point. Running high slope pentodes like 6U8's or 6BL8's etc into a cathode coupled regeneration circuit is the thing of which parasitics and paranoia are born.

The real way to go for a two tube terror is to run a high slope mixer such as a 6AJ8 into a single IF transformer. The two coils in this will provide superior selectivity and gain compared with a regenerative horror. The signal thence proceeds to a diode high slope pentode such as 6BV7. Power supply under the Marquis of Queensbury (RF) rules can be diode rectifiers; after all, selenium rectifiers were used way back.

As I remarked earlier, the real problems are the three coils; aerial, oscillator and IF transformer. Winding the first two isn't too hard, but the IF transformer is a bit more painful. However, one of your regular advertisers (L.E. Chapman) still offers them. Also, they could be wound, at a pinch.

B. M. Byrne, Indooroopilly, Qld.

Comments on record reviews

I would like to support the plea for broadening the scope of your record reviews. Whilst not being one of the younger readers referred to I do include myself in the ranks of electronic music lovers and admit to a craving for more than perpetual pop or wallpaper music. Your reviews enable me to learn some of what is to be heard by way of non garbage without becoming a musician. But only just.

To argue for a certain type of music begs the question of how to define what is good, but I have been driven to despair by the apparent rule that if a track doesn't have a vocal in it then it is unbroadcastable. Having to endure vocalists that can't sing, opening their mouths and ruining what promised to be a very interesting track, I strongly support the idea of your column giving a little more attention to the instrumental scene

Such music is worth paying good money for but unfortunately recording companies and general retailers seem to be geared to the charts and if a release doesn't sell like hot cakes it is withdrawn. An artist daring to be different is battling and the discerning listener whose taste falls between the pops and classics has to be quick off the mark to catch it if indeed it ever finds its way into the typical local shop.

Each month I scan your reviews with a faint hope of picking up something different and now and again it pays off. But generally the selection is very narrow. Surely with a bit of prodding it might be possible to convince the industry that there is a market for up to the minute instrumental works if only the public knew the stuff had been recorded.

Ray Foster, Darlington, W.A.

The myth of Edison

I am surprised that the myth of Edison and the carbon filament electric light bulb has once again been published, this time in your September article on Nikola Tesla.

As far as I am aware, Edison got stuck with platinum filaments at the same time that Joseph Swan was demonstrating his carbon filament bulbs in lighting the Savoy Hotel in London. Swan was unable to sell his ideas in very conservative England, so he went into partnership with Edison in the Edison-Swan Electric Light Co., to produce the Ediswan lamps.

G. Nichols, Electrojac, Waiotemarama, Hokianga, New Zealand.

TO THE ELECTRONICALLY



• (Professionals, Hobbyists, Students & Enthusiasts.)

For over 40 years Radio Despatch Service has been serving the electronics industry. Our team of sales personnel can assist you with your requirements. We carry an extensive range of components, switches, batteries, connectors ... and the popular Texas Instruments Home Computer & Software.



MULTI-**METERS**

UNIVERSITY • FLUKE



CALCULATORS

- CASIO HEWLETT PACKARD • TEXAS
- INST

RADIO

869 George St., Sydney NSW 2000 (Near Harris St.)

> Tel. 211 0816 211 0191

Open: Mon-Fri 8.15am to 5.30pm Thursday night late shopping till 8.30pm Sat 8am to 11.45am




Instruments

TI-99/4 Home Computer

"QUALITY COMES FIRST" has been our trading principle for over 40 years. This enables us to give you the best in service and the ensuring durability in what you buy and best in products guarranteed satisfaction

MAIL ORDERS TO RADIO DESPATCH SERVICE 869 George St., Sydney 2000 Tel. (02) 211 0191 • 211 0816

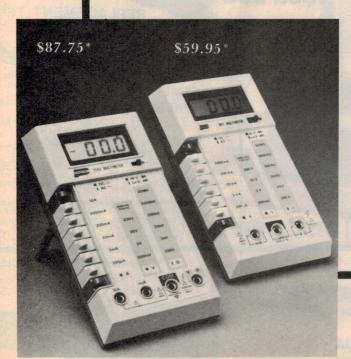A DMM you can be proud of . At a price you can afford!



Basic DCV accuracy 0.1% (7040) Battery life to 2000 hrs Brilliant quality LCD display Current ranges to 10A (7040) 3 1/2 digits

A breakthrough in price, performance and quality! Our new Models 601 and 7040 Digital Multimeters are superb quality instruments that will serve you faithfully for many years. They feature all the accuracy, facilities and rugged serviceability that you're ever likely to need. — At a remarkably low

Ask at your local stockist about the 601 and 7040 for unbeatable value.

*Prices do not include sales tax



PERFECTION IN MEASUREMENT Sydney 439 3288 Melhourne 580 7444

(Incorporated in Victoria)

Xvpar246



OUR COMPUTERISED INVENTORY SYSTEM AND LOW OVERHEAD ALLOWS US TO GIVE YOU FAST DELIVERY OF YOUR ORDERS AND LOWEST POSSIBLE PRICES.


130mm DUAL-TRACE TRIGGERED

SWEEP OSCILLOSCOPE Bandwidth

- Sensitivity
- DC ~ 15 MHz 10 mV/div
- Sweep Time 0.5 μs/div ~ 0.5 s/div

\$540 +\$10 Freight

● A vertical amplifier provides as wide a bandwidth as DC to 15 MHz, high a sensitivity as 10 mV/div. and a low input capacitance ● A sweep rate extends from 0.5 µsec/div to 0.5 sec/div in 19 ranges Further, TV vertical and horizontal syncs are available for measuring video signals and, with its x5 magnified sweep, its range of application is extremely wide ● Very easy X-Y operation of high input sensitivity for Lissajous measurements ● Dimensions: 260(W) x 190(H) x 385(D) mm; Weight: 8.4 kg

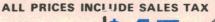



C10 Data Cassette Tape \$1.10
C20 Data Cassette
Tape \$1.20

MICRON 12

Green Phosphor Monitor Features: 12" screen. Front controls, on/off ront controls, on/on, contrast/reverse, bright-ness, Power: 240V/ 50Hz or 12V DC, Input: RCA type, DC Output Jack: 12V/1.1 Amp — power your Micro direct without a power pack, Randwidth: 10Hz to Bandwidth: 10Hz to 20MHz the resultant definition is truly amazing for a low cost monitor.



Adjustable Azimuth DATA CASSETTE

At last a Data Cassette
Recorder/Player you can
afford. The Micron D 1120
is fully adjustable azimuth
(absolutely essential in our
opinion) and incorporates
tailored audio frequency
response audio stage
together with low distortion.

POST AND PACKING CHARGES

	OUDER ANTOL	rar
POST & PACKING	\$5 - \$9-99	\$1.00
FOR GOODS SENT	\$10 - \$24-99	\$2.00
BY STANDARD	\$25 - \$49 -99	\$2.50
MAIL IN	\$50-\$99-99	\$3.00
AUSTRALIA ONLY	S100 OR MORE	\$3.50

MAIL ORDER ONLY (NO SHOP SALES)


VERBATIM VEREX 12 MONTH WARRANTY

51/4 SOFT SECTORED

\$35.00/10

S-Side **Double Density**



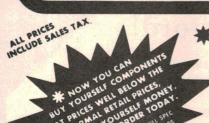

PRICES CORRECT AT TIME OF PUBLICATION **BUT SUBJECT TO CHANGE** WITHOUT NOTICE





SOLDER SUCKER

Quality de-solder tool with Teflon tip and nozzle sweeper.

REPLACEMENT TIP

\$1.25ea

case

P-80

QUALITY PRODUCT MADE IN JAPAN MONEY BACK GUARANTEE



LOWEST PRICED TOP QUALITY **BREADBOARD**

2N 200 + 640 Holes

\$9.50 each

MPIB51-\$312 MPIB52-\$422 MPIB91-\$510 MPIB92-\$594

PHONE FOR BEST PRICES ON MITSUBISHI SLIM LINE DRIVES & POWER SUPPLIES

Probe

Max Input 1.5 MHz

LEDs HI-LOW-PULSE

80cm leads KEY to LEDs on back of probe Input

Strong Aluminium

Impedance 300k

0

11.50 Logic

LOGIC PROBE

- * Directly powered from circuit under test (5 V)
- * Tested to 12.6 MHZ * DTL/TTL CMOS Threshold selector
- Circuit loading 30UA approx.
- * High-Low pulse or memory led indication. Impulse mode pulse length is extended to enable visual observation. In memory mode any detected level is continuously displayed until reset.



3800A

5" Drive Cases with power supplies

For 1 Drive \$55.00 For 2 drives .



MAII OPDED

MAII OPDED

RAAII ODDER

	MAI	L OR	DER	N	IAIL	OR	DE	R		MAII	L OR	DER	
7400 39 7400 39 7402 40 7403 48 7404 50 7406 55 7407 48 7408 48	74LS109 74LS112 74LS122	75 74S132 79 74S133 60 74S135 54 74S136 48 74S138 772 74S139 84 74S140 66 74S151	.84 4060 4063 1.27 4066 2.50 4068 1.20 4070 94 4070 45 4071	1.00 DS75 1.40 DS75 5.50 FD17 4.0 FD17 3.6 FD17 3.6 FD17 3.8 ICL7	454 .66 71 21.00 91 39.00 93 39.00 95 35.00 06 17.50	UA2901 UA3086 UA4136 UAA170 UAA180 ULN2003 WD1393	.96 .75 1.65 5.00 4.50 1.80 65.00	SH1605 UA317T UA317K UA309K UA494 UA7805 UA7805K	2.40 5.04 .84 2.16		TIP125 TIP127 TIP2955 TIP3055 2m301 2m697	.92 .22UF/35V .2 .99 .33UF/35V .2 1.60 .47UF/35V .3 1.87 1UF/35V .3 1.14 1.5UF/35V .3 4.30 2.2UF/35V .3 .59 3.3UF/35V .3	AIL
7410 48 7411 48 7413 45 7414 51 7416 60 7417 51 7420 48	74LS126 74LS132 74LS136 74LS138 74LS139 74LS151	745153 66 745157 45 745158 90 745161 72 745174 60 745175	1.30 1.40 1.40 1.20 4.80 4075 4076 4077	.35 ICL7 .34 ICL76 .36 ICM7 .86 ICM7 .34 ICM7 .36 ICM7 .34 L120 .80 L121	60 4.80 217A 17.50 218A 18.00 555 1.95 556 2.70 2.82	WD1691 XR2206 XR2207 XR2208 XR2211 XR2216 XR2240 XR2243	17.50 5.95 5.50 3.40 7.20 2.80 3.00 3.20	UA7806 UA7808 • UA7808K UA7812 UA7812K UA7815 UA7815K UA7818	2.38	AC188 1. AD149 2. AD161 1. AD162 1. AF127 1. BC107	10 2N2219A 70 2N2222 2N2222A 2N2369 2N2484	65 4.7ÜF/35V 5 10UF/35V 5 65 ELECTRO PCB 42 1UF/50V 1 60 4.7UF/25V 1 60 4.7UF/25V 1 96 33UF/25V 1)RD
7421 35 7423 40 7425 35 7426 50 7427 51 7430 50 7432 48 7437 54	74LS153 74LS154 74LS155 74LS156 74LS157 74LS158 74LS158	72 74S189 40 74S194 72 74S242 71 74S253 72 74S257 74 74S258 86 74S283	4.80 4086 1.86 4089 3.95 4093 1.40 4094 1.30 4099 1.40 4104	2.70 LF35 1.20 LF35 2.70 LF35 1.00 LF35 1.00 LF35	.62 .94 .5 1.66 .7 1.25 .8 4.75 .8H 6.50	8726 8728 8795 8796 8797 11090 95H90	2.34 2.76 2.20 2.30 2.30 14.00 14.50	UA7818K UA7824 UA7824K UA78H05K UA78H12K UA78HGKC UA78L05	2.38 .82 2.38 8.30 9.95 10.00 .46	BC108 BC108C BC109 BC109C BC177 BC178	35 2N2647 40 2N2894 35 2N2904 40 2N2905 40 2N2905A 42 2N2906 42 2N2907	30 30F/25V 1 2.50 47UF/25V 1 53 100UF/25V 1 73 220UF/25V 2 73 330UF/25V 3 73 470UF/25V 4 50 1000UF/16V 4 50 1000UF/25V 1 50 200UF/25V 1 50 200UF/25V 1	2
7437 54 7438 48 7440 48 7442 52 7444 1.60 7445 98 7446 98 7447 84	74LS161 74LS163 74LS164 74LS165 74LS170 1. 74LS173 74LS174	84 745287 84 745288 84 745289 91 74C00 74C00 74C02 75 74C04	2.90 5.00 4174 4175 4194 4409 4411	1.10 LH00 1.10 LH00 5.60 LM10 12.00 LM30	02 10.95 042CH 9.60 70-1H 15.90 71-1H 17.50 CH 6.50 4H 3.17	MICRO 2102 2112 2114 2532 2564 2708	2.40 8.00 2.50 6.95 16.50 8.00	UA78L12 UA78L15 UA78M05 UA78M12 UA78P05K UA78S40 UA7905	.50 .46 .82 .82 15.70 3.50 .96	BC212 BC318 BC327 BC328 BC546 BC547 BC547	25 2N2907A 18 2N3019 18 2N3053 18 2N3054 18 2N3055 12 2N3302 2N3440	69 ELECTRO AXIAL 225 470F/63V 21 1.30 10F/63V 21 53 2.20F/63V 21 1.13 3.30F/25V 22	
7448 1.60 7451 35 7454 35 7470 52 7472 41 7473 63 7474 51	74LS190 1. 74LS191 1. 74LS192 7. 74LS193 1. 74LS194 7.	74C08 74C10 74C10 74C14 74C20 74C30 74C30 74C32 74C32 74C32	.40 4469 .40 4495 .65 4500 .46 4502 .58 4503 .45 4507 1.30 4508	3.50 LM30 14.00 LM31 3.80 LM31 5.80 LM31 1.40 LM32 3.5 LM32 1.20 LM32	0 2.16 1-14 1.30 8 1.97 9 2.05 2 1.95 5 4.50	2716 27128 2732 2764 2816 2911 2912	4.95 55.00 6.80 9.50 40.00 32.00 22.00	UA7905K UA7908 UA7908K UA7912 UA7912K UA7915 UA7915K UA79HGKC	2.35 .96 2.38 .96 2.35 .98 2.38 16.90	BC548C BC549 BC549C BC550 BC556 BC557	12 2N3441 18 2N3442 12 2N3563 18 2N3564 18 2N3565 18 2N3565 18 2N3566 12 2N3567 12 2N3568	2.78 10UF/160V 31 18 10UF/16V 21 18 10UF/25V 22 18 10UF/63V 22 18 22UF/25V 22 18 22UF/63V 22 18 47UF/16V 22	IAIL
7475 .72 7476 .54 7483 .78 7485 .84 7486 .54 7489 3.50	74LS221 74LS240 1. 74LS241 1. 74LS242 74LS243 . 74LS244 1.	84 74C73 74C73 74C74 74C83 90 74C85 90 74C86 60 74C89	70 4510 -90 4511 2.20 4514 1.50 4515 5.50 4516	1.05 LM33 1.05 LM33 2.60 LM34 1.95 LM35 1.10 LM35 .96 LM37	4 1.60 5Z 1.63 6Z 1.55 9 1.80 8 .66 8AN 1.42 4 4.80	2920 4116 150NS 4164 150NS 6116P3 6502 6502A 6505 6507	120.00 2.96 8.95 9.90 10.20 10.80 13.50 9.60	UA79M05 UA79M12 OPTO 4N25 4N26 4N28 4N32	90 90 1.20 1.20 1.20 1.20	BC558 BC558B BC559 BC559B BC637 BC639	18 2N3569 12 2N3569 18 2N3638 12 2N3640 2N3641 42 2N3642 40 2N3643 40 2N3644	18 47UF/25V 2: 18 47UF/63V 2: 18 100UF/25V 3: 18 100UF/63V 4: 18 220UF/16V 2: 18 220UF/16V 2: 18 220UF/25V 3: 18 220UF/63V 6:	9
7490 .62 7492 .66 7493 .75 7495 .75 7496 .96 7497 1.50 74107 .40 74122 .72 74123 .66	74LS248 74LS249 1.74LS251 74LS253 74LS257 74LS258 74LS258	55 74C93 74C95 80 74C107 70 74C150 60 74C151 60 74C154 96 74C154	1.40 4519 1.60 4520 1.10 4521 4.10 4522 4.10 4526 2.90 4526 5.10 4528	.68 LM37 .96 LM38 2.60 LM38 1.50 LM38 1.25 LM38 1.25 LM38	7 2.30 0-8 1.20 0-14 1.10 1 2.05 2 1.75 3 2.05 6 1.10	6520 6522 6522A 6532	3.40 9.00 11.80 12.00 22.00 17.00 5.60	4N33 4N35 MCT6 MCT2 FND357 FND500 FND507	1.50 1.20 1.90 1.20	BCY70 BCY71 BD135 BD136 BD137	52 2N3646 64 2N3702 2N3704 55 2N3771 47 2N3772 2N3773 50 2N3819	18 220UF/63W 6 18 470UF/16V 4 470UF/25V 5 27 470UF/63V 8 1500UF/16V 8 1000UF/25V 8 1000UF/35V 9 2500UF/16V 1.1 2500UF/16V 1.1	ER
74123 66 74125 57 74126 67 74145 53 74147 220 74148 1.25 74150 1.92 74151 72	74LS273 1. 74LS279 74LS283 72LS290 74LS293 74LS298	45 74C160 10 74C161 55 74C162 74C163 60 74C164 81 74C165 84 74C165	1.30 4529 1.30 4531 1.50 4532 1.40 4534 1.50 4538 1.50 4539 1.65 4541 1.14 4543	1.30 LM39 1.50 LM56 6.00 LM56 1.60 LM56 .80 LM18 1.30 LM18	4CH 4.70 5 1.20 6 2.05 7 .90 30 3.20 86 6.00	6809 6810 6820 6821 6840	8.60 5.00 16.00 3.85 3.40 3.55 6.60	FND800 TIL31A TIL81 BPW50 CQY89 MOC3020 MOC3021	4.20 2.50 2.00 2.00 .75 2.90 2.98	BD233 BD235 BD236 BD237 BD238 BD262	50 2N3866 2N3904 55 2N3906 55 2N4032 72 2N4033 2N4033 2N4036 96 2N4121 96 2N4236	1.26 2500UF/25V 1.9 20 2500UF/50V 2.6 20 2500UF/50V 2.6 4700UF/35V 3.4 ELECTRO 85 METAL CAN 20 2500UF/80V 3.5 1.80 4000UF/75V 5.8	
74153 5.8 74154 2.16 74155 .78 74156 .83 74157 .66 74160 1.12 74161 .96	74LS365 74LS366 74LS367 74LS368 74LS373 74LS374	80 74C174 60 74C175 70 74C192 60 74C193 60 74C195 74C200 20 74C201	1.10 1.44 1.70 1.20 1.65 1.65 1.295 4558 4560		17-14 2.70 80 1.05 89 2.90 24 3.40 00 .84 05 1.60	6844 6845 6847 6850 6852 6854 6875	15.50 15.50 8.80 3.80 4.20 9.60 11.00	MAN72A MAN74A FCD820C FCD825C FCD850C FPT100B MSM3914 MSM3916	1.50 1.50 1.10 1.10 1.50 1.50 8.50 8.50	BD437 BD647 BD677 BD681 BD682 BDV64B	94 2N4236 62 2N4237 20 2N4250 81 2N4258 71 2N4355 71 2N4356 80 2N4401	1.25 5600UF/40V 4.1 21 8000UF/75V 8.9 27 ELECTRO 23 BIPOLAR 20 2.2UF/50V 3 .80 4.7UF/50V 3 18 6.8UF/50V 3	MA
74162 1.20 74163 .70 74164 .86 74165 .96 74166 1.32 74167 3.00 74174 .72	74LS377 1. 74LS378 74LS390 74LS393 1. 74LS447 1. 74LS629 4.	62 74C240 50 74C244 72 74C373 96 74C374 02 74C901 02 74C902 74C904 50 74C906	2.20 4569 4572 2.35 4583 2.60 4584 2.60 4585 2.50 4599 90 9300 90 9300 75 9302	1.20 LM39 .90 LM39 1.05 LM39 4.20 LM39 LM42	11 2.00 14 3.50 15 3.95 16 3.90 50 2.10 150 1.80 06 9.90	68B00 68B21 68B40 68B45	36.00 9.90 4.40 8.40 18.20 4.90 12.40 6.90	TLG123 SGS 3mm GREEN TLR123 SGS 3mm RED TL0123 SGS 3mm YELLOW	.16	BDY96 3. BDY97 3. BF115 BF167 BF173	50 2N4402 50 2N4403 75 2N4416 75 2N4427 70 2N5088 06 2N5089 78 2N5179	18 10UF/50V 4 18 22UF/50V 4 140 GREENCAPS 15 .001UF/100V 1: 27 .0015UF/100V 1: 56 .0022UF/100V 1: 66 .0033UF/100V 1:	0
74175 72 74176 1.20 74177 1.10 74180 1.02 74182 1.30 74184 3.50 74190 72 74191 1.20	74LS670 1. 81LS95 1. 81LS96 1. 81LS97 1. 81LS98 1. 74F00	74C906 74C907 85 74C908 85 74C910 74C911 74C912 74C914 98 74C915	75 9304 1.60 9307 12.95 9308 11.85 9309 12.50 9310 2.20 9311 1.95 9312	2.00 MC1 ⁴ 2.50 MC1 ⁴ 2.50 MC1 ⁴ .82 MC1 ⁴ 1.10 MC1 ⁴ 2.10 MC1 ⁴ .75 MC3 ³	1.56 1.80 1.66 14.00 1.66 14.00 1.66 14.00 1.60 14.00 1.80 1.80 1.80 1.80	8085A 8086 8088 8155 8156 8185	10.80 59.00 48.00 9.80 9.80 39.00 60.00	TLG113 SGS 5mm GREEN TLR113 SGS 5mm RED TL0113 SGS 5mm YELLOW Z0160	.16	BF198 BF199 BF337 BF458 BF459 BF469 BF470	22 2N5190 22 2N5191 2N5192 2N5193 70 2N5195 2N5210 95 2N5245	88 0039UF/100V 1: 98 0047UF/100V 1: 98 0056UF/100V 1: 0068UF/100V 1: 0082UF/100V 1: 010F/100V 1: 011F/100V 1:	DEI
74192 84 74193 96 74194 80 74195 67 74196 1.20 74197 94 74198 1.80	74F02 74F04 74F08 74F10 74F11 74F20	98 74C917 98 74C918 98 74C920 98 74C922 98 74C922 97 74C925 96 74C927	12:00 9314 1:90 9316 5:90 9318 5:60 9320 5:40 9321 7:80 9322 7:90 9324	.72 MM5 1.45 MM5	11.00 186 3.50 1116 1.70 66740 16.00 303 6.50 337 15.00	8206 8212 8214 8216 8224 8226	65.00 120.00 3.80 9.50 3.70 4.80 3.70	RECT. RED 20162 RECT. GREFN 20164 RECT. YELLOW FLS010 5mm LED CLIP	.25 .25 .25 .04	BFY50 BFY90 1 BU126 2 BU208 2 BU326A 2 BUX80 3	31 2N5303 69 2N5401 10 2N5457 90 2N5458 2N5459 90 2N5461 95 2N5485 45 2N5486	4.70 0130F100V 1 20 020E7100V 1 60 033UF100V 1 74 047UF100V 1 82 056UF100V 1 72 082UF100V 1 82 082UF100V 1	
74199 1.75 74221 2.10 74251 1.35 74279 .70 74283 90 74290 .90 74293 1.10	74F74 1. 74F86 1. 74F109 1. 74F138 1. 74F139 1. 74F151 1.	10 74C928 40 74C929 45 74C930 92 74C941 92 74C989 92 4000	6.80 9334 5.80 9338 6.12 9340 2.50 9368 8.60 9370 LINEAR ET	1.60 MN30 1.68 MSM 3.60 NE53 1.70 NE55 1.20 NE55	001 16.50 58372 15.00 0 2.30 8 2.25 1 2.40 34 1.50	8228 8231 8237 8238 8243 8251A 8253	47.00 11.90 7.90 8.50 9.00	DIODES IN4148 IN914 IN4001 IN4002 IN4004 IN4007	.05 .05 .06 .06 .08	MFE131 1. MJ413 4. MJ802 6. MJ1001 2. MJ15003 5. MJ15004 5.	45 2N5486 80 2N5590 90 2N5591 90 2N5770 2N5777 2N5873 50 2N5944 70 2N5946	17.80 1UF/100V 1 20.00 15UF/100V 1 19 22UF/100V 2 1.75 33UF/100V 3 15.50 47UF/100V 3 1UF/250V 8	
74365 .90 74366 .90 74367 .90 .74368 .90	74F158 1. 74F175 3. 74F181 5. 74F182 3. 74F189 8.	92 4000 92 4001 92 4002 12 4006 50 4007 00 4008 64 4009	35 AD570 AD7524 ADC0800 90 ADC0804 ADC0808 90 ADC0808 90 ADC0807 70 ADC0817	14.20 OM33 14.90 OM35 5.50 SAB0 12.60 SAK1 8.00 SN76	11 12.00 15 19.50 10 9.30 600 7.20 40 1.50 477 7.20	8255A 8257 8259 8271 8272 8273 8274	6.95 11.90 10.90 106.00 33.00 65.00 46.00	IN5404 IN5408 0A47 0A90 0A202 0A636 P600G	.24 .27 .46 .18 1.14 .96	MJ4032 9 MJ4035 11 MJ4502 5 MJE340 MJE350 1 MJE521 1	2N5961 20 2N6027 20 2N6084 80 2N6121 30 2N6122 22 2N6123 69 2N6124	25 3.3UF/250V 2.3 58 3.3UF/250V 2.8 22.00 6.8UF/250V 2.8 6.8UF/250V 4.4 77 10UF/250V 5.9 74 GREENCAPS 78 HIGH VOLTAGE	
74LS00 45 74LS01 45 74LS02 45 74LS03 45 74LS04 45 74LS05 45 74LS08 45 74LS10 45	74F191 4. 74F194 2. 74F241 4. 74F243 4. 74F244 4	27 4010 62 4011 58 4012 20 4013 66 4014 20 4015 34 4016 04 4017	62 ADC1210 35 AY-3-1015 35 AY-3-8910 48 BR1941 1.10 BR1943 96 CA3028 51 CA3036 CA3039	58.00 1A72 6.50 TCA2 10.00 TL06 11.50 TL06 12.00 TL07 2.52 TL07 5.76 TL07 2.05 TL07	20 10.50 1.40 2 1.80 1.30 2 1.70 3.60	8275 8276 8282 8283 8284 8284 8286 8287 8288	46.00 26.00 8.50 8.40 11.00 8.40 8.40 26.50	6A400V BAW62 BA102 0A91 0A95 IN3492 25A100V	.59 .30 .70 .27 .26	MJE800 MJE2955 2 MJE3055 2 MPSA05	61 2N6125 20 2N6126 20 2N6129 19 2N6130 19 2N6131 20 2N6133 20 2N696	81 01UF/630V 2 98 022UF/630V 2 140 033UF/630V 2 180 047UF/630V 3 180 1UF/630V 4 130 33UF/630V 4 130 33UF/630V 5	RDE
74LS11 45 74LS12 45 74LS13 45 74LS14 51 74LS20 45 74LS21 45 74LS26 45 74LS27 45	74F257 2. 74F258 2. 74F350 3. 74F352 2. 74F353 2. 74F373 4.	38 4018 38 4019 80 4020 38 4021 38 4022 78 4023 4023	96 CA3039 1.02 CA3059 60 CA3081 .84 CA3130 .96 CA31307 .96 CA31407 .72 CA3146	5.80 TL07: 5.80 TL08: 1.44 TL08: 1.74 TR16: 96 TR18 1.92 TR19 2.65 UA30	.60 2 1.40 4 2.70 53 6.70 83 9.95	8289 8291A 8292 8293 Z80CPU Z80ACPU Z80BCPU	35.00 47.00 38.00 29.00 5.40 5.90 11.20	1N3492R 25A100V .IN5060 BRIDGES VJ448 10A400V BR154	2.10 .35	MPSA42 MPSA56 MPSA92 MPF102 MPF103 MPF105 MRF237 4	27 284683 25 28C1017 56 28C1061 79 28C1096 79 28C1106 50 28C1226	70 CERAMIC 3.10 1 PF 0 .83 1.5PF 0 .86 2.2PF 0 4.80 2.7PF 0 .95 3.3PF 0	20
74LS30 45 74LS32 45 74LS33 45 74LS37 45 74LS38 45 74LS40 45	74F533 74F534 4. 74S00 74S00 74S02	98 4025 51 4026 4027 4027 4028 4029 63 4030 66 4031	36 CA3401 1.30 DAC0800 60 DAC0808 96 DAC1220 1.05 DM8121 59 DM8130 3.50 DM8131	3.20 UA30 2.50 UA30 12.50 UA31 2.50 UA31 2.50 UA32 2.95 UA32	1H 1.50 5H 1.50 8 1.70 1 .62 1H 1.60 4 .84	Z80P10 Z80AP10 Z80510 Z80A510 Z80CTC Z80ACTC Z80ACTC	5.15 5.80 14.50 16.00 5.30 6.50 15.50	15A400V BR254 25A400V BR354 35A400V P04 6A400V RS204	3.50 3.95 4.50 1.50	MRF475 6 MRF901 3 TIP31 TIP31A TIP31B TIP31C	2SC945A 2SD350A 2SJ49 2SK134 -3N201 SCR & TRIAC	39 4.7PF 0 3.30 5.6PF 0 6.50 6.8PF	MA
74LS42 62 74LS48 72 74LS48 72 74LS49 1.50 74LS51 45 74LS54 45 74LS55 45 74LS73 45	74504 74505 74508 74510 74511 74515	62 4033 60 4034 54 4035 60 4040 554 4041 63 4042 78 4043	1.95 DM8310 2.70 DM8310 1.20 DM8312 .90 DM8316 1.20 DS8820 .83 DS8830 .92 DS8833	.58 UA34 .58 UA55 .82 UA55 1.70 UA70 1.70 UA71 1.90 UA71	8 1.40 3 72 5 41 6 1.05 9 72 0 75 1 90	Z80ADMA 8741A 8748-8 8749 -8755A VOLT RFGS LM309H		2A400V INLINE SB204 2A400V W04 -1.5A400V ZENERS	.96 .75 .48	TIP41B 1	66 C103D 67 C106D 79 C122D 80 C122E 99 C230D 06 Q4010L4 Q4015L5 16 Q6010L5	1.75 22PF 2.30 27PF 6.80 33PF 1.90 39PF 2.70 47PF	8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8 8
74LS74 55 74LS75 55 74LS76 55 74LS83 72 74LS85 55 74LS86 45 74LS90 60	74\$20 74\$30 74\$32 74\$32 74\$51 74\$64 74\$74	52 4044 58 4046 62 4047 54 4048 63 4049 60 4050 65 4051	72 DS8836 1.20 DS8859 1.05 DS8869 5.8 DS75107 5.4 DS75108 5.4 DS75110 1.10 DS75150	1.50 UA72 2.05 UA72 2.05 UA72 1.26 UA73 1.58 UA74 1.50 UA74	3 60 3H 1.70 5 2.90 9 1.20 1 39 1H 1.15 7 1.20	LM350K	7.50 2.20 12.00 6.80 8.60 6.30 4.50 18.90	1N4733A 5.1V 1 WATT 1N4734A 5.6V 1 WATT 1N4736A 6.8V 1 WATT 1N4740A 10V 1 WATT	24 24 24 24	TIP42 TIP42A 1 TIP42B 1 TIP42C 1 TIP111 1 TIP112 1	93 Q6015L5 25 Q6025H 30 S4015L5 32 S4025H 04 SC141D 10 SC146D 17 SC151D	3.50 68PF 9.80 82PF 2.20 STYROSEAL	ORD
741593 .72	74586 745112 745113	84 4052 87 4053 00 4055	1.15 96 2.66 DS75451 DS75452	1.50 72 72 UA14 UA14	58 .55 88 .96 89 .96	LM79L05 LM79L12 LM79L15	.70 .67 .62	104742A 12V 1 WATT 105349B	24		45 ST2 ST4 TANTALUM 1UF 35V	150PF 630V 180PF 630V 29 220PF 630V	ER

MAIL ORDER

MAII ORDER

MAIL ORDER

MAIL ORDER MAIL ORDER MAIL ORDER





ORDER

MAIL ORDER



GREAT 40 WATT



GENERAL PURPOSE

Sults small appliances, le. Turntables, Tape Decks, Shavers etc. Variable frequency adjustment enables speed control of turntables. Works as a trickle charger when mains power is available. EASY CONSTRUCTION & VALUE PLUS



FLUORESCENT LIGHTING



Electronics Australia Project. Tests Bipolar Transistors, Diodes, Fets, SCR's and PUT's. Excellent service aid for the hobbyist and serviceman. Complete kit and instructions. K 2525

SATURDAY ARVO KITS

RADIO MIC \$6.50 K1106. ALIEN INVADERS \$13.95 SOUND BENDER K1492 \$29.50 COURTESY LIGHT EXTENDER \$3.95

SOUND EFFECTS PACK K1607 \$17.50 (CONTAINS PARTS FOR ALL 5 PROJECTS)

ACTIVE NOW STOCK A FULL RANGE OF KITS PHONE FOR FURTHER **DETAILS OF KITS AVAILABLE**

DIGITAL FREQUENCY METER See Electronics Aust. Mag. Dec. 81-Feb. 82 500 MHZ, 7 DIGIT RESOLUTION PLUS PERIOD MEASUREMENT FEATURE



IMPORTANT NOTES:

(1) This project is well within the scope of the "not so experienced" as virtually all components

re contained on a single PCB.

(2) USE ONLY THE SPECIFIED INTERSCIL LSI — BEWARE OF INFERIOR KITS THAT DO NOT CONFORM TO THE K 2501 Pre-scaler CORIGINAL DESIGN.

* Prepunched and screened front panel, no drilling or filling required. * Bright high efficiency 7 segment display. * Frequency ranges 0-10 MHz, 0-50 MHz, 10-50 MHz (with optional pre-scaler) * 4 gating times — 01, 1, 1, 10 seconds. * 4 period measuring ranges 1, 10, 100 and 1000 input cycles give 0.1 uS resolution. * High input sensitivity — 10 mV to 30 MHz, 100 mV at 50 MHz @ 1M input impedance, 200 mV at 500 MHz @ 75 ohms input impedance. * High accuracy — typically better than .005%/count uncalibrated.

Costs a fraction of commercial counters. EXCLUSIVE KIT FFATURES:

EXCLUSIVE KIT FEATURES:

IC sockets provided throughout, Low aging 10,000 MHZ XTAL. Thermalloy heatsink for 5V regulator. Quality Pactec Instrument Case with tilting

K 2500 (50 MHZ version). \$ 26.00 (add for 500 MHZ version)



Versatile, low cost and easy to build. Plugs straight into the microbee I/O port. Sultable for 2716, 2732, 2532, 2732A and 2764 Egroms. Burn your games programmes and eliminate cassette

your games programmes and eliminate cassette loading time.

KIT FEATURES & Sockets for all other IC'S & 1 x 2716 supplied — get started straight away & Front Panel and Mains (SEC approved) transformer & 28 pin and 16 pin wire wrap sockets to flush mount personality plugs (2 included) and ZIF socket (included) & DB 15 Plug & Complete to last nut and bolt.



BASED ON EA LM 317K PROJECT Every workshop, school and hobbyist should get one now!



Overload and short circuit protected \$39-95

Full voltage and current metering.
3-32 volt output at 1 AMP.
Uses LM 317 K variable regulator.

Full instructions and every last part included



Electronics Australia Project. Measures 1PF 99.99 UF. 240V Mains Powered. Bright LED Display. Easy to build. Complete kit of parts and full instructions.

K 2520 .

\$45

Shortwave Scene

by Arthur Cushen, MBE



FEBC operating from Saipan on shortwave

The Far East Broadcasting Company has begun operating from Saipan in the Northern Marianas. The shortwave service follows the introduction of a medium wave station and joins KYOI as a second signal from Saipan.

With the callsign KFBS and using 100kW, this is the first of five transmitters; a further transmitter will be delivered this month, while three more are expected to begin operation in 1984. KFBS's first 100kW transmitter was first used in 1942 as KGEX San Francisco and later was located at the VOA Okinawa transmitting site while the other four units to be installed will be new 100kW transmitters. The initial broadcasts are being carried on a three beam antenna system.

The tentative schedule is 0900-1100UTC on 15115kHz in Russian; 1100-1300UTC on 15150 in Mandarin; 1300-1400 on 9575kHz in Russian and 1500-1600UTC on 15110kHz in Ukranian.

FEBC Saipan has been operating for some months on medium wave as KSAI 936kHz, and has increased power to 10kW with the installation of a new 75 metre tower.

VOICE OF PEACE

Verification has been received of reception of The Voice of Peace operating from a ship located nine kilometres from Tel Aviv. Broadcasts on 6240kHz have been heard at around 2030UTC and according to Stuart Vint, Station Engineer, the transmitter is a home-made 400W unit. Plans are under way to increase the power to 10kW and use the present frequency to evaluate reception. The address of the station is The Voice of Peace, PO Box 4399, Tel Aviv, Israel, and the verification is a handwritten letter.

DIXON REACTIVATED

The Voice of America relay station at Dixon, California, has been reactivated after being in mothballs for several years. The site south of San Francisco was first used in 1942 for Office of War Information transmissions and in 1944 became a relay base for the Voice of America, with the major antenna

systems beamed on the South Pacific. Transmitters were extended and in 1969 when the writer visited the station new 250kW units were being installed. By 1976 the transmitting site had eight transmitters — three 250kW, one 200kW, two 100kW and two 50kW units. VOA Dixon operates 1130-1400UTC on 6040, 9540, and 11920kHz and at 0000-0300 on 9505, 11950 and 15250kHz to the Caribbean area.

AMERICAN NEWS

ARGENTINA: According to a report from Gabriel Ivan Barrera of Buenos Aires in the NZ DX Times, Radio El Mundo and Radio Splendid have ceased shortwave transmissions and now operate only on medium wave and FM. This will mean that 5985, 6120, 9710, 9740, 11755, 11880 and 15280kHz have been vacated and could be used by Radio Argentina Exterior.

BRAZIL: Radio Braz, Brazilia operates on 15290kHz with two transmissions in English 1800-1900UTC to Europe and 0215-0315UTC to North America. This new frequency provides good reception at 1900 after the English program when German is carried up to 1955UTC.

USA: KGEI San Francisco has been heard with a Russian broadcast on 9675kHz, opening at 0930UTC and switching to Japanese at 1130UTC with gospel programming to close-down at 1230UTC.

NEW BBC TRANSMITTING SITE

Plans for a £40 million transmitter site have been announced as part of a 10 year plan by the United Kingdom Government to increase the audibility of the External Service of the BBC. The intention of the program is to provide modern transmitters and antenna arrays of sufficient power to maintain improved reception qualities and keep abreast of the increased power used by the BBC competitors. One proposal is for an

expansion of the External Services of the BBC and the site will house six 300kW transmitters and 30 associated antenna systems about seven kilometres north of Stratford on Avon in Warwickshire. Because of technical problems the existing BBC sites at Skelton, Rampersham, Woofferton and Daventry cannot be extended. The Crowborough station which consists of two 100kW transmitters will cease to operate and the new transmitters will be operated by the Communications Engineering Department of the Foreign Office, which currently operates the Crowborough station and the relay bases at Cyprus and Masirah.

SCHEDULE CHANGES

AUSTRIA: Broadcasts from Vienna to Australia are 0700-0900UTC on 15270 and 17830kHz and 1000-1200UTC on 15420 and 17825kHz. English is carried at 0830-0900 and 1030-1100UTC. Transmissions to the Far East are at 1300-1500UTC on 15290kHz and 2100-2300UTC on 7170 and 9740kHz.

BELGIUM: Brussels broadcasts in English at 1915-2000 on 5985 and 15590kHz, 2200-2245UTC on 5895 and 9900 and 0030-0115UTC on 5910 and 9880kHz.

Notes from readers should be sent to Arthur Cushen, 212 Earn Street, Invercargill NZ. All times are UTC (GMT). Add eight hours for WAST, 10 hours for EAST and 12 hours for NZT.

DO YOU WANT TO BE A RADIO AMATEUR?

The Wireless Institute of Australia, established in 1910 to further the interests of Amateur Radio, conducts a Correspondence Course for the A.O.C.P. and L.A.O.C.P. Examinations conducted by the Department of Communications. Throughout the Course, your papers are checked and commented upon to lead you to a successful conclusion.

For further information, write to

THE COURSE SUPERVISOR W.I.A. (N.S.W. DIVISION)

P.O. BOX 1066 PARRAMATTA, N.S.W. 2150.

REVIEWS OF RECENT

Records & Tapes

CLASSICAL POPULAR • SPECIAL INTEREST



MENDELSSOHN

Symphonies Nos 4 and 5. Berlin Philharmonic Orchestra conducted by Lorin Maazel. DGG Resonance Series (analog) 2535 171.

I have a vague idea — which I have been unable to confirm — that when this performance was released many years ago it was thought in some quarters to be a rival to Toscanini's. This was in a period of almost mystic reverence for Toscanini.

The reason for this worship was that he could always be relied upon to play the music strictly as it was indicated in the score and on this his concentration was magnetic. But his sheer personal drive prevented any hint of coldness in his readings. One felt one was in the presence of controlled incandescence.

If this praise was merited it could easily have spoiled the talented young Maazel who, however, has continued, unaffected, to follow his brilliant career. Now for a few words about the Fifth. Mendelssohn was of Jewish stock though his father deserted his faith and turned Christian - to not much purpose to his son in later Nazi years. In 1962 I was in Hamburg and went to a very good restaurant in the basement of the Town Hall. There on the pedestal of one of the columns that support the building were engraved the names of famous German composers born in that city. In 1962 Mendelssohn's name had still been left erased. This is strange because the young Mendelssohn had embraced his new faith with all the excited enthusiasm of the convert. This is shown in the Fifth by his bold quotations from the Lutheran

litany in his music — the Dresden Amen at the beginning, a phrase also used by Wagner as part of the Grail Theme in Parsifal, and a fantasia, in the Finale, of the Lutheran hymn Ein Fest Burg is Unser Gott. The attestations of faith were almost truculently included in the score.

The first movement confirms this faith in the earliest bars followed by a fervent allegro recorded with a wide range which is never allowed to become unwieldy.

The dainty accuracy of the second movement is most alluring although some critics might find it a little facile. The Finale, the famous Lutheran hymn, is a fine technical achievement in its variety and ceaseless invention. The whole symphony is beautifully played and the sound, which I think must surely have been reprocessed, is excellent.

The Fourth Symphony (the Italian) is still popular and appears frequently on contemporary programs. Its first movement is invigorating, the playing beyond praise. The second is sometimes called the Pilgrims' March and at the pace taken here would have needed a brisk step. Marked andante con moto it is much more like a moderato. The third movement resembles a northern landler rather than a southern minuet. Nothing Italian here. But the Finale atones with a prestissimo Salterello, a Neapolitan dance much like a Tarantella.

The gay cover painting by Mendelssohn himself is pleasing if not very original. I strongly recommend the whole production. (I.R.)

JANACEK

Sinfonietta. Taras Bulba, Rhapsody for Orchestra. Vienna Philharmonic Orchestra conducted by Sir Charles Mackerras. Decca Digital Disc SXDL 7519.

As Beecham was to Delius and Sargent to Elgar and Boult is to Vaughan Williams, Mackerras is, at any rate to British ears, to Janacek. Mackerras spent the last years of his higher musical training in Czechoslovakia where he learned the language and the nature of the Moravian people well enough to appreciate the subtle effect of this tongue on Janacek's music.

His present recording is superior to that

he made some years ago. Mackerras now uses the composer's original score though if he had to get it from Janacek's almost indecipherable manuscript I pity him. The sound is therefore often much different from the first recorded version, first because of the unaltered music, and secondly because this one is digitally recorded.

The first "fanfare" movement comes off very well except for slight over-resonance in the drums until later in the movement when the trumpet theme is developed. Its unique style, right outside the general trend of central European music, is apparent in the first bar. The second movement is in complete contrast with its odd juxtaposition of themes. But then, under Mackerras, everything is contrasted in this powerful drive of a performance. Next comes the third movement, taken almost caressingly, despite its vast changes of tempos.

The ostinatos of the fourth movement give it a scherzo-like quality, yet in a way unlike it since Mackerras seems to be looking forward to a later period of musical development. In the Finale he brings everything together with brilliant panache. Strongly recommended.

I am equally delighted with Taras Bulba where Mackerras avoids a Sibelius-like desolate effect with the opening cor anglais solo by careful lyrical shaping of the line. The ensemble in the second movement is superb with the violent revengeful repeated figures snapping as if they had teeth. The Finale is right up to the standard of the previous ones and reflects great credit on all concerned with the production, orchestra, engineer and still more importantly conductor who demonstrates how he can bring the fiercest emotion to the music without sacrifice of lyricism. (J.R.)

MANTOVANI

EVERGREEN MANTOVANI. The Mantovani Orchestra. RCA Silver Sound Series. Digitally mastered stereo SSL-0004.

Everything was right for Mantovani in the '50s and early '60s, with a constant flow of rich melodies to match his singing strings, from composers like Gershwin, Kern, Berlin and Loesser.



But, say the jacket notes, the late '60s and '70s saw the entrenchment of rock 'n roll and a shrinking of the melodic maestro's options towards the "three B's" of popular music — The Beatles, Bacharach and Bossa Nova.

But things have changed yet again in the '80s, with renewed demand for melodic popular music and the emergence of high rating "good music" radio stations.

And now, of course, Mantovani also has access to digital technology and a better chance to cope with the "edginess" that can so easily mar the recording and reproduction of massed strings. This particular recording was made on 3M digital equipment, in Winnipeg, Canada, and custom pressed in virgin vinyl. There is certainly no surface noise and the sound quality is good but the modest dynamics of this kind of music provides no sonic drama to exploit the potential of the system.

But, if you're overdue for another infusion of the Mantovani sound, this one will give 12 tracks and a playing time of about 38 minutes: Evergreen (the title track) – Can't Smile Without You – Mull

Of Kintyre — What I Did For Love — Just The Way You Are — Annie's Song — I Write The Songs — You Make Me Feel Brand New — Nobody Does It Better — Let It Be Me — Plaisir d'amour — Weekend In New England.

Okay for pleasant listening but not a digital demonstration disc. (W.N.W.)



SYDNEY SYMPHONY ORCHESTRA

Conductor Patrick Thomas in a concert of short pieces by Offenbach, Delius, Schmidt, Weber, Haydn, Elgar, Scarlatti, Berlioz and Goossens. Made by the ABC for Philips, 410377-1.

Here's a local recording made by the ABC for Philips. The program consists of what Beecham would have called "Lollypops" as he referred to a similar collection of his own he made many years ago. The orchestra is the Sydney Symphony under talented conductor Patrick Thomas, the sound, indeed the production, under the supervision of that reliable expert Eric Clapham.

And very good it is. In all they play nine shortish pieces, with a very few exceptions very well indeed. Let's get rid of the gripes first.

I thought the end of the Delius Marche Caprice a trifle sharp in pitch. I thought the dynamic range so wide that at normal levels the softer parts of Weber's Clarinet Concerto are almost inaudible. I would have liked a very slightly lighter touch in the Good Humoured Ladies' Suite. At its present weight it tends ever so slightly to worthiness though the playing is never less than first class. I also thought some parts of Caractacus could have had a touch more brass.

Now for the very many good points. The band plays with exemplary accuracy, brilliant attack and release, good tone and unquestionable obedience to the conductor's many expressive turns of interpretations. These are everywhere apparent. A Berlioz Reverie and Caprice gets full treatment and a premier recording of Haydn's Overture to The Fisherwoman adds a note of respectability to the whole goodnatured exercise. The various soloists all acquit themselves splendidly.

And Eugene Goossens who must always be remembered as a most efficient musician finishes the whole excellent production with a set of variations, on a French folksong. It's all a credit to our resources. (J.R.)

COPLAND

Fanfare for the Common Man, Rodeo. Louis Lane conducting the Atlanta Symphony Orchestra. Digitally mastered stereo, Telarc DG-10078. [From P. C. Stereo Pty Ltd, PO Box 272, Mount Gravatt, Qld 4122. Phone (07) 343 1612.]

The very first sound from this disc, on

BILLCO ELECTRONICS

SHOP 2, 31 PULTNEY ST, DANDENONG 3175 PHONE: (03) 791 8655

Our range of printed circuit boards for all current E.A. & E.T.I. circuits and large stock of Components, Instrument cases, "Izumiya" P.C. Artwork, Single and D.S. Copper Board, Ristron Coated Board, Breadboard Systems, OK Wire Wrap Equipment, backed up by friendly helpful staff makes us the best one-stop electronic shop.

425 HIGH ST, NORTHCOTE 3070 VIC





PH METER \$129



OVER 200 NOW SOLD EA INVERTER INCLUDING TRANSFORMER 300 WATTS



Anywhere in Australia

Tacho/dwell meter with digital display







with probes

Eprom S55.00

Programmer JANUARY EA 1982 INCLUDES TEXTOOL SOCKET

SPECIFICATIONS FOR 300W INVERTER

Nominal Supply Voltage	
Output voltage	see table
Frequency	$50Hz \pm .005\%$
Regulation	see table
Maximum Load	300VA
Current Limiting	30A (primary)
Efficiency	see table

Resistive load W	Output voltage (RMS)	Input current (A)	Efficiency (%)	Battery life 40Ah/20h rate (minutes)
no load	210	1.2	0	
40	235	4.5	60	240
100	240	11.3	62	80
140	240	15.0	69	60
200	240	20.1	78	50
240	240	24.0	79	32
300	235	29.6	82	28



REMOTE INFRARED TV SOUND CONTROL



Designed to relieve the Designed to relieve the long-suffering TV viewer from painful, brain-killing advertisements, our TV Sound Control provides remote control of volume. It gives eight steps of control, including full off, when total silence is called for. Give yourself a break and relieve advertising tedium today.

540

STEREO SYNTHESISER FOR TUNERS AND **VCRs**

Enjoy the benefits of stereo sound from your video cassette recorder, TV or AM tuner with this Stereo Synthesiser. The circuit uses just four ICs and is easy to build.





Duel Tracking Power Supply


CHATH SP

EA POWER UP

\$38.50

EA NOV 1982

9,465

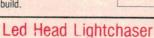



100w Sub-Woofer






EA DIGITAL READOUT FOR SW RECIEVERS

\$72.00 COMPLETE

OCTOBER FA 1982



OCTOBER EA 1982

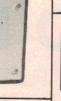



Want to add digital frequency readout to an AM radio or shortwave communications receiver that uses an old-fashioned analog dial? This unit features a bright four-digit LED display, 1kHz resolution, and a 0.2s update time that's fast enough to follow the tuning knob.

SPECIFICATIONS

Ranges (full scale): 0-10MHz and 10-30MHz (optional).

Display: Four digit

Resolution: 1kHz with division switch set to divide by one; 10kHz with division switch set to divide by 10.

Sensitivity: Less than 100mV from 500kHz to 30MHz.

Offset trequency: Prototype set to 455kHz, but any offset frequency can be programmed


EA THEREMIN

headband extra)

EA EASY-TO-BUILD

FREEZER ALARM

\$34.50

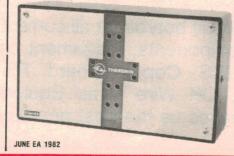

EA ELECTRONIC STARTER FOR



FLUORESCENT LAMPS

OCTOBER EA 1982

Records & Tapes Continued



side 1 track 1, is a huge transient from the drums, which thunders and shimmers in a way that cannot but fail to catch the ear of a hifi devotee; it's just so hard and clean. And "clean" is the adjective that best describes the whole of this recording, even though much of remaining sound is quite restrained, as throughout the Appalachian Spring Suite.

Born in 1900, Aaron Copland has frequently been described as the "dean of American composers" although Leonard Bernstein, who came to know him well, prefers to think of him as a father figure of American music.

"Aaron," he said "has a particular genius for taking raw elements - natural resources, so to speak - and making them into a serious language of his own.

"He's not partisan by nature. The one thing he's been partisan about all his life is the cause of American music. Aaron was always in the forefront of that parade."

In his generous jacket notes on the present recording, Steven Ledbetter points out that, until the middle of the last century, American music was synonymous with hymn tunes, theatrical songs and popular ditties, music for the home, for dancing and marching - all of it far removed from accepted "culture".

It was into that setting that Copland came.

The first item, "Fanfare for the Common Man", was composed during World War li in response toa commission from Eugene Goossens, then conductor of the Cincinnati Symphony Orchestra. It has proved the most enduring of the particular group of 10 fanfares, reviewed some time ago in these columns.

"Rodeo", composed as a ballet in 1942, was intended as a successor to Copland's popular "Billy the Kid" but it is most commonly heard nowadays, as here, as a four-part suite.

City bred, Copland borrowed from the traditions of the wild west for the four segments: "Buckaroo Holiday" with melodies from two popular songs; "Corral Nocturne", original atmospheric music; "Saturday Night Waltz", a touch of the genteel out west; "Hoe-Down", inspired by the square dance tune "Bonyparte"

"Appalachian Spring" (Suite) is Copland's own orchestral rearrangement of his popular ballet of the same name, originally scored for 13-piece chamber group. Listening again to the latter version on a 1978 3M digital recording, I tended to prefer it for the more open structure of the smaller group, but the fact remains that the Suite was acclaimed in 1945 as Copland's finest composition, being awarded the Pulitzer Prize for that year and the Award of the Music Critics Circle for the 1944/5 season.

Some may feel that the new recording has too much of the concert hall and not enough of the simple quaker farmhouse in the hills of Pennsylvania, where the original ballet was supposed to be set. But perhaps I quibble and, as I remarked earlier, the digitally mastered sound is very clean and, in itself, a reward for the technically minded listener. (W.N.W.)



BERLIOZ

Symphonie Fantastique. The Utah Symphony Orchestra conducted by Varujan Kojian. Reference Recordings 2-record set. Distributed by M. R. Acoustics, PO Box 165, Annerley, Qld 4103. Phone (07) 48 7598.

This two-record set is a little unusual in that it has been mastered to run at 45rpm which means that the symphony occupies three of the four sides. Rather than leave the fourth side blank (or with a 15-minute piece from Berlioz or some other composer) the recording company have elected to make it an extra copy of side three. The idea behind this is that audio enthusiasts will probably want to play side three more often and will thus welcome the extra copy. Hmm.

The reason for recording at 45rpm is to enable a larger dynamic range than would otherwise be possible using the standard 33rpm speed. In fact the jacket notes warn about the dynamic range and specifically about side three which contains the "March to the Scaffold" and "Dream of a Witches' Sabbath".

My experience was that, provided you do not turn up the quiet passages to the point where surface noise becomes noticeable, the dynamic range was handled without any problems by my system. But while I noted that surface noise is not a problem at usable volume control settings, tape hiss is noticeable if you are reasonably keen-eared.

Overall the dynamic range of the record is impressive but I found the balance between bass and treble too weighted towards the bass end of the spectrum. Violins lacked bite and trumpets lacked blare. I was a little disappointed in the performance of the orchestra too. Compared with other versions of the Fantastic Symphony that I have this one is too ponderous and slow. The bursts of frenzied passion and fury in the first movement, for example, are just not frenzied enough, in my opinion. (L.D.S.)

PICTURE OF THE YEAR

CAREFUL HE MIGHT HEAR YOU. Original film soundtrack album composed and conducted by Ray Cook. Stereo, Syme Entertainment Pty Ltd, L-38092. Distributed by Festival.

Adapted from a novel by Sumner Locke Eliot, the new Australian film "Careful He Might Hear You" is a joint production of the Syme organisation and the NSW Film Corporation. It was nominated for 13 of the 14 Australian Film Institute awards - indeed in all the categories for which it was eligible. It carried off eight of them, including the coveted Best Australian Picture of the

Music for the film was composed by Ray Cook, Australian born and educated at the Adelaide High School, the Adelaide Conservatorium of Music and the Sydney Conservatorium. Music has been his life ever since.

Following early but valuable experience with the Philip Street Theatre in Sydney and the Australian Broadcasting Commission (1956-1960), Ray Cook did the rounds of the main London theatres as Pianist, Assistant Musical Director, and Musical Director

Records & Tapes Continued

for a variety of major productions, directed productions in France, America, Canada and Australia, becoming involved also in ballet and TV drama production.

The film is about a 6-year-old boy "PS" (Nicholas Gledhill) who, following the death of his mother, becomes the victim of an emotional tug-o-war between two of his aunts (Wendy Hughes and Robyn Nevin).

It's a poignant story — or so I understand from those who have seen it — and Ray Cook's music has about it an introspective quality that permeates all the tracks, the titles of which summarise the film. I quote those on side 1:

Main Theme — PS Overhears Lila and George — PS and Lila — The Meeting — Vanessa's Mansion — PS Saying His Prayers — The Cricket Match — PS' Piano Practice — PS Meets His Father. Six more tracks follow on side 2.

As with most soundtrack albums, its greatest appeal will probably be to those who have enjoyed the film but, even outside that context, it can provide a pleasant orchestral background to everyday activities.

Recorded in the AAV Studios in

Melbourne, the sound quality is well up to normal standards. (W.N.W.)


TURN OFF TV AND RELAX!

NOCTURNE. James Galway, flute, with the National Philharmonic Orchestra conducted by David Measham. Stereo, RCA Red Seal ARL1-4810.

Recorded in February 1983, at the CBS Studios in London, this new James Galway release is made to order for relaxation, whether you choose to switch off and listen actively, or simply to switch off and let the sound create its own atmosphere.

You may have heard track 1, "Clare de Lune", so many times that it has become repetitive but, somehow, James Galway seems always to come up with arrangements and a refinement in presentation that imparts new interest to the classical evergreens that help make up this album:

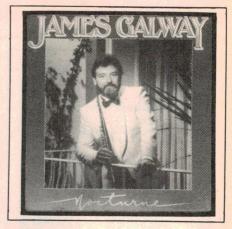Clare de Lune (Debussy); Nocturne in E-Flat (Chopin); Dreamers (Hamlisch); Pan and the Birds (Mouqet); Meditation from "Thais" (Massenet); Berceuse from the



"Firebird" (Stravinsky); Berceuse from "Dolly" Suite (Faure); En Bateau from "Petite Suite" (Debussy); Nocturne (Lili Boulanger); Nocturne No 5 in B-Flat (Field); Consolation No 3 in D-Flat (Liszt); Morning from "Peer Gynt" Suite (Grieg).

No statements are made on the jacket as to the technique or quality of the recording but the uniform level of these arrangements presents no special problems, anyway. Sufficient to say that the sound and the surface are both very clean, with no hint of noise or distortion anywhere.

It's a delightful recording, with a wide potential appeal. (W.N.W.)

Master the Microprocessor

Learn how Microprocessors really work the practical way.

The Purpose of this Course

There is a considerable. expanding and world-wide demand for people with a real knowledge of microprocessors and general computer technology. Such people are needed to design and evaluate systems and to assess and develop the enormous range of possible applications, both present and future, of microprocessors and to understand the installation and servicing of the main types of equipment of which they may form the most vital component. (A microcomputer has

(A microcomputer has already been produced to replace the mechanical programmer on a domestic washing machine, for example.)

example.)
This Course provides the necessary basic information to enable a student to really understand the functioning of microprocessors and their supporting circuitry,

usually referred to as the "hardware". This is backed up by showing how to program a microcomputer (or produce its "software") in the most fundamental form of computer language called "machine code", No previous knowledge of computers is necessary, though a little basic knowledge of electronics plus digital and logic circuits will be found helpful.

A special introductory short course is available to provide this back-ground information, if required by an individual student on the course without extra fee.


Student—Tutor Contact

A qualified Tutor is available to every Student throughout this Course in order to deal with any queries which may arise and to assess certain questionnaires which are issued to Students throughout the period of training.

Certificate

Issued to all Students completing the Course successfully. Course covers main requirements of the City and Guilds Certificates in Computers.

Practical Self Study Course

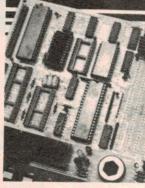

FREE COLOUR BROCHURE

Post coupon now: The Australian School of Electronics Pty. Ltd., P.O. Box 108, Glen Iris, Victoria, 3146. Offices at: 219 Balaclava Rd., Caulfield North.

Please send your brochure without any obligation to:

Name								
Addre	SS							

.Postcode.

How the Course is organised

The basis for the practical work in the Course is the Microcomputer. This is supplied completely assembled and ready to use.

use.
The Course text is carefully arranged in sequence so that each new section follows logically from previous work. Hardware description and programming technique progress together, so that the Student is discouraged from treating them as distinctly separate subjects. Following each section of descriptive text, detailed instructions are given in order to use the Microcomputer to provide a practical demonstration of each new function or technique. This provides a very powerful way of learning precisely how the

system operates, and

enables any possible ambiguities in the Student's

mind to be quickly resolved.

Sony PCM Adapter

... continued from p39

14 and 16-bit digital systems and are much better than comparable analog systems. The rapid increase in distortion above OdB is caused by the system running out of bits with which to encode the signal. This situation actually occurs at +0.8dB - the same level at which the overload warning is activated. Because levels above +0.8dB cannot be encoded, they are simply clipped off, resulting in rapid increases in distortion with further increases in signal level.

As expected, wow and flutter in the PCM-701ES output signal was too low to measure with out test equipment and for all intents and purposes may be considered zero.

Since the PCM-701ES must be teamed with a VCR of some sort, the ease with which the VCR tape transport controls work determines to a large extent the ease of using the whole system. For our review Sony supplied us with an SL-C9AS VCR which worked extremely well with the PCM-701ES.

During our review the PCM-701ES worked very well providing tapes which were indistinguishable from the original program source. One dropout did occur during playback of a tape, however since this was once only (it did not occur on subsequent playbacks) we can assume that it was due to a transient piece of dirt or oxide on the VCR heads. This did point up the need to keep the VCR heads clean since operation of the muting circuitry during dropouts puts quite a hole in the music and is much more noticeable than say a scratch in an analog system.


The PCM-701ES is available from hifi retailers who stock Sony equipment and carries a suggested retail price of \$1349. Further information may be obtained from a Sony retailer or from the head office of Sony (Australia) Pty Ltd at 453-463 Kent St, Sydney 2000. (J.S.)

Solution for November



Electronics Australia

DECEMBER CROSSWORD

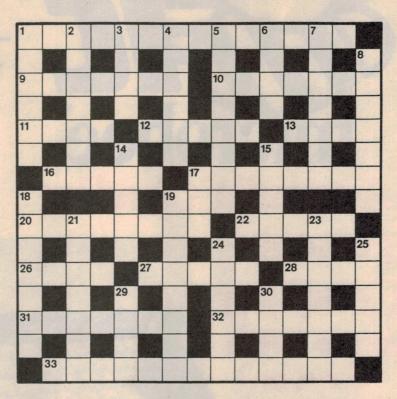

ACROSS

- 1. These are used in all solid-state devices. (14)
- 9. Having a phase difference. (7)
- 10. Scientist famous for his electromagnetic work. (7)
- 11. Name of an early passive satellite. (4)
- Magnetic unit. (5)
- 13. Metal sheeting. (4)
- 16. Name of a dark space in gas-discharge tubes. (5)
- 17. Likely place to find an electronic counter salesman? (6, 2)
- 19. Spectral hue. (3)
- 20. Fast method of data transfer. (8)
- 22. Said of resistors with linear relationship between voltage and current. (5)
- 26. Visible electric discharges. (4)
- 27. Relating to charged atoms. (5)
- One of a TV's guns. (4)
- 31. Electrons released from a cathode. (7)
- 32. Starting impulse. (7)
- 33. Rechargeable device. (9, 4)

DOWN

- 1. Joining alloy. (6)
- Units of resistance. (7) 3. Processed piece of a
- semiconductor. (4)
- What a metal-detector enthusiast hopes to find.
- Possible state of a semiconductor hole. (8)
- Prefix meaning a factor of 1012. (4)
- 7. Transmitted an RF signal.
- Graphical marks. (1-1, 5)
- 14. Unit of energy. (5)
- 15. What causes
- photoemission? (5)
- Unit measuring ratio of voltage, etc. (3)
- 18. Electro-acoustic device.
- 19. Made a reproducible store of data. (8)
- Pick up radio signals. (7)
- 23. Said of unlawful transmissions. (7)
- 24. Electronic network. (6)
- 25. Unit of inductance. (5)
- Prefix meaning a millionth 29. of pico. (4)
- 30. Substance used as dry cell electrode. (4)



Australia's leading

ersonal

Computer Now with **Jaycar** Dealer



AR ELECTRONI No. 1 FOR COMPUTERS.

Microbee features:

- 16K and 32K.
- Non-Volatile CMOS RAM.
- Programmable RS232 Serial Port.
- Programmable 8 Bit I/O Port.
- Display 64 x 16 and 80 x 24 screen format.
- 6545 Programmable VDU Driver.
- Cassette Interface, 300 and 1200 baud.



DIRECT CONNECT MODEM KEY FEATURES * DIRECT ATTACH AUTO ANSWER MODEM * 300 BPS FULL DUPLEX (CCITT V21) * 1200 BPS HALF DUPLEX (CCITT V23) * 75 BPS BACK CHANNEL (FULL V23) AUTO DIAL BELL FREQUENCIES INCLUDED TELECOM APPROVED 1 YEAR WARRANTY * NO ADJUSTABLE CIRCUITRY DESIGNED IN AUSTRALIA MADE IN AUSTRALIA THIS IS NOT A "TOY" UNIVERSAL DATA MODEM

ADAPTOR LEAD

You could simply plug this adaptor lead into your telephone socket if you were allowed to. It plits to two sockets. One for the YC-1350 Modem (special fitting) and the other for a telephone. No need to disconnect the phone ever! ONLY \$29.95

Jayr.ar has made a bulk purchase to bring them to you at the incredibly low price of \$399. Amazing value for a FULL DUPLEX unit.

MICROBEE CARRY CASE

Carry your MicroBee around without risking damage! Glittering brown vinyl rigid enclosure measures 355(W) x 245(D) x 75(H)mm. Incorporates the MicroBee logo emblem on box.

FANTASTIC VALUE AT \$12.50

information pricing

KITS-KITS-KITS-KITS-KITS-KITS-

ETI 733 RTTÝ Convertor. Ref: ETI April 1983. This simple project allows you to hook up your MicroBee to a HF receiver and print radio teletype messages on a monitor screen. Listen to world news for FREE!!

Cat. KE-4654

ONLY \$17.95

ONLY \$17.95
ETI 649 MicroBee Light Pen. Ref: ETI August 1983. This simple, low cost device plugs into the Bee's 8 bit port. The "pen" gives you an entry into the world of light pens and interactive software.

SHORTFORM \$19.50
SPECIAL PROBE CASE TO SUIT (as specified in ETI article) Cat. HB-6400 \$19.95

ETI 668 MicroBee EPROM Programmer. Ref: ETI February 1983. This simple, low cost EPROM programmer just plugs into the Bee's I/O port and enables you to save programs in any of the 5 different common EPROMs available (2716, 2532, 2732, 2732A, 2764). Kit comes complete with 'Personality' plug and all IC sockets.

\$39.95

Parallel Interface Kit for the MicroBee. Includes 15 pin 'D' plug — add \$15.00 if Centronics plug required.
\$15.00 Cat. KE-7017 \$15.00





ECTRONIC AGENCIES SOFTWARE & PERIPHERALS



DISASSEMBLER By Dreamcards
Some may say "Not another Disassembler". But
this one has a difference. It allows you to set out
where the data fields are so the computer is saving
time, not rying to disassemble data. A program
you shouldn't be without.
Cat. XE-6915 \$15.00

Two top quality programs for the price of one. The best Hangman we've seen yet on side A and a superb version of Bartleship on side B. Both have excellent graphics. have excellent graphics. Cat. XE-6920

CANNIBALS AND MISSIONARIES

CANNIBALS AND MISSIONARIES

The old logic problem game of transferring 3
Cannibals and 3 Missionaries from one side of a river to the other in a boat that holds two. If there are more Cannibals than Missionaries on either side at any time the Cannibals revert to their favourite form of feeding.

Cat XE-6925

\$14.95

COMPOSER BEE

This is a very well written program for music. This program allows you to compose, play, edit, transpose as well as being able to load and save your music. A program that has been a long time in the writing and well worth buying.

WORD ADVENTURE

WORD ADVENTURE

A program with very good graphics using little characters to entice the user to think what word is either a synonym, antonym or homonym of the word they are showing. Everytime you get it wrong you are given more clues. After the clues run out you must face the Dragon when you must spell the word he is holding correctly before you.

Cat. XE-6935

PONTOON

A quality fast moving card game where up to 6 players can play against the computer who is

MUSIC – B – MYTEK

MusicB is a music Composer/Editor that lets you create and save music and sound effects with a flexibility that makes chopsticks of the Basic PLAY command. MusicB is a great way to learn and play music! Comprehensive instructions are included. at XE-7010

TRSBEE - MYTEK

TRSBEE - MYTEK
TRSBEE is a package of three programs that loads TRS-80 Model 1 and 3 program tapes into the MicroBee without any additional hardware. Although some program editing will still be required prior to their running, the majority of program typing time is saved by TRSBEE. The first program loads TRS-80 BASIC programs into MicroWorld BASIC. Most prgrams may then be edited and run. The second program in the package loads any TRS-80 machine code file into MicroBee memory. The third program loads TRS-80 assembler files into the MicroBee EDITOR/ASSEMBLER. Any TRS-80 Model 1 or 3 tape may be loaded. TRSBEE opens up a whole new world of possible software on your MicroBee MicroBee! Cat. XE-7005

HOUSEHOLD REGISTER

This program will simplify the task of determing the value of your home's contents for insurance purposes, as well as providing descriptions of all listed items in the event of their loss or destruction. Effects are catalogued by name, description and value. Nine separate rooms are provided, and up to 28 items may be listed in each.

Cat. XE-7000

STAT PACK — STATISTICS

This program is a general purpose graph plotting, linear regression, line of best fit and correlation program. It features a t-test of significance for the correlation coefficient and, if no evidence of correlation is found, a determination of minimum sample size is performed.

BASIC TUTORIAL

Is a super teaching aid for any classroom. Basic Tutorial is a set of 9 interactive exercises designed for teaching Basic to the computer novice. No previous knowledge is assumed. Basic Tutorial uses a unique double screen technique to display uses a unique double screen technique to display both the normal computer output and the tutorial exercises at the one time. This allows the student to use the MicroBee in the normal way, while the tutorial instructions appear in the lower half of the screen.

Cat. XE-6880 \$20.00

MACHINE CODE TUTORIAL - MYTEK

MACHINE CODE TUTORIAL – MYTEK
consists of 8 interactive exercises designed for
teaching machine code programming and related
topics as they apply to the MicroBee computer.
Only a general knowledge of the BASIC language
is assumed. Machine Code Tutorial is designed to
bridge the gap bewteen BASIC programming
and being able to understand and use typical
Z80 manuals.
Cat. XE-6855 \$25.00

This program is designed to speed up and simplify the task of framing a usable financial budget. Applications range from personal or household to small business finances. A quality program. Cat. XE-6850 \$15.95

Basic decoder and listing formatter
This programme will be an invaluable aid to any one taking first steps in understanding machine code or wants to expand their library of proven machine code routines. Decode will (a) print imbedded machine code routines fully and accurately (b) print all unprintable characters (c) provide a clearer, easier to read listing and send all output to a printer if so required. ED ASM is not required.

Cat. XE-6765 \$15.95

This program is a well written data base manage ment system that utilised the MicroBee to its fullest to provide a Data Management System similar to those found on larger and more expensive systems. This comes complete with large bound manager.

Asteroids Plus is one of the finest high resolution graphic arcade games available for the MicroBee computer. It features 3-D point by point resolucomputer. It reatures 3-D point by point resolu-tion graphics, shields, sound effects, intelligent objects, guided missiles, black holes and a score board. If you enjoy playing computer games, you will be captivated by Asteroids Plus. Cat. XE-6297 \$22.50

ASTEROIDS PLUS - MYTEK

BEEZ 80 - MYTEK

This secret code disassembler will disassemble any code sequence. Nothing is illegal. It will allow you to program with codes that no other disassembler can decipher!

SPACE INVADERS

One of the most popular programmes ever released. This version was written especially for the Micro-

A new language for the MicroBee. Comes complete with interpreter on one side of the tape and supporting programs on the other side. As well as this it includes a very well written, bound

PSYCHOTEC By Dreamcards

Psychotec provides a striking example of artificial intelligence, allowing a dialogue in English between computer and operator, the computer playing the role of psychiatrist and the operator being a "patient" on the couch. Leaves other "similar" types for dead.

Cat. XE-6875 \$15.95

MERLIN By Dreamcards

MeHLIN by Dreamcards
Merlin is a 32K adventure set in England during
the dark ages. Your task is to search through the
dark forest inhabited by robbers, outlaws and
creatures with awesome magic powers to find a
legendary sword. An excellent adventure.

Cat. XE-6870

\$25.00.

PROGRAMMING HINTS

Consists of a collection of modules which you may use to improve your own BASIC programs. They are all linked together under a menu driven display which allows you to RUN or LIST each module to see how they work.

Cat. XE-6895

LOG - GENERAL PURPOSE INDEX

This program is designed to suit a wide range of records where indexing (and later searching) can be on one or two words, or on a string of up to 15 characters. Each record consists of its index heading, plus up to 12 lines of text. Each line can contain up to 41 characters.

Cat. XE-6890 \$15.95

"You are a tank running around a maze gathering all the supplies you can. It sounds easy, but you have a guided missile hot on your trail. Your only defence is a remote controlled mine which you drop and explode at will. A very fast joystick or key controlled game. Cat. XE-6960

PENETRATOR

A low resolution graphic version of the popular game "Scrambler". You must defeat the rockets and bomb the radars in an effort to get to the next stage which is even harder. This game can be either controlled by a Joystick or by keys. Being in Lores graphics it is a very fast game. If you are bored with the same land pattern you can devise your own.

SPACE PATROL

A lot like Penetrator but in high resolution graphics. You must battle your way through the various stages where at the last stage you have four chances of blowing up a neutron bomb shelter. If you are successful, the next round is

METEOR RESCUE - MYTEK

METEOR RESCUE – MYTEK
Your mission is to rescue stranded astronauts.
You are the commander of the Landing Module
docked in space with the mother ship. It is your
responsibility to guide the landing module
through a meteor field, down to the surface of
the planet, to land safely on a landing pad. An
astronaut will then run to your landing module
and you will blast off. You must use your lasers
if necessary and dock with the mother ship
again. A total of six astronauts must be shuffled to the mother ship.
Cat. XE-7020
\$17.50

CORVILLE CASTLE

Corville Castle is an adventure which will take you to a far away place of mystic castles, fierce monsters and evil warlocks. You must enter the warlocks castle and find some dark secret which will help you to destroy the warlock. But remember, you only have until dusk.

Cat. XE-6285

DEFENDER

for the MicroBee Computer

Fast Furious Action Game



DEFENDER - FROM MYTEK

This long awaited program is finally available. Defender needs no introduction. The Defender arcade game is one of the most popular ever produced and the Mytek version is brilliant, a rival for Asteroids Plus.

Cat. XE-7036

DESTROYER

\$22.5i \$22.50 DESTROYER

Pour are the UFO and you must destroy the enemy city buildings before you can land. You have no control over the UFO except for the three bombs on every pass you make over the city. But beware the UFO gets lower with every bass. Good graphics and sound.

Cat. XE-7048

\$22.50

\$22.50

\$22.50

\$4.95

COULOMBS LAW

This program is another in the series of Physics simulations. The first part is a tutorial and the second is a simulation of the experiment.

Cat. XE-7049

BACKGAMMON – FROM MYTEK

This game conforms exactly to that set down in the official rules of the International Backgammon Association, including the rules of doubling

Two programs to help make life easier for the Pools and Lotto enthusiast. The first program chooses your numbers for the week and the second program allows you to input your numbers into a program and when Lotto night arrives you can input the winning numbers and the computer will check your Lotto for you.

S14.95 POOLS AND LOTTO

This program allows you to input 20 words and the computer will create a Wonder Word puzzle. This can be either sent to a printer or solved on the screen or let the computer solve it. Just the program for Wonder Word GEO-TECH DRAWING

This is the first tape in a series to assist students in grasping the fundamentals of geometric and technical drawing. It uses good graphics with excellent explanations.

Cat. XE-7047 \$14.95

Incorporating

ELECTRONIC AGENCIES

SHOWROOMS

117 YORK STREET - PHONE: (02) 264 6688 and 267 1614
TELEX: 72293

Cnr. CARLINGFORD & PENNANT HILLS ROAD - PHONE: (02) 872 4444

115 - 117 PARRAMATTA ROAD - PHONE: (02) 745 3077

121 FOREST ROAD - PHONE:

NUMBER 1 FOR KITS

POST AND PACKING CHARGES \$5 - \$9.99 (\$1.50) \$10 - \$24.99 (\$3.20) \$25 - \$49.99 (\$4.50) \$50 - \$9.99 (\$6.50) \$100 - \$198 (\$8.00) Over \$199 (\$10) ree INSURANCE for Road & Registered Post over \$200" bulky items (over 20kg.) sent Comet Road Freight \$12.00 anying the sent of t

in Australia.

SHOP HOURS CARLINGFORD, CONCORD & HURSTVILLE
- Fri 9am — 5.30pm: Sat — 9am — 12pm: Thurs night 8.30pm
SHOP HOURS SYDNEY
- Fri 8.30am — 5,30pm. Sat — 8.30am — 12pm: Thurs night 8.30pm

MAIL ORDERS AND CORRESPONDENCE: BOX K 39 HAYMARKET, SYDNEY 2000



Micronews

New portable is a world beater

The most significant new computer of 1983 would have to be the Dulmont Magnum. With a full 16-bit processor and up to 256K bytes of RAM in a portable, battery-powered package the Magnum is an exceptional product by world standards — designed and manufactured in Australia.

President Computers will be distributing the Magnum through their 187 outlets nationwide. Managing director Tom Cooper goes so far as to say that the Magnum will establish Australia as the leader in the portable computer market. Certainly the development and production of the machine is a landmark for the Australian computer industry.

The Magnum computer is a "briefcase portable" measuring $305 \times 280 \times 50$ mm (W × D × H) when the LCD screen is folded down over the keyboard. The processor is the Intel 80186, an upward-compatible enhancement of the 8086 with a two-channel DMA controller, three 16-bit timers, interrupt controller, bus controller and clock circuit on the chip.

Essentially the 80186 provides significantly improved performance over the 8088 and at the same time reduces the manufacturing costs of the system.

The liquid crystal display of the Magnum is mounted in the front half of the top cover, which can be locked in one of a range of positions to allow the best viewing angle. The screen displays eight lines of 80 characters each, with fully-formed upper and lowercase characters.

In conjunction with the compact, typewriter-style keyboard the LCD screen makes the Dulmont Magnum a true "go anywhere" computer. Twelve user-definable function keys and a "Help" key integrated with the software available for the Magnum, allow a "menu-driven" approach which is certain to appeal to new users.

The operating system of the Magnum is MS-DOS 2.0, and various applications programs are contained in 128K bytes of internal Read Only Memory. As standard the Magnum comes with word processing software, an electronic spreadsheet program, a planner/diary based on the internal clock and calendar of the machine, and Basic-86 for those who wish to write their own programs.

Optionally available will be an accounting package and an engineering planning and calculation package, plus

other software running under MS-DOS. Two 128K byte ROM packs can also be plugged above the keyboard, allowing the on-board software to be further expanded

Peripherals and expansion capacity have not been ignored. Two RS-232C serial ports and a Centronics parallel printer port are included as standard, together with a video output which supplements the LCD screen with an 80 × 25 line display on a video monitor. IBM-PC compatible dual double-sided 13cm disk drives will be available in an expansion interface which also includes an additional 256K bytes of RAM and a power supply for the system.

Another expansion box is under development with an eight slot motherboard which will take IBM-PC expansion boards. The intention is that anything which can be added to the PC will be compatible with the Magnum hardware.

Manufacturer of the Magnum, Dulmont, is jointly owned by Dulmision, a leading Australian supplier of electrical power line fittings, and Tramont, a subsidiary of the Belgian Tractionel group. Dulmont was formed in May this year when it became clear that the Magnum project would require substantial funding and international

80 Micro programs on cassette

LOAD 80 is a "magazine on cassette" containing the programs which appear in each monthly issue of the US "80 Micro" magazine for the TRS-80 Model 1, Model 111 and System 80 computers.

A companion cassette, "COLOR LOAD 80", appears quarterly and contains Basic and machine code programs for the TRS-80 Color Computer. Each cassette contains on average 20 ready to run programs.

LOAD 80 and COLOR LOAD 80 cover new screen routines, games, business programs, utilities and educational programs. Both are now available in Australia at a recommended retail price of \$19.95 from Australia Computer Software, PO Box 450, Malvern, Vic, 3144. Phone (03) 20 4947.

backing if it was to be marketed in a manner suited to the unique new concept.

Printronics did the circuit boards, chips came from overseas, and research and development was initially supported by a \$350,000 grant from the Department of Science and Technology.

As a result of these combined efforts the Magnum is set to make a considerable impact on the portable computer market, both in Australia and overseas.



SOME COMPUTERS ARE BETTER THAN OTHERS

	SPECTRAVIDEO SV 328	SPECTRAVIDEO SV 318	APPLE II E	ATARI 800	COMMODORE 64	BBC MODEL B	DRAGON 32	SPECTRUM
COMPUTING POWER FEATURES BUILT-IN ROM EXPANDABLE TO BUILT-IN EXTENDED MICROSOFT® BASIC BUILT-IN RAM EXPANDABLE TO	48K	32K	16K	10K	20K	16K	16K	16K
	96K	96K	N/A	42K	N/A	64K	N/A	N/A
	YES	YES	YES	ADDITIONAL CO	ST NO	NO	YES	NO
	80K*	32K***	64K	48K	64K	32K	32K	16K
	256K**	256K**	64K	NO	N/A	32K	64K	48K
KEYBOARD FEATURES NUMBER OF KEYS USER DEFINE FUNCTIONS SPECIAL WORD PROCESSING GENERATED GRAPHICS (FROM KEYBOARD) UPPERILOWER CASE	87	71	63	61	66	73	53	40
	10	NO	N/A	4	8	10	N/A	N/A
	YES	YES	NO	NO	NO	NO	NO	NO
	YES	YES	NO	YES	YES	YES	YES	YES
	YES	YES	YES	YES	YES	YES	YES	YES
GAME/AUDIO FEATURES SEPARATE CARTRIDGE SLOTS BUILT-IN JOYSTICK COLORS RESOLUTION (PIXELS) SPRITES SOUND CHANNELS OCTAVES PER CHANNEL A.D.S.R. ENVELOPE	YES	YES	NO	YES	NO	NO	YES	NO
	NO	YES	NO	NO	NO	NO	NO	NO
	16	16	15	128	16	16	9	8
	256x192	256x192	280x160	320x192	320x200	256x640	256x192	256x192
	32	32	N/A	4	8	?	16	?
	3	3	1	4	3	1	3	?
	8	8	4	4	9	3	5	3
	YES	YES	NO	NO	YES	YES	NO	NO
PERIPHERAL SPECIFICATIONS CASSETTE AUDIO 110 BUILT IN MIC DISK DRIVE CAPACITY (LOW PROFILE)	2 CHANNEL YES YES 256K YES	2 CHANNEL YES YES 256K YES	1 CHANNEL NO NO 143K NO	2 CHANNEL YES NO 92K NO	1 CHANNEL NO NO 170K NO	2 CHANNEL ? NO 100K NO	? NO ? NO	? NO ? NO
CPIM® COMPATIBILITY (Standard 80 column CPIM® 22 programs) CPIM I*	YES YES	YES YES	NO**** NO	NO NO	NO**** NO	YES NO	NO NO	NO NO

Specifications are subject to change without prior notice Microsoft is a registered trademark of Microsoft Corporation CPIM is a registered trademark of Digital Research, Inc. * 64K user addressable plus 16K graphic support
** 240K user addressable plus 16K graphic support
*** 16K user addressable plus 16K graphic support
**** Apple II can accept modified 40 or 80 Column CP/IM
***** Commodore 64 accepts 40 column CP/IM

OURS IS MUCH BETTER

When you start comparing Spectravideo's SV-318 to other personal computers, you'll find there really is no comparison. The SV-318 is the only logical choice, because it does more than some computers costing 4 times as much. And its abilities simply embarrass other computers in this price range.

The SV-318 isn't just more capable. It's <u>much</u> more capable. No other computer at even <u>twice</u> the price comes near its 32K ROM expandable to 96K. Or to its 32K RAM expandable to 144K. And no other computer has a built-in joystick/cursor control—an immeasurably useful feature when it comes to playing your favorite video game. Further, the SV-318 has, as its resident "language" Extended Microsoft Basic, the industry standard. It even has built-in CP/M (standard 80-column program), so you can immediately utilize over 10,000 existing software programs.

The SV-318 isn't just more expandable. It's much more expandable. Unlike many other so-called computer systems, all our important peripherals are available at once. That means you can get almost full usage out of your SV-318 from the day you buy it. With the Super Expander, Data Cassette, Floppy Disk Drive, Dot Matrix Printer, Graphic Tablet and SV-800 Series Expansion Cartridges, there's almost no end to the work you can do. Or to the fun you can have. The SV-318 is well designed to interface with new options as they become available, too. All this adds up to a computer you'll grow into, not out of.

The SV-318 is not only eminently affordable, it's the first real bargain of the computer age! Besides business application, home budgeting, word processing, programming and self-teaching, the SV-318 is the best entertainment value in town. Not only can you use it with your TV or color monitor to play hundreds of different video games,



FOR UNDER \$500

with the optional SV-105 Graphic Tablet you can draw pictures, graphs, charts and other visual images on your TV screen. Considering what you get for what little you pay, the SV-318 is once again the only logical choice.

Whether you're investing in your first computer, or are already well versed in today's most important machine, you'll find that the SV-318 is the only logical choice for you.



VIC: 70 St. Kilda Road, St Kilda, 3182 Ph; (03) 537 2000 N.S.W.; Box 474, Edgecliffe, 2027 Ph; (02) 328 1190, W.A.; Jerdon Agencies, 25 Gladstone St., East Perth, 6000 Ph; (09) 328 5299 QLD: Franklin Agencies, 3 Marie St., Milton, 4064 Ph; (07) 369 0496 TAS; Dennington Enterprises, 46 Canning St., Launceston, 7250 Ph; (03) 318 551, S.A.; Ben Marcus, P.O Box 2470, Adelaide Ph; (08) 211 7766

Micronews

IBM PC to be made in Australia

IBM has announced plans to produce its Personal Computer in Australia. A plant in Wangaratta, 220km north-east of Melbourne will be converted for PC manufacture.

Since the IBM PC was released late in 1981 it has taken over 25% of the world market for personal computers, with estimated sales of over one million units. Sales in Australia, though, have not been up to expectations and this may be one reason behind the decision to set up manufacturing here.

Wangaratta will join Boca Raton, Florida, and Greenock, Scotland as PC production centres and will be used to supply markets in Australia, New Zealand and South-East Asia.

Announcing the plan, Mr Brian Finn, managing director of IBM Australia, said that local manufacturers could supply about 25% of the components of the Personal Computer. IBM has stated that it will purchase an estimated \$27 million worth of computer components from Australian manufacturers over the first five years of the plant's operation.

Along with hardware manufacture IBM will also set up a software centre in NSW which will acquire products from local industry and market them through IBM's worldwide distribution channels.

Eventually, according to Mr Finn, the company intends to transfer production of Personal Computer software from the



2001st Sirius computer delivery

Two thousand Sirius computers have been sold in Australia since its introduction in July 1982, and to mark the occasion Barson Computers recently presented the 2001st to the Shell Company of Australia.

According to Julian Barson, "wide acceptance by large Australian corporations has been instrumental in establishing Sirius as probably the top

selling microcomputer in its category". Monthly sales of the Sirius computer are around 230, with the larger capacity 2.4MB and 10MB hard disk systems representing 70% of the total.

For further information on the Sirius machine contact Mr J. Barson, Barson Computers, (03) 419 3033 or Bill Saunders, BS Microcomp, (03) 614 1433.

United States to Australia.

In the United States IBM has recently abolished a clause in its standard software acquisition contract which limited royalties to program authors to

\$US100,000. The change was in reponse to complaints from authors that IBM's terms for software acquisition compared unfavourably with those of other companies.

Micro colour matching system

Microcomputers are making an impact in many fields, but entirely new applications are rare. One such, however, is a new colour measurement system introduced by Instrumental Colour Systems. Based on a Z80A microprocessor system, the desk-top unit can store and manipulate colour data for a range of colour measurement and control applications. With 64K of RAM and twin dual minifloppy disk drives, the



computer can also be used for many standard business applications when not at work in the laboratory or quality control department.

Called the Micromatch 2000, the system incorporates some of the most popular features of larger units made by Instrumental Colour Systems Ltd of England, who specialise in colour control and colour matching applications. Colour sensing is by means of a high precision spectrophotometer and data on up to 1000 colour standards can be stored and processed.

Applications of the Micromatch are seen in the textile, clothing, printing, paint and plastic industries and some of the more unusual tasks undertaken so far include matching the frames of sunglasses, cocoa blending, and ensuring that Army khakis are indeed uniform.

The Micromatch is being distributed in Australia and New Zealand by Hardie Trading Ltd.

LORLIN supa-switches from C&K

MAINS SWITCHES

Type MS - Rotary action DPST, suitable for inductive circuits

Type PBMS — Pushbutton (push on/push off). Ideal for TV industry. Both types 4A at 250V, 80A. surge.

PRINTED TRACK SWITCH

Type PT — Offering outstanding, cost saving design - multibank.

ROTARY WAFER SWITCHES

Type CK - Inexpensive totally enclosed, single bank 12 position, 1, 2, 3 & 4 pole.


MINIATURE ROTARY SWITCH

Type RA - 1" diameter. Up to 12 position - multibank

SECURITY KEY SWITCHES

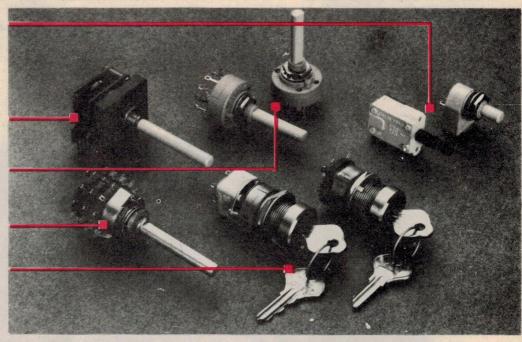Types KMS and KRA -Random or common keys key trapping facilility. Mains switch at 4A, 250V, 80A. surge or RA rotary wafer, multi position.





C&K Electronics (Aust.) Pty Limited

Office: 15 Cowper St, Parramatta NSW 2150 PO Box 229, Parramatta 2150. Telephone 635 0799. Telex AA23404 Agents: Melb. 598 2333. Adel. 277 3288. Bris. 36 1277. Perth 458 7111. Hobart 34 2233. Launceston 31 6533

Obligation free and comprehensive data is yours for the asking.

MITSUBISHI

DISK DRIVES & MONI


The Mitsubishi flexible disk drives are fully compatible and interchangeable with industry standard interfaces such as Shugarl.
Mitsubishi drives offer state-of-the-art engineering at a low cost, with features that quality conscious users are looking for; such as higher density/greater disk capacity, enhanced access times and higher MTBF.
For example, the Mitsubishi 5½ inch flexible disk drive has twice the density of the proportional drives.

(96tpl) of conventional drives. Now you can store twice the amount of data o

(96tpl) of conventional drives. Now you can store twice the amount of data on the same sized disk media.

The Mitsubishi drives employ an advanced steel band head positioning mechanism which results in a fast access lime of only three milliseconds track to track. A patented circular gimbal head support design ensures stable read/write operation and long media life.

A most limportant feature of the drives is the direct drive brushless D.C. motor that eliminates A.C. power requirement and belt drive problems.

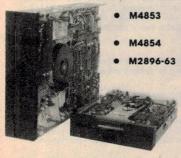

Slimline 5.25 inch DSDD 1.0Mbyte Unformatted

Call us for super competitive prices

WHY NOT UPGRADE YOUR PERSONAL COMPUTER SYSTEM BY ADDING 1 OR 2 MITSUBISHI DRIVES NOW!



6D Villiers Street North Parramatta, NSW 2151 Phone 683 3922 Telex 74654



SV-1290X 12" GREEN MONITOR

Mitsubishi Electric's leadership in CRT and TV technology lies behind this unit, with its rapid, accurate and highly legible display of the most complex alphanumeric or graphic data. Note the advantages:

- Sharp focusing and wideband circuitry give high resolution display. Band width 25 MHz (TYP).

 Low-distortion deflection circuit and generously rated high-voltage power supply ensure accurate display.

 Efficient, effective design and rigorous quality control make
- for high reliability.
- P31 (green) phosphor type. Black, non-glare screen
- Attractive, modern design, equally suitable in the factory, office or home.

ALL US FOR SPECIAL CHRISTMAS PRICE

FLASH! WE ARE NOW AN AUTHORISED COMMODORE DEALER. CALL US OR DROP IN FOR KEEN PRICES ON VIC 20 AND COMMODORE 64.

Counter sales welcome — bring cash or Bankcard. Mail orders also gladly accepted.
Plus 20% Sales Tax if applicable. Prices do not include freight.

RITRONICS WHOLESALE

425 HIGH STREET NORTHCOTE 3070 MELBOURNE (03) 489-8131 48-50 A'BECKETT STREET MELBOURNE (03) 347-9251

"BIG BOARD

PARALLEL

for clarity.

FPROMs shown only

STD Bus Connector

Prototyping Area

Jim Ferguson, the designer of the "Big Board" distributed by Digital Research: Computers, has produced a stunning new computer that we will begin shipping in November called "Big Board II", it has the following features:

4 MHz Z80 — CPU AND PERIPHERAL CHIPS
The Ferguson computer runs at 4 MHz. Its monitor code is lean, uses Mode 2 interrupts, and makes good use of the Z80-A DMA chip.

64K DYNAMIC RAM + 4K STATIC CRT RAM + 24K E(E)PROM OR STATIC RAM

"Big Board II" has the three memory banks. The first memory bank has eight 4164 RAMs that provide 60K of user space and 4K of monitor space. The second memory bank has two 2Kx8 SRAMs for the memory-mapped CRT display and space for six 2732

As, 2Kx8 staticRAMS, or pin-compatible E(E)PROMs. The third memory bank is for RAM or ROM added to the board via the STD bus. Whether bought as a bare board, a full kit, Or assembled and tested, it comes with a 450nS2732 EPROM containing the monitor

MULIPLE-DENSITY CONTROLLER FOR SS/DS FLOPPY DISKS

The new Ferguson single-board computer has a multiple-density disk controller. It can use 1793, 1797, or 8877 controller chips since it generated the signal with TTL parts. The board has two connectors for disk signal with 34 pins for 5.25" drivers, the other with 50 pins 8" drives.

VASTLY IMPROVED CRT DISPLAY
The new Ferguson SBC uses a 6845 CRT controller and 8002 Video Attributed controller to produce a display that will rival the display of quality terminals. Characters are formed by a 5x7 dot matrix on 15.75 KHz monitors and 7x9 dot matrix on 18.60 KHz monitors. The display is user programmable with the default display 24 lines of 80 characters. 8002a chip supplied for 18 to 60 kHz monitors

STD BUS CONNECTOR

The Ferguson computer brings its bus signals to a convenient place on the PC board where users can solder an DSTD, bus cards can be plugged directly into it, and it can aswell be connected by bus cable to industry-standard card cages.

The new Ferguson computer has a Z80-A DMA chip that will allow byte-wise data transfers at 500K bytes per second and bit serial transfers via the Z80-A S10 at 880K bytes per second with serial processor overhead, though the monitor for the new computer uses the DMA chip mainly for transferring data to and from disk, the chip can readily be used for other things since its "wait/ready" pin can be connected under software control to some half a dozen signal lines. When a hard-disk subsystem is connected to the "Big Board II" via its "SASI" interface, the DMA chip makes breathtaking disk performance possible

"SASI" INTERFACE FOR WINCHESTER DISKS
The "Big Board II" implements the Host portion of the "Shugart Associates Systems Interface". Adding a Winchester disk drive is no harder than attaching a floppy-disk drive. A user simply 1: Runs a 50-conductor ribbon cable from a header on the board to any of several inexpensive controller cards for Winchester drives that implement the controller portion of the SASI interface. 2: Cables the controller to an appropriate drive, and 3: Provides power for the controller-card and drive. Since our CBIOS contains code for communication with hard-disk, that's all a user has to do to add a Winchester to a

A Z80-A S10/0 = TWO ASYNCHRONOUS/SYNCHRONOUS SERIAL PORTS

A PARALLEL KEYBOARD PORT = FOUR OTHER PARALLEL PORTS USER 1/0

The new Ferguson single-board computer has one parallel port for an ASCII keyboard and four others for user-defined 1/0. When the computer is powered-up or reset, the monitor looks for a carriage-return at the keyuboard and serial ports. If the first carriagereturn the monitor gets comes from the parallel keyboard, the monitor uses the board's video display circuitry to communicate with the user via a CRT. If the first carriagereturn is typed at an ASCII terminal attached to a serial port, the monitor autabauds and makes the terminal the system console.

TWO Z80-A CTCs = EIGHT PROGRAMMABLE COUNTERS/TIMERS The new Ferguson computer has two Z80-A CTCs. One is used to clock data into and

out of the Z80-A S10/0, while the other is for systems and application use.

PROM PROGRAMMING CIRCUITRY AND SOFTWARE

The new Ferguson SBC has circuitry and drivers for programming 2716s, 2732(A)s, or _ pin-compatible (E)EPROMs. Software \$25 extra.

CP/M with Russell Smith's CBIOS for the new Ferguson computer is available for S220. The CBIOS is available separately for \$65

Actual board size: 39.6cm x 22.2cm. 5 inch BIOS being developed. Approx price S95. Pricing and Availability:

In single quantities, full kits cost \$695 inc. tax , and A&T'd computers cost \$895. There are attractive discounts that range to 35% for OEM's and dealers. For details about them please call Rod Irving on (03) 489 7099. ie: 3 Ferguson II "Big Board" are less 20% off the one-off price, hard disks disk controllers, boxes and power supply to suit both 8" & 51/4" systems will be available

Bare board with main chips now available (includes PCB, Manual, PALS, Monitor ROM, SMC chips). You have to add rest of components at \$395 + tax

Errors and omissions excepted

Available ex-stock



C. Itoh PRINTERS

FROM ROD IRVING ELECTRONICS



Pro/Writer Printer 8510

Print Features: Number of columns—136 col. max. Print Speed—120 CPS. Frint Direction—Single-directional and Bidirectional, Switch Selectable. Throughput Speed—From 44 to 182 Jpm. Characthr spacing (max. number of columns per line)—Pica 10 CPI (80), Double Width 5 CPI (89), Double Width 5 CPI (89), Double Width 6 CPI (49), Proportional Double Width Proportional Line Spacing—Variable to 1/144". Print Width—203 mm (8") max.

Forms Type: Fan Fold Rell or Cut Sheet Width—113 mm to 254 mm (4.5" to 10.0"). Total Thickness—0.05 to 0.28 mm (0.002" to 0.011"). Number of Copies—Original + 3 copies nominal.

The second secon

The Model 1550 is a compact desk-top dot matrix serial impact printer used for data communication terminals, hardcopy of CRT displays, peripheral terminals for minicomputers and microcomputers, and small-sired business systems.

The character format is a dot matrix of (RI) 39(V), or 8(H) x 8(V) or 8(H) x 8(V). The character format is a dot matrix of (RI) 39(V), or 8(H) x 8(V). The character can be printed per line at 10 list main features are. © Compact desk-top dot matrix printer = 136-column print • Lightweigh • Low power-consumption • High-quality printe • Bit image graphics • Graphic Symbols • Prints in six different languages • High reliability • Low cost.

F-10 Printmaster Daisy Wheel

Printer

Print Speed: 40 CPS. Print Method: Static Print Impact. Number of Printable Columns:
138, 163, Variable Character Spacing: 1/120 Inch (minimum). Line Spacing: 1/48.

Return Time: 900 msoc. Line Feed Time 40 msoc. Paper Width: 406 mm (maximum).
Print Character: 58. Printwheel: Industry Standard 56 Character Wheel. Interface:
Industry Standard 8-bit Parallel, RS328-C Compatible, X-ON, X-OFF, 12-bit Quime and
Dablo Compatible. Dimensions: 574 mm W x 405 mm d x 153 mm it (22.5 W 15.8 ° DX
6 ° H). Weight: 14 kg (30.8 lbs.) with cover and power supply. Noise: Less than 68 Db (1M

Special Prices till Nov 30th 1983

Serial Interface

*

Parallel Interface

EXCEPTED

ERRORS AND OMISSIONS

tax exempt

P* \$795 (\$695) S** \$1095 (\$945)

P* \$995 (\$895) S** \$1395 (\$1295f*

P* \$1950 (\$1675) S** \$2100 (\$1775)



SCHOOL AND CLUB BULK BUYS

- High quality, non-glare CRT
 Compact and Lightweight with all Controls Inside
 Front Panel.
 All units 100% Factory Burned-in.
 800 lines centre resolution.
 Suitable for Apple and other computers.
 (Apple is a registered trademark of Apple Computer.
 Computer, Inc.)
 Green or Orange Phosphor available.
 18 MHZ.
 First Shipment arraying middle of huge. 1083

Green Phosphor \$179 (\$152 Exempt)

Orange Phosphor \$179 (\$152 Exempt)

GREAT VALUE

GREAT VA

st Arrived Patented **New Head** A NEW PRINTER NOW! CP-80/I, 80-COLUM

SPECIFICATIONS

Functional Specifications

Printing method — Serial impact dot matrix
Printing format — Alpha-numeric — 7 x 8 in 8 x 9 dot
matrix field. Semi-graphic (character graphic) — 7 x 8
dot matrix. Bit image graphic — Vertical 8 dots parallal
horizontal: 640 dots serial/line
Character size — 2.1 mm (0.083")-W x 2.4mm (0.09")-H-7 x

8 dot matrix

Character size — 21mm (0.083)-W x 24mm (0.09 FH-/x 8 dot matrix
Character set — 228 ASCII characters. Normal and italic alpha-numeric fonts symbols and semi-graphics
Printing speed — 80 CPS 640 dots/line per second Line feed time — Approximately 200 msec at 423mm (1/61) line feed
Printing direction — Normal — Bidirectional logic seeking. Superscript and bit image graphics — Undirectional. Felt to right.
Dot graphics intensity — Normal — 640 dots/190 5mm (7.51) line horizontal Compressed characters — 1.280 dots/190mm (7.51) line horizontal Line spacing — Normal — 423mm (1/61).
Programmable in increments of 0.35mm (1/721) and 0.118mm (1/2161).
Columns/line — Normal size — 80 columns. Double width — 40 columns. Compressed print — 142 columns.

Compressed/double width — 71 columns
The aboves can be mixed in a line
Paper feed — Adjustable sprocket feed and friction feed
Paper type — Fanfold Single sheet. Thickness — 0.05mm
(0.002") to 0.25mm (0.01"). Paper width — 101.6mm
(4") to 254mm (10").
Number of copies — Original plus 3 copies by normal
thickness paper

chonical Specifications

ibbon — Cartridge ribbon (exclusive use), black Ribbon — Carfridge ribbon (exclusive use) black MTBF — 5 million lines (excluding print head life) Print head life — Approximately 30 million characters (replaceable) Dimensions — 377mm (14.8°) -W x 295mm (11.6°) -D x 125mm (4.9°)-H incl. sprocket cover.

125mm (4 9")-H incl. sprocket cover

Parallel CP80 \$479 (\$410 exempt)
Serial CP80 \$595 (\$515 exempt)

Prede Deiding Partical CONDITION OF THE

425 HIGH STREET, NORTHCOTE 3070. MELBOURNE. (03) 489-8131 NOW OPEN AT 48-50 A'BECKETT STREET, MELBOURNE (03) 347 9251

TO ORDER: Heavy items sent Skyroad Freight on Mail Order Phone 481-1436. Wholesale Cus Phone: 489-7099. Mail Orders to RITRONICS WHOLESALE, P.O. Box 235, Northcote 3070. Minimum P&P SZ. Add extra for heavy items, registration and certified mail. Prices and specifications subject to change without notice.

EXQIA Date.

Hame.

Micronews

Kits for S-100 bus

Rod Irving Electronics now has available S-100 boards and kits from Research and Scientific Engineering, and Australian company producing a range of economical computer hardware.

First off the rank is the RASE80 CPU board, which provides a 4MHz Z80, battery-backed real-time clock/calendar, 2K of CMOS RAM, space for up to 16K of EPROM, two RS-232C serial ports, three 8-bit parallel ports and a Centronicscompatible parallel printer interface. The on-board memory can be disabled to allow the use of a full 64K in an expanded system.

We had a chance to examine the bare board and manual and were impressed both by the quality of the double-sided, plated-through board and the extensive documentation. At \$295 plus tax for a complete kit, or \$350 assembled and tested the RASE80 board seems like very

good value.

Complementing the CPU board is the RASEFDC, an S-100 floppy disk controller board based on the Western Digital WD1795 double density controller chip. Any mixture of 13cm and 20cm doublesided and single-sided disk drives can be used with the board, and again the quality of the board and documentation is first class.

With either CP/M or MP/M the RASEFDC and RASE80 CPU boards are fully supported with boot BIOS and XBIOS routines and a full assembly language listing of the required software is provided. Price for the floppy disk controller board is \$295 for the kit and \$350 assembled and tested (all prices are plus sales tax).

Bare boards for both the processor and floppy disk controller are available at \$180 and \$150 respectively. Manuals for both boards can be purchased

separately for \$15 and \$12.

Additional boards are under development, including a 256K dynamic RAM board, a video controller, hard disk controller and an input/output board.

Rod Irving also has available a range of disk drives and disk drive cases, including single and dual cabinets for 13cm and 20cm drives, with or without in-built power supplies. Fabricated from black enamelled steel plate, the cases for 13cm drives are available for \$39 (single) and \$59 (dual drives) or \$79 and \$99 with power supply.

For further information on the RASE boards or the disk drive cabinets contact Rod Irving Electronics, 425 High Street, Northcote, Vic, 3070. Phone (03) 489

8131



Big expansion of Atari range

Futuretronics Australia Pty Ltd. exclusive Australian distributors of the Atari range of computers and video games, introduced the new Atari XL range of computers, peripherals and software at the Melbourne Home Show.


The new Atari line-up includes more than 35 new products, including the Atari 600XL home computer (16K RAM) and the Atari 800XL machine with 64K of RAM, a new line of printers and a CP/M module to allow this operating system to be used with the 600 and 800XK 800XL machines.

Also announced is a "Touch Tablet Controller" which enables the user to paint pictures, draw diagrams and write text using the touch of a finger or a stylus. Remote control wireless joysticks, a light pen and a track ball controller also feature in the new range.

Software for the new computer sytems already includes some 2000 programs for the 800XL and 1500 for the 600XL. one of the largest ranges available for any machine on the market. New releases include Atari Logo, new games based on Walt Disney productions and Atariwriter, a full screen word processing system.

Joint managing directors of Futuretronics Australia Pty Ltd, Harry Chojna and Peter Alpar said at the introduction of the new Atari products. "Our objective is to capture the major share of the Australian home computer market. We now have the products to do this and we know that Atari will be a force to be reckoned with. They are the best in the world today and no one competing against us can make such a product offering. It is a commitment by Atari and Futuretronics Australia Pty Ltd to deliver to the marketplace the products that are needed".

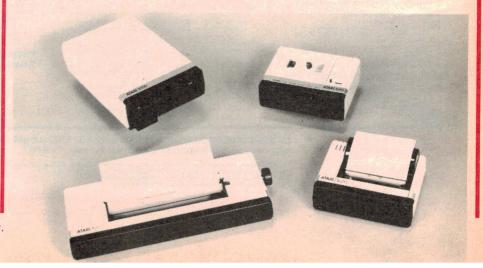For further information on Atari products contact Futuretronics Australia Pty Ltd, 1076 Centre Rd, Oakleigh, Vic 3166. Phone (03) 579 2011.





Compact Four Colour Printer/Plotter at only \$

Unbelievable! Now every computer user can afford a high resolution 4 colour printer/plotter. Yes, this remarkable plotter can not only print text in four bright colours, it can produce designs, pie or bar charts....even maps!

Yet it is amazingly simple—with four ball point pen elements, print medium replacement is easy and economical—and avoids many of the problems that occur with more complicated types.

Look at these amazing features:

- Suits all standard Centronics-type computer interfaces.
 Uses non-coated (economical!) standard paper (114mm wide rolls).
- All operations (colour, type size, graphics/text, etc) software controlled under simple BASIC 'LPRINT' statements.
- Minute 0.2mm resolution and minimum step size
- Standard 96 ASCII character set
- 10 characters per second printing speed

Paper Rolls To suit X-3245 printer. Quality! \$650 cat X-3246.

Pen Sets

for the X-3245. \$750 EA

AME VALUE FOR ACCESSORIES Fan-form Paper To suit X-3268 2000 sheets. Cat X-1189

printer that's quick and quiet

Everything about this outstanding new BX-80 printer from Dick Smith Electronics says 'quality'! A super-fast print speed of 80 characters per second, the latest patented technology of 'in-line' print needles...the BX-80 has all the features you want and need. And to add to the already-impressive list, this superb unit is amazingly quiet in operation!

Yes! The BX-80 will produce excellent graphics. And yes—it operates via normal software control. Combine it with virtually any computer which uses a standard Centronics printer interface! And by the way—an excellent manual, complete with program samples, is provided! What value!

Features:

- 40 column (double width) to 142 columns per line
- Fan form (sprocketed) or friction feed (single sheet) stationery.
 Proportional and bold face printing, plus super-scripting
- and sub-scripting
- Very easy to move around—it weighs just 5.3kgs!
- Head life quoted at an amazing 30 million characters!
- Outstanding value for money!

Cat X-3268

for only

The Computer Specialist



A620/TH

FASTER, FASTER FOR GOODNESS SAKE, FASTER ...

AED RELEASES PSEUDO DISK FOR "UNIVERSE" AND OTHER S100 SYSTEMS

In this column over the last five months we have examined the various features and innovations of the AED UNIVERSE S100 microcomputer system. This month sees the end of this mini series, however, up to date information will be published from time to time in the electronic press.

In response to the ever increasing demand for more speed from single-user and in particular multi-user computer systems, AED have released a high speed silicon memory drive device for almost any S100 computer system including the AED UNIVERSE supercomputer II.

The AED pseudo disk offers greater storage capacity than the original U.S device referred to as SEMIDISK and comes with a considerably more economical price tag. The device is I/O driven and requires no hand-shaking during both read and write operations, and therefore runs at a very high speed. Performance is even faster with advanced processors using block I/O transfer capability (ie Z80, 8088, 8086, 80186, 80286, 16032, etc). The actual speeds achievable are up to 4 times the data transfer rate of 8" double density floppy drives (8 times that of 5.25" inch drives) with zero seek time, no head load time, and no latency. In practice the device responds at lightning speed compared to floppy and hard disk counterparts. The pseudo disk I/O approach has proven to be considerably faster than the Godbout COMPUPRO equivalent referred to as MDRIVE and is also less expensive (BRAVO AUSTRALIS).

The device is referred to by AED as UNDISK and is ideal for applications that require considerable disk I/O such as compiling programmes, much referenced data files, disk based sorts, and in particular multi-user and network systems where multiple disk accessing are the norm and speed is the order of the day.

The simple I/O driven nature of the card makes it compatible with almost all S100 systems (even poorly designed ones). The UNDISK totally complies to the IEEE 696 S100 specification as do all S100 products manufactured by AED.

To make installation easy AED supplies a special programme that loads itself above your CP/M operating system and automatically links itself into the CP/M bios jump table to install the necessary routines. The drive is then simply accessed as CP/M drive "M".



We can help you with:

• CONSULTANCY • SERVICE CONTRACTS • CUSTOM SOFTWARE • STANDARD SOFTWARE

The choice is yours.

For information about this product or a complete UNIVERSE information kit contact:



Sydney: AED COMPUTERS, 24 DARCY ST, PARRAMATTA, NSW 2150.

Phone: (02) 689 1744. Telex: AA70664 GIRFRI.

Melbourne: AED COMPUTERS (MELBOURNE), ELSTON MICRO, 53 WAVERLEY RD,

EAST MALVERN, VIC 3145.

Phone: (03) 211 5542. Telex: AA30624 ME447.

Canberra: AED COMPUTERS (CANBERRA), 217 NORTHBOURNE AVE, CANBERRA 2601.

Phone: (062) 47 3403 Telex: AA62898 HARSUR.

Micronews

Keyboard enhancement for Color Computer

Paris Radio Electronics now has available a "drop-in" replacement keyboard for the Tandy TRS-80 Colour Computer. The new keyboard is easily installed on the existing mounting posts and simply plugs into the keyboard connector but provides full-size, full stroke typewriter keys to replace Tandy's pushbutton style keyboard.

Key lay-out and colour scheme is identical to that of the original Colour

Computer keyboard.

All mounting hardware is provided with the keyboard, including a face plate to match the finish of the Colour Computer. Be aware however that installation of the new keyboard requires



opening the case of the computer, which voids any Tandy warranty on the system.

For further information on the new keyboard plus a range of software and magazines for the Colour Computer contact Paris Radio Electronics, Shop 1, 165 Bunnerong Rd, Kingsford, NSW, 2032. The postal address is PO Box 380, Darlinghurst, NSW, 2010. Phone (02) 344 9111.

Texas Instruments drops prices, introduces more software

Texas Instruments has announced significant price reductions on its range of TI-99/4A computer peripherals. Biggest reduction is on the disk controller board, reduced from \$199 to \$100. Disk drives, currently selling at \$499, have been reduced by 18%.

Other peripherals subject to price reductions are the peripheral expansion box (one-third off), 32K memory expansion board (also one-third off) and the RS232 interface board.

"The new peripheral prices make the more sophisticated software such as Microsoft Multiplan and TI Writer more affordable and attractive for home users," according to Claudio Ellero, marketing manager for TI's consumer group. "With the new one year warranty and low peripheral prices the 99/4A is the most competitive home computer on the market today," says Claudio.

Putting substance into Tl's intensive marketing promotion of the TI-99/4A is

the announcement that Texas Instruments has produced 52 educational program cartridges for the machine, covering a wide variety of subjects and levels.

Educational software for the 99/4A also includes PLATO courseware on disks. Texas Instruments has the exclusive distribution rights from Control Data Corporation for distribution of the PLATO basic and high school skills learning series.

FOR TRS-80 MOD 1+111 AND SYSTEM 80

COLOR LOAD 80

FOR TRS-80 COLOR COMPUTER
YOU HAVE READ 80 MICRO

SAVE HOURS OF TYPING AND FRUSTRATION

*TRS-80 and Color Computer are Tradmarks of Radio Shack, a division of Tandy Corp.

Australian Computer Software
P.O. BOX 450 MALVERN, 3144, VIC. PHONE (03) 20-4947.

CASSETTE
OR LOAD 80
COLOR LOAD 80

ONLY \$19.95EA

(SEE ELECTRONICS AUST:
'MICRONEWS' OF THIS ISSUE FOR
MORE INFORMATION)

ALLOW 14 DAYS DELIVERY

I wish to order:

□ LOAD 80 \$19.95 S.T.I.

☐ COLOR LOAD 80 \$19.95 S.T.I.

Address

Post and Packing \$2.00

DEALER ENO. WELCOME

IN GE

425 HIGH ST. NORTHCOTE 3070 VIC PHONE (03) 489 8131

50V 5A LABORATORY POWER SUPPLY



New switchmode supply can deliver anywhere from three to 50V DC and currents of 5A at 35V or lower. Highly efficient

EA May, June 1983

\$140.00

OVERLOAD INDICATOR



Will detect even slight overload conditions and is not affected by load impedance or varying supply voltages. E.A. JUNE '83

\$75.00




An "Effects Unit" that can create phasing, flanging, echo, reverb and vibrato effects. E.A. JUNE '83

EPROM PROGRAMMER

\$43.00

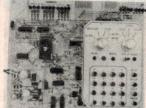No need for a Micro with EA's great Eprom Programmer suitable for 2716/2758 Eproms





ELECTRONIC METRONOME

\$18.90

Great new Metronome Circuit with low current drain (less than one milliamp) drives a Loudspeaker and a Led Indicator. EA January 82




31/2 DIGIT LCD CAPACITANCE METER

Handy pocket size Digital Capacitance Meter, runs off a 9V battery and measure 1pF to 19.99uF in just three ranges. EA March 82






DUAL TRACKING POWER \$83.50

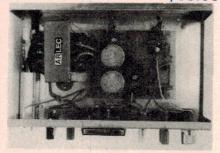

Built around positive and negative 3-Terminal Regulators, this versatile dual tracking Power Supply can provide voltages from $\pm 1.3V$ to $\pm 22V$ at currents up to 2A. In addition, the Supply features a fixed +5V 0.9A output and is completely protected against short circuits, overloads and thermal runaway. EA March 82

VOICE OPERATED RELAY

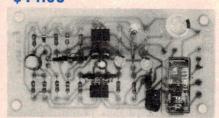

EA's great new Voice Operated Relay can be used to control a tape recorder, as a VOX circuit for a transmitter, or to control a slide projector. EA April 82

SOUN' TRIGGERED

\$26.50

This easy to build sound or light operated many feature. Catch those spectacular and humorous moments like that time your motherin-law slipped on the moss covered patio and broke



"LE GONG"

\$14.95

October 80

The "Le Gong" Doorbell with those unmistakable chimes generated by the LSI. A must for the man who has everything! EA February 81



LED LEVEL METER

\$27.00

Build a Led level Meter with simultaneous peak and average display plus 60dB dynamic range. This kit is ideal for any application requiring a wide dynamic range level display. ETI 458



DIGITAL THERMOMETER: 31/2 DIGIT LCD

\$79.00

Measure temperatures from below freezing point to around boiling point. EA February 82



FUNCTION GENERATOR \$79.50




This Function Generator with digital readout produces Sine, Triangle and Square waves over a frequency range from below 20Hz to above 160kHz with low distortion and good envelope stability. It has an inbuilt four-digit frequency counter for ease and accuracy of frequency setting. EA April 82


LOTTO/POOL'S SELECTOR

\$22.50

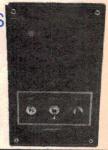You have to be in it to win it Take the chance out of winning the Pools as well as Lotto, and build the great new Pools/Lotto Number Selector. EA July 81



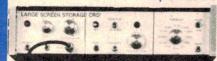
LARGE SCREEN TV STORAGE CRO ADAPTER \$119.00



For a low cost Storage CRO with Synchronised Display, Flectronic Graticule, One-Shot Triggering and Optional Storage of up to four Screen Displays it can't be beaten. EA

LOW OHMS **METER** \$34.50

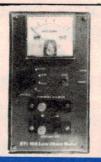How many times have you cursed your Multimeter when you had to measure a low-value resistance. Well alas, with the "Low Ohms Meter" you can solve those old problems and in fact measure resistance from 100 Ohms down to 0.005 Ohms, ETI 158 November 81



SOUNDBENDER

\$29.00

Have great fun creating your own recording effects with music and voice. The Sound Bender can receive from Electric Guitar, Microphones, etc. February 82



48-50 A'BECKETT ST, MELBOURNE 3000 VIC

Micronews



"Compumate" adds intelligence to Atari video games machine

Videoactive Electronics, Australian distributors of Spectravision Atari-compatible video game cartridges and the new Spectravideo SV318 and SV328 personal computers, has released an add-on keyboard for the Atari 2600 games machine.

The "Compumate" add-on keyboard transforms the 2600 into a computer, adding 16K of built-in Read Only Memory, 2K of programmable memory, a Basic interpreter and a 42-key flat membrane-switch keyboard. A cassette interface is included in the keyboard, allowing a standard audio cassette recorder to be used for storing programs.

Also provided by the add-on is a two channel sound generator with a range of two octaves and a "magic easel" program that allows the user to create pictures and graphics in up to ten colours.

Software will be available on cassettes for the system, with six titles released so far, including typing and maths tutoring programs, graphics and an educational game.

For further information contact Videoactive Electronics, 70 St Kilda Rd, St Kilda, Vic. 3182. Phone (03) 537 2000.

Magazines for MC-10, portables

Users of the Tandy MC-10 computer will be pleased to know that an Australian version of "MiCo" magazine is now available. The first issue runs to 62 pages and includes technical details, programs and comparisons with the TRS-80 Color Computer. (It turns out that the MC-10 can run many of the programs written for the Color Computer.)

Also available from Greg Wilson is "MiCo Exposed", an annotated disassembly of the Microsoft Basic of the MC-10. The assembly language listing of the interpreter is accompanied by detailed comments and a wealth of other useful information for the dedicated programmer.

TRS-80 Color Computer users should also be aware of "Australasian Rainbow", with news, programs and articles of interest for the Color Computer. Details of all publications are available from Greg Wilson, PO Box 9, Potts Point, NSW, 2011.

THE NEW MICROPROFESSOR MPF-I PLUS



A COMPLETE Z-80 BASED MICROCOMPUTER SYSTEM FOR HARDWARE/SOFTWARE TEACHING & DEVELOPMENT

The Micro-professor I PLUS gives you all you need to join the growing world of microcomputing.

It's a fully developed, tested and proven system that gives you step-by-step, start-to-finish hands-on instruction.

The powerful software features are:

- Interactive Monitor
- Two Pass Assembler
- Line Assembler
- Text EditorDisassembler

Optional languages include BASIC & FORTH

In addition to its instructional power, the MPF-IP shows you how to breadboard & prototype your own microprocessor-based hardware. It lets you create the software you need to make the hardware work in your specific application.

The MPF-IP Microprocessor system comes complete with: Z-80 processor; 4K-Byte RAM; 8K-Byte ROM; 20 Digit, 14 segment alphanumeric green tube display; 49 key-Keyboard; Z-80 bus, for external interfacing; battery back-up for RAM; cassette input/output, built-in speaker; mains adaptor and three essential user's manuals.

MPF-I PLUS OPTIONS:

WIFF-I FLUS OF HONS.	
IOM-MPF-IP, Input/Output and Memory Board	\$132.00
PRT-MPF-IP, Printer Board	\$105.00
EPB-MPF-IP, Eprom Programming Board	\$159.00
SSB-MPF-IP, Speech Synthesizer Board	\$159.00
SGB-MPF-IP, Sound Generation Board	\$105.00
AC/DC-Mains Adaptor (for IOM, PRT, SSB & SGB)	\$ 11.50

- * ALL PRICES PLUS 20% SALES TAX, IF APPLICABLE.
- * Micro-Professor is a trade mark of Mulitech Industrial Corporation. *Z80 is a trade mark of Zilog Inc

Distributed by:



EMONA ENTERPRISES PTY LTD.

CBC Bank Bldg, 661 George St, Sydney NSW, 2000. Tel (02) 212-4815, Tlx AA74500

Also available from: VIC: Radio Parts Group 329 7888 SA: International Communication System P/L 47 3688 WA: HINCO Engineering P/L 38 4477 QLD: Baltec Systems 369 5900 TAS: D & I Agencies 23 1755 ACT: Electronic Components P/L 80 4654.

A Solemn Pron

Dear Customer

ALTRONICS


Altronics has experienced incredible growth in the past year (What recession??). I'm firmly convinced this is due to our energetic approach to our business and our ability to provide our valued customers with quality products at competitive prices. To further improve our service we have installed an INWATS phone service whereby bankcard holders may ring an order to us for the cost of a local call (around 12 cents)). That's right — from anywhere in Australia up to 6pm Eastern Standard Time.

We promise that this service together with our Overnight Jetservice Delivery will be superior to that offered by any other Australian Supplier for the products we advertise in this magazine. Should you find otherwise you can return your purchase to us for a full refund plus \$5 for your inconvenience Regards.

ALTRONICS

Sizes 135 × 91 × 39

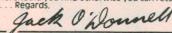*This offer is made in good faith and subject to Stock Availability.






A FREE "LEATHER LOOK" CARRY CASE WITH EVERY Q1001 OR Q1002 **PURCHASED THIS MONTH**



UNIVERSAL MULTIMETER PORTABLE WITH BENCH STAND * 23 RANGES *

20,000 OHMS/Volt DC * 10,000 OHMS/Volt AC Mirror backed scale * Overload protected Unique carry handle doubles as a bench stand * Unique carry nandle doubles as a bench stand
* High-impact resistant case * Uses 1 AA Penlight
battery (incl.) * Comes complete with battery,
test leads and instructions. RANGES: DC Voltage
0-.25, 1, 2.5, 10, 25, 100, 250, 1000. AC Voltage 0-10,
25, 100, 250, 1000. Decibels 20 to + 22 db. DC
Current 0-50, 500 UA, 0-5, 50, 500MA. OHM Meter
0-6 megohms in 4 ranges, 30 ohms centre scale.

\$24.50 \$22.50 4 or more.....

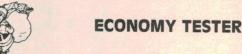



OVERLOAD

ALTRONICS

ALTRONICS

DAY

JETSERVICE DELIVERY NEXT

BANKCARD

0

PROTECTED High 2000 OHMS/Volt sensitivity overload protected. Dimensions 90 x 60 x 30. Mirror back scale prevents Parallax error. Complete with test leads and instructions. Uses 1 AA Penlight batt. (incl.)
Ranges: DC and AC 0-10,
50, 250, 1000V. Decibels: 10 to + 22 db. DCA 0-100MA. OHMS 0-1 meg.

OHM in 2 ranges 01001... \$14.50

4 or more \$13.00

PROFESSIONAL QUALITY SOLDER SUCKERS

Not to be compared with Inferior "Hobby types". Saves countless hours in fault finding and repair of complex PCB's. SINGLE HANDED OPERATION SELF CLEANING PLUNGER LONG LIFE TEFLON TIP DOUBLE DIAPHRAGM **DUAL O-RING SEAL** 225mm x 20mm(d) 50mm STROKE if you order this POWERFUL month ASK FOR SUCTION A FREE REPLACEMENT **TIP CAT. T1241** YOU MUST ASK! T1240.. only \$11.95

* PANBRAKE SHEET METAL BENDER

T1241. Replac tip. \$1.95

Our Panbrake Sheet Metal Bender proved to be so incredibly popular that the 1st shipment went in no time. Now at last they're back in stock. Make your own chassis and save a



New low direct import price!

TECHNICIAN'S UTILITY PARTS CASE




Lightweight and durable This Parts Case is a MUST!

Featuring:— Clear lid (tell contents at a glance); Positive action snap lock; 30 partition combina-tions.

INTERLOCKING PARTS DRAWER

Unique side and top/bottom keying system allows you to use just a few or build a whole wall of drawers as your parts expansion dictates. Quality designed drawer slides will not "stick" or seize. Slide handle also takes or seize. Slide handle also takes ident, cards. Single or double drawers available

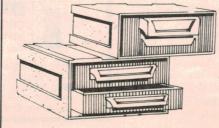H0435 Single Way..... H0436 Double Drawers.....



SHEETMETAL NIBBLING

TOOL cuts any shape cut out in steel aluminium or plastic. Very easy to use. Capacity steel .6mm. Aluminium 1.6mm. T2355 \$16.95

"Leather Look" Carry Case Included at No Extra Cost

HOLE PUNCH SET Fantastic Value

A must for every enthusiast or serviceman. Cuts holes in metal up to 1.6 mm (16 gauge). Set of 5 punches and tapered reamer.

Punch sizes: 16mm 18mm 20_{mm} 25mm 30mm



T2360..... \$18.50


DE-SOLDER BRAID



ALTRONICS ALTRONICS ALTRONICS ALTRONICS

ALARM CONTROL MODULE

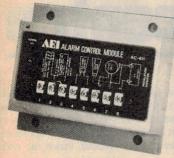EASY TO INSTALL * BUILT IN SIREN DRIVER —
DIRECTLY DRIVES LOW COST 8 OHM HORN SPEAKERS, SIREN HORNS AND MECHANICAL BELLS * LOW POWER 12V DC OPERATION.



The AC-811 is a low cost professional burglary protection system which detects the presence of an intruder who breaks into your home, office or business. The system also allows connection of emergency panic buttons, wall vibration switches smoke wall vibration switches, smoke and heat sensors, as well as freezing or flooding detectors to form a complete protection system

EXIT/ENTRY DELAY BOTH N/C AND N/O CONTACTS Ideal for homes, offices, factories shops, caravans, any area requiring protection.

\$5042.. Only \$39.50

DELUXE ABS INSTRUMENT CASE

Case color light grey front-rear panels black

ALTRONICS

LXU

DELIVERY

BANKCARD JETSERVICE

Our superb new instrument case will give your projects the professional appearance they deserve.

* Internal mounting posts enable a wide combination of PCB's, Trans-

formers, etc. to be accommodated (screws supplied).

PCB guide rails provided internally allow vertical PCB positioning to several locations

Removable front and rear panels. Attractive textured finish one side and plain the reverse side. (Enables direct engraving, silk screen printing etc. to


* Great for test instruments and other high grade projects.

Overall Size: 200W x 160D x 70mmH

10 UP .. \$11.50

OEM'S — Manufacturers -- Bulk Users: Your product will look like it's straight out of "Hewlett Packard's" factory with this brilliant low cost case. Contact our Wholesale Department for Bulk Prices

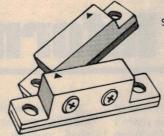FULLY ENCAPSULATED REED SWITCH & MAGNET SETS



Powerful Magnet Self-Adhesive or Screw Mount.

N/C Reed & Magnet \$5055......\$2.50 10 up......\$2.10

N/O Reed & Magnet \$2.95 S5056..... \$2.75 10 up.....

LOW COST WEATHERPROOF HORN SPEAKER

5 WATT 8 OHM

Fully weatherproof. New unique voice coil construction ensures high dependability on full drive

Sultable for PA Intercom and security

\$9.50 C2010.....



WEATHER PROOF SIREN HORN

12V DC operated — Deafening Siren Wail. Super handy for audio signalling, security systems etc. Current drain 500MA approx. Completely weatherproof. Attractive off-

\$22.50 S5058.....



008 999 007 FREE

(09) 328 1599 PERTH METRO AREA & SERVICE

All Mail Orders: Box 8280, Stirling St, Perth WA 6000.

ALTRONICS RESELLERS

Please note that resellers may not have all the items advertised in stock, and as resellers have to bear the cost of freight, prices may be slightly higher than advertised. ALTRONICS reseller prices should however represent a considerable saving over our competitors' prices. WESTERN QUEENSLAND

VICTORIA
CITY
All Electronic
Components 662 3506
Ellistronics 602 3499
MaGraths
Electronics 347 1122
SUBURBAN
BENTLEIGH
Absolute Electronics. 557 3971
BOX HILL SOUTH
Eastern
Communications 288 3107
Talking Electronics 550 2386
FOOTSCRAY
Acron Electronics 689 1911
SOUTH CROYDEN
Truscott Electronics 723 3860
COUNTRY

Lindrea & Johnson. ... 41 1411

A & M Electronics. . . . 24 4588

... 23 3380

.... 21 8866

BENDIGO

Electronic and Digital Services.

SHEPPARTON

WODUNGA

	The state of the s
A PROPERTY AND A PARTY OF THE P	AUSTRALIA
CITY	COUNTRY
Delsound P/L 229 6155	ALBANY
SUBURBAN	BP Electronics 4
BIRKDALE	ESPERANCE
Wholesale Sound	Esperance
Accessories 207 2502	Communications 7
FORTITUDE VALLEY	
St. Lucia Electronics 52 3547	GERALDTON
PADDINGTON	Geraldton TV and
ECO Technics 369 1474	Radio
SALISBURY	KALGOORLIE
Colourview Wholesale275 3188	Todays Electronics 2
SLACKS CREEK	MANDURAH
David Hall Electronics. 208 8808	Kentronics 3
COUNTRY	WYALKATCHEM
CAIRNS	D & J Pease 8
Thompson Instrument	CIETARIA
Services 51 2404	NT
GLADSTONE	DARWIN
Purley Electronics 72 4321 IPSWICH	Radio Parts Darwin 8
P & P Electronics 281 8001	Ventronics 8
NAMBOUR	ALICE SPRINGS
Nambour Electronics 41 1604	Ascom Electronics 5
PALM BEACH	Farmer Electronics 5
The Electronics Centre. 34 1248	
ROCKHAMPTON	TASMANIA
Purley Electronics 2 1058	CITY
TOOWOOMBA	D & I Agencies
Hunts Electronics 32 9677	GEORGE HARVEY
TOWNSVILLE	
Solex	Hobart

WESTERN		
AUSTRALIA		
COUNTRY		
ALBANY		
	41	2681
ESPERANCE		
Esperance		
Communications	71	3344
GERALDTON		
Geraldton TV and	21	2777
Radio	21	2111
Todays Electronics	21	5212
MANDURAH	-	2212
	35	3227
WYALKATCHEM		
D & J Pease	81	1132
NT		
DARWIN	01	0500
Radio Parts Darwin		
Ventronics	01	3491
ALICE SPRINGS Ascom Electronics	52	1712
Farmer Electronics		
ranner ciectronics	32	2307
TASMANIA		

Phone toll free 6am - 8pm (EST) for personal service, or take advantage of our 24 Hour 7 day p/week Bankcard phone order service. Give your name address with postcode, phone number, bankcard number and expiry date then your order — and presto your order will be process-
ed and back to you in a flash. — Please nominate Jetservice if you want
overnight delivery.
\$2.50 DELIVERY AUSTRALIA WIDE We process your order the day received and despatch via Australia Post. Allow approx. 7 days from day you

post order to when you receive goods. Weight limited 10kgs. \$4.50 DELIVERY AUSTRALIA WIDE We process your order day received and despatch via Jetservice for delivery next day.

BANKCARD HOLDERS CAN PHONE ORDERS UP TO 8PM (EST) FOR NEXT DAY DELIVERY — SOUNDS INCREDIBLE DOESN'T IT? Alright you cynics just try us! Weight limit 3,3kgs. Jetservice cannot deliver to P.O. box numbers

(Australia Post would have a fit). \$10.00 HEAVY HEAVY SERVICE — AUSTRALIA WIDE All orders over 10kgs must travel on the heavy service, that is — road express. Delivery time days average

NEW

SUBURBAN		
CHRISTIES BEAG	CH	
Force Electronics		3366
ELIZABETH GRO		
A.E. Cooling	255	2249
KESWICK		
Freeway Electric		
Wholesalers	297	2033
PROSPECT		
Jensen Electronics	269	4744
COUNTRY		
PORT PIRIE		
G.F. & J.A. Pointon	32	514
d.i . & J.A. i dinton	. 02	314
ACT	5333	
CITY	and the	
Electronic	00	
Components	. 80	465
Scientronics	. 54	833

ADN Electronics. . . 212 5505 Protronics 212 3111

SOUTH

AUSTRALIA CITY

SOUTH WALES
CITY
Avtek Electronics 267 8777
David Reid Electronics 267 1385
Electronic Agencies 29 2098
Jaycar 264 6688
Radio Despatch 211 0191
SUBURBAN
CONCORD
Electronic Agencies 745 3077 DEE WHY
David Rvall
Electronics 982 7500
ENFIELD
Avtek
LEWISHAM
PrePak Electronics 569 9770
MATTRAVILLE
Creative Electronics 666 4000
COUNTRY
ALBURY
Webb's Electronics 25 4066
BATHURST
Sound of Music 31 4421

BROKEN HILL Crystal TVCOFFS HARBOUR		4803
Coffs Harbour Electronics	52	5684
Tomorrows Electronics		7246
Kurri Electronics NEWCASTLE		
D.G.E. Systems George Brown & Co NOWRA		
Vimcom Electronics PENRITH		
Acorn Electronics PORT MACQUAR	RIE	
Hall of Electronics RICHMOND		
Vector Electronics TOUKLEY		
TES Electronics WINDANG		
Madjenk Electronics	96	5066

RESELLERS WANTED IN ALL AREAS (including WA).

Phone: STEVE WROBLEWSKI (09) 381 7233 for details.

ALTRONICS **ALTRONICS ALTRONICS** ALTRONICS

23 2842

34 2233

31 6533



TRIP METER: As an off and on reader of your magazine over the past few years, I wonder if you can help me with a design or an already existing design for something I wish to build.

I am a student at Swinburne and although I am majoring in accounting and data processing I have kept up a relationship with hobby electronics — I am able to successfully construct kits and circuit designs up to the moderately difficult level and am able to modify some simpler circuits to suit my own needs. But I am yet to find (given reasonably limited resources) anything near what I need.

What I am after is this: There exists a device (called a "Halda") which is a combined odometer/trip meter incremented in 100ths of a kilometre. This is used for navigation as route instructions are given in so many 100ths of a kilometre in such a direction.

Now being a student with big ideas of dabbling in rallying I can't afford \$400-\$500 for a new one or even \$200-\$300 for a serviceable second-hand one. So what I'm after is a design for an electronic version of the same but the closest thing I can find is the economy gauge mentioned (so I'm told by word of mouth) in an EA sometime last year.

I assume it worked on the principle of using a reed switch to record two impulses per turn of the tailshaft, dividing that number again by the ratio (3.89:1), dividing that result by how many times the circumference of the wheels (207.3cm) is divided in a kilometre (483.092) times.

Now assuming you could work out the distance travelled, could you not stop there and display that cumulative amount with the option of resetting it at any point? I personally don't know enough about electronic design to solve that but I know that myself and many others (not only at Swinny) would appreciate an easy-to-build project along these lines.

• There are two ways in which such a project could be obtained. One way would be to modify our Car Computer project which was described in "Electronics Australia" from July to September 1982, or two, use the event counter described in July 1983 together with a suitable interface for the distance sensor.

We are unable to undertake these modifications at the moment but we shall publish your letter in the information pages and see if reader interest justifies such a project.

WIZZARD: First I would like to express my appreciation for a really great magazine; it is consistently both informative and interesting and one looks forward each month to receiving it.

Recently I purchased a Dick Smith Wizzard computer as a low cost way of being introduced to computers (admittedly to play games). I now find that Dick Smith will not be fully supporting this machine with software but only periodically with games cartridges.

In American magazines I have seen advertisements for "cartridge adapters" enabling, for example, VIC 20 machines to use Atari cartridges. The Wizzard also uses a 6502 microprocessor so I assume that a cartridge adapter would also be

possible. Could you maybe run an article on such an item? Dick Smith in his recent advertisement has claimed that sales of this unit have reached 12,000 so surely such an article would have a wide appeal.

You might also consider a review of the machine as well.

I trust that my suggestion will at least receive some consideration as I realise that a magazine such as yours has quite a lot to cover but the future is definitely leaning towards computerisation and "games" are a major part of computers. (P.M., Lakemba, NSW).

• Simply to say that two computers use the same microprocessor does not guarantee that the same software can be run on both machines, even if the hardware incompatibilities can be overcome by a cartridge adapter. There would also be differences in the size and configuration of memory and in the control of the video display and sound generator to be considered.

Feedback on the EPROM Programmer

EPROM PROGRAMMER TRAP: In your Information Centre of September 1983, R.I., of Jindalee Qld, told of his EPROM Programmer (described in EA January 1982) which "blows up" chips. In response, you suggested to him some obvious areas of possible trouble.

It would seem that this problem may be common as I had an identical problem. The programmer destroyed both National and Hitachi 2716s when the S3 (program-ready, +25V) switch was operated. A check of all signals showed the levels to be OK and the timing to be correct. The +25V line was stable.

Closer inspection showed that throwing S3 generated a narrow spike on the OE line of the 2716. The spike went up to about +6.7V (exceeding the absolute maximum rating). By isolating pin 20 of the 2716 from pin 8 of IC9d which drives it, it was determined that the spike was not generated by IC9d, but was being induced into the interconnecting line.

The track feeding OE, pin 20, runs parallel for a considerable distance to

the track feeding +25V to Vpp, pin 21. By cutting the track at OE, pin 20, and at pin 8 of IC9d and reconnecting them directly via a length of wire the level of the spike was considerably reduced.

Then I replaced all aluminium electrolytic capacitors with tantalum types. With these two modifications completed, the programmer produced correctly programmed EPROMs rather than consistently dead EPROMs.

Another modification considered worthwhile is to increase the value of the $.01\mu\text{F}$ capacitor connected to the program switch to $0.1\mu\text{F}$. The switches supplied were not high quality, with considerable contact bounce on releasing the depressed switch. This resulted in a second 50 millisecond pulse being generated on switch release, and could result in chip damage (though not the cause of the problem of dead chips as discussed above).

The increased capacitor value eliminates the switch bounce problem. (S.C., Carine WA).

We do not have sufficient information on the Wizzard to say whether such an adaptation is possible. In most cases the simpler solution is to write a program from scratch for a particular machine.

However, perhaps other users of the Wizzard are in a better position to consider your suggestion, and we would welcome contributions along the lines you suggest.

The Wizzard games machine was reviewed in our October 1982 issue.

PLAYMASTER 114: I have in my possession, in perfect working order, a Playmaster 114 program source, bought a number of years ago by my father (see EA Oct. 1965 and Sept. 1966). After pulling it, dusty from an attic, I now have it running; however, having grown up after the "valve era", I have trouble interpreting the circuit, so I hope you can assist me.

Firstly, can you tell me briefly how this receiver compares with modern ones, say the DX-100? Similar sensitivity? What? Would the digital readout for shortwave receivers be compatible with the 114, and if so, where exactly on the local oscillator should I connect it; and in the 114 is the local oscillator frequency 455kHz higher than the tuned signal frequency, as the article in Sept 1966 doesn't say, If not, can you tell me what it is?

I know turning the clock back this far may be a tall order, but I hope you can help me. (J.V., Wahroonga, NSW).

• We have not performed comparison tests on either the Playmaster 114 tuner or the Realistic DX-100 but we would assume that both receiver designs would have roughly the same order of sensitivity. As far as bandwidth is concerned, the Playmaster tuner could be expected to have a wider bandwidth than the later solid state DX-100 and the distortion of both designs would probably be on a par.

The local oscillator in the Playmaster 114 followed normal practice in being 455kHz above the tuned frequency. The most likely usable point of connection for the frequency readout circuitry would be to the triode grid of the 6AE8 via a small capacitor of say 10pF.

DWELL EXTENDER: I have some queries about electronic ignition systems that I would like answered, if possible, through your Information Centre.

Firstly, congratulations on a fine magazine, one which I have been reading for about 15 years. Being both an electronics and car enthusiast I have followed with interest the development of electronic ignition systems.

I have constructed the dwell extender featured in the February 1970 edition and although it works once the motor is

Electronics Australia Reader Service

"Electronics Australia" provides the following services:

PHOTOSTAT COPIES: \$3 per project, or \$6 where a project spreads over multiple issues (price includes postage). Requests can be handled more speedily if projects are positively identified, and if not accompanied by technical queries. We reserve the right to supply complete back issues instead of photostats, where these are available.

CHASSIS DIAGRAMS: For the few projects which require a custom metal chassis (as distinct from standard cases) dyeline plans showing dimensions are normally available. \$3 including postage.

PC BOARD PATTERNS: High contrast, actual size transparencies: \$3, including postage. Please specify positive or negative.

PROJECT QUERIES: Members of our technical staff are not normally available to discuss individual projects, either in person at our office, or by telephone.

REPLIES BY POST: Limited to advice concerning projects published within the last three years.

Charge \$3. We cannot provide lengthy answers, undertake special research, or discuss design changes. Nor can we provide any information on commercial equipment.

OTHER QUERIES: Technical queries outside the scope of "Replies by Post" or submitted without fee may be answered in the "Information Centre" pages, at the discretion of the Editor.

COMPONENTS: We do not sell electronic components. Prices and specifications should be sought from advertisers or agents.

BACK ISSUES: Available only until our stocks are exhausted. Within six months of publication, face value plus 30c for post and packing for each issue. Seven months and older, \$3 (includes post and packing and storage fee).

REMITTANCES: Must be negotiable in Australia and made payable to "Electronics Australia". Where the exact charge may be in doubt, we recommend submitting an open cheque endorsed with a suitable limitation.

ADDRESS: All requests to the Assistant Editor, "Electronics Australia", Box 163, Chippendale, 2008

running, I cannot get the motor started using it. I have also built the August 1970 CDI, eventually modifying it to your April 1978 circuit incorporting a tachometer drive, and more recently your TAI system, eventually modifying it to MKII specifications. My "hotted" sports car seems to give better performance using the CDI system, possibly due to fouled plugs.

In various journals I have seen advertisements for "reactive discharge ignition" systems originating from the UK. These units reportedly have all the advantages of both systems.

There are also CDI circuits around with an inductor in series with the SCR anode (presumably to extend the spark time). I have also read of a rectifier being installed across the ignition coil primary with the same intention. Whilst I appreciate that you dislike commenting on other than your own circuits, I am confused and any comments would be apppreciated.

A large Australian company has been advertising a Hall Effect unit to replace the contact points. The advertisement says to watch your magazine for details of TAI conversion. Can you tell me when these details are to be published? (R.P., Adelaide, SA).

• Your last question, regarding the Hall Effect unit to replace contact points, is answered in this issue on page 42. As far as "reactive discharge" ignition systems are concerned they are merely a transistorised ignition system with a fancy name. Sometimes they are also referred to as "inductive discharge" systems, to differentiate them from capacitor discharge systems.

The likely reason for having an inductor in series with the anode of the SCR in CDI designs is to avoid the possibility of

dv/dt switching when the inverter restarts and applies voltage to the SCR. The diode across the coil in some designs may have been included to bypass the coil impedance during the charging of the storage capacitor and thus reduce charging time.

We can only speculate as to why the dwell extender will not allow your car to start. Possibly the dwell time constant of the circuit is too short and will not allow sufficient spark duration to enable starting to occur. Thanks for the favourable comments on the magazine.

SUB-WOOFER ENCLOSURE: I followed with much interest your articles on designing sub-woofer enclosures in 1981 and '82 and have recently purchased the kit offered by Jaycar Pty Ltd without the enclosure. It is concerning enclosure design that I have written to you.

My application calls for an enclosure with restricted depth. This would mean that there would be insufficient distance to accommodate the 72mm vent as suggested in the enclosure design, with the appropriate clearance behind it (>1 x diameter). According to Brian Davies' article on this subject, published in your journal, reducing the length of tube by reducing the diameter of the port may increase air turbulence effects.


For my application, then, I see three possibilities of overcoming this problem:

1. Split the tube into two shorter lengths.

- 2. Bend the tube through 90°.
- 3. Site the vent in another face.

The first has the attraction that the vent holes can be easily hidden by the normal fabric facing over the speaker baffle board. My question is, is it possible to do this, or is one dependent upon a continuous length for a given diameter

Continued on page 154

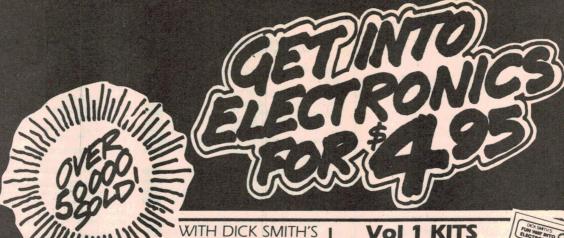

This is the top selling Fun Way Into Electronics Vol. 1 that has proven that electronics can be fun. For the raw beginner, this book introduces 20 exciting projects that can be built by using a unique 'breadboard' construction system - no soldering, so it's safe. Each project is fully illustrated so that mistakes are virtually impossible.

This top-selling book is now into it's fourth printing proving just how popular it has been. Don't Cat B-2600

ONLY

Vol 1 KITS

Kit to build projects 1-10

You can build any of the first ten projects from 'Fun Way Into Electronics' with this kit. It even includes the base board on which you assemble the circuits! Cat K-2600

Kit to build projects 11-20

This kit contains the slightly more specialised components which, together with the components from kit 1, will enable you to make any of the projects in the book. \$ 790

Cat K-2610



PARENTS PLEASE NOTE

All Fun Way Into Electronics kits are battery powered so they are completely safe. Also, Fun Way Vol. 1 kits require no soldering.

FUNWAY VOL. 2 20 MORE PROJECTS

After mastering Fun Way Vol. 1 what better way to go than Vol. 2. In Vol. 2 you are introduced to printed circuit boards and soldering. Both are fully explained and illustrated and they give you the choise of making your own boards or buying ready made. The basic laws of electronics, plus chapters on component codes,

FUNWAY VOL 2 KITS FROM

MULTI-PURPOSE LED

FLASHER \$2.95 A really simple kit that can be used as a warning device. elect-ronic jewellery, etc. Cat K-2621

DING DONG DOORBELL

Welcome visitors to your home with this integrated circuit door-bell! Cat K-2622

MORSE CODE TRAINER This simple oscillator circuit

lets you learn Morse code the easy way! Cat K-2623.

UNIVERSAL TIMER

\$5.50 Use it as an egg timer, a dark-room timer, etc: in fact, it's got a lot of applications! Cat K-2624

ELECTRONIC DICE

electronically! Simple circuit has other uses too. Cat K-2625

MONOPHONIC ORGAN Easy to build, and easy to play!

And it even has 'vibrato' - just like the big ones! Cat K-2626

POCKET TRANSISTOR

RADIO. \$7.95 Simple to build, and it's nice and small. Listening is so much more fun! Cat K-2627

TOUCH SWITCH

One touch on, next touch off-or on while touched. Dozens or 'on while touched'. Dozens of uses in the home. Cat K-2628

MOSQUITO REPELLER

Do they really work? Research suggests they might. Find out for yourself. Cat-K 2629

SIMPLE AMPLIFIER

A useful little amplifier for all those projects needing audio amplification. Cat K-2630

WIRELESS MIC.

\$6.50 A tiny transmitter that can be received on any FM receiver. A great little kit! Cat K-2631

LIGHT ACTIVATED SWITCH \$5.50

Highly useful for alarms, night light switches, etc etc. Sensitive and reliable. Cat K-2632

METAL/PIPE LOCATOR

\$6.50 A simple BFO circuit you can use to find metals, pipes, wiring, etc – maybe gold! Cat K-2633

SOUND ACTIVATED

SWITCH \$6.95 Picks up sound waves and trips a relay. Use as a telephone bell extender, too. Cat K-2634

HOME/CAR BURGLAR

ALARM . \$6.50 Leam how burglar alarms work when you install your own! For home or car. Cat K-2635

ELECTRONIC SIREN \$4.95

Great for alarm use – or where any warning is required. Good for kids toys, too! Cat K-2636

LED LEVEL DISPLAY ...\$8.95

This fascinating project shows you the audio level of any amplifier. Cat K-2637

INTERCOM UNIT

Communicate! Build this intercom and talk between rooms. etc. Cat K-2638

LED COUNTER \$7.95 MODULE

Learn how digital circuits work by building a counter. Count slot car laps, etc. Cat K-2639

SHORTWAVE RECEIVER \$6.95

Listen in to the exciting world of shortwave radio: amateurs, foreign countries! Cat K-2640

SCHOOLS, RE-SELLERS, ETC.: We'll negotiate a special price for bulk quantities on either books or kits, or both!







10 exciting new projects using integrated Circuits.

At last - the latest addition to our incredibly popular 'Fun Way series. And this one gets right into the big time, using both digital and linear integrated circuits in a variety of

projects.
Yes, there are still projects for the beginner—and there are projects for the more advanced. And we're sure you'll find the projects even more satisfying, more fun both to build

Plus, like the other 'Fun Way' books, special cut-out labels to give your projects a real professional finish.

Hurry! Get your copy now . . . ideal Christmas gift.

100 pages

10 brand new and exciting projects to build and use Every project fully explained with printed circuit layouts, etc.

Especially written to suit all ages and experience levels.

Cat B-2610

ONLY

Schools, Re-sellers, etc:

We offer discounts to quantity (above 10) purchasers. Call our wholesale division on (02) 888 3200

GET YOURS KITS FROM

\$795

Minder

.....\$7.95

A multi-purpose project for the car: 'lights on' warning, 'door open' warning, plus a burglar Cat K-2660 alarm flasher.

Two-Up

\$9.95
Australia's national game – now done electronically because King George pennies are hard to get! Cat K-2661

Lil Pokey

\$19.95 It's a barrel of fun to play. And you don't risk losing your shirt like on the real thing. Cat K-2662

Nocturnalis Stridulus Gryllidae

Whaaa! That's a cricket to you. Hide it in a dark room and it starts chirping. Turn the light on and it stops. It's infuriating! Cat K-2663

Mini Colour Organ\$12.95

Like a disco - but battery operated so it's safe! Connect to your radio. etc for a LED lightshow. Cat K-2664



Light & Sound

.....\$8.95 Another multi-talented project. Sound effects, flashing lights – continuity tester, Morse code oscillator . . . it's got the lot. Cat K-2665

Combination Time Lock Switch

.....\$12.95 Make it into a game . . . or use it as a real alarm component. It's that good! Just try getting into this one without setting off the alarm.

Cat K-2666

Mini Stereo Amplifier

Just the shot for 'Walkie' stereo – now you can listen to it in your bedroom through speakers! Or make yourself a PA amplifier. Cat K-2667

Binary Bingo

.....\$19.95

A game of skill and reaction time and a valuable teaching aid! It might sound pretty simple to play -but try it and see! Cat K-2668

Mini Synth

Wow! A real musical synthesiser, with decay, frequency doubling & halving, tremolo . . . unique circuit uses YOU as the note generator! Cat K-2669

A647/LL

to achieve the appropriate box tuning? The second choice has a similar advantage but I do not have any design principles on which to work.

The third suggestion poses some other difficulties in relation to siting the box within the area intended. Specifically the port hole will obviously require some clearance on its outer end to clear walls/floor, etc. Would the same requirements as occur on the interior end of the tube (ie≥1 x diameter) also prevail for its outer end? This dimension will obviously control the size of a plinth, should the port be sited in the base of the speaker.

I would be grateful for any assistance or further suggestions you can provide me with and for this I would like to offer my thanks in advance. I have much enjoyed your articles in this series and also on improving the sound quality of electronic organs. I would like to suggest another article in the vein of the latter: practical suggestions on making the accoustically "dead" environment in the home into an acceptably "live" one. (C.L., Glen Waverley, VIC.)

• Any one of your three suggestions could be satisfactory, provided you can actually tune the box to the correct frequency. The easiest course would be to put the vent on another face of the enclosure. We would assume that the

outer end of the vent would also have to be unrestricted.

Your suggestion on an article on domestic acoustics is an interesting one although many homes have a different problem in that the listening room is too "live" due to the hard reflecting surfaces of large windows and unadorned floors and walls

RF EXPOSURE: I have come across the terms 0.4W/kg (sometimes 0.4W/kg⁻¹) and 100Wm⁻² in connections with continuous exposures to radio frequencies in the range 30MHz to 30GHz. This presumably refers to incident radiation absorbed by the body so that 0.4W/kg indicates an absorption of 28W for an average man. I understand that these figures suggest limits to absorption for people exposed to such radiation.

I would be grateful for technical information as to how these figures or limits might relate to actual practice. For example, are there exposure limits set for technicians working in situations where such radiation may apply — in TV broadcasting stations, for example? And, if so, how is the broadcast power (peak output power?) related to the suggested limits stated above.

My query really arose from technicians servicing equipment such as radar installations used in World War II for coastal defence. The power output of equipment used, according to Denis Taylor in "Introduction to Radar and Radar Techniques", was about 200kW (some 1MW) with a frequency of 200MHz and pulse repetition frequency of 1/25 sec. Antennas consisted of an array some 20ft long, consisting of multiple dipoles. According to my informant these antennae were serviced while in operation.

With these powers would technicians have been subject to absorption in excess of the limits above? My informant, in the absence of any measurements of field strength, states that sparks could be drawn from a wire fence some hundreds of yards in front of the antennae. (C.M., Mosman Park, WA)

• We published an article entitled, "Microwaves: a health hazard" in the October 1981 issue. This gave safe exposure limits for microwaces of 1mW/cm² as the evolving US standard and 10μW/cm² as the Russian standard. We have also seen the same figures of 0.4W/kg of body weight quoted in a paper delivered by Arthur W. Guy, PhD, Dept of Rehabilitation, University of Washington. By any standard, the technicians concerned were almost certainly exposed to very dangereous levels of radiation. Photostats of our article are available at \$3.00.

BEST SELLER BEST ELECTRONICS SOURCES WIRELESS TELEPHONES PORTABLE FACSIMILES & MICRO COMPUTERS (DESK TOP & PORTABLE)

- 50-300 Km Long Distance VHF Mobile/Portable Wireless Telephones.
- Cordless/Handy Phone & Citizen Band (CB) 200/400 channels Radios.
- Amateur Communication Equipments (Yaesu/Icom/Kenwood) & Antennas.
- Portable Facsimile Transceiver, Transmit & Receive Documents/Pictures Through Normal Telephone.
- Business/Home Entertainment Microcomputer Best Software/Hardware Support, Fully Compatible with Apple II, CP/M.

(IE)

 Car Driving Computers, Automobile/Marine Electronic Accessories.

All item are ex-stock and prompt delivery. For more details, please call, telex or write to:

Airmail Order Available at Best Export Price



WORLDWIDE TRANSCEIVER



TS-430S AMATEUR (HF/SSB) RADIOS




PORT-A-FAX





TR-9130

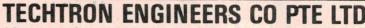LOW COST MICROCOMPUTER MEMORY 64K TO 256K FULL SOFTWARE HARDWARE SUPPORT




10, Anson Road, #02-97A,1st Floor, International Plaza, Singapore 0207. Republic of Singapore. Cable: 'MICSYSTEMS' SINGAPORE

Tel: 2209442/2237618 Telex: RS 20067 MITECH

NEW! LOW COST SWITCHERS

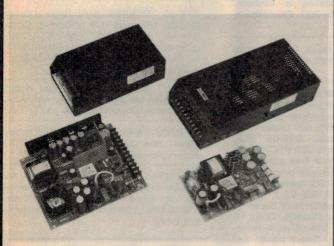Here is a range of switching power supplies for the budget conscious user. They are designed especially for micro to medium computer systems and use a series flyback design to provide multiple outputs.



			Max. power	
Model	Outputs			Price
HSC40-20	5V 3A, 12V 2.5A	open		
		frame	40 Watt	\$60
HSC40-31	5V 2.5A, 12V 2A, -12V			
	0.25A	open		
		frame	40 Watt	\$60
HSC55-41	5V 6A, -5V 0.5A, 12V			
	2.5A, -12V 0.5A	enclosed	55 Watt	\$80
HSC75-32	5V 3A, 24V 2.2A, -12V			
	0.2A	open		
		frame	75 Watt	\$95
HSC125-40	5V 10A, 12V 3.5A, -12V			
	0.5A separate 12V 2.5A	enclosed		
			Watt	\$150

- *Short circuit protection *Over power protection *Input surge protection
- *90-130V or 180-260VAC user selectable
- *Input frequency 40-440 Hz *Overvoltage protection

ALL PRICES PLUS SALES TAX AND FREIGHT. **DELIVERY FROM STOCK**



A DIVISION OF TELCON AUSTRALIA PTY. LIMITED

Suite 104/11 Spring Street, Chatswood 2067.

Telephone 02-411 1323

Telex AA 20149 Attn ST-18

MAIL ORDERS: BOX 156, DEE WHY, NSW. 2099. TELEPHONE 93-1848.

SUPER SPECIAL **GRAMO MOTOR** AND PICKUP

speed 33-45-78 includes cartridge and stylus turnover



P&P NSW \$2.75 INTERSTATE \$4.20 WA, NT \$5.20

SUPER SPECIAL FM STEREO KITS



and if detector. Circuit diagram supplied.

ONLY \$22 PP \$1.40

Send stamped envelope for copy of Electronics Australia magazine review of the units

SUPER SPECIAL

SPEAKER SYSTEMS 30 Watt RMS each. Size 19 x 11 in x 61/4 \$58 pair



PP. NSW \$7, interstate \$11, WA, NT \$14

TRANSISTORS AD161-162 \$1 pair 100 mixed Capacitors, fresh stock, all handy values \$2 __AD149 \$2 pair 100 mixed resistors, handy values \$2

BSR DELUX RECORD PLAYER

11 INCH TURNTABLE. CUING DEVICE SHIELDED MOTOR, MAGNETIC CARTRIDGE



MSP SPEAKERS 8 INCH DUAL CONE 15 OHM



8 WATT PP NSW \$1.80 INTERSTATE \$2.75 WA, TAS, NT, \$4.

DUAL VU METER \$3



CLOCK MODULE

CIRCUIT DIAGRAM SUPPLIED

888

including transformer and touch micro switches to suit.

SLIDE POTS

.50 cents
.50 cents
.50 cents
.50 cents
50 cents
50 cents
.30 cents
30 cents
.30 cents
.50 cents
. oo oomto

VU & BALANCE METERS



100uA \$2.00 STEREO VU \$3.00

TV COLOUR POWER SUPPLY BOARDS KRIESLER S25



P-P NSW \$2.80 INTERSTATE \$3.60 WA NT \$6

TUNING CAPACITORS 3 GANG \$2

POTS ROTARY

1/2 Meg	300
1 Meg	300
100K	300
100K Switch	500
50K Double Pole Switch	500
7,500	300
10K Switch	500
250K	300
50K	300
20K	300
10K Min Pots	250
50/ohm	500
1/2 or 1 Meg Switch	500
1/2 1 meg dual Concentric tapped at 1	100K \$1
2 meg ganged double pole switch	S
1.5 meg dual ganged	500
2 meg ganged log	Si
1 meg dual ganged	S
1/2 meg dual ganged LIN	750
25K. 50K dual ganged Concentric	
double switch	S
200K single line	300
20K wire wound	750
dual log 10K	750
100K dual ganged linear pots	750
10K sub min log pots	500
250K ganged pots	750
25K lin ganged pots	750

SPECIAL MAGNAVOX SPEAKERS

10-inch, 20 watts, RMS 8 or 15 ohm



P&P NSW \$2.50, INTERSTATE \$3.60, WA, NT \$5.00

SPECIAL MICROPHONE



EA marketplace EA marketplace

FOR SALE

VZ-200 SOFTWARE: 8K Programs: Lottoselector, Race horse selector, Metric conversions. 24K goldmine adventure. \$5 per game. 2 for \$9. 3 for \$12. 4 for \$14. Free Two-up game with each purchase of 2 or more programs. Post free in Australia. Leon Young Software Co. P.O. Box 265 Bunbury WA 6230.

SUPER 80: Disassembler \$9. Siemens Teleprinter \$60 & \$90. Vowels, 93 Park Dv, Parkville, 3052

WIND DRIVEN GENERATORS: Solar Panels, Inverters, Fluorescent Lighting. For information: Pioneer Wind & Solar, 19 Balowrie St., Yowie Bay NSW 2228.

EL GRAPHIX: Upper/Lower case Graphics Kit 4 for the Super-80 Computer. Full Upper and lower case characters • 160 versatile graphics characters • 9 new monitor commands • Graphics subroutines built in Centronics AND RS 232 routines built in VDU page Dump/VDU shift/rotate/fill routines • Complete Kit only \$55.50 inc p/p • Upgrade Kits 1, 2 or 3 only \$25.00 inc p/p • Even upgrade Dicks "Deluxe" Kit \$27.50 inc p/p. El Graphix PO Box 278 Croydon 3136 Victoria Phone (03) 725 9842 (after 7 pm)

CIRCUIT BOARD MATERIALS: Including copper clad epoxy glass board 1 oz single and double sided. Teflon double sided board. Riston coated negative acting board, cut to size. Riston developer, 3M Scotchcal film and developer. Marking Pens Etc. Australian Printer Circuits P/L, 73B Osborne Ave, Springvale. Phone 547 6860.

PACKET RADIO IS HERE: 200 Baud with error correction. Use your computer for QSO's, transfer blocks of memory or disk files. Program written for Tandy model 1 and 3 and

System 80. Source code convertible for other Z80 computers. All this is "Synchronous Packet Using The Software Approach" by Robert Richardson. 220 pages. \$28.00 + \$3.00 P & P. 2SSD disks also available for \$15.00 each postpaid. Circuits and boards available for Simple Mod/Demond and Computer Interface Unit. Some copies of the disassembled series in stock. Morse, RTTY and ASCII from your computer without costing a kilobuck. Northern Digital, PO Box 333, Charlestown,

"RISTON": Negative resist PCB material. Write for information sheet, Kalex, Box 174, Heidelberg, 3084.

SUPER 80 SOFTWARE: ASSEM-BLER/EDITOR. General purpose text editor and Zilog mnemonic assembler program to run on any size SUPER 80. Includes 18 page instruction manual. \$35.45. Fully proportional (analog) dual JOYSTICKS with four push buttons for real time games with Assembly manual. Interface program and demo game. KIT \$39.95 (game on tape \$10). MONITOR V1.2 and V2.2 Original source listings of two versions of Super 80 Monitor program with comments. Great for learning machine code. \$11.95 each. REAL-TIME GAMES: Snake, Smart bomb, and Invaders. Three games on cassette for

2290. (049) 43 8981.

\$14.95. "THINKER" games tape - includes Othello, Life, and 3-D Nought & Crosses \$14.95. Blank C-10 COMPUTER TAPES good quality \$1.50 ea (7 for \$10.00). Write to: Pelatronics, PO Box 807, Toowong, Q. 4066. Include \$2 P&P.

DISPLAY ADVERTS IN MARKETPLACE

are available in sizes from a minimum of

CLASSIFIED RATES \$3.60 for 40 letters

CLOSING DATE is six weeks prior to the

on-sale date. Issues are on sale the first

or part thereof per insertion payable in

2cm x 1 col rated at \$15 for a col cm.

advance. Minimum 80 letters.

Wednesday of each month.

UV LIGHT BOX: Commercial and hobbyist types available. See Advertisement on page 101. Kalex, phone (03) 458 2976.

PCB ETCH TANK: Commercial and hobbyist types. See advertisement on page 101. Kalex, phone (03) 458 2976.

SPECTRUM SOFTWARE: UK and Aust. bargain prices. Also custom programming service. Send SAE for details. Softpac Enterprises, 109 Kennedy St, Sth Hedland WA 6722.


READER SERVICE

BUILD YOUR OWN: Microcomputer circuits using Z80 chip at lowest possible cost. Full details and circuits in easy to read book with monitor PROM able to run hex keypad & 8 digit LED display. Book & monitor PROM \$30. RKO Electronics, PO Box 219, Springvale 3171.

COMPUTER CLINIC: Repairs and sevices Tandy, Commodore, Apple, System 80, Microbee, Osborne, etc, disk drives and printers. Bankcard. (07) 269 8573. PO Box 68, Aspley, Qld 4034.

Radio Pty Ltd Tel. (02) 587 3491 IS THE ONLY COMPANY WHICH MANUFACTURES AND SELLS EVERY PCB & FRONT PANEL published in EA and ETI 651 Forest Road Bexley 2207 **AUSTRALIA** RING FOR INSTANT PRICES 24 HOUR TURNAROUND SERVICE

Next month in Electronics Australia**

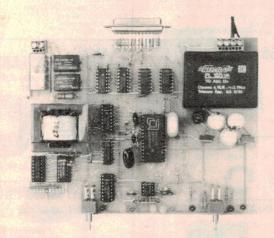

PLUS: Ignition killer for cars

Sprinkler controller

New direct-connect modem

Coming next month, our new direct-connect modem project offers switch-selectable 300 and 1200 baud operation, auto-dialing and auto-answer features, and can be used with both the CCITT (Australia) and Bell (United States) standards.

Remote control for Touch-lamp Dimmer

If you want the convenience of infrared remote control for your Touch Lamp Dimmer, this is the unit for you. The circuit adds directly to the Touch Lamp Dimmer and has a range of around 15 metres.

- * * Although these articles have been prepared for publication, circumstances may change the final content. However, we will make every attempt to include the articles featured here.
- Telecom's mobile telephone system



GENUINE FACTORY PRICES


Rugged top quality Aust made brand new bargains - all with factory warranty

		33						
Model	Size	Cone Type	V/Coil	Reson Hz	Freq Hz	Watts Rms	Price Ea or	2 for
6110	30cm	Ribbed surround	8 or 15 Ohms	65	50-8000	30	\$36.50 or	\$69.00
6160	30cm	Twin cone	8 or 15 Ohms	65	50-15000	30	\$38.50 or	\$71.00
6180	30cm	Foam surround	8 Ohms	30	30-4000	60	\$42.50 or	\$80.00
4310	38cm	Straight surround	8 or 15 Ohms	45	40-6000	60	\$69.00 or \$	132.00
4510	38cm	Straight surround	8 or 15 Ohms	45	40-6000	100	\$89.00 or \$	170.00
4350	38cm	Hi-Fi	8 or 15 Ohms	30	30-4000	120	\$69.00 or \$	132.00
			NEW FOOMON	V DANK	25			

NEW ECONOMY RANGE

8 HiFi	20cm Foam surround	8 Ohms		50	40-4000	40	\$17.50 or	\$33.30	
10 HiFi	25cm Foam surround	8 Ohms		50	40-4000	50	\$21.70 or	\$41.00	
12 HiFi	30cm Foam Surround	8 Ohms		40	30-4000	50	\$27.50 or	\$52.00	
8 PA	20cm Rugged paper	8 Ohms		70	60-8000	20	\$14.90 or	\$28.00	
10 PA	25cm Rugged paper	8 Ohms		70	60-8000	25	\$18.50 or	\$34.00	
12 PA	30cm Rugged paper	8 Ohms		60	50-6000	30	\$22.75 or	\$42.50	
Pack -	Postage add for one	25/30cm model NSW	\$3.50.	Intersta	te \$5. For tw	0 25/30	cm models f	NSW \$5.	

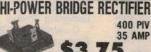Interstate \$7. For one 38cm model NSW \$4.00. Interstate \$6.00. For two 38cm models NSW \$7. Interstate \$8.50.



35 AMP \$3.75 P-P 75c

HIGH GRADE POTTER AND BRUMFIELD RELAY \$3.50

KU series 240 VAC operation • 3 sets of 240V 10 amp change over contacts • perspex cover and mounting base included • size 50mm x 37mm x 35mm • excomputer • as new condition. At less than 1/3 of the normal price.

240V 50Hz 5 AMP

MAINS FILTER

Professional Quality.

Also ideal audio gear, receivers, etc.

P-P \$1.50





MAGNAVOX 6W HI-FI WOOFER

8 ohm 20 watt • Freq respon 50-6500Hz. Reson 45Hz. Rolled foam surround ● High compliance suspension ● Barium ferrite magnet ● Excellent linearity at high power (ideal mid-range in systems

EACH

P-P NSW \$2.75 INTERSTATE \$4.50

(Normal factory price in 100 lots \$18 each).



!KEEP IT COOL!

4" sq 230V and 115V 50/60Hz 3" sq 115V 50/60Hz

EX-COMPUTER FAN MOTORS

EXCELLENT WORKING ORDER GUARANTEED Amps Power Supplies Electronic Equipment will operate far more efficiently • Imp protected •

\$8.95 EA

P.P. NSW \$2.50 **INTERSTATE \$3.50**



STEP DOWN TRANSFORMER

240VAC to 115VAC 500VA

APPROVED. DOUBLE WOUND. FUSE PROTECTED

P-P NSW \$7.50 SA, Q, V, T \$11.50 WA, NT \$15.50

2SD200 = BU205 TRANSISTOR

NPN VCBO



POWER

TRANSISTORS

140V 20AMP

MJ15003 NPN

MJ15004 PNP

\$7.90 P-P \$1

VCEO 700V

• 2.5 AMPS 4 FOR \$3.75 P-P 750

A1 QUALITY TRANSISTORS 2N3055

10 FOR \$6. P-P \$1.50

DIODE IN 4004. 50 FOR \$2.50

REGULATORS

7805 + 5V. 7905 - 5V 1A

10 MIXED \$6.50 P.P. \$1.50



TRANSMITTING TRANSISTOR

2N3927. NPN. 175MHZ 12W. GOLD PLATED.

2 FOR 30 -50 P-P \$1.50



TRANSISTORS

BD135 NPN. 45V, 1A, 8W

10 FOR \$1.95 P-P \$1

SPEED **GEARED MOTOR**



12V TO 18VDC INPUT

SPEEDS CALCULATED WITH 12V APPLIED. 3000RPM DIRECT DRIVE. 105RPM, 19RPM, 4.5RPM THROUGH GEARS. CURRENT 5 AMPS. HT OUTPUT 450VDC. 60mA. ALL SHAFT DIA 1/4"






12V HIGH POWER

105dB WARBLER TONE. at 1 METRE INDOOR/OUTDOOR IDEAL FOR CAR, HOME, BOAT ETC

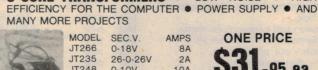SZI-95 INTERSTATE \$2.85 HI-POWER CAR SPEAKERS



MODEL JT266 0-18V JT235 26-0-26V JT248 0-10V JT249 8.5-0-8.5V & 15VCT JT274 0-9.5V & 2X 0-12V

36-0-36V

JT320

TRIAXIAL 3-WAY

AMPS 8A 2A 10A 4A 1A

C-CORE TRANSFORMERS . LOW NOISE . HIGH

10A 1A 2A

ONE PRICE ■95 ea

ADD P-POST: NSW \$3.50. V O SA T \$4.50. WA. NT \$5.50

150 - 0 - 150 VOLTS DC

P-P \$1.50



MASTER INSTRUMENTS TOP QUALITY 3" FLUSH MOUNT PANEL METER

15 × 23CM. (6" × 9" WOOFER. 234" MIDRANGE. 2" TWEETER.) 100W. MAX. 35 W.R.MS. 4-8 OHMS.
FREQ. 60-20,000 HZ. ROLLED FOAM SURROUND IN BUILT CROSSOVER. CHUNKY 570G. FERRITE MAGNET. SUPERSOUNDSOUNDSUPER



OR

P-P NSW \$2.50 INTERSTATE \$3 GRILLES \$5 PR.

P-P NSW \$3.50 INTERSTATE \$4.50

RED ROTATING DISTRESS BEACON

12 VOLT 2A Ideal for Car, Truck, Boat.

Also Disco

WISHING YOU ALL A MERRY CHRISTMAS

INDEX TO VOLUME 45 — JANUARY 19

The state of the s								
General Features			The inventive genius of			Marantz CD-73 compact		
actician i catales			Nikola Tesla	Sep	p22	disc player	May	p44
The work of the ship's radio			Absolute value amplifiers	Sep	p32	Marantz SD 820 DBX	,	
officer	Jan	p10	Valves are dead but not			cassette deck	Jun	p52
Scanners and scanning	Jan	p16	forgotten	Sep	p94	Kenwood KVA-502 audio-	00	P-0-2
Expedition to the antarctic			Superweapon software woes	Oct	p12	video amplifier	Aug	p46
P2	Jan	p22	New concept digital		and the same of th	Record clamps & anti-static		
The growing peril of space			multimeter	Oct	p16	mats	Sep	p50
debris	Feb	p12	The inventive genius of			Yamaha R-100 AM/FM	ООР	poo
Prospects for cable TV	Feb	p16	Nikola Tesla Pt 2	Oct	p22	stereo receiver	Oct	p44
Alan Blumlein: Wartime radar			How to obtain better TV			Sony PCM adapter for VCRs	Dec	p38
pioneer	Mar	p14	reception Pt 4	Oct	p88	conj i cin adapter for vorio	200	poo
The new smart missiles	Mar	p74	New concept in energy		poo	Audio/Video Electro	nioc	
Electromagnetic pulse	Apr	p14	management	Oct	p104		HIICS	
Anzcan — Cable to Canada.	Apr	p20	Televising the Bathurst 1000	Nov	p12	Laser tests for loudspeakers	Jan	p30
Wind generator	Apr	p24	The inventive genius of		P.2	The compact disc	Feb	p32
Planes that radar can't see.	May	p12	Nikola Tesla Pt 3	Nov	p20	What's inside a CD player	Mar	p28
Wind generators Pt 2	May	p18	Frequency modulation and		PLO	Compact disc: Controls and		
Personal Robots are here	Jun	p12	sidebands	Nov	p24	programming	Apr	p40
Mitsubishi RM-101			How to obtain better TV		PLT	Producing compact discs	May	p36
movemaster robot	Jun	p20	reception Pt 5	Nov	p90	Servo system in video tape		
An interview with Barry			Designing Rhythm		poo	recorders	May	p22
Jones	Jun	p29	Generators Pt 1	Nov	p84	Hifi sound but lofi ears: An		
Australian heart pacemakers	Jun	p32	Across the Pacific by	1400	po+	exasperating human		
How to obtain better TV			Helicopter	Dec	p28	problem	Jun	p44
reception	Jun	p94	Designing Rhythm	DCC	PZO	Phillips: VCRs, videodiscs,		
Fifth generation computers.	Jul	p12	Generators Pt 2	Dec	p78	compact discs	Jul	p42
TV for the deaf	Jul	p20	Electronic Ballast for	Dec	pro	Cassettes forge ahead	Aug	p38
AM transmissions & the time			fluorescent lamps	Dec	p86	KEF KM1 monitor		
domain	Jul	p24	nadrodociii iampo	DCC	poo	loudspeakers	Sep	p42
UFO's: Time for rational						Audio-technica "sound		
studies	Jul	p32	Hifi Reviews			burger": Personal		
How to obtain better TV			niii neviews			stereogram	Oct	p33
reception Pt 2	Jul	p82	Teac synthesised AM/FM			Albums on compact disc	Nov	p38
Thermal shock	Aug	p12	tuner	Jan	p38	Home video cameras	Dec	p12
A flight on the nasa		and the second	Technics way; smallest RQ-					
observatory	Aug	p20	SJ1 portable player	Feb	p41	The Serviceman		
Aircraft design	Aug	p26	Meridian M3 interactive			A tale of two Sanyos: Same		
How to obtain better TV	1 4 3	CE TEST	system	Mar	p36	symptoms, different fault.	Jan	p68
reception Pt 3	Aug	p100	Technics SL-Q20 automatic		BASE	Catching the set that		7.0
Electronic fuel injection	Sep	p14	turntable	Apr	p44	bounces — With dignity	Feb	p74
					1 - 6 -	- J		-

-					
Col	net	rill	cti	on	2

Constructional			
Remote infrared TV sound control	Jan	p40	6/CTV/6
Plugpack regulator	Jan	p52	2/PS/53
Playmaster Hifi AM tuner Pt 2	Jan	p58	2/TU/51
The "led-head" lightchaser	Jan	p72	3/MS/101
Transistor assisted ignition	Feb	p44	3/TI/17
Optoelectronic trigger	Feb	p56	3/TI/18
Moisture alarm	Feb	p58	3/MS/102
Playmaster Hifi AM tuner Pt 3	Feb	p64	2/TU/52
Remote TV sound control Pt 2	Feb	p78	6/CTV/7
Wheatstone bridge and resistance			
box	Feb	p82	7/B/15
Analog fuel consumption meter	Mar	p42	3/AU/34
Playmaster hifi AM tuner Pt 4	Mar	p54	2/TU/53
Brown out protector	Mar	p60	2/PC/36
3½ digit multimeter	Mar	p86	7/M/62
Car computer battery back up	Mar	p102	3/AU/35
Build your own solenoid	Mar	p108	8/DT/124
Stereo simulator	Apr	p48	1/MS/26
Touch-lamp dimmer	Apr	p58	2/PC/37
Balanced 8-channel master mixer	Apr	p74	1/MX/16
Universal preamplifier for MC		and the same of th	
cartridges	Apr	p84	1/PRE/34
How to make a buzzer	Apr	p90	8/DT/125
Electronic roulette wheel	May	p48	3/EG/25
50V/5A power supply Pt 1	May	p58	2/PS/54
Balanced 8-channel master mixer			
Pt 2	May	p66	1/MX/17
Alcohol breath tester	May	p82	3/MS/103
50V/5A power supply Pt 2	Jun	p56	2/PS/55
Effects unit	Jun	p68	1/EM/58
Amplifier overload indicator	Jun	p86	1/MS/27
Tacho/dwell meter for engine tune-	10 4500	AZZ-ZYNI	0.714/40
ups	Jul	p54	3/TM/18

±12V 50V/5A power supply	Jul	p62	2/PS/56
4½ digit LCD event counter	Jul	p66	'7/CL/36
Fridge alarm	Jul	p90	3/MS/104
Design and build a relay	Jul	p102	8/DT/129
Touch lamp timer	Aug	p52	2/PC/38
Video amplifier	Aug	p62	6/MS/10
2MHz 4½ digit frequency meter	Aug	p78	7/F/32
Electronic wattmeter	Sep	p54	7/M/63
In-circuit transistor tester	Sep	p62	7/VT/17
40-channel UHF transceiver	Sep	p72	3/TC/14
Soil heater	Sep	p86	2/PC/39
Video enhancer	Oct	p52	6/MS/12
Speed sentry for cars	Oct	p60	3/AU/36
40-channel UHF transceiver Pt 2	Oct	p79	3/TC/15
Nail finder	Oct	p84	3/MS/105
TV pattern generator	Nov	p56	7/RO/64
Parabolic microphone	Nov	p64	1/MA/59
40-channel UHF transceiver Pt 3	Nov	p78	3/TC/16
1920's Style wireless set	Nov	p46	4/VR1/16
Breakerless ignition for your car	Dec	p42	3/TI/19
Chase 'n' chomp	Dec	p52	3/EG/26
VK powermate	Dec	p62	2/PS/58

Microprocessors — Constructional

Chunky graphics for the super-80 Datum microprocessor trainer:	Jan	p80	2/CC/79
software	Jan	p86	2/CC/80
Compuvoice for TRS-80	Apr	p92	2/CC/81
Memory expansion for the ZX-80	May	p88	2/CC/82
Centromics to RS-232C interface	Jul	p96	2/CC/83
Modified listing for EPROM			
programmer	Jul	p106	2/CC/84
Compumuse music synthesiser	Aug	p90	2/CC/85
Super-80 printer interface	Aug	p87	2/CC/86

B3 to DECEMBER 1983

I						
l	Where did all the microvolts	crise (s	-	Hex display for EPROM		
1	How to acquire a CRO —	Mar	p96	programmer	Jan	p78
I	and still need one!	Apr	p68	Suppressed zero car voltmeter	Feb	p71
Ì	When there is nothing wrong	o Wales	d malica.	Stripper modification for wire		,
l	- but the set won't go!	May	p76	wrapping	Feb	p71
Ì	Success, frustration — and a	tim	200	500MHz prescaler for digital		-
ļ	Minor components can	Jun	p80	Burnout protector for	Mar	p68
1	cause expensive faults	Jul	p72	ohmmeter ranges	Mar	p68
1	De-gauss guesses and fuse	TO SE	hasons (Loudspeaker protection for		
ì	confusion	Aug	p70	high-power amps	Mar	p68
1	The corrosive spirit of in- house service	Sep	p68	Current limiting for the VK	Mar	p71
1	Fires in TV sets — one	ocp	poo	Analog multiplexer and op	Mar	p71
Ì	certain cause	Oct	p66	amp D-A converter	Mar	p71
1	Linearity, tripler repair — and	THE REAL PROPERTY.		Model railway signal override	SMEK OF	4 -44
١	earrings!	Nov	p70	system	Apr	p72
Î	TV fires	Dec	p72	Power failure indicator Cassette interface for the	Apr	p72
١	CONTRACTOR OF THE SECOND	Hall	60 HINE.	VIC-20 personal computer	May	p72
1	Forum			Low-cost pushbutton		
١	Where's there's smoke			sequential switch	May	p72
1	there's a TV set —			Hold function for digital frequency meter	May	n72
1	perhaps	Jan	p26	Low cost economy meter	May	p72
	Recording is out of the rut.	Feb	p26	with km/l readout	May	p75
1	AM sidebands — here we go			Audio indicator for the heart	S pouls	
ı	again!	Mar	p22	rate monitor	Jun	p77
1	detectors work	Apr	p32	Updating the pools/lotto selector	Jun	p77
1	Radiocommunications — a	1917	ELYTON TOUR SE	Quiz game adjudicator	Jun	p79
1	new act with old problems	May	p32	Leading zero blanking for		
1	Wholesale, retail, sales tax and all that!	lun	-10	playmaster AM tuner	Jun	p79
1	t was nothing like this in the	Jun	p40	Extra RAM for the DREAM 6802 microcomputer	Jul	p79
1	"good old days"	Jul	p38	Digital clock monitor with	Jui	pro
1	Old circuits never die		Approved	audible output	Jul	p79
1	They are simply brought		a page	Composite video signal		
1	up to dateet's buy an argument	Aug	p34 p36	generator using NOR	test	-01
1	Aging ears — as sluggish as	oeb	pso	gates	Jul	p81
1	they say?	Oct	p30	VIC-20	Jul	p81
1	Why buy a home computer?	Nov	p32	Reverse polarity protection		1191
1	Ve mustn't kill CD for the sake of a few easy bucks	Doo	224	circuit	Jul	p81
1	sake of a few easy bucks	Dec	p34	Wide range low distortion sweep oscillator	Aug	p73
1	Personal Computer	2		PCB pattern suggestion	Aug	p73
- 1	The Microbee low cost			Modified light chaser gives		
1	personal computer	Feb	p94	cylon eye display	Aug	p77
1	Computing on the go with		o or other	EPROM adapter for EA programmer	Aug	p77
	the Otrona 512	Feb	p118	Tachometers and CD ignition	Aug	pri
1	he AED universe super		-101	systems	Aug	p77
	computer II	Mar	p134	Electronic detent circuit	Sep	p82
	computer	Apr	p122	Mounting small speakers Battery indicator for small	Sep	p82
	National Panasonic's			boats	Sep	p82
	JB-3000 computer	May	p120	Transient muting for		
	he Commodore 64: For home or business	Jun	p130	preamplifier	Sep	p82
	he VZ-200: Colour	oun	proo	Regulated enlarger power	Sep	p83
1	graphics and sound	Jul	p130	Beeper for the Super-80	Sep	p83
	he Cromemco C-10SP	A	-106	Mains derived TTL clock	Sep	p83
	Computer system OKI electric if800 "all-in-	Aug	p126	Frequency doubler uses one		
	one" computer	Oct	p94	Glow plug driver for model	Oct	p69
	he Microbee IC	Nov	p124	aeroplanes	Oct	p69
	andy model 100 portable	Das	202	IC sockets and double sided		
	omputer Julmont Magnum portable	Dec	p92	boards	Oct	p69
	computer	Dec	p136	Wide range capacitance	Oct	270
	Control of the Contro	SAND !	HOSOFF	meter	Oct	p70
	Circuit & Design Ide	200		controls booster fans	Oct	p70
		-43	A COUNTY	Dual trace CRO adapters	Nov	p76
	mproved triangle-to-sine-	lon	270	Effective joystick	Nov	p77
	wave converter 're-regulator for EA power	Jan	p78	Improving the solenoid NiCd charger	Nov Dec	p77
	supply	Jan	p78	Stereo sound for TV	Dec	p82

Notes & Errata

Notes & Ellata		
Compuvoice (October 1982,		
2/CC/75)	Jan	p133
Fluorescent light starter		-100
(October 1982, 2/PC/33) Ultrasonic rule (August	Jan	p133
1982, 3/MS/94)	Feb	p133
Fluorescent starter (October		
1982, 2/PC/33)	Feb	p133
EPROM programmer hex		
display (January 1983,		-110
CDI page 79)	Mar	p149
(January 1983, 2/CC/79)	Apr	p141
Car computer (August 1982,	, pi	ріті
3/AU/31)	Jun	p149
Optoelectronic trigger		
(February 1983, 3/TI/18)	Jul	p149
TV CRO adapter (May 1980,	Jul	n140
7C/31)	Jui	p149
1982, 3/MS/95)	Oct	p133
LCD 41/2-digit event counter		
(July 1983, 7/CL/36)	Oct	p133
Electronic wattmeter		
(September 1983,	Nov	5140
7/M/63)	NOV	p148
meter (October 1983, CDI		TANK I
page 70)	Nov	p148
Absolute value amplifier		
(September 1983,		
8/DT/130)	Nov	p148
supply (June 1983,		
2/PS/55)	Nov	p148
Watered F	A DESCRIPTION OF THE PERSON OF	SUPPLIES TO

AN INTRODUCTION TO DIGITAL

ELECTRONICS


FOURTH EDITION

Electronic equipment now plays an important role in almost every field of human endeavour. And every day, more and more electronic equipment is "going digital". Even professional engineers and technicians find it hard to keep pace. In order to understand new developments, you need a good grounding in basic digital concepts, and An Introduction to Digital Electronics can give you that grounding. Tens of thousands of people — engineers, technicians, students and hobbyists — have used the previous editions of this book to find out what the digital revolutions is all about. The fourth edition has been updated and expanded,

to make it of even greater value.

> ONLY \$4.50 + 90c p&p

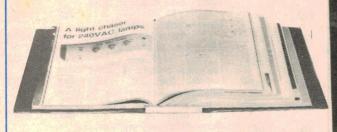Available from "Electronics Australia", Regent St, Chippen...
mail order from "Electronics Australia 163, Chippendale, 2008. PRICE \$5.40. **EA Magazine Holders**



The binders and magazine holders are available over the counter from Electronics Australia. 57 Regent Street. Sydney, NSW — Price: \$5.10 binders. \$4.50 holders.

Mail orders should be sent to Electronics Australia, PO Box 163, Chippendale, NSW 2008.

Prices including postage are:

Holders: \$5.50 NSW; \$5.60 other states: or six for \$29.00 NSW; \$31.50 other states, \$A33.00 NZ.

Binders: \$7.00 NSW; \$8.50 other states: or six for \$33.00 NSW; \$36.00 other states, \$A37.00 NZ.

EA PC BOARDS AND FRONT PANELS

Some readers have problems obtaining PC boards and front panels for projects. Many of our advertisers sell these items and their advertisements should be checked in the first instance. Failing that, below is a list of firms which produce or sell PC boards and front panels

NSW

Dick Smith Electronics, 125 York Street, Sydney, 2000. Telephone 290 3377. DSE also has branches and resellers throughout Australia.

Jaycar Electronics 117 York Street, Sydney 2000. Telephone 29 2098.

115-117 Parramatta Road, Concord, 2137. Telephone 745 3077.

Radio Despatch Service, 869 George Street, Sydney 2000. Telephone 211 0816.

RCS Radio Pty Ltd, 651 Forest Road, Bexley, NSW 2207. Telephone: 587 3491

Rod Irving Electronics, 425 High Street, Northcote, 3070.

Telephone 489 8131.
48 A'Beckett Street.

48 A'Beckett Street, Melbourne 3001. Telephone 347 7917 347 9251.

Kalextronics,

101 Burgundy Street, Heidelberg 3084. Telephone 743 1011.

Shop 11, Regional Shopping Centre, Melton 3338. Telephone 743 1011.

Sunbury Printed Circuits,

Lot 14, Factory 3, MacDougal Road, Sunbury 3429. Telephone 744 2714

WA Altronics,

105 Stirling Street, Perth 6000. Telephone 328 1599.

Jemal Products, 5 Forge Street, Kewdale, 6105 Telephone (09) 451 8726

N.Z. Marday Services, PO Box 19 189, Avondale, Auckland.

Mini Tech Manufacturing Co Ltd, PO Box 9194, Newmarket.

Printed Circuits Limited, PO Box 4248, Christchurch.

SUBSCRIPTION SERVICE



Subscription Rates

\$29.00 per year within Australia \$31.00 per year elsewhere

Make sure you receive every copy of the magazine by ordering it from your newsagent or the publisher. For publisher subscriptions post this coupon, with your remittance to Electronics Australia Subscription Dept, John Fairfax & Sons Ltd, GPO Box 506, Sydney 2001. Subscription will start with first available issue.

ADVERTISING INDEX

ADVERTISER	P	AGE
Ace Radio		157
Active Electronics	124, 125,	126
AED Micro Computer		
Products		144
Altronics	32, 33, 76	
	109, 148,	
Ampec Electronics		95
Amtex Electronics	101	155
Applied Technology	104,	44
Audio Engineering Audioson Int.		37
Aust. Computer Softwar	· 0	145
Aust. School of Electron		132
Avtek Electronics	1100	111
BGR Computers	68, 69, 70	
Billco Electronics		129
Birkenhead Electronics		48
C & K Electronics		139
Castle Electronics		22
David Reid Electronics		35
	41,60,61	
	102, 118,	
	143, 152,	
Daneva Aust.		36
Eastern Communication		112
Ellistronics	24, 25, 26	
Elmeasco	2	, IFC
Emona Enterprises		147
Emtronics Ferguson Transformers		75
Harman Australia		14
Geoff Wood Electronics		57
	11, 50, 51	
	3, 99, 134,	
Kalextronics		101
Kearney Sayers		89
L. E. Chapman		155
McGraths		17
Melbourne Machinery C	o.	97
Micro Store		139
Parameters		123
Radio Despatch Service		123
RCS Radio	10.10	156
Rod Irving Electronics	18, 19	
	140, 141, Colour se	
Sanyo Scientific Electronics	Colour se	88
Sheridan Electronics	114,	
Sharp	114,	IBC
Skarbek Trading	Colour se	
Stotts		117
Systems Reliability		47
Technicraft		81
Techtron Engineering		154
Texas Instruments		3C +
	colour se	
Truscott Electronics		58
Union Carbide		113
Video Active Electronics	S	137
Wayne Green Inc.		45
Wireless Institute of Aus	ST.	156
		-

The first choice is Sharp Stereo Video

We used to think of video as something separate from the home stereo system. Now, Sharp has brought them together to create the audio/ visual entertainment centre.

Two-channel home videos record and playback with stereo sound. They have been designed from the outset to integrate with your stereo system. You simply connect the audio output of the video to your amplifier, the same way you'd connect a cassette player. Arrange your speakers, one each side of your TV set, and you're ready to enjoy dynamic stereo video.

It's like having a stereo cinema in your living room.

SHARP VC-386 — Affordable Brilliance

The features are advanced, the operation is simple. 2 channel stereo sound, Dolby*, automatic front loading and 8 function remote control.

Video search at 10 x forward and reverse, noiseless still frame function and 14-day 5-event programmable timer are all part of this highly featured video.












TEXAS INSTRUMENTS HOME COMPUTER

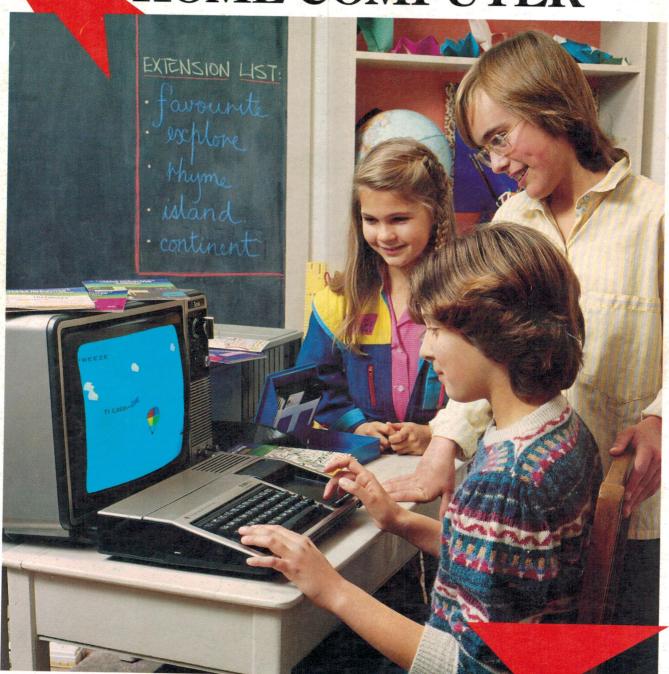

A limitless learning environment for children to give them the Educational Edge. Texas

Creating useful products and services for you.

TEXAS INSTRUMENTS

TEXI0086 B